



# UNIVERSITI TUN HUSSEIN ONN MALAYSIA

## FINAL EXAMINATION SEMESTER II SESSION 2010/2011

COURSE NAME	:	DIGITAL ELECTRONICS
COURSE CODE	:	DEE 2123
PROGRAMME	:	2 DEE / DET
EXAMINATION DATE	:	APRIL/MAY 2011
DURATION	:	3 HOURS
INSTRUCTION	:	ANSWER (FIVE) 5 QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF (EIGHT) 8 PAGES

- Q1** (a) What is the difference between digital and analog quantities ? Give an example for each quantity .  
(4 marks)
- (b) Explain two advantages of using digital technique and give a reason to support each explanation.  
(8 marks)
- (c) Convert the following numbers:
- (i)  $01001011_2$  to decimal
  - (ii)  $0100\ 0101_{\text{BCD}}$  to decimal
  - (iii)  $87_{10}$  to hexadecimal
  - (iv)  $87.125_{10}$  to binary
- (8 marks)
- Q2** (a) Write the truth table and Boolean expressions for AND and OR gates.  
(4 marks)
- (b) Sketch the output waveforms for the NAND and NOR gates with the given input waveforms in Figure Q2(b).  
(6 marks)
- (c) Write down the Boolean expression for the output Z for the circuit in Figure Q2(c).  
(4 marks)
- (d) Draw the logic circuits which will implement this logic function.  
 $(\overline{AC} + B) + \overline{ACD}(C + \overline{B})$   
(6 marks)
- Q3** (a) Write down DeMorgan's theorem.  
(2 marks)
- (b) Apply the laws and theorems of Boolean and DeMorgan to simplify each of the following logic equations:
- (i)  $F = (\overline{A} + B).AC + \overline{A.B.C}$
  - (ii)  $F = \overline{\overline{(A + B)}(C + D)}$
- (7 marks)


- (c) From the truth table shown in Table Q3(c):
- (i) Use Boolean algebra to find the simplified equation for Z in the sum-of-products form.
  - (ii) Draw the simplified circuit using NAND gates only.
- (11 marks)
- Q4** (a) From each of the Karnaugh maps in Figure Q4(a), obtain the minimum SOP expressions.
- (10 marks)
- (b) From the truth table shown in Table Q4(b):
- (i) Write the standard sum of product (SOP) equation.
  - (ii) Write the standard product of sum (POS) equation.
  - (iii) Use a K map to obtain the minimum SOP and POS equations
  - (iv) Will the SOP circuit produce the same output as the POS circuit? Why ?
- (10 marks)
- Q5** (a) Determine the largest decimal number that can be represented with :
- (i) 8-bit unsigned binary
  - (ii) 8-bit signed binary
  - (iii) 8-bit BCD
- (6 marks)
- (b) The following are 8-bit two's-complement binary numbers. Calculate their sums and express the results in decimal. State if there is any overflow in the sums.
- (i)  $01011111 + 00100001$
  - (ii)  $00010110 + 11111111$
- (6 marks)
- (c) Compare the binary and Gray code values for the decimal 31 and 32 sequence. What characteristic is most important about the Gray code ?
- (8 marks)

- Q6**
- (a) Draw the truth table of a half adder, obtain the Boolean expressions for the SUM and CARRY outputs and then draw the resulting logic circuit.  
(5 marks)
- (b) Produce a truth table for a full adder. Use the Karnaugh map method to simplify the Boolean expressions for the SUM and CARRY outputs. Then draw the resulting minimum circuit.  
(10 marks)
- (c) Show that a full adder circuit can be constructed using two half adders.  
(5 marks)
- Q7**
- (a) What is the function of :  
(i) a decoder  
(ii) an encoder  
(6 marks)
- (b) Describe an application of the decoder and encoder.  
(4 marks)
- (c) With the aid of a circuit diagram and truth table, describe the operation of a 3-line-to-8-line active LOW output decoder  
(10 marks)


**FINAL EXAMINATION**

SEMESTER /SESSION : II / 2010/2011  
 COURSE : DIGITAL ELECTRONIC

PROGRAMME : 2 DEE / DET  
 COURSE CODE : DEE2123

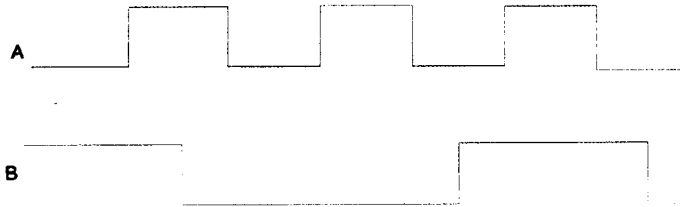

**Figure Q2(b)**

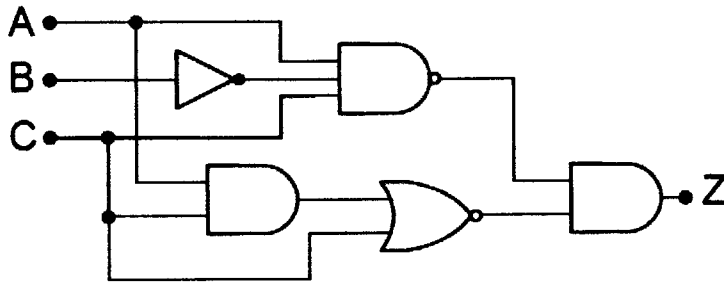

**Figure Q2(c)**

**FINAL EXAMINATION**

SEMESTER /SESSION : I / 2010/2011  
COURSE : DIGITAL ELECTRONIC

PROGRAMME : 2 DEE / DET  
COURSE CODE : DEE2123

**Table Q3(c)**

A	B	C	Z
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

### FINAL EXAMINATION

SEMESTER /SESSION : I / 2010/2011  
 COURSE : DIGITAL ELECTRONIC

PROGRAMME : 2 DEE / DET  
 COURSE CODE : DEE2123

A·B \ C·D		C·D			
		00	01	11	10
A·B	00	1	1	1	1
	01	1	1	0	0
	11	0	0	1	0
	10	0	0	1	1

(i)

A·B \ C·D		C·D			
		00	01	11	10
A·B	00	0	0	X	0
	01	1	1	X	0
	11	1	1	X	X
	10	1	0	X	X

(ii)

**Figure Q4(a)**

**FINAL EXAMINATION**

SEMESTER /SESSION : I / 2010/2011

PROGRAMME : 2 DEE / DET

COURSE : DIGITAL ELECTRONIC

COURSE CODE : DEE2123

**Table Q4(b)**

<b>A</b>	<b>B</b>	<b>C</b>	<b>X</b>
<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>0</b>