



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2011/2012**

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS II
COURSE CODE : BEF 12503
PROGRAMME : BEF
EXAMINATION DATE : JUNE 2012
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS FROM
PART A AND ANY ONE (1)
QUESTION FROM PART B

THIS PAPER CONSISTS OF TEN (10) PAGES

PART A (Answer ALL Questions)

- Q1** (a) Describe briefly the relationship between the instantaneous voltage drops across the inductor with the current flowing through it. Write its instantaneous voltage and instantaneous current equations. (5 marks)
- (b) The current $i(t)$ flowing through the inductor of 10 mH. If the instantaneous voltage waveform across the inductor terminal is shown in Figure Q1(b) and assuming the initial current $i(0) = 0$, find;
- (i) The piecewise equation of the voltage, $v(t)$ (5 marks)
 - (ii) The current, $i(t)$ and sketch the waveform (5 marks)
 - (iii) The power, $p(t)$ stored in the inductor and sketch the waveform (5 marks)
 - (iv) The energy, $e(t)$ induced in the inductor and sketch the waveform (5 marks)
- Q2** (a) Define briefly the natural response and step response of supplying energy in a circuit. (4 marks)
- (b) A capacitor of 25 μF is being charged through 5 $\text{k}\Omega$ and 1 $\text{k}\Omega$ resistors from 180 V(dc) source as shown in Figure Q2(b). The switch A is at position B for a long time and goes to position C at $t = 0$ s. Given the general equation of current is $i(t) = Ae^{-t/\tau}$. By applying step response analysis, determine:
- (i) The current flowing at $t = 0^+$ (4 marks)
 - (ii) The Current drop rate at $t = 0^+$ (3 marks)
 - (iii) The Capacitor voltage rise rate at $t = 0^+$ (3 marks)
 - (iv) The Resistor voltage drop rate at $t = 0^+$ (3 marks)
 - (v) The Time taken by capacitor voltage to reach 100 V (4 marks)
 - (vi) The Energy stored by the capacitor when it is fully charged (4 marks)

- Q3** (a) Plot the appropriate waveforms and diagrams for the following functions in time-domain and phasor-domain forms, respectively.

(i) $v(t) = 1 \cos(\omega t + 45^\circ)$ (ii) $v(t) = 1 \cos(\omega t + 225^\circ)$ (iii) $v(t) = 1 \cos(\omega t - 315^\circ)$

(9 marks)

- (b) A circuit is shown in Figure Q3(b) is connected with a source, $V(\text{rms}) = 240 \text{ V}$, 50 Hz frequency and having phase angle -300° .

- (i) Sketch the appropriate phasor-domain circuit

(2 marks)

- (ii) Calculate the total circuit impedance

(2 marks)

- (iii) Calculate the currents of I_1 , I_2 and I_3 in phasor-domain and time-domain forms, respectively

(6 marks)

- (iv) Find the voltages across inductor, V_1 and capacitor, V_2 in phasor-domain and time-domain forms, respectively

(4 marks)

- (v) Sketch the appropriate current and impedance diagrams, respectively in phasor-domain

(2 marks)

PART B (Answer any ONE (1) Question)

- Q4** (a) Sketch the response signal for *overdamped*, *critically damped* and *underdamped* of a RLC circuit. (6 marks)
- (b) A series RLC circuit is shown in Figure Q4(b). The switch is assumed at position *A* for a long time and move to position *B* when $t > 0$. Applying step response analysis on the circuit,
- (i) Sketch the equivalent circuit at $t < 0$ (2 marks)
 - (ii) Evaluate the initial voltage, $v(0)$ across the capacitor at $t < 0$ (2 marks)
 - (iii) Sketch the equivalent circuit at $t > 0$ (2 marks)
 - (iv) Determine the damping factor, α (2 marks)
 - (v) Obtain the resonance frequency, ω_0 (2 marks)
 - (vi) Find the roots characteristic s_1 and s_2 (2 marks)
 - (vii) Determine the steady state value of voltage across the capacitor, $v(\infty)$ (3 marks)
 - (viii) Evaluate the complete response of $v(t)$ at $t > 0$ (4 marks)

- Q5** (a) Explain the concept of i - v relations in phasor domain if a circuit consists of purely R , purely L and purely C respectively. Include any appropriate equations and diagrams to support the explanation. (12 marks)
- (b) A circuit shown in Figure Q5(b) consists of supply voltage, $V(rms) = 240$ V with phase angle 340° and the frequency is 50 Hz. The circuit is connected with an inductor element, $L = 10$ mH.
- (i) Determine the voltage across the inductor in phasor-domain and time-domain (3 marks)
- (ii) Determine the current flowing through the inductor in phasor-domain and time-domain (4 marks)
- (iii) Sketch the resulting phasor diagrams of Q5(b)(i) and Q5(b)(ii) (6 marks)
- Q6** (a) Figure Q6(a) shows a general impedance relationship network. From the general network, describe all individual passive elements in phasor-domain. Include any appropriate equations and diagrams to support the explanation. (12 marks)
- (b) The sinusoidal voltage source in the circuit as depicted in Figure Q6(b) is developing a voltage equal to $22.36 \cos(5000t + 26.565^\circ)$ V.
- (i) Find the Thevenin impedance, Z_{TH} with respect to the terminal a-b (2 marks)
- (ii) Find the Thevenin voltage, V_{TH} with respect to the terminal a-b (2 marks)
- (iii) Draw the Thevenin equivalent circuit (3 marks)
- (iv) If the terminal a-b is connected with a capacitor element 10 μ F, find the new circuit impedance and sketch the new impedance and voltage diagrams in phasor domain (6 marks)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2011/2012
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : BEF
 COURSE CODE : BEF12503

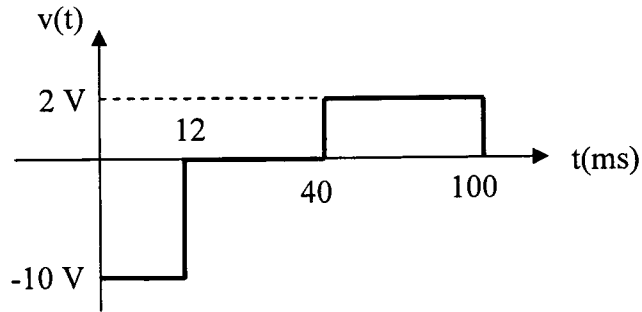


FIGURE Q1(b)

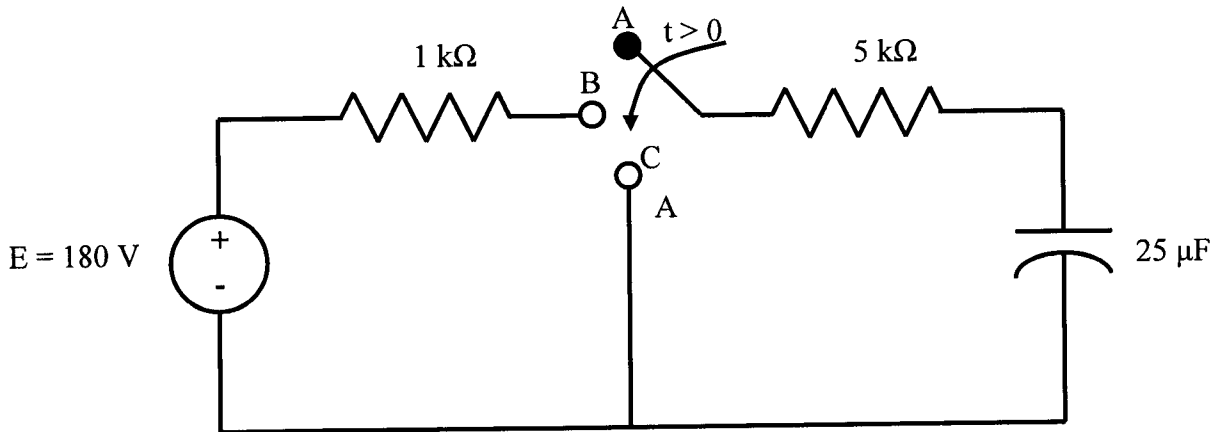


FIGURE Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2011/2012
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : BEF
 COURSE CODE : BEF12503

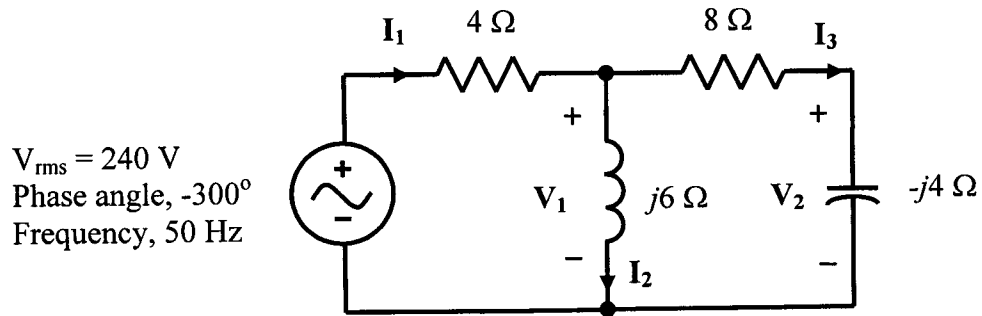


FIGURE Q3(b)

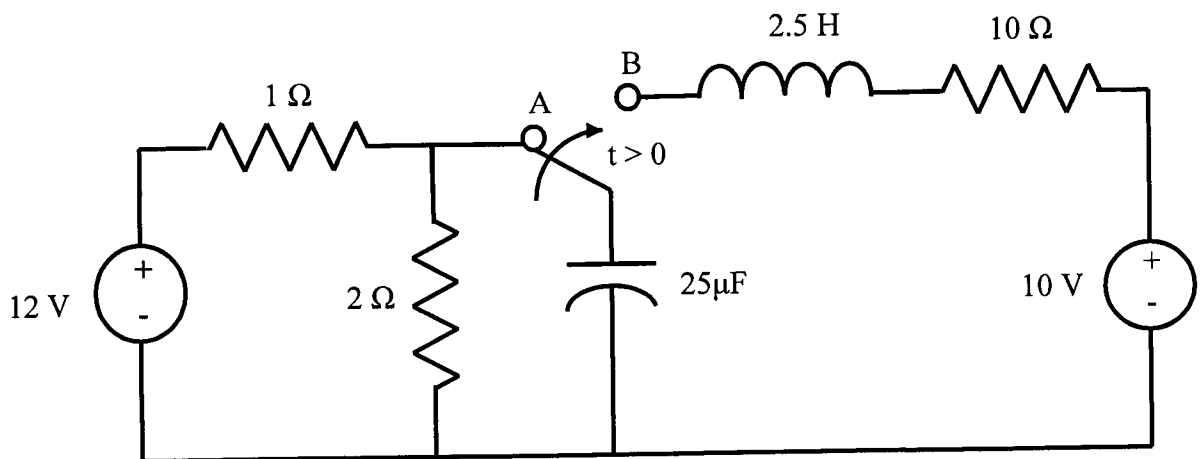


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2011/2012
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : BEF
 COURSE CODE : BEF12503

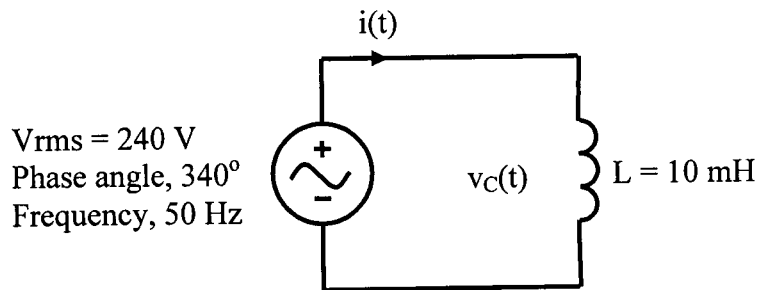


FIGURE Q5(b)

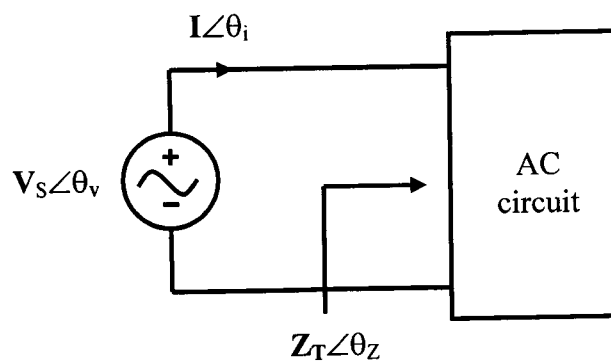


FIGURE Q6(a)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2011/2012
COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : BEF
COURSE CODE : BEF12503

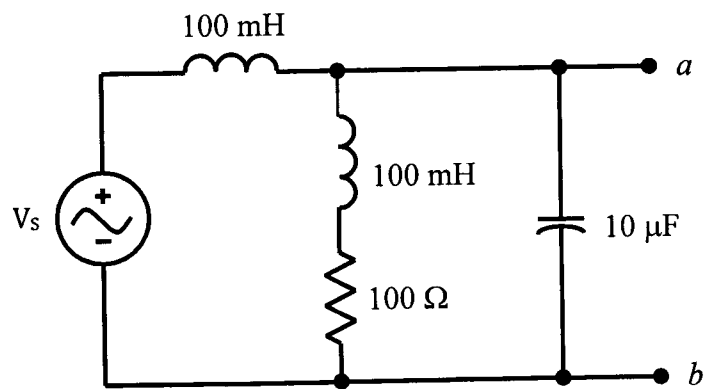


FIGURE Q6(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2011/2012
 COURSE : ELECTRIC CIRCUIT ANALYSIS II

PROGRAMME : BEF
 COURSE CODE : BEF12503

Formulas :

$$\tau = RC$$

$$i(t) = I_o e^{-\frac{t}{RC}}$$

$$y = e^{\frac{t}{\tau}}$$

$$\ln(y) = \ln\left(e^{\frac{t}{\tau}}\right)$$

$$\frac{t}{\tau} = \ln(y)$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$$

$$\alpha = \frac{R}{2L}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$v(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t}, \text{ Over damped}$$

$$v(t) = V_s + (A_1 t + A_2) e^{-\alpha t}, \text{ Critically damped}$$

$$v(t) = V_s + e^{-\alpha t} (A_1 \cos \omega_d t + A_2 \sin \omega_d t), \text{ Under damped}$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$