

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2011/2012**

COURSE NAME : ELECTRICAL TECHNOLOGY

COURSE CODE : BEE 10403/BEE 1223/BEX10303

PROGRAMME : BEE

EXAMINATION DATE : JUNE 2012

DURATION : 2 HOURS 30 MINUTES

INSTRUCTION : ANSWER ALL QUESTIONS IN PART A
ANSWER TWO QUESTIONS IN PART B

THIS PAPER CONSISTS OF EIGHT (8) PAGES

CONFIDENTIAL

PART A

Q1 (a) In a linear circuit, the voltage source is

$$v_s = 12\sin(10^3t - 24^\circ)\text{V}$$

- (i) What is the angular frequency of the voltage? (1 mark)
 - (ii) What is the frequency of the source? (1 mark)
 - (iii) Find the period of the voltage. (1 mark)
 - (iv) Express v_s in cosine form. (1 mark)
 - (v) Determine v_s at $t = 2.5$ ms. (3 marks)
- (b) Let $\mathbf{X} = 8\angle 40^\circ$ and $\mathbf{Y} = 10\angle -30^\circ$. Evaluate $(\mathbf{X} + \mathbf{Y})/\mathbf{X}$ and express the result in polar form. (4 marks)
- (c) Transform the following sinusoids to phasors.
- (i) $-10\cos(4t + 75^\circ)$ (2 marks)
 - (ii) $5\sin(20t - 10^\circ)$ (2 marks)

- Q2** (a) Name **TWO (2)** differences between time domain, $v(t)$, and phasor domain representation, V , of a signal. (4 marks)
- (b) Given the RLC circuit shown in **Figure Q2(b)**, determine the
- (i) total load impedance (3 marks)
 - (ii) current, I , flowing in the circuit (2 marks)
 - (iii) voltage drop across the inductor, L (4 marks)
 - (iv) phase angle difference between V_s and I (2 marks)

Q3 A coil of 800 turns is uniformly wound on an iron ring of mean circumference 45 cm and uniform cross-sectional area 5 cm^2 , and has a resistance of 25Ω . The relative permeability of the iron at the working flux density is 800. If the coil is connected to a 20 V d.c supply, identify:

- (a) the m.m.f (3 marks)
- (b) the magnetic field strength (4 marks)
- (c) the magnetic flux in the iron (4 marks)
- (d) the reluctance of the iron ring. (4 marks)

- Q4**
- (a) What is quantization of charge? (2 marks)
 - (b) Find the number of electrons that constitute one coulomb. (2 marks)
 - (c) Define dielectric constant. (2 marks)
 - (d) The plates of a capacitor of capacitance C are charged to a potential V . Write an expression for the energy stored in a capacitor. (2 marks)
 - (d) Refer to the circuit shown in **Figure Q4(e)**, determine:
 - (i) the total capacitance. (1 mark)
 - (ii) the voltage across each capacitor (2 marks)
 - (ii) the energy in each capacitor. (4 marks)

PART B

- Q5** (a) Mention the difference between the balanced polyphase system and unbalanced polyphase system. (4 marks)
- (b) A balanced 120 V-rms wye-connected three-phase source with positive phase sequence is connected to two balanced three-phase loads connected in parallel. Load #1 is wye-connected with $Z_Y = (30 + j40) \Omega$ and Load #2 is delta-connected with $Z_\Delta = (60 - j45) \Omega$. The line impedance per phase is $Z_l = (2 + j4) \Omega$ as shown in **Figure Q5(b)**. Given the phase angle of line to neutral voltage at the source terminal, V_{an} , is zero, determine:
- (i) the total impedance of the circuit (3 marks)
 - (ii) the line current, I_a (3 marks)
 - (iii) the line-to-neutral voltage across the parallel load, V_{AN} (4 marks)
 - (iv) the total real and reactive power drawn from the source (6 marks)
- Q6** (a) Describe the properties of an ideal transformer and draw the elementary model of a transformer. (5 marks)
- (b) An ideal transformer supplies a power of 400 W to a 250 Ω load when the primary winding is connected to a 240 V supply. Determine the:
- (i) voltage across the load (3 marks)
 - (ii) turns ratio (3 marks)
 - (iii) primary current (3 marks)
- (c) A transformer has a rated output of 200 kVA at a power factor of 0.8. Determine the:
- (i) rated power output (3 marks)
 - (ii) reactive power. (3 marks)

- Q7** (a) For a DC motor,
- (i) Explain a basic DC motor operation for a complete revolution shown in **Figure Q7(a)** (4 marks)
 - (ii) List down or draw all of the possible losses in a DC motor (4 marks)
 - (iii) Explain the difference between a shunt DC motor and a series DC motor. (2 marks)
- (b) A 200 V shunt DC motor shown in **Figure Q7(b)** has an armature resistance of 0.2Ω and a field resistance of 100Ω . During no load, the line current draws 5.0 A while the motor is running at 2000 rpm.
- (i) At full load, the line current is 40 A, calculate the full load speed. (5 marks)
 - (ii) At full load condition, if the field resistance is increased to 150Ω , calculate the new full load speed. Assume the line current has not changed. (5 marks)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2011/2012

PROGRAMME : BEE

COURSE NAME : ELECTRICAL TECHNOLOGY

CODE : BEE 10403/BEE 1223/BEX10303

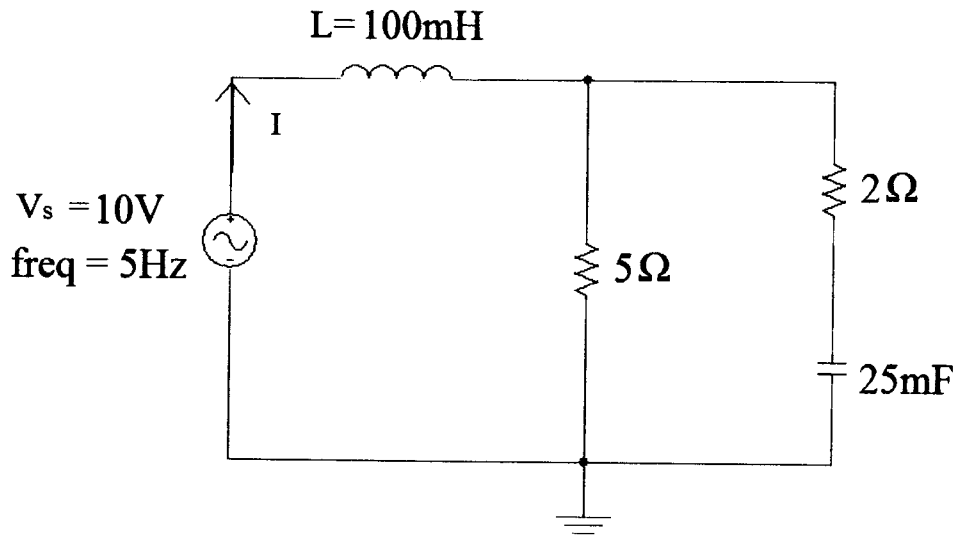


FIGURE Q2(b)

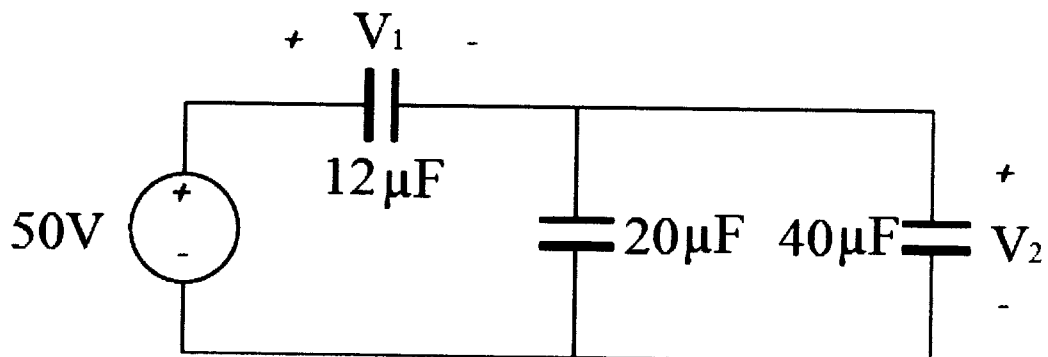


FIGURE Q4(e)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2011/2012

PROGRAMME : BEE

COURSE NAME : ELECTRICAL TECHNOLOGY

CODE : BEE 10403/BEE 1223/BEX10303

120 V-rms
wye-
connected
three-phase
source

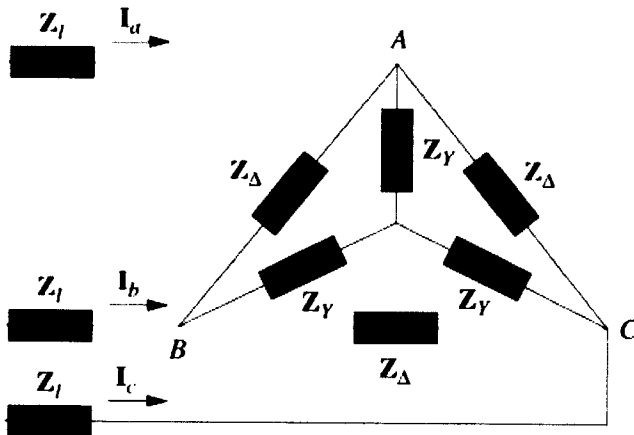


FIGURE Q5(b)

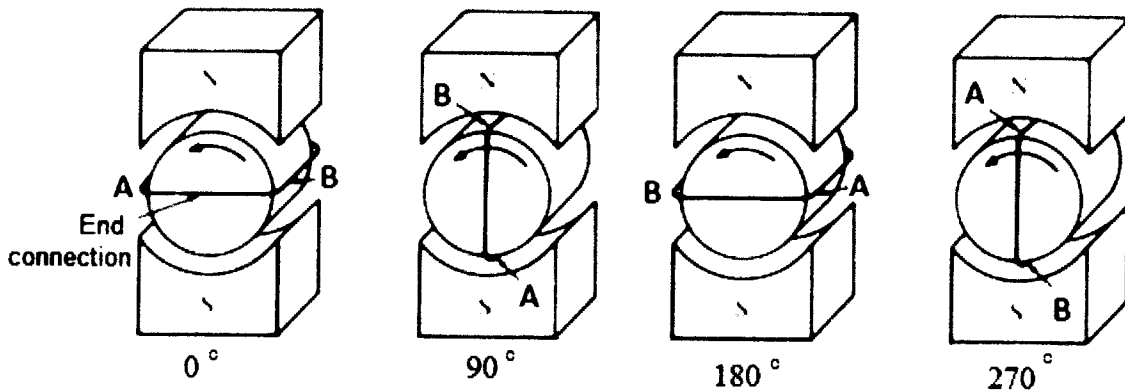


FIGURE Q7(a)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2011/2012

PROGRAMME : BEE

COURSE NAME : ELECTRICAL TECHNOLOGY

CODE : BEE 10403/BEE 1223/BEX10303

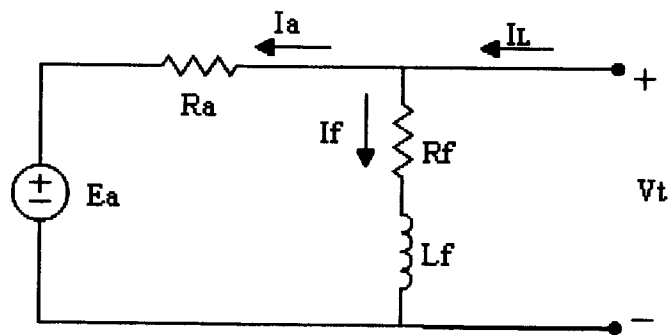


FIGURE Q7(b)