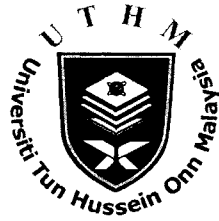


CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2011/2012**

COURSE NAME : ELECTRONIC DEVICES AND APPLICATION
COURSE CODE : BEE 2273 / BEX 21003
PROGRAMME : BEE
EXAMINATION DATE : JUNE 2012
DURATION : 2 HOURS 30 MINUTES
INSTRUCTION : ANSWER **FIVE (5)** QUESTIONS ONLY

THIS PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

- Q1** (a) Explain with the aid of a figure the internal block diagram of an operational amplifier. (5 marks)
- (b) Operational amplifier is used to perform mathematical operation. **Figure Q1(b)(i)** shows one of the applications of operational-amplifier. The input waveforms of V_1 (CH1) and V_2 (CH2) are shown in **Figure Q1(b)(ii)**.
- (i) Determine the expression of output, V_o in terms of V_1 and V_2 . (6 marks)
- (ii) Based on the answer in part Q1(b)(i), name the operation performed by this circuit. (1 mark)
- (iii) Based on the inputs given, draw the output waveform generated from this circuit if the resistor, R is equal to $2\text{ k}\Omega$. Show all the steps involved. (8 marks)
- Q2** (a) The circuit in **Figure Q2(a)**, is an integrator circuit.
- (i) Determine the rate of change of the output voltage in response to the input square wave, when output voltage is initially zero and the pulse width is $100\ \mu\text{s}$. (6 marks)
- (ii) Determine the output and draw the waveform. (4 marks)
- (b) Determine the output of a differentiator for the triangular wave input as shown in **Figure Q2(b)**. (10 marks)
- Q3** (a) The circuit in **Figure Q3(a)** is a type of oscillator used to perform the switching function.
- (i) Name the oscillator type and explain the operation of the circuit. (8 marks)
- (ii) Draw the output response of the integrator, (V_o) if the output of the comparator is a rectangular waveform. (2 marks)

- (b) The circuit in **Figure Q3(b)** is a basic FET Colpitts oscillator.
- (i) Design a tank circuit for the oscillator which can be loaded to a point where Q (quality factor) is equal to 4 (the oscillator has frequency of 7.18 kHz, $C_1 = 0.1 \mu\text{F}$ and $C_T = 0.091 \mu\text{F}$).
(8 marks)
 - (ii) Using the value of C_1 , C_2 and L , calculate the new frequency produced by the oscillator if it is loaded to a point where $Q = 1$.
(2 marks)

- Q4** (a) A 555 timer can be configured to run in the astable mode.
- (i) Draw and label clearly the circuit for astable mode multivibrator using a 555 timer, resistors, R_1 and R_2 , and capacitors C_{ext} and C_1 .
(2 marks)
 - (ii) Design an astable multivibrator which has duty cycle of 60% and output frequency of 5 kHz using C_{ext} value of $0.022 \mu\text{F}$ and C_1 value of $0.01 \mu\text{F}$.
(9 marks)
 - (iii) Explain how the astable multivibrator can be set to become a Voltage-controlled oscillator (VCO) and how the output frequency is varied.
(4 marks)
- (b) **Figure 4(b)** is the phase-shift oscillator circuit. Determine the value of R_f necessary for the circuit to operate as an oscillator and calculate the frequency of oscillation. Given that $R_1 = R_2 = R_3 = 5 \text{ k}\Omega$ and $C_1 = C_2 = R_3 = 0.01 \mu\text{F}$.
(5 marks)

- Q5** (a) **Figure Q5(a)** is the shunt regulator using the combination of an Op-amp and a bipolar junction transistor.
- (i) Calculate the power rating that R_1 should have if the maximum input voltage, V_{in} is 12 V. (given $R_1 = 20 \Omega$, $R_2 = 1.2 \text{ k}\Omega$, $R_3 = 10 \text{ k}\Omega$ and $R_4 = 10 \text{ k}\Omega$).
(5 marks)

- (ii) If the power rating of the regulator is 10 W, what is the new value of R_1 ? (given input voltage, $V_{in} = 12$ V, $R_2 = 1.2$ k Ω , $R_3 = 10$ k Ω and $R_4 = 10$ k Ω).
(5 marks)
- (i) Most of the regulators use some kind of excess current protection in the form of current limiting mechanism.
- (i) Draw and clearly label the series regulator with constant current limiting.
(4 marks)
- (ii) Referring to **Figure Q5(a)**, if the maximum current that the regulator can provide to load is 1 mA, what is the value of R_4 ?
(2 marks)
- (iii) Fold-back current limiting is also the current limiting mechanism. Draw and clearly label the series regulator with fold-back current limiting.
(4 marks)
- Q6** (a) With the help of waveform diagram, explain briefly the difference between Class A and Class C amplifiers.
(4 marks)
- (b) **Figure Q6(b)** is a power amplifier.
- (i) Determine the class of the amplifier.
(2 marks)
- (ii) Assume $\beta_1 = \beta_2 = \beta_3 = 200$ for all transistor, determine the voltage gain, A_v and power gain, A_p of the amplifier if the output is connected with 8 Ω load.
(14 marks)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II 2011/2012
 COURSE: ELECTRONIC DEVICES AND APPLICATION

PROGRAMME: BEE
 SUBJECT CODE: BEE2273/BEX21003


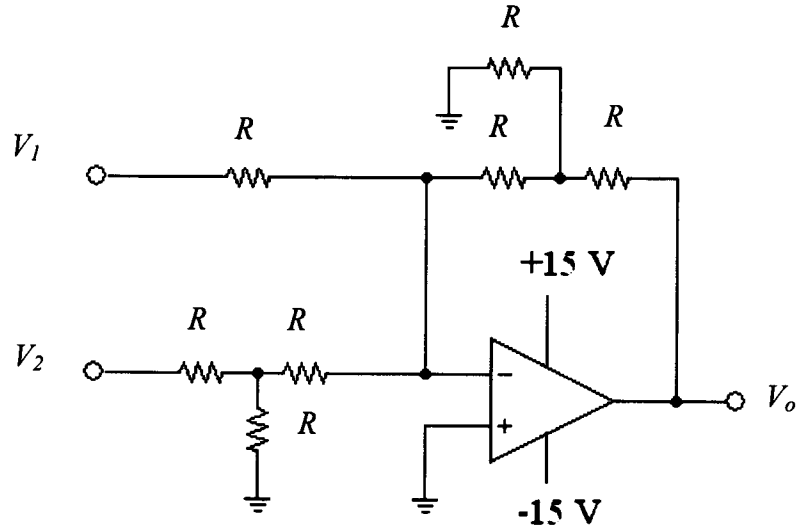


FIGURE Q1(b)(i)

Voltage

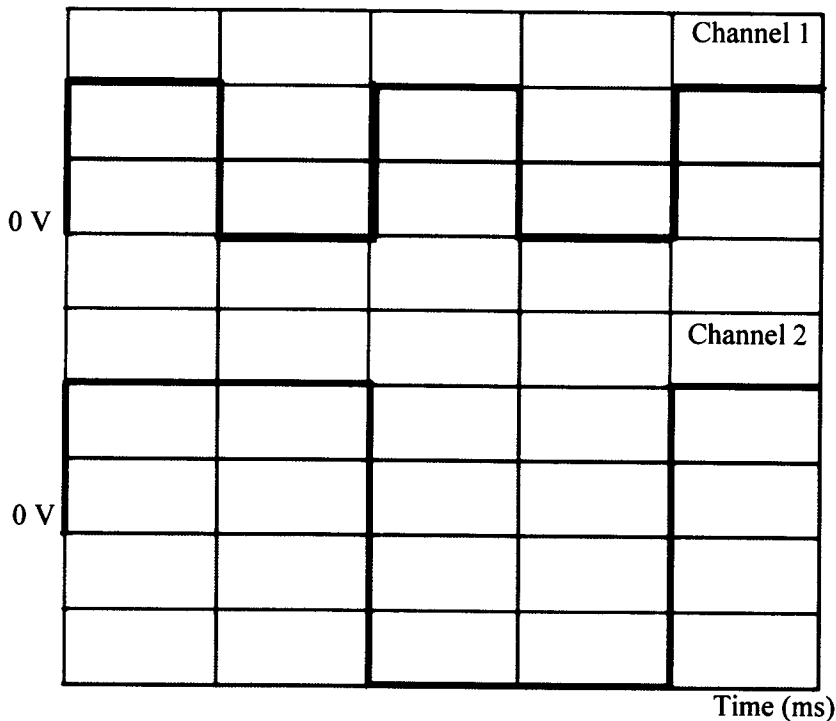

Channel/	CH1:1 V/div
Division	CH2: 0.5 V/div
<hr/>	
Time/	Division : 2.5 ms/div

FIGURE Q1(b)(ii)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II 2011/2012
COURSE: ELECTRONIC DEVICES AND APPLICATION

PROGRAMME: BEE
SUBJECT CODE: BEE2273/BEX21003

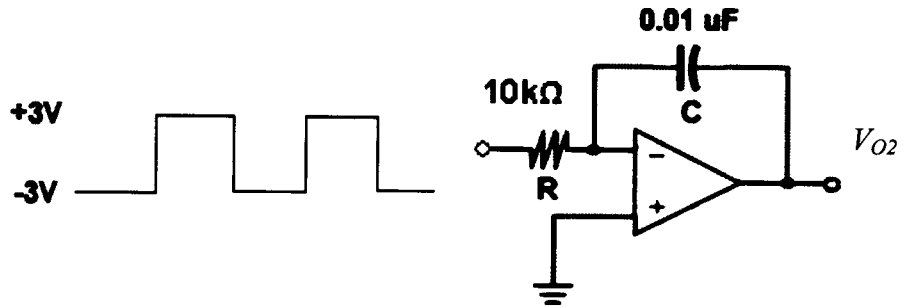


FIGURE Q2(a)

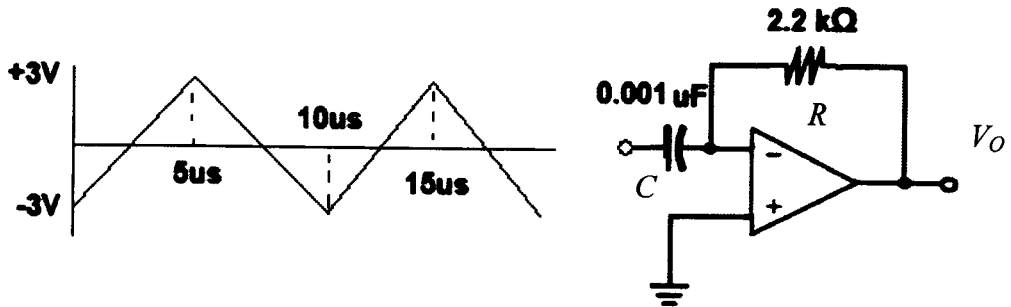


FIGURE Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II 2011/2012
 COURSE: ELECTRONIC DEVICES AND APPLICATION

PROGRAMME: BEE
 SUBJECT CODE: BEE2273/BEX21003

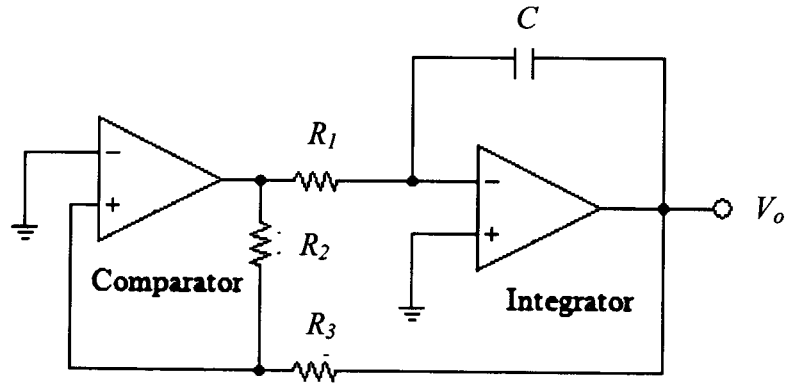


FIGURE Q3(a)

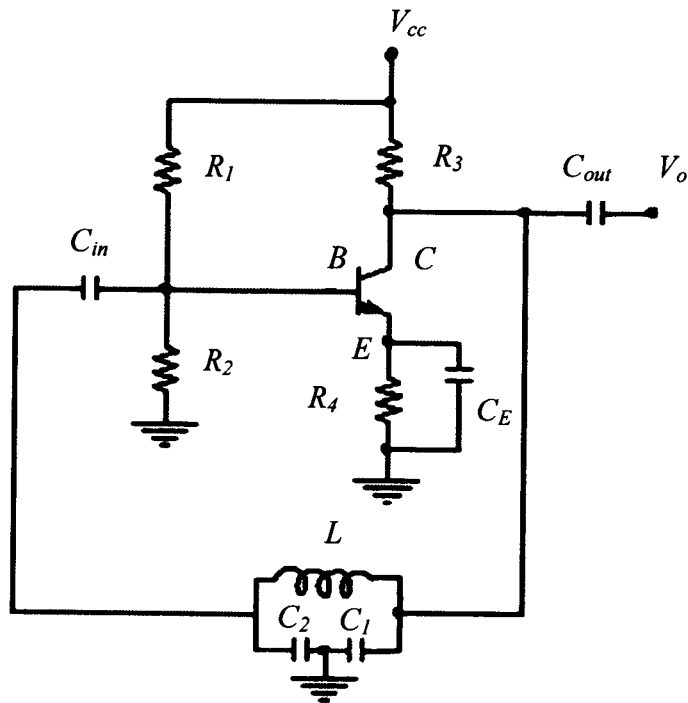


FIGURE Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II 2011/2012
 COURSE: ELECTRONIC DEVICES AND APPLICATION

PROGRAMME: BEE
 SUBJECT CODE: BEE2273/BEX21003

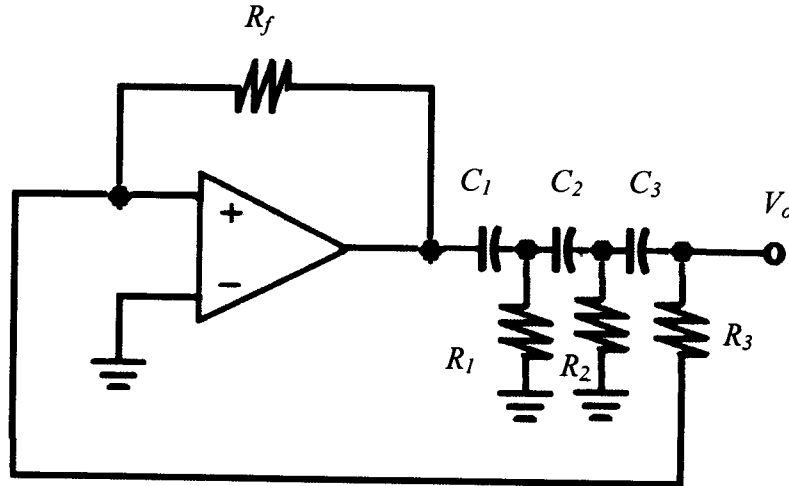


FIGURE Q4(b)

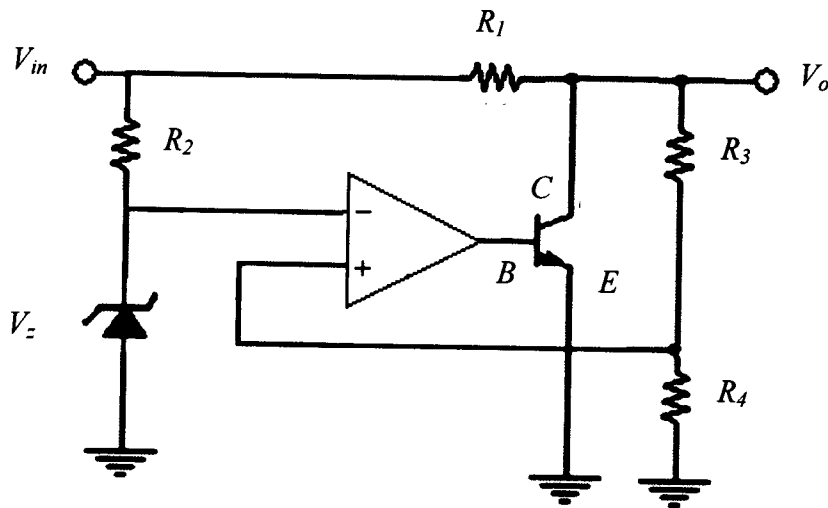


FIGURE Q5(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II 2011/2012
 COURSE: ELECTRONIC DEVICES AND APPLICATION

PROGRAMME: BEE
 SUBJECT CODE: BEE2273/BEX21003

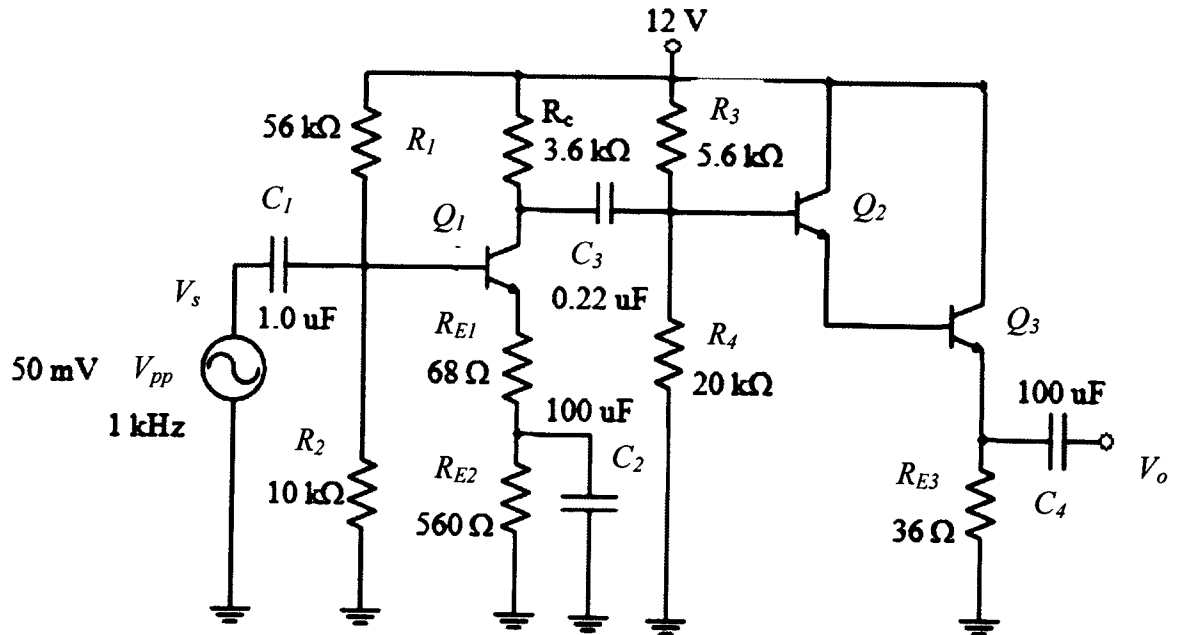


FIGURE Q6(b)