



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : ANALOG ELECTRONICS/
ELECTRONIC PRINCIPLES

COURSE CODE : BEL 10203/ BEE 2113/ BEX 20603

PROGRAMME : BEB/ BEH/ BED/ BEU/BEE

EXAMINATION DATE : JUNE 2013

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

- Q1** (a) (i) Diode is a structure constructed from extrinsic semiconductor materials. Name the two types of extrinsic semiconductor materials used in constructing the diode. (1 mark)
- (ii) Explain briefly the action that takes place when the two materials in part **Q1(a)(i)** are put closely to each other. (4 marks)
- (b) A bridge rectifier circuit in **Figure Q1(b)** is connected to a step down transformer with the turns ratio of 5:1. Sketch and label the input voltage, V_{in} and output voltage, V_o of the rectifier. Assume the diodes are Silicon. (5 marks)
- (c) The circuit in **Figure Q1(c)** is used to drive an electrical appliance, represented by a load, R_L . For the zener diode, its breakdown voltage is 8.2 V. The voltage of unregulated power supply, V_O is 15 V.
- (i) Calculate the current across zener diode, I_Z . (3 marks)
- (ii) Calculate the zener power, P_Z and power dissipation of R_S , P_{R_S} . (2 marks)
- (iii) Find the no load zener power, $P_{Z(NL)}$ (2 marks)
- (iv) In order to protect the zener diode used in this regulator, the full-load zener current is set to be 5 times of its knee current. If its knee current is 1 mA, determine the minimum recommended load resistance. (3 marks)
- Q2** (a) (i) By using the characteristics of **Figure Q2(a)**, find all resistors values for the common emitter BJT amplifier circuit using voltage divider bias configuration for *npn* silicon. The voltage at the emitter of the transistor (V_E) is to be one fifth of the supply voltage. Assume $\beta R_E \geq 10R_2$. (10 marks)
- (ii) Hence, construct the circuit having a bypass capacitor, C_E configuration. (2 marks)

- (b) (i) If a $1\text{ k}\Omega$ resistor is connected at the output as a load, R_L , draw the AC equivalent circuit and determine the input and output impedances, Z_i and Z_o .
(6 marks)
- (ii) Hence, show that the loaded voltage gain, $A_{V(WL)}$ may be written as (assuming the transistor AC output resistance $r_o = \infty$):

$$A_{V(WL)} = \frac{V_o}{V_i} \approx -\frac{R_C // R_L}{r_e}$$

Evaluate this expression.

(2 marks)

- Q3** (a) Name two parameters of an E-MOSFET that are not specified for D-MOSFETs.
(2 marks)
- (b) For the n -channel D-MOSFET in **Figure Q3(b)**, the $I_{DSS} = 20\text{ mA}$, $V_p = -2\text{ V}$ and $y_{os} = 10\text{ }\mu\text{S}$:
- (i) find the quiescent values, I_{DQ} and V_{GSQ} by using the graphical method.
(7 marks)
- (ii) determine the transconductance, g_m
(2 marks)
- (iii) draw the AC equivalent circuit and calculate the input impedance, Z_i , output impedance, Z_o and voltage gain, A_v .
(7 marks)
- (iv) if a $10\text{ k}\Omega$ resistor is connected at the output as a load, R_L , calculate the voltage gain with load, $A_{v(WL)}$.
(2 marks)

- Q4** (a) **Figure Q4(a)** is an amplifier circuit that only amplifies the signals of specified frequencies. Assume that the BJT transistor has an infinite value of AC collector resistance, r_o (or r_c):
- (i) calculate the mid-band gain of this amplifier.
(4 marks)
- (ii) draw the low frequency AC equivalent circuit and determine the dominant low cut-off frequency.
(7 marks)

- (iii) draw the high frequency AC equivalent circuit and determine the dominant high cut-off frequency. (6 marks)
- (iv) Sketch the normalised magnitude response of this filter. Clearly indicate the break frequencies and bandwidth in the diagram. (3 marks)

Q5 (a) For the basic Class B push pull amplifier in **Figure Q5(a)**:

- (i) state the condition of upper and lower transistor (1 mark)
- (ii) calculate the current, I and V_o and sketch the input and output voltage waveform. State clearly any assumption made in your calculations. (5 marks)
- (iii) calculate the efficiency, η (4 marks)
- (iv) determine the power dissipated by each transistor, P_Q . (2 marks)

(b) Compute the values of R_C , R_E and V_{CC} of a basic differential amplifier in **Figure Q5(b)** so that it can produce a differential gain, A_d of 127, with an $I_{CQ} = 1.3$ mA. Assume $V_{CE} = \frac{1}{2}V_{CC}$. (8 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II / 2012/2013
 COURSE: ANALOG ELECTRONICS/
 ELECTRONIC PRINCIPLES

PROGRAMME: BEB/ BEH/ BED/ BEU/ BEE
 COURSE CODE: BEL10203/BEE2113/BEX20603

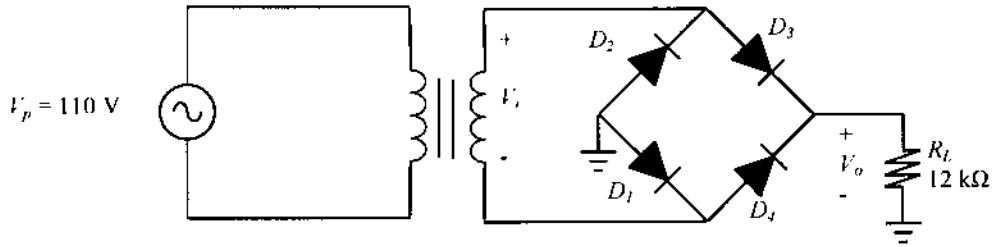


FIGURE Q1(b)

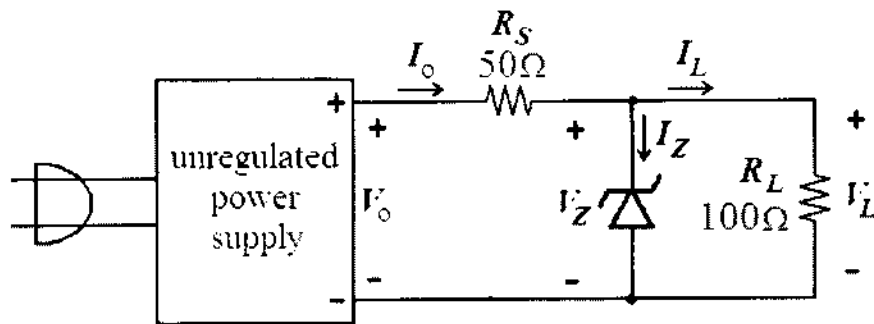


FIGURE Q1(c)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II / 2012/2013
 COURSE: ANALOG ELECTRONICS/
 ELECTRONIC PRINCIPLES

PROGRAMME: BEB/ BEH/ BED/ BEU/ BEE
 COURSE CODE: BEL10203/BEE2113/BEX20603

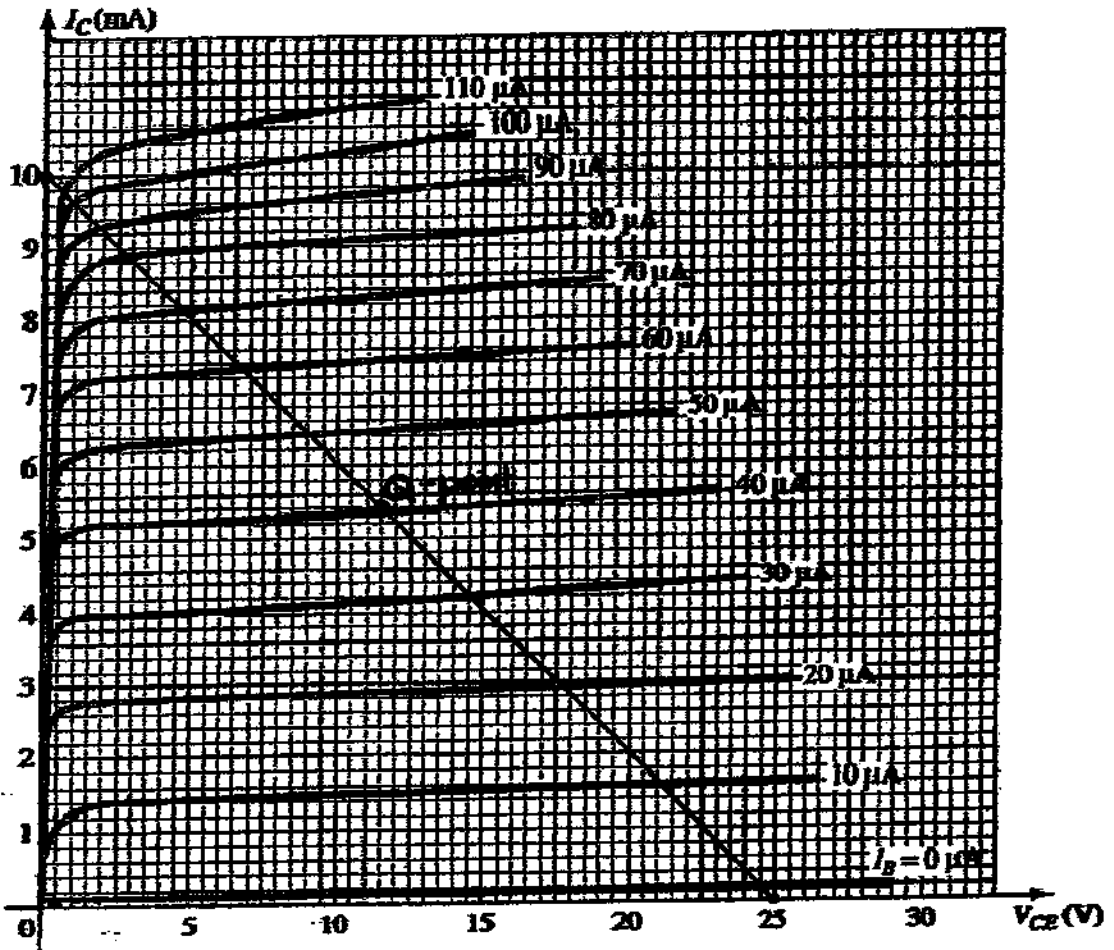


FIGURE 02(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II / 2012/2013
 COURSE: ANALOG ELECTRONICS/
 ELECTRONIC PRINCIPLES

PROGRAMME: BEB/ BEH/ BED/ BEU/ BEE
 COURSE CODE: BEL10203/BEE2113/BEX20603

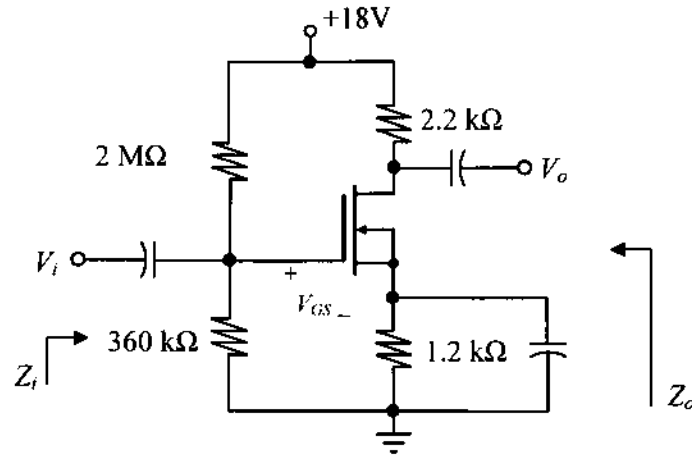


FIGURE Q3(b)

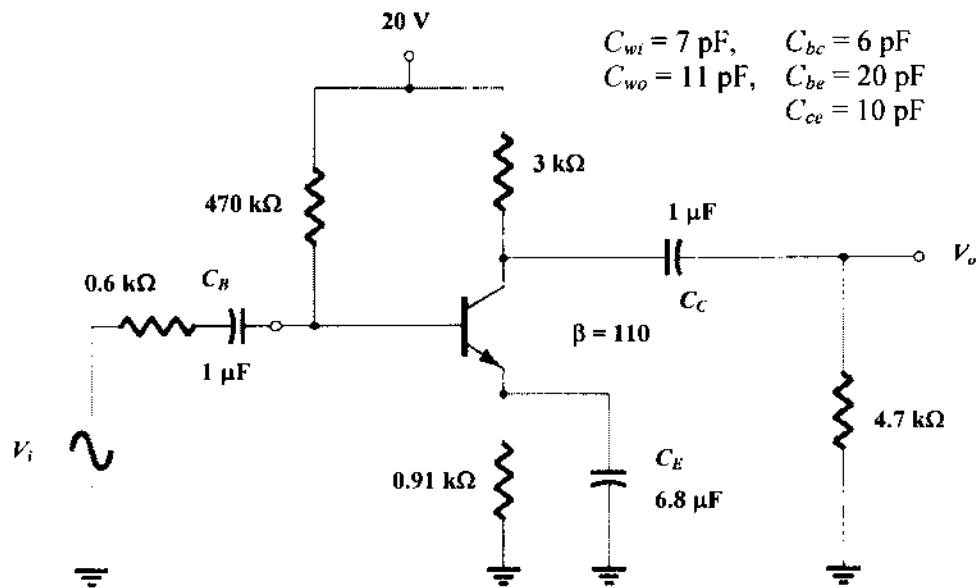


FIGURE Q4(a)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II / 2012/2013
 COURSE: ANALOG ELECTRONICS/
 ELECTRONIC PRINCIPLES

PROGRAMME: BEB/ BE11/ BED/ BEU/ BEE
 COURSE CODE: BEL10203/BEE2113/BEX20603

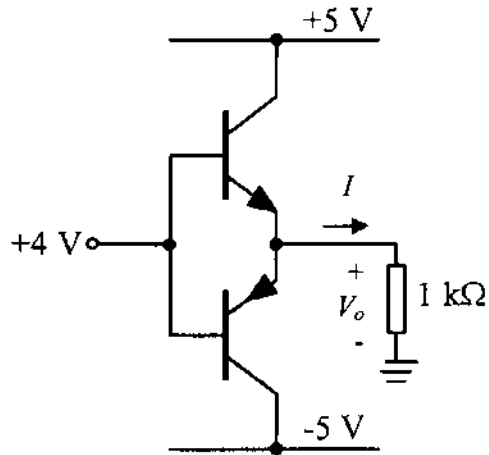


FIGURE Q5(a)

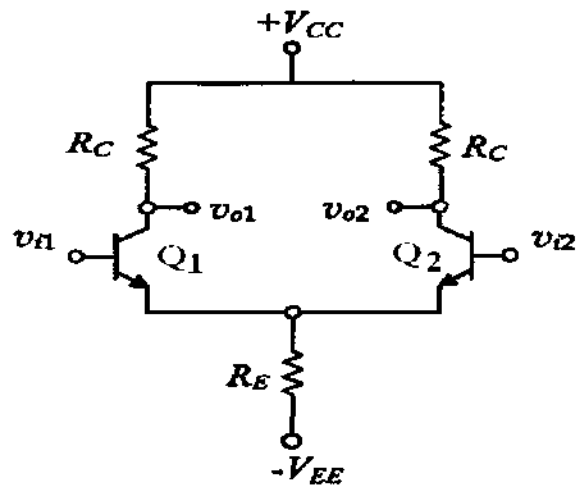


FIGURE Q5(b)