

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

**COURSE NAME : ELECTRONIC CIRCUITS ANALYSIS
AND DESIGN**

COURSE CODE : BEL 30403

PROGRAMME : BED / BEU

EXAMINATION DATE : JUNE 2013

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

CONFIDENTIAL

- Q1 (a)** State the advantages of operational amplifier with feedback network. (4 marks)
- (b)** Based on input signal V_i in **Figure Q1 (b)(i)**, analyze and sketch the waveforms of V_{O1} , V_{O2} and V_{O3} , in **Figure Q1 (b)(ii)**. Assuming the initial voltage across the capacitor is zero. (16 marks)

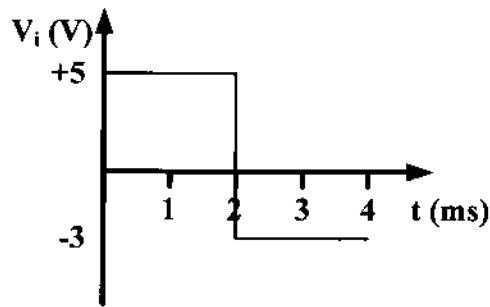


FIGURE Q1 (b)(i)

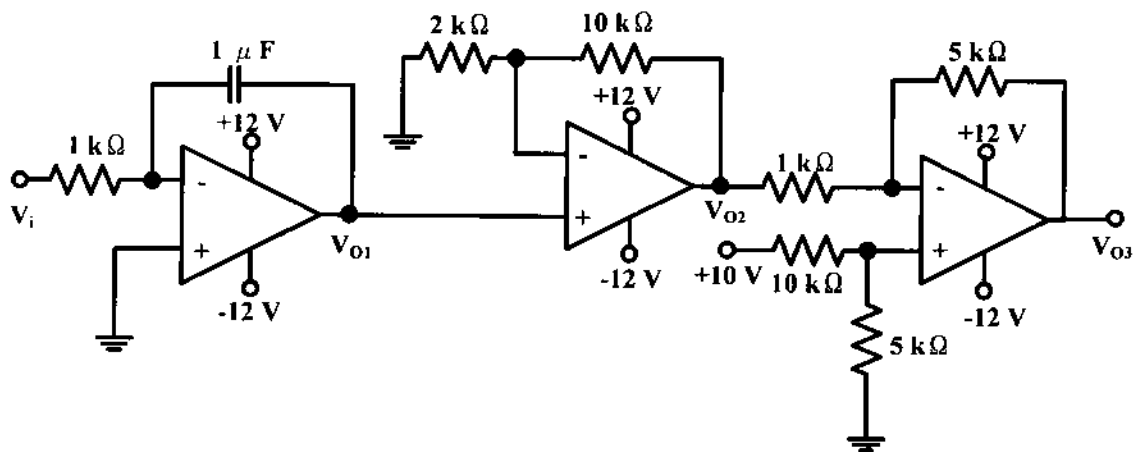


FIGURE Q1 (b)(ii)

- Q2 (a)** Explain the pass-band, transition-band and stop-band in frequency response of filter with the aid of diagram. (4 marks)
- (b) Figure Q2 (b)** shows a third-order high-pass filter circuit. For this circuit,
- (i) Calculate the cut-off frequency of this filter. (2 marks)
 - (ii) Determine the roll-off rate and gain (in dB) of this filter. (6 marks)
 - (iii) Sketch and label completely the frequency response of this filter. (3 marks)
 - (iv) Propose the alternative design of filter in **Figure Q2 (b)** using Sallen-Key high-pass filter. Justify the advantages of the design. (5 marks)

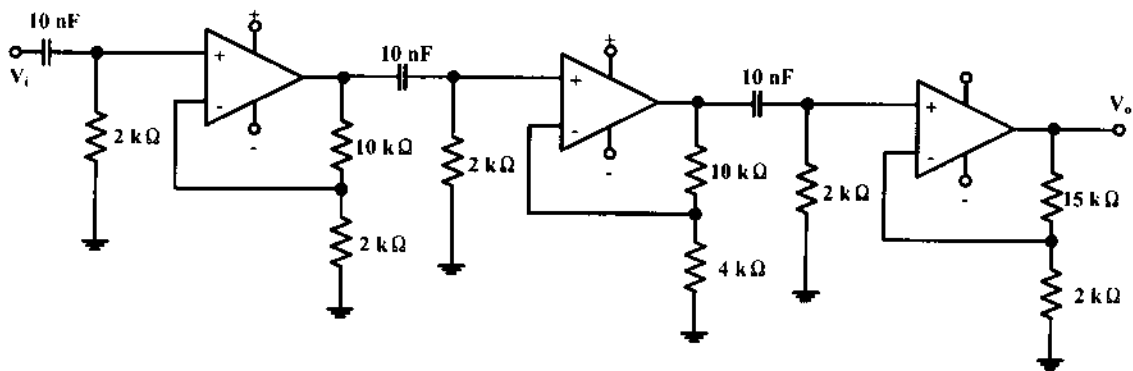


FIGURE Q2 (b)

- Q3 (a)** Systems without feedback have a gain of 75 dB, low cut-off frequency of 20 kHz and high cut-off frequency of 75 kHz. A negative feedback network with feedback factor $\beta = 0.0025$ is connecting to the system to increase the bandwidth of frequency. Analyze and sketch the frequency response of the system with feedback network.

(8 marks)

- (b)** Figure Q3 (a) shows a voltage controlled oscillator (VCO) using 555 timers. Illustrate the output waveform, V_o at pin 3 and the capacitor voltage, V_{C1} at pin 2, if the potentiometer R_5 is connected at point A. Show all calculation. Assume the diode, D_1 is ideal.

(12 marks)

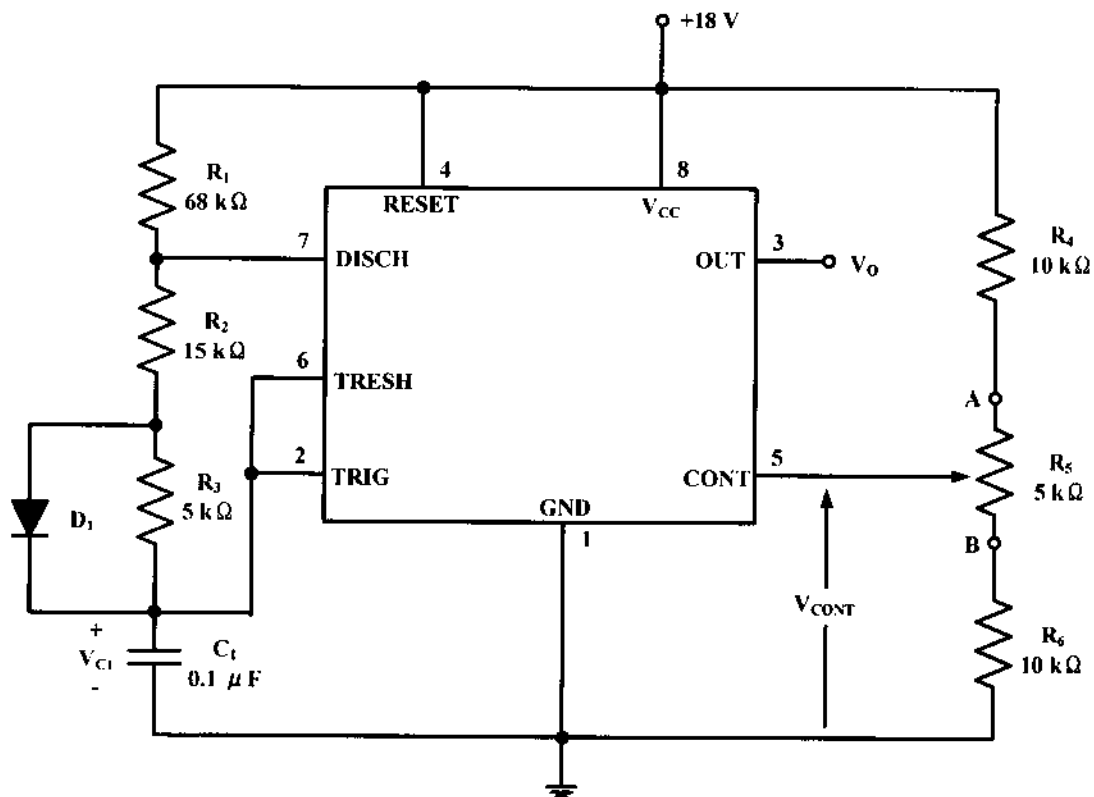


FIGURE Q3 (a)

Q4 (a) An oscillator circuit in **Figure Q4 (a)** will maintain its oscillation when $A\beta = 1$.

- (i) Briefly explain how the circuit can be acts as an oscillator. State the name of the oscillator. (4 marks)
- (ii) Calculate R_2 if the oscillation frequency of the circuit, $f_o = 13\text{kHz}$. (4 marks)
- (iii) Derive the relationship between R_a and R_b so that this circuit will sustain its oscillation. (2 marks)

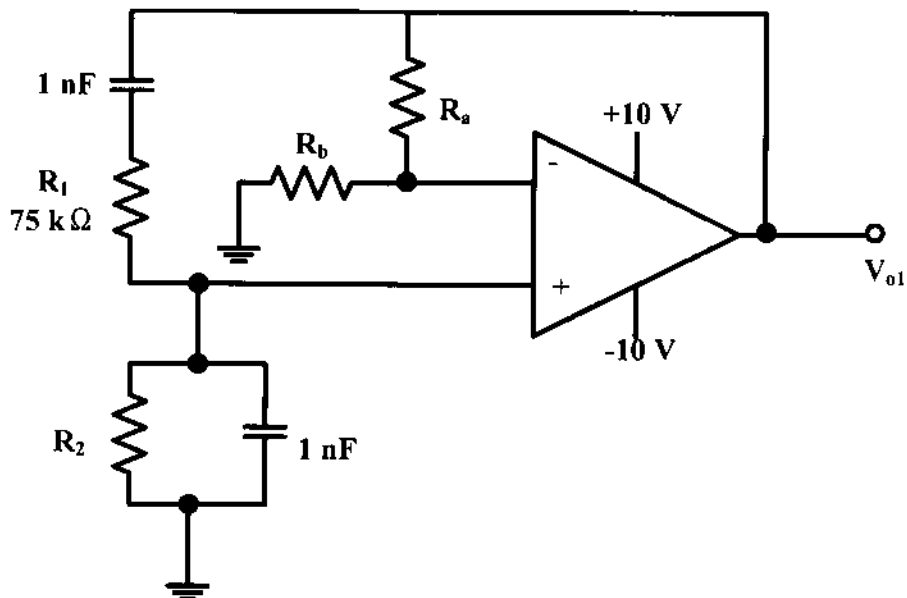


FIGURE Q4 (a)

- (b) The output V_{o1} in **Figure Q4 (a)** is now connected to the input V_i in **Figure Q4 (b)**. Analyze the output V_{o2} . Show all calculation. Assuming breakdown voltage of Z_1 and Z_2 are 4.7 V.

(10 marks)

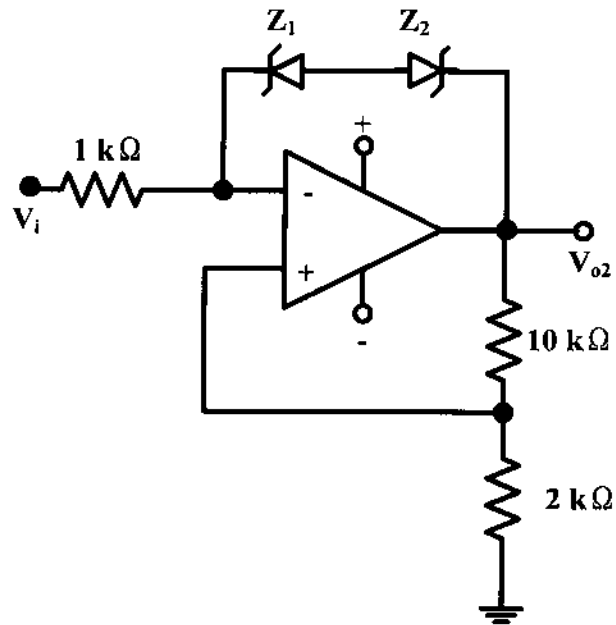


FIGURE Q4 (b)

Q5 Figure Q5 shows the circuit diagram for a simple DC power supply.

- (a) Analyze the output waveform if a load current, I_L is 0.2A and voltage across R_L , V_L is 12V. Assuming a ripple factor across the load is 15%. Show all calculation. (9 marks)
- (b) Calculate the number of primary winding, N_P and smoothing capacitance C if AC source is 110 V_{rms} operating at 50 Hz. (6 marks)
- (c) An additional RC filter is connected to the circuit in **Figure Q5** to reduce the ripple voltage. Analyze the new ripple factor (%) if the value R and C are 50Ω and $1000 \mu F$, respectively. (5 marks)

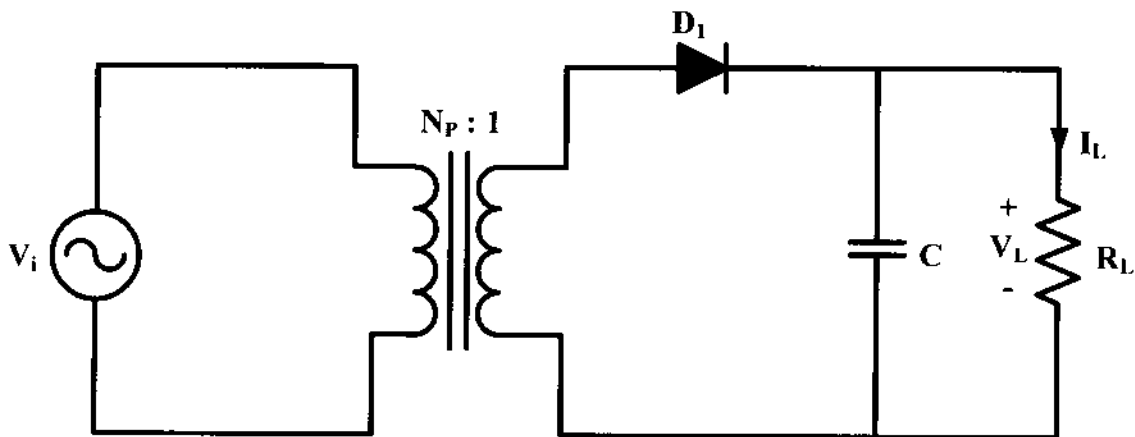


FIGURE Q5

- END OF QUESTION -