



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : POWER ELECTRONICS
COURSE CODE : BEF 34503 / BEX 42303 / BEE 4113
PROGRAMME : BEF / BEE
EXAMINATION DATE : JUNE 2013
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

- Q1** (a) List down four (4) function of diode. (4 marks)
- (b) List two (2) important device parameters that must be considered when selecting rectifier diode (2 marks)
- (c) Define peak-inverse-voltage (PIV) in rectifier circuits. (2 marks)
- (d) Sketch the symbol and discuss the features of the following power electronic devices. (6 marks)
- (i) Metal Oxide Semiconductor Field-Effect Transistor (MOSFET)
 - (ii) Silicon Controlled Rectifier (SCR)
- (e) Figure Q1(e) shows the power electronic switch signal and output waveforms that operated at 20 kHz. V_d and I_o are the voltage and current across the output during on and off switch signal. The output power dissipated after the rise time is 3 W where the rise time, t_r is 50 ns. The total power dissipated during switch off (T_{off}) is 9.75 W. If the current flowing through the switch is 4 A during on signal, formulate: (11 marks)
- (i) the turn-off interval time, t_{off} , of the switch
 - (ii) the average switching power loss
 - (iii) the current rise time, t_r , if the turn-off crossover interval $t_{c(off)} = 300$ ns. Assume the rise time is equal to fall time
- Q2** (a) List four (4) advantages of bridge rectifier (4 marks)
- (b) A center-tapped transformer uncontrolled rectifier is shown in Figure Q2(b) has an ac input source of $V_s = 120 \sin \omega t$ at 60 Hz and purely resistive load of $R = 30 \Omega$. (4 marks)
- (i) Sketch the waveform of output voltage, V_o , output current, I_o and voltage across diode D_1 and D_2 against ωt (magnitude of each waveform should be note clearly).
- (c) Both of the diode D_1 and D_2 in Figure Q2(b) are then replaced by thyristor T_1 and T_2 and the other parameters are remaining the same. (17 marks)
- (i) Demonstrate the average output voltage, $V_{o,avg}$ across the load.
 - (ii) If the average output current, $I_{o,avg}$ is 2.25A. Formulate the firing angle, α of the thyristor.
 - (iii) Formulate the rms output voltage, $V_{o,rms}$.
 - (iv) Calculate peak-inverse-voltage (PIV) of thyristor T_2 .
 - (v) Calculate the power absorbed by the load.
 - (vi) Calculate the power factor of the circuit.
 - (vii) Calculate the efficiency of the circuit.

- Q3 (a)** List the advantages and disadvantages of Pulse Width Modulation (PWM) in power electronics applications.

(4 marks)

- (b) The full-bridge inverter with DC input voltage of 240V, load resistor and inductor of 10Ω and 20mH respectively and operated at 60 Hz frequency. Formulate:
- (i) the amplitude of the Fourier series terms for the square-wave load voltage
 - (ii) the amplitude of the Fourier series terms for load current.
 - (iii) power absorbed by the load.
 - (iv) the THD of the load voltage square-wave inverter.
 - (v) the THD of the load current for square-wave inverter.
 - (vi) Design the inverter which produces THD less than 10% and calculate the voltage amplitude at the fundamental frequency, the required DC input supply and the new THD of the current.

(21 marks)

- Q4 (a)** Explain briefly the operation of the converter in Continuous Current Mode (CCM) and Discontinuous Current Mode (DCM).

(6 marks)

- (b) A buck converter has the following parameters: $V_s = 12\text{ V}$, $D = 0.6$, $L = 150\text{ mH}$, $C = 150\text{ }\mu\text{F}$ and $R = 10\text{ }\Omega$. The switching frequency is 40 kHz.
- (i) Sketch the equivalent circuit of the buck converter.
 - (ii) Calculate the output voltage, V_o .
 - (iii) Derive the maximum and minimum inductor currents.
 - (iv) Calculate the maximum and minimum inductor currents.
 - (v) Calculate the output voltage ripple.
 - (vi) Sketch the waveforms of inductor voltage, inductor current and capacitor current for the given buck converter circuit.
 - (vii) Based on the calculations in Q4(c)(iv), give your conclusion.

(19 marks)

- Q5** Two analysis to find the performance of the single-phase half-wave AC voltage controller as shown in Figure Q5 (b). The AC voltage controller has a parallel resistive loads of $R_1 = 4\Omega$ and $R_2 = 2\Omega$ respectively and the input voltage is $V_s = 200 V_{\text{rms}}$, 50 Hz. The first experiment is conducted with on-off control where the thyristor switch on is $n = 100$ cycles while the off is $m = 50$ cycles. The second experiment is conducted at delay angle of thyristor T1 when $\alpha = \pi/2$. Compares the performance of AC voltage controller for both experiments in term of
- (i) the rms output voltage
 - (ii) the input power factor (PF)
 - (iii) the average input current at thyristor
 - (iv) the average current flows in R_1 and R_2 .

(25 marks)

-END OF QUESTIONS-

FINAL EXAMINATION

SEMESTER/SESSION : II/2012/2013
 COURSE NAME : POWER ELECTRONICS

PROGRAMME : 3BEF/ 4BEE
 COURSE CODE : BEF 34503/
 BEX42303/
 BEE4113

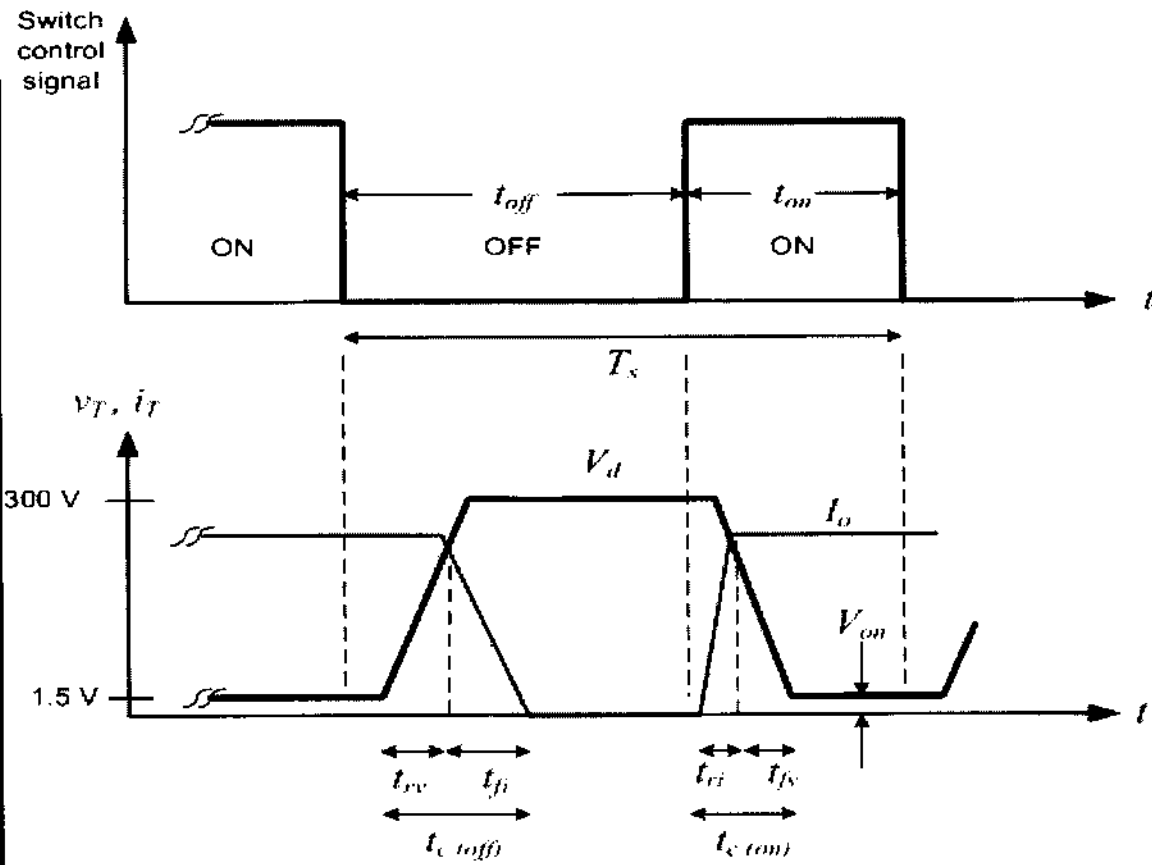


FIGURE Q1(e)

FINAL EXAMINATION

SEMESTER/SESSION : II/2012/2013
 COURSE NAME : POWER ELECTRONICS

PROGRAMME : 3BEF/ 4BEE
 COURSE CODE : BEF 34503/
 BEX42303/
 BEE4113

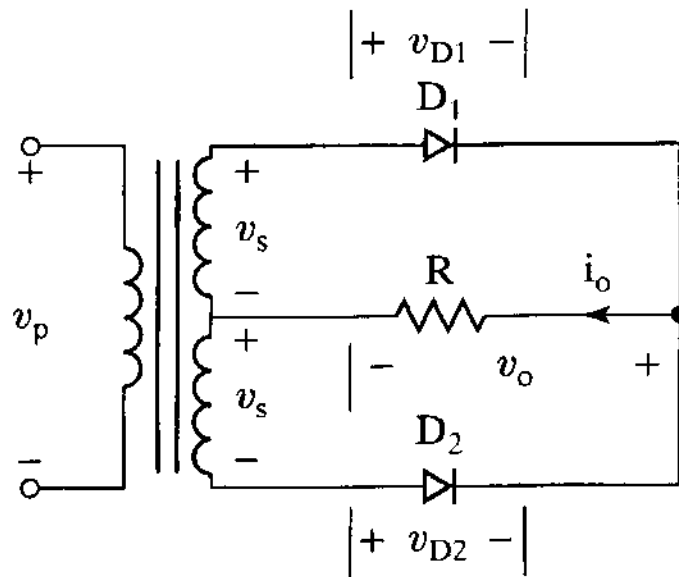


FIGURE Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION : II/2012/2013
 COURSE NAME : POWER ELECTRONICS

PROGRAMME : 3BEF/ 4BEE
 COURSE CODE : BEF 34503/
 BEX42303/
 BEE4113

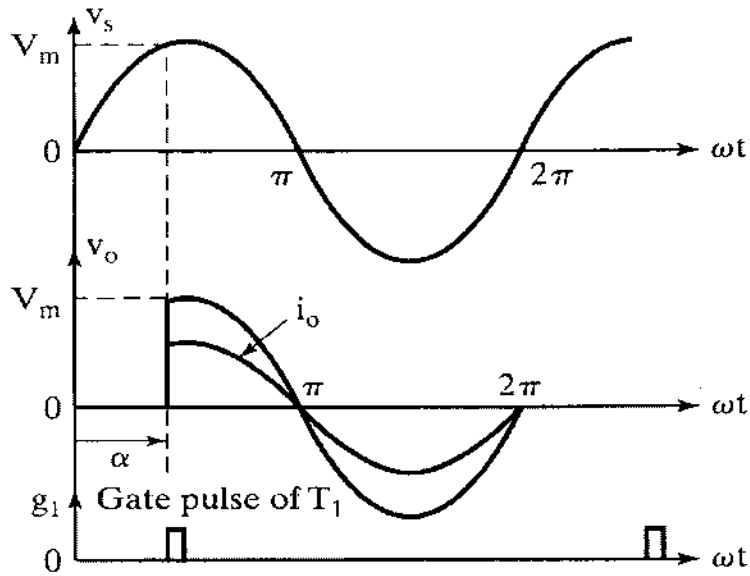
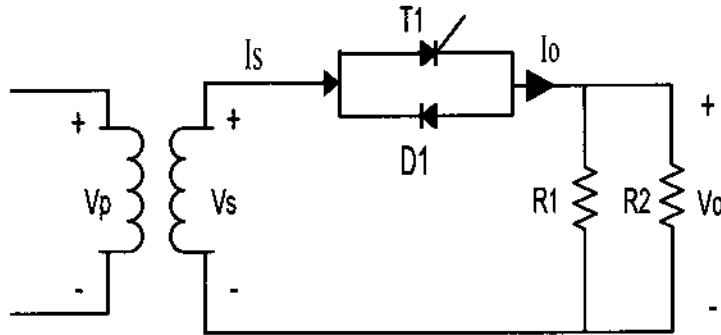


FIGURE Q5(b)