



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : TRANSFORM CIRCUIT ANALYSIS
COURSE CODE : BEF 22803
PROGRAMME : 2 BEF
EXAMINATION DATE : JUNE 2013
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

Q1 (a) Figure Q1(a) shows the output voltage at a converter. Write the equation using the step function formula for Figure Q1(a). (5 marks)

(b) Express the function of $f(t) = \sin(\omega t)$ is equal to $\frac{\omega}{s^2 + \omega^2}$. (5 marks)

(c) Figure Q1(c) shows the impulse response $h(t)$ and input signal $u(t)$. Calculate the convolution of the two signals $h(t)$ and $u(t)$. (10 marks)

Q2 (a) Solve the Laplace transform of each of the following function:

(i) $f(t) = 40e^{-8(t-3)}u(t-3)$.

(ii) $f(t) = (5t - 10)[u(t - 2) - u(t - 4)] + (30 - 5t)[u(t - 4) - u(t - 8)] + (5t - 50)[u(t - 8) - u(t - 10)]$.

(10 marks)

(b) Determine the inverse transform for the function,

$$V(s) = \frac{2}{s^3 + 12s^2 + 36s}$$

(10 marks)

Q3 (a) Figure Q3(a) shows the electrical circuit for a typical electric system.

- (i) Determine the transfer function for $H(s) = \frac{V_o(s)}{I_g(s)}$.
- (ii) Show the poles and zeros value for $H(s)$.
- (iii) Plot the locations of the poles and zeros in root locus plant and with stability explanation.

(10 marks)

(b) The numerical expression for a transfer function is

$$\frac{v_o}{v_i} = \frac{110s}{(s + 10)(s + 100)}$$

- (i) Draw the bode diagram for the amplitude for the transfer function given above.
- (ii) Calculate the amplitude of $v_o(t)$ in steady state if the $v_i(t) = 5\cos(500t + 15^\circ)$.

(10 marks)

Q4 (a) The Fourier transform of $f(t)$ is given by,

$$F(\omega) = 0, \quad -\infty \leq \omega < -2;$$

$$F(\omega) = 2, \quad -2 < \omega < -1;$$

$$F(\omega) = 1, \quad -1 < \omega < 1;$$

$$F(\omega) = 2, \quad 1 < \omega < 2;$$

$$F(\omega) = 0, \quad 2 < \omega < \infty.$$

Evaluate $f(t)$ for functions above

(7 marks)

(b) Figure Q4(a) shows the circuit consists of R and C with the value of 1000Ω and $0.1\mu\text{F}$ respectively. The input voltage $V_s(t)$ to the source is shown in Figure Q4(b).

- (i) Developed the Fourier series of the input ramp voltage waveform shown in Figure Q4(b).
- (ii) Solve the RMS value of the capacitor voltage, $v(t)$ for Figure Q4(a).

(13 marks)

- Q5** (a) The current in a 40Ω resistor is given by $i = 20e^{-2t}u(t)A$. By using the Parseval theorem calculate the total energy dissipated in the resistor which can be associated with the frequency band of $0 \leq \omega \leq 2\sqrt{3}$ rad/s.

(8 marks)

- (b) The input voltage to the low pass RC filter shown in Figure Q5(b) is

$$v_i(t) = 15e^{-5t}u(t).$$

- (i) Find the percentage of the 1Ω energy available in the input signal is available in the output signal.
- (ii) Calculate the percentage of the output energy is associated with the frequency range of $0 \leq \omega \leq 10$ rad/s.

(12 marks)

-END OF QUESTIONS-

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2012/2013
 COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEF
 COURSE CODE : BEF 22803

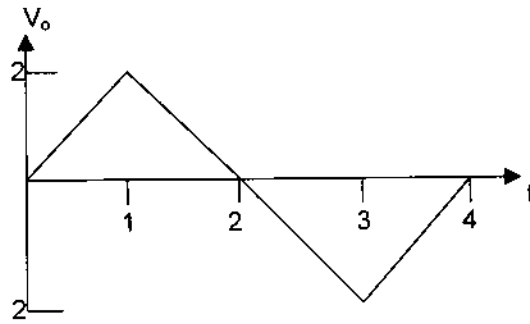


FIGURE Q1(a)

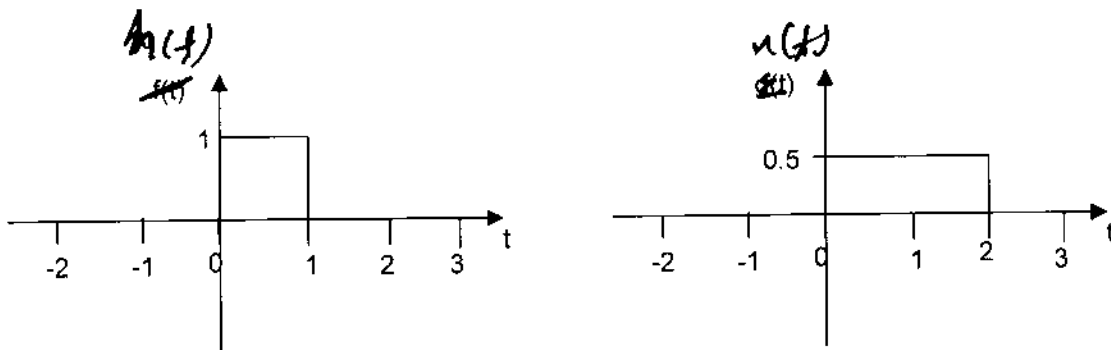


FIGURE Q1(c)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER II/ SESSION 2012/2013
 COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEF
 COURSE CODE : BEF 22803

11	$t^n e^{at}$	$\frac{n!}{(s-a)^{n+1}}$	$s > a$
12	$t \sin at$	$\frac{2as}{(s^2 - a^2)^2}$	$s > 0$
13	$t \cos at$	$\frac{s^2 - a^2}{(s^2 + a^2)^2}$	$s > 0$
14	$t \sinh at$	$\frac{2as}{(s^2 - a^2)^2}$	$s > a $
15	$t \cosh at$	$\frac{s^2 + a^2}{(s^2 + a^2)^2}$	$s > a $
16	$y'(t)$	$sY(s) - y(0)$, and $Y(s) = L\{y(t)\}$	
17	$y''(t)$	$s^2Y(s) - sy(0) - y'(0)$	
18	$e^{at} f(t)$	$F(s-a)$	
19	$t^n f(t), n=1,2,\dots$	$(-1)^n \frac{d^n}{ds^n} F(s)$	
20	$\mu_a(t) f(t)$	$e^{-as} L\{f(t+a)\}$	
21	$\mu_a(t) f(t+a)$	$e^{-as} L\{f(t)\}$	
22	$f(t)$	$\frac{\int_0^{\infty} e^{-st} f(t) dt}{1 - e^{-T}}$	
23	$\int_0^t f(\tau) g(t-\tau) d\tau$	$F(s)G(s)$	
24	$\int_0^t f(\tau) d\tau$	$\frac{1}{s} F(s)$	