

# UNIVERSITI TUN HUSSEIN ONN MALAYSIA

# FINAL EXAMINATION **SEMESTER I SESSION 2013/2014**

COURSE NAME

INSTRUMENTATION &

MEASUREMENT

COURSE CODE : BEH 20403 / BEX 20703

PROGRAMME : BEJ/BEE

EXAMINATION DATE : DECEMBER 2013

DURATION

: 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

Q1 (a) In an experiment being conducted by a group of students, they are given three sets of data reading of load weight. They need to determine which set of data has the most precision reading between these three data. If the data are:

 $A = \{50.30, 49.75, 49.60, 50.45, 50.00, 51.05, 49.85\},$   $B = \{50.20, 50.15, 49.90, 49.85, 49.95, 50.00, 50.95\}, \text{ and }$   $C = \{50.05, 50.10, 49.65, 50.30, 52.05, 48.85, 50.00\}.$ 

(i) Determine the arithmetic mean of all data in set A, set B and set C.

(3 marks)

(ii) Calculate the average deviation of all sets of data.

(3 marks)

(iii) Obtain the standard deviation of all sets of data.

(3 marks)

(iv) Identify which set of data has the most precision reading and give a reason.

(1 mark)

(b) List two (2) advantages of a dual slope integrating type (DVM) over single slope Ramp integrating type (DVM).

(2 marks)

(c) Figure Q1(c) shows a block diagram of Dual Slope DVM. Briefly explain the principle of Dual Slope DVM.

(8 marks)

Q2 (a) A basic D'Arsonval movement with a full scale deflection of 50  $\mu$ A and an internal resistance of 500  $\Omega$  is shown in Figure Q2(a). It is to be converted into a 0 – 10 V, 0 – 25V and 0 – 50V multi-range DC voltmeter using individual multipliers for each range. Calculate the value of  $R_1$ ,  $R_2$  and  $R_3$ .

(10 marks)

(b) Figure Q2(b) shows a (Permanent Magnet Moving Coil) PMMC instrument with internal resistance of 500  $\Omega$  and full scale deflection current of 50  $\mu$ A. Identify the value of  $R_1$  and  $R_2$  for a multi-range DC ammeter with current ranges of 0 - 50mA and 0 - 100mA.

(10 marks)

Q3	Figure Q3 shows a commercial AC voltmeter using a PMMC instrument instrument has 100 $\Omega$ coil resistance and an FSD of 1 mA. Shunt resistor is g while forward-bias resistance of each diode is 200 $\Omega$ .			
	(a)	Brief	ly explain the function of shunt resistor, $R_s$ and diode $D_2$ .	
				(2 marks)
	(b)			100 V. 5 marks)
	(c)	Deter	rmine the AC sensitivity of the voltmeter.	(3 marks)
Q4	Figure Q4 shows an AC bridge that balanced at a frequency of 1 kHz and has the following constants:			
		Arm Arm	AB: $1 \text{ k}\Omega$ Resistor, BC: $2 \text{ k}\Omega$ Resistor in parallel with 0.25 $\mu\text{F}$ Capacitor, CD: $500 \text{ k}\Omega$ Resistor AD: unknown $R_x$ , Resistor and $L_x$ , Inductor.	
	(a)	Derive the AC bridge balance condition and find the unknown impedance of arm AD. (14 marks)		
	(b)	Briefly explain the type of AC-Bridge and its advantages. (4 marks)		4 marks)
	(c)	Derive and find the Q factor of this AC-bridge. (2 marks)		2 marks)
Q5	(a)	Signal A and B from one system were displayed through an oscilloscope as illustrated in Figure Q5(a). Determine:		
		(i)	The amplitudes or peak voltage	(2 marks)
		(ii)	Peak-to-peak voltage	(2 marks)
		(iii)	Period (	(2 marks)

(iv) Frequency

(2 marks)

(v) Phase difference of two signals

(2 marks)

(b) Explain the differences between sensor and transducer.

(5 marks)

(c) Figure **Q5(c)** shows a displacement transducer with a shaft stroke of 3.0 inch is applied in the circuit. The total resistance of the potentiometer is  $5 \text{ k}\Omega$  and the applied voltage,  $V_T$  is 5.0 V. Determine the value of output voltage,  $V_o$  when the wiper is 0.9 inch from B.

(5 marks)

- END OF QUESTION -

### **FINAL EXAMINATION**

SEMESTER/SESSION

: 1/2013/2014


**COURSE NAME** 

: INSTRUMENTATION & MEASUREMENT

PROGRAMME : BEJ/BEE

COURSE CODE: BEH 20403/

BEX20703

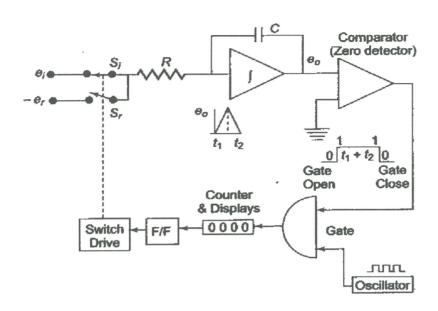

## FIGURE Q1(c)

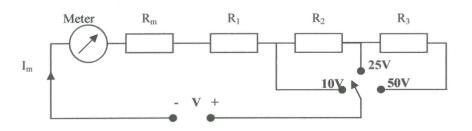


FIGURE Q2(a)

## **FINAL EXAMINATION**

SEMESTER/SESSION

: 1/2013/2014


COURSE NAME

: INSTRUMENTATION & MEASUREMENT

PROGRAMME : BEJ/BEE

COURSE CODE: BEH 20403/

BEX20703

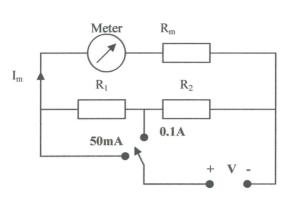

## FIGURE Q2(b)

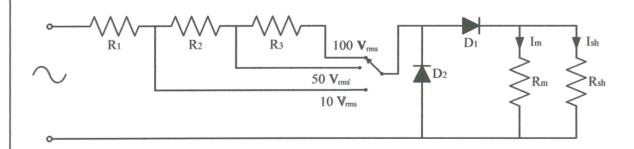


FIGURE Q3

## **FINAL EXAMINATION**


SEMESTER/SESSION : 1/2013/2014

COURSE NAME


: INSTRUMENTATION & MEASUREMENT

PROGRAMME : BEJ/BEE COURSE CODE: BEH 20403

BEX20703

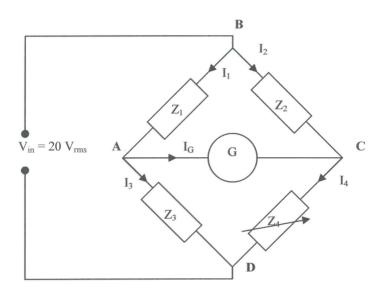

## **FIGURE Q4**

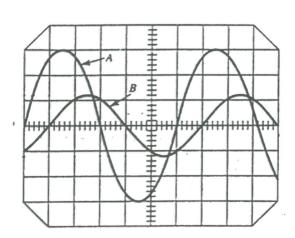

TIME/DIV setting at 0.2 ms, and VOLTS/DIV setting at 500 mV

## FIGURE Q5(a)

## **FINAL EXAMINATION**

SEMESTER/SESSION : 1/2013/2014

**COURSE NAME** 

: INSTRUMENTATION & MEASUREMENT

PROGRAMME : BEJ/BEE

COURSE CODE: BEH 20403

BEX20703

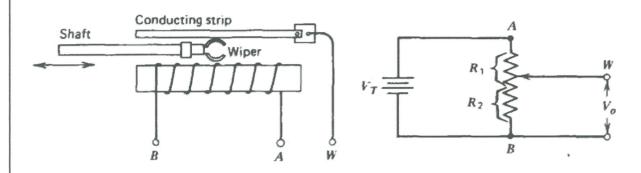


FIGURE Q5(c)