

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2013/2014**

COURSE NAME : POWER SYSTEM ANALYSIS &  
PROTECTION  
COURSE CODE : BEF43303/BEX44703/BEK4223  
PROGRAMME : BEV/BEE  
EXAMINATION DATE : JANUARY 2014  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

**CONFIDENTIAL**

- Q1** (a) Electric power system can be represented by one-line diagram (OLD). Define OLD and give two (2) advantages of this representation.

(4 marks)

- (b) A 30 MVA, 13.8 kV, three-phase generator has a sub-transient reactance of 15%. The generator supplies two motors over a transmission line having transformers at both ends as shown in **Figure Q1(b)**. The motors have rated inputs of 20 MVA and 10 MVA, supplied with 12.5 kV with  $x'' = 20\%$ . The three-phase transformer T1 is rated 35 MVA, 13.2/115 ( $\Delta/Y$ ) kV with leakage reactance of 10%, while the three phase transformer T2 is rated at 30 MVA, 12.5/116 (Y/ $\Delta$ ) kV with leakage reactance of 10%. Series reactance of the transmission line is  $80 \Omega$ .

- (i) By taking generator rating as base, determine the per-unit (p.u) reactance for T1, T2, transmission line, motor 1 and motor 2

(10 marks)

- (iii) Design the impedance diagram for system shown in **Figure Q1(b)**

(3 marks)

- (iii) Design the reactance diagram with all reactances in per-unit value obtained in **Q1(b)(i)**.

(3 marks)

- Q2** (a) Use Gauss Seidal method to find the solution of the following equations:

$$x_1 + x_1 x_2 = 10$$

$$x_1 + x_2 = 6$$

With the initial estimation of  $x_1^{(0)} = 1$  and  $x_2^{(0)} = 1$ . Continue the iteration until  $|\Delta x_1^{(k)}|$  and  $|\Delta x_2^{(k)}|$  are less than 0.001.

(5 marks)

- (b) **Figure Q2(b)** shows the one-line diagram of a simple three-bus power system with generation at bus 1. The magnitude of voltage at bus 1 is adjusted to 1.05 per unit. The scheduled loads at buses 2 and 3 are as marked on the diagram. Line impedances are marked in per unit on a 100MVA base and the line charging susceptances are neglected.

- (i) Using the Gauss-Seidel method, determine the phasor values of the voltage at the load buses 2 and 3, accurate to 4 decimal places. Perform hand calculation until the second iteration.

(9 marks)

- (iii) Calculate the slack bus real and reactive power. (3 marks)
- (iii) Evaluate the line current  $I_{12}$  and hence, the line flow  $S_{12}$  between busbar 1 and 2. (3 marks)
- Q3** (a) Figure Q3(a) shows the OLD for a three phase system in which a generator supplies a load through a step-up transformer, a transmission line, and a step-down transformer. The transformers are ideal and the turn ratios are line to line values. Evaluate the per unit current if the terminal voltage of the generator is 480 V line to line. (10 marks)
- (b) Referring to the schematic of a power system as shown in **Figure Q3(b)**, as a power system engineer,
- (i) Design the zones of protection in which the system should be divided (4 marks)
- (ii) Determine which circuit breakers should open for the fault occurring at point F1 and F2. (2 marks)
- (iii) Identify which breaker provides the primary and secondary protection for the fault occurring at F2 (3 marks)
- (iv) Suggest the location of the fault if a single fault has resulted in the operation of breakers B5, B6, B7 and B8. (1 marks)
- Q4** (a) A current transformer (CT) is marked '5P20'. Based on the rating i.e. '5P20', describe the type and accuracy of the CT. (3 marks)
- (b) Give two (2) examples of instrument transformers commonly used for power system protection. Draw a schematic diagram for each transformer to show the circuit connection in power system. (4 marks)

- (c) A CT with a rated current ratio of 200:5 A gives a secondary output current ( $I_S$ ) of 8.0 A. By using the excitation curve and secondary resistance for multi-ratio CT given in **Figure Q4(c)**,
- (i) Calculate the CT primary input ( $I_P$ ) if the load impedance ( $Z_B$ ) =  $0.5\Omega$  (5 marks)
  - (ii) Compute the CT ratio error (2 marks)
  - (iii) If an overcurrent relay set to operate at 10 A, is connected to the CT, determine whether the relay will detect a 1.3 kA primary fault current when the load impedance is  $Z_B = 5\Omega$ . Justify your answer with numerical analysis. (6 marks)

- Q5** (a) A 30 MVA, star-delta transformer is to be protected by a differential protection system. The transformer is supplied from a 132 kV grid. The current ratio of the current transformer on the 132 kV side are 250/5A while those on the 33 kV side are 600/5 A. If the impedance of the transformers is 6%, and a 3-phase fault occurs on the 33 kV side of the transformer outside its zone of protection.
- (i) Sketch circuit diagram to represent and summarize the above problem. Label with appropriate technical data and indicate the fault location (3 marks)
  - (ii) Determine the primary current  $I_P$  and secondary current  $I_S$  for the 30 MVA transformers at the CTs' output. Ignore the impedance of the cables (4 marks)
  - (iii) Determine the average restraint current  $I_r$  and operating current  $I_o$  in the relay (3 marks)
  - (iv) The bias characteristic of the relay is  $y = mx + c$  where  $y$  is the operating current,  $x$  is the average restraint current and  $m$  is slope. Draw the characteristic curve of this relay on a graph paper, if the percentage bias setting is set to 25 % and relay setting current,  $I_{set} = 15$  A (3 marks)

- (v) On the characteristic curve, clearly indicate the operating point of the relay due to this fault. Determine whether the relay will operate and state your reason

(3 marks)

- (b) Briefly describe the principle operation of Induction Disc Relays.


(4 marks)

**- END OF QUESTIONS -**


**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2013/2014  
 COURSE NAME : POWER SYSTEM ANALYSIS &  
 PROTECTION


PROGRAMME : BEV/BEE  
 COURSE CODE: BEF43303/  
 BEX44703/  
 BEK4223

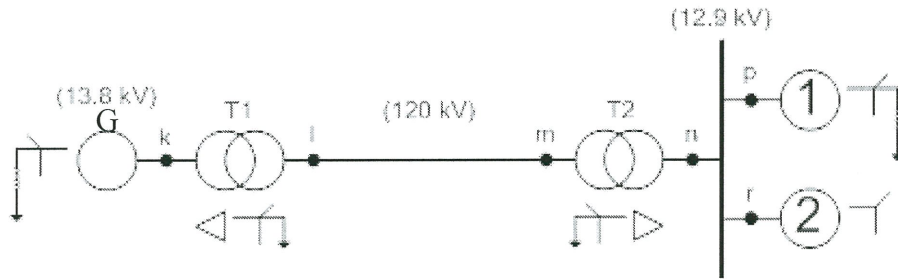

**FIGURE Q1(b)**

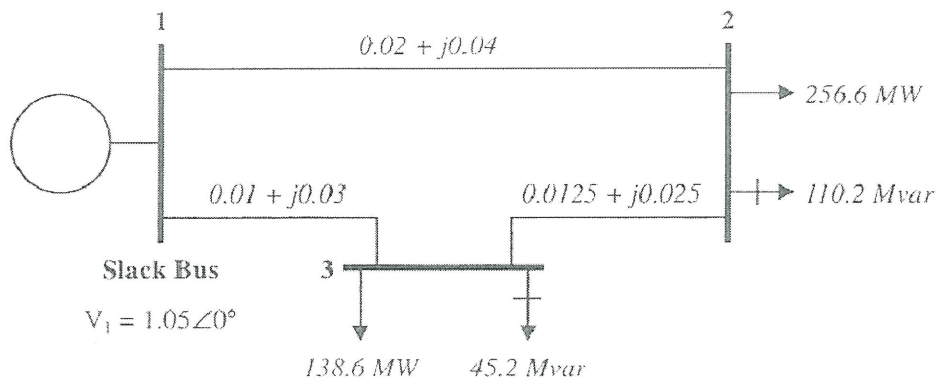

**FIGURE Q2(b)**

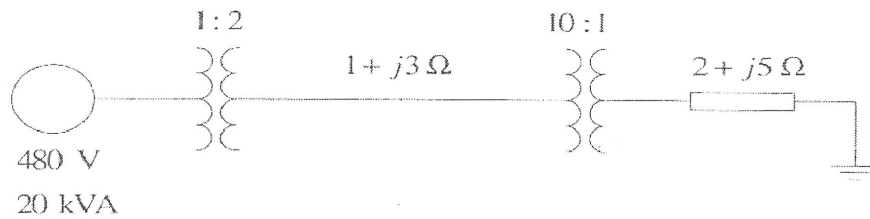


**FIGURE Q3(a)**




**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2013/2014  
 COURSE NAME : POWER SYSTEM ANALYSIS &  
 PROTECTION

PROGRAMME : BEV/BEE  
 COURSE CODE: BEF43303/  
 BEX44703/  
 BEK4223

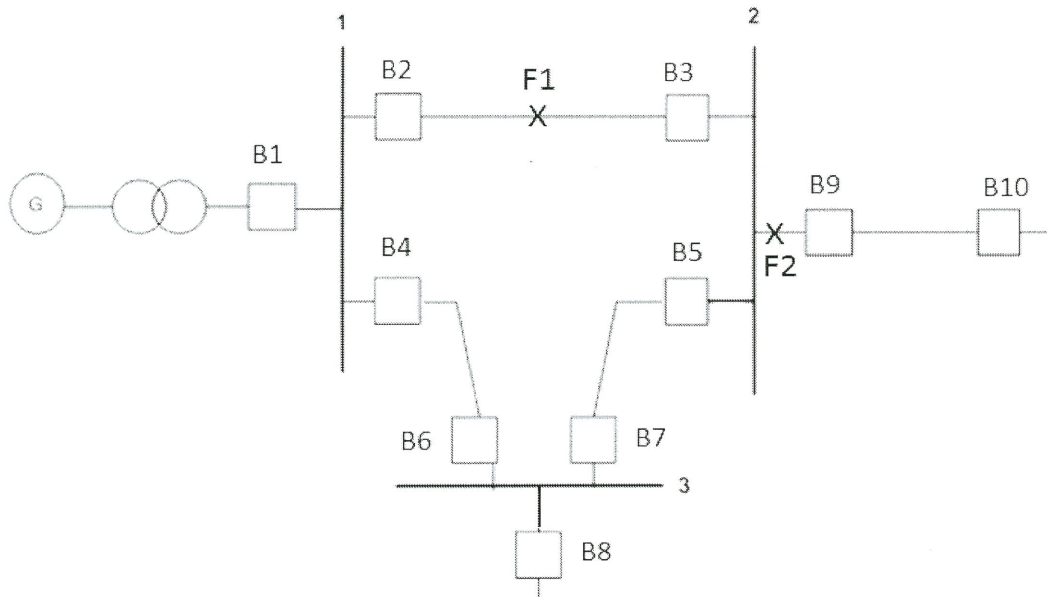

**FIGURE Q3(b)**

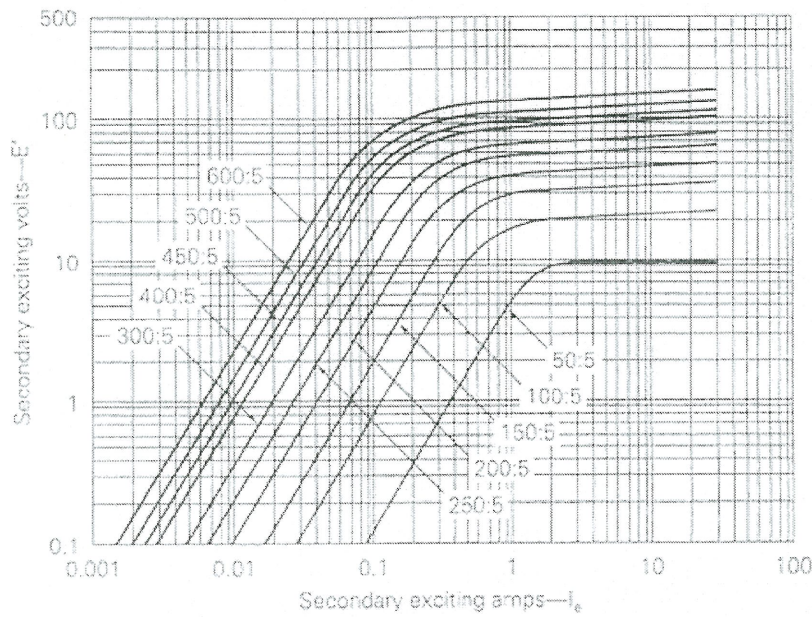

| CT ratio | Secondary resistance $\Omega$ |
|----------|-------------------------------|
| 50:5     | 0.061                         |
| 100:5    | 0.082                         |
| 150:5    | 0.104                         |
| 200:5    | 0.125                         |
| 250:5    | 0.146                         |
| 300:5    | 0.168                         |
| 400:5    | 0.211                         |
| 450:5    | 0.230                         |
| 500:5    | 0.242                         |
| 600:5    | 0.296                         |

**FIGURE Q4(c)**

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2013/2014  
 COURSE NAME : POWER SYSTEM ANALYSIS &  
 PROTECTION

PROGRAMME : BEV/BEE  
 COURSE CODE: BEF43303/  
 BEX44703/  
 BEK4223

*Formula:*

*Conversion of a given base per-unit impedance on a new base:*

$$Z_{new(pu)} = Z_{old(pu)} \left( \frac{kV_{base(old)}}{kV_{base(new)}} \right)^2 \left( \frac{MVA_{base(new)}}{MVA_{base(old)}} \right)$$

*Nominal T model:*

$$V_S = 1 + \frac{YZ}{2} V_R + Z + \frac{Z^2 Y}{4} I_R$$

$$I_S = YV_R + 1 + \frac{ZY}{2} I_R$$

*Gauss Seidal power system analysis:*

$$Q_i^{(k+1)} = -\text{Im} g \left\{ V_i^{*(k)} \left[ V_i^{(k)} \sum_{j=0}^n y_{ij} - \sum_{j=1}^n y_{ij} V_j^{(k)} \right] \right\} \quad j \neq i$$

$$V_i^{(k+1)} = \frac{\frac{P_i^{sch} - jQ_i^{sch}}{V_i^{*(k)}} + \sum_{j=1}^n y_{ij} V_j^{(k)}}{\sum_{j=0}^n y_{ij}} \quad j \neq i$$

$$I_{ij} = y_{ij} (V_i - V_j) \text{ and } I_{ji} = -I_{ij}$$

$$S_{ij} = V_i I_{ij}^* \text{ and } S_{ji} = V_j I_{ji}^*$$

$$S_{Lij} = S_{ij} + S_{ji}$$