

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2013/2014**

COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

COURSE CODE : BEF22803

PROGRAMME : BEV

EXAMINATION DATE : JANUARY 2014

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTIONS PAPER CONSISTS OF SEVEN (7) PAGES

CONFIDENTIAL

- Q1** (a) **Figure Q1(a)** shows an output of a system. Write the function in terms of unit step functions and find the Laplace transform of the function. (5 marks)

- (b) Solve the Laplace transform of $f(t)$ below.

$$f(t) = \begin{cases} t^2 & 0 \leq t < 1 \\ t + 2 & t \geq 1 \end{cases}$$

(10 marks)

- (c) Given $x(t) = u(t)$, $h(t) = e^{-t} \cdot u(t)$. Evaluate $y(4)$ where $y(t) = x(t) * h(t)$. (10 marks)

- Q2** (a) Find the inverse Laplace of the following:

(i) $s(s^2 + 4s + 6)^{-1}$

(ii) $\frac{se^{-8s}}{s^2 - 4s + 3}$

(12 marks)

- (b) On a semi log paper, sketch the Bode plot for

$$H(j\omega) = \frac{640(j\omega + 1)(0.01j\omega + 1)}{(j\omega)^2(j\omega + 10)}$$

(13 marks)

- Q3** (a) **Figure Q3(a)** shows an RC circuit with an independent current source. Find an expression for $v(t)$. (5 marks)

- (b) In a circuit as shown in **Figure Q3(b)**, the switch is kept closed for a long time and opened at $t = 0$ s. Produce $v_o(t)$ using Laplace method. (20 marks)

- Q4** (a) A signal is given as:

$$f(x) = \begin{cases} 0 & -\pi < x < 0 \\ 1 & 0 < x < \pi \end{cases}$$

Construct the Fourier series of the above function.

(7 marks)

- (b) Deduce the Fourier transform of $v_i(t) = 30e^{|t|}$ for $-\infty \leq t \leq +\infty$, as shown in **Figure Q4(b)**.

(5 marks)

- (c) In **Figure Q4(c)**, produce $v_o(t)$ using Fourier method if the values of resistors R1 and R2 are 20Ω and 80Ω , respectively, while the value of capacitor C is 0.125 F .

(13 marks)

-END OF QUESTIONS-

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER I/ SESSION 2013/2014
COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEV
COURSE CODE : BEF 22803

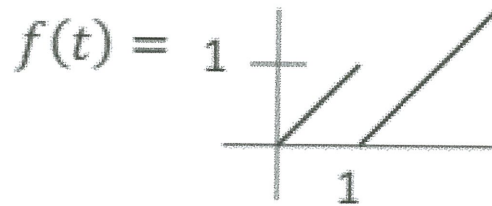


FIGURE O1(a)

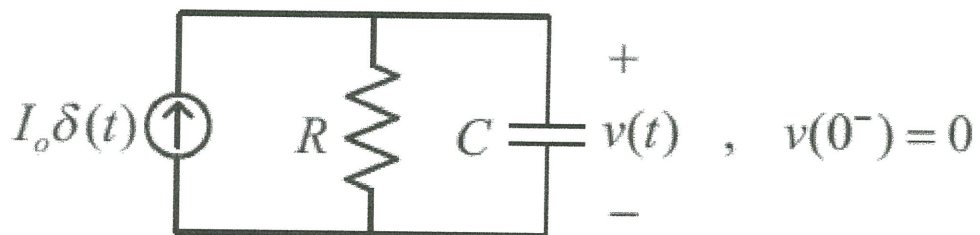


FIGURE O3(a)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER I/ SESSION 2013/2014
COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEV
COURSE CODE : BEF 22803

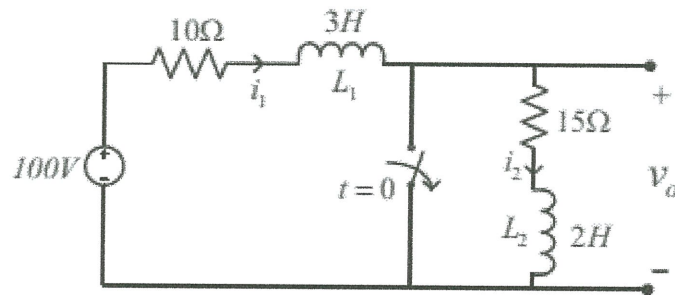


FIGURE Q3(b)

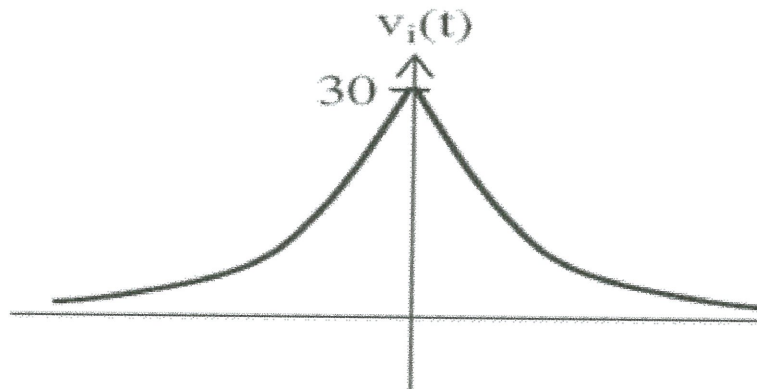


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER I/ SESSION 2013/2014
COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEV
COURSE CODE : BEF 22803

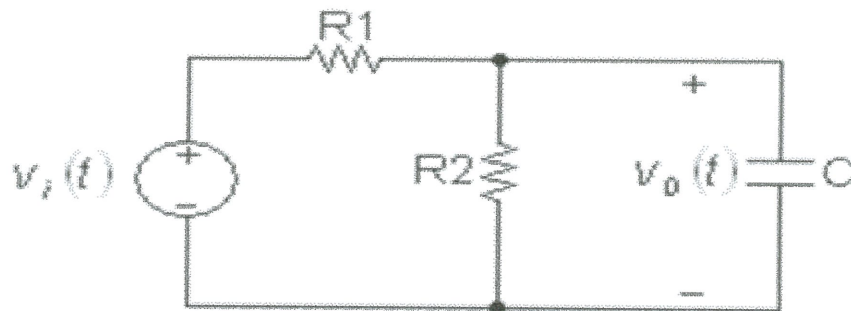


FIGURE Q4(c)

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER I/ SESSION 2013/2014
 COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEV
 COURSE CODE : BEF 22803

Laplace Transform Table

	$f(t)$	$F(s)$	
1	1	$\frac{1}{s}$	$s > 0$
2	t	$\frac{1}{s^2}$	$s > 0$
3	$t^n, n=1,2,\dots$	$\frac{n!}{s^{n+1}}$	$s > 0$
4	e^{at}	$\frac{1}{s-a}$	$s > a$
5	$\sin at$	$\frac{a}{s^2+a^2}$	$s > 0$
6	$\cos at$	$\frac{s}{s^2+a^2}$	$s > 0$
9	$e^{at} \sin bt$	$\frac{b}{(s-a)^2+b^2}$	$s > a$
10	$e^{at} \cos bt$	$\frac{s-a}{(s-a)^2+b^2}$	$s > a$
11	$y'(t)$	$sY(s) - y(0), \text{ and } Y(s) = L\{y(t)\}$	
12	$y''(t)$	$s^2Y(s) - sy(0) - y'(0)$	
13	$e^{at} f(t)$	$F(s-a)$	
14	$t^n f(t), n=1,2,\dots$	$(-1)^n \frac{d^n}{ds^n} F(s)$	
15	$f(t)u(t-a)$	$e^{-as} L\{f(t+a)\}$	