

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2013/2014**

COURSE NAME : ANALOG ELECTRONICS
COURSE CODE : BEL 10203
PROGRAMME : BEJ
EXAMINATION DATE : JUNE 2014
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF THIRTEEN (13) PAGES

CONFIDENTIAL

- Q1**
- (a) Describe and differentiate the processes that result in a bonding structure as illustrated in Figure **Q1(a)(i)** and **Q1(a)(ii)**. Hence determine the result of each process. (5 marks)
- (b) The circuit in Figure **Q1(b)** is a centre-tapped rectifier. Referring to this circuit;
- (i) Summarize the operation of a centre-tapped rectifier. (4 marks)
- (ii) Draw and label the input, V_i and output waveforms V_{out} if Switch S1 and Switch S2 are closed but Switch S3 is opened. (4 marks)
- (iii) Draw and label the output waveforms V_{out} if all switches are closed. (2 marks)
- (c) Design a clamper circuit to perform the function indicated in Figure **Q1(c)**. Prove your design with calculation. (5 marks)
- (d) Figure **Q1(d)** shows the Zener regulation circuit. V_{in} is 40 V, R_1 is 50 Ω , R_L is 100 Ω and the breakdown voltage of the zener diode is 20 V. Find:
- (i) the voltage drop across the load resistance R_L . (1 mark)
- (ii) the current through the load resistor R_L , (1 mark)
- (iii) the voltage drop across R_1 , (1 mark)
- (iv) the current through R_1 , (1 mark)
- (v) the current through the zener diode. (1 mark)

Q2 Figure **Q2** shows a common emitter amplifier which is to be manufactured using transistors with a nominal β value of 200.

(a) Determine the collector bias current when $\beta = 200$, taking into account the base current of the transistor. (3 marks)

(b) Evaluate the collector bias current in the cases $\beta = 150$ and $\beta = 250$. Conclude the results. (3 marks)

(c) Draw a small-signal equivalent circuit of the amplifier and hence prove that the voltage gain may be written as:

$$\frac{-R_C}{r_e + R_E}$$

You may neglect the transistor's small-signal output resistance, r_o . (4 marks)

(d) Evaluate the expression given in **Q2(c)** by assuming $\beta = 200$. (4 marks)

(e) Determine the voltage gain of the amplifier if the emitter resistor, R_E were bypassed using a capacitor? (2 marks)

(f) If the amplifier in Figure **Q2** has an applied load, R_L of 4.7 k Ω , a source resistance, R_S of 1.5 k Ω , an input capacitor, C_S of 1 μ F, an output capacitor, C_C of 1 μ F and an emitter capacitor, C_E of 100 μ F;

(i) Draw its AC equivalent circuit for low frequency response. (2 marks)

(ii) Determine the low cutoff frequencies f_{LS} , f_{LC} and f_{LE} . (6 marks)

(iii) State the dominant frequency, f_L and sketch the frequency response. (1 mark)

- Q3** A Field Effect Transistor (FET) circuit has a MATLAB plot of the transfer characteristics curve and the bias line as in Figure **Q3**. Based on the specifications given as follows:

$$V_{DD} = 15 \text{ V}, V_{DS} = 5.475 \text{ V and } I_1 = I_2 = \frac{V_{DD}}{R_1 + R_2} = 16.67 \mu\text{A};$$

- (a) Design the circuit (with bypass capacitor). Hence determine the value of all resistors. (12 marks)
- (b) Draw the AC equivalent of the circuit and calculate its input impedance Z_i , output impedance Z_o and voltage gain A_v . Assume $r_d \geq 10R_D$. (8 marks)
- Q4** (a) For the BJT cascade amplifier of Figure **Q4(a)**,
- (i) calculate the emitter current I_E , for each stage. (2 marks)
- (ii) draw the AC equivalent circuit. (3 marks)
- (iii) calculate the voltage gain of each stage and the overall AC voltage gain. (5 marks)
- (b) For the Darlington network of Figure **Q4(b)**,
- (i) determine the DC bias voltages, V_{B1} , V_C , and V_{E2} and currents, I_{B1} and I_{E2} . (5 marks)
- (ii) draw the AC equivalent circuit, then calculate the mid-band voltage gain, $A_v = V_o/V_i$. (5 marks)

Q5 Figure **Q5** shows the class-B power amplifier circuit. Given that $R_{b1} = R_{b2} = 3.9\text{k}\Omega$, supply voltage, $\pm V_{cc} = \pm 20\text{V}$, $R_{load} = 10\Omega$, $R_i = 47\Omega$ and $C_{in} = 1\ \mu\text{F}$. For this figure;

- (a) Explain the circuit operation. (4 marks)
- (b) Draw the maximum peak output voltage, $V_{op(max)}$ across the Rload. (2 marks)
- (c) Calculate the circuit efficiency if the peak output voltage, V_{op} across the Rload is 10V. (4 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
COURSE CODE : BEL 10203

 


FIGURE Q1(a)(i)

 


FIGURE Q1(a)(ii)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
COURSE CODE : BEL 10203

 


FIGURE Q1(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
COURSE CODE : BEL 10203

 


FIGURE Q1(c)

 


FIGURE Q1(d)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
 COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
 COURSE CODE : BEL 10203

 


FIGURE Q2

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
 COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
 COURSE CODE : BEL 10203

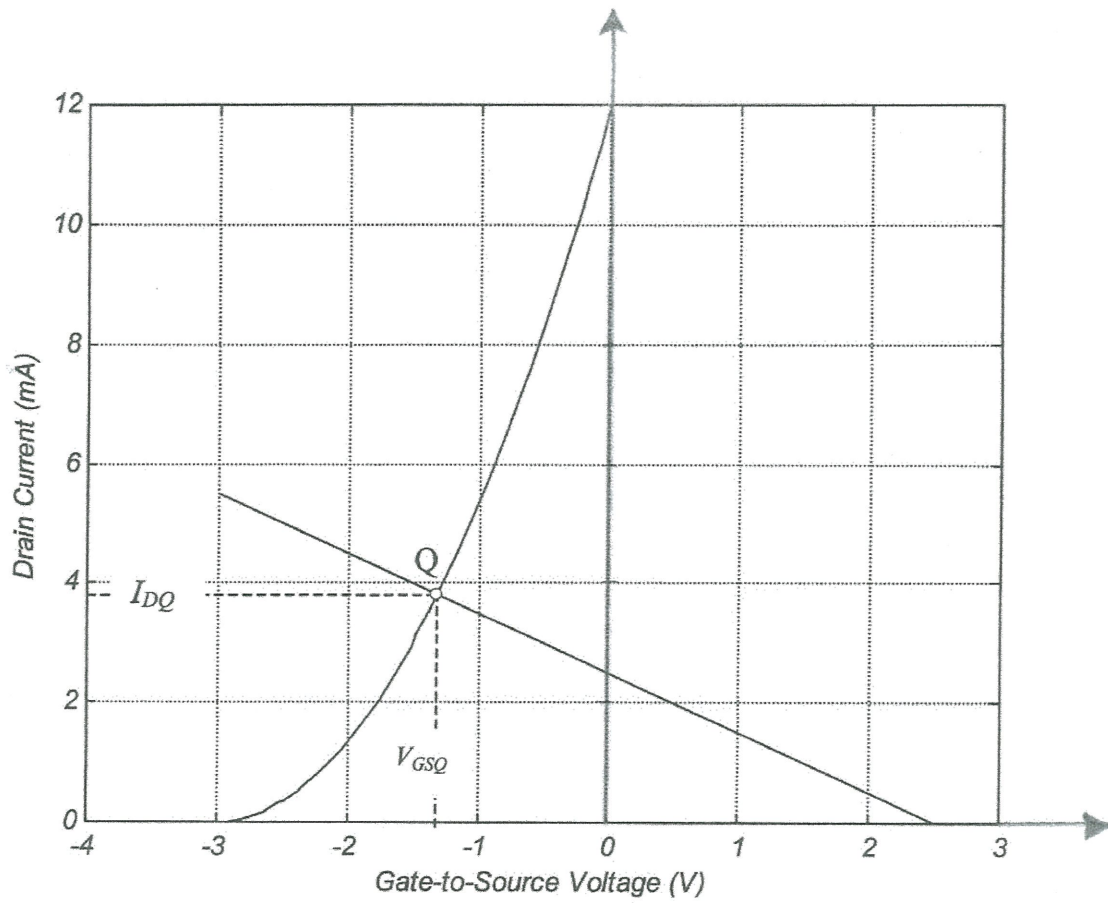


FIGURE Q3

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
 COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
 COURSE CODE : BEL 10203

 


FIGURE Q4(a)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
 COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
 COURSE CODE : BEL 10203

 


FIGURE Q4(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2013/2014
 COURSE NAME : ANALOG ELECTRONICS

PROGRAMME : BEJ
 COURSE CODE : BEL 10203

 


FIGURE Q5