

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2013/2014**

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I
COURSE CODE : BEF 12403
PROGRAMME : BEV
EXAMINATION DATE : JUNE 2014
DURATION : 3 HOURS
INSTRUCTION : ANSWER **ALL** QUESTIONS

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

- Q1** (a) Differentiate between supermesh and supernode. (8 marks)
- (b) Figure **Q1(b)(i)** and Figure **Q1(b)(ii)** show I-V characteristics and representation (circuit model) for an ideal dc current source, respectively. Produce I-V characteristics and representation for a practical dc current source. (8 marks)
- (c) Refer to Figure **Q1(c)**, using nodal analysis:
- (i) Solve for V_2 . (7 marks)
- (ii) Find the power of I_{S1} . (2 marks)
- Q2** (a) Differentiate between power and energy in an electrical circuit. (4 marks)
- (b) Using only a voltmeter and a 1Ω resistor, recommend how current I_o in Figure **Q2(b)** can be read directly with the voltmeter. (6 marks)
- (c) In Figure **Q2(c)**, determine I_x using superposition rule. (15 marks)
- Q3** (a) Relate the maximum power transfer theorem with efficiency in an electrical circuit. (4 marks)
- (b) Predict the efficiency of a system if,
- (i) $R_{load} = R_{source}$ (2 marks)
- (ii) $R_{load} = \infty$ or $R_{source} = 0$ (2 marks)
- (iii) $R_{load} = 0$ (2 marks)
- (c) The circuit shown in Figure **Q3(c)** is a model for a common-emitter bipolar junction transistor amplifier
- (i) Determine a load resistance, R_L so that maximum power is transferred to it from the amplifier. (7 marks)
- (ii) Calculate the total power absorbed in part Q3(c)(i). (8 marks)

Q4 Figure **Q4(a)** shows a resistive circuit whose voltage $v_s(t)$ has waveform as shown in Figure **Q4(b)**.

- (a) Produce the time expression for voltage $v_o(t)$. (14 marks)
- (b) Sketch the waveform of $v_o(t)$. (2 marks)
- (c) Solve for the average and effective values of voltage $v_o(t)$. (7 marks)
- (d) Calculate the average power dissipated by the $2\ \Omega$ resistor. (2 marks)

– END OF QUESTION –

FINAL EXAMINATION

SEMESTER/SESSION	: II/ 2013/ 2014	PROGRAMME	: BEV
COURSE NAME	: ELECTRIC CIRCUIT ANALYSIS I	COURSE CODE	: BEF 12403

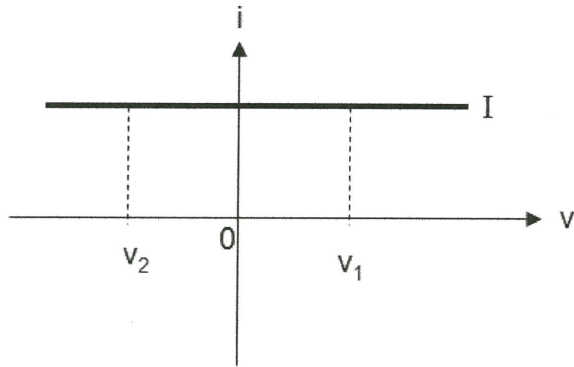


FIGURE Q1(b)(i)

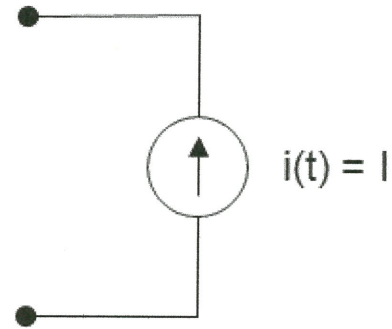


FIGURE Q1(b)(ii)

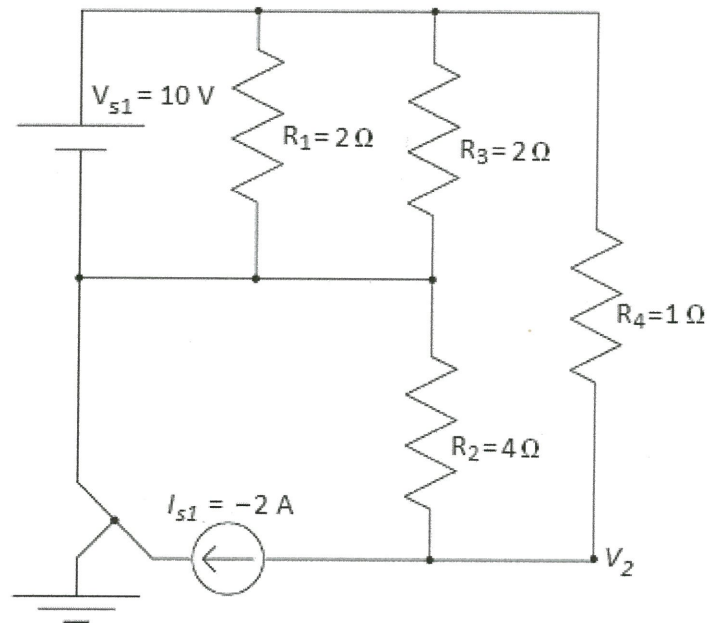


FIGURE Q1(c)

P
FINAL EXAMINATION

SEMESTER/SESSION	: II/ 2013/ 2014	PROGRAMME	: BEV
COURSE NAME	: ELECTRIC CIRCUIT ANALYSIS I	COURSE CODE	: BEF 12403

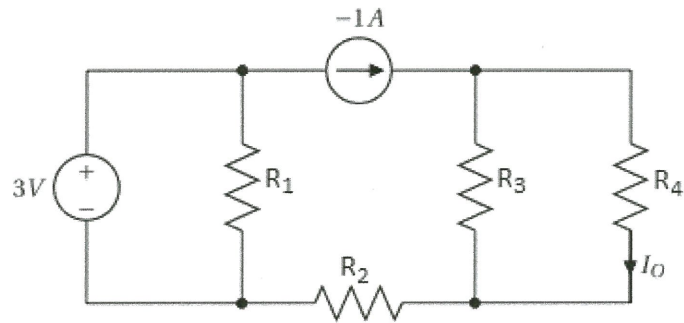


FIGURE Q2(b)

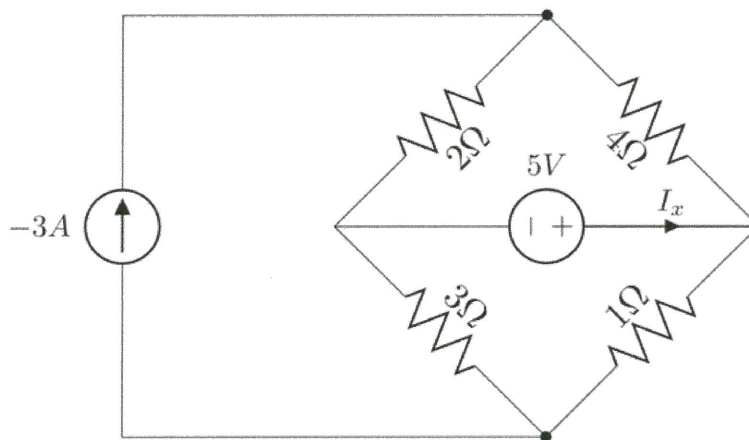


FIGURE Q2(c)

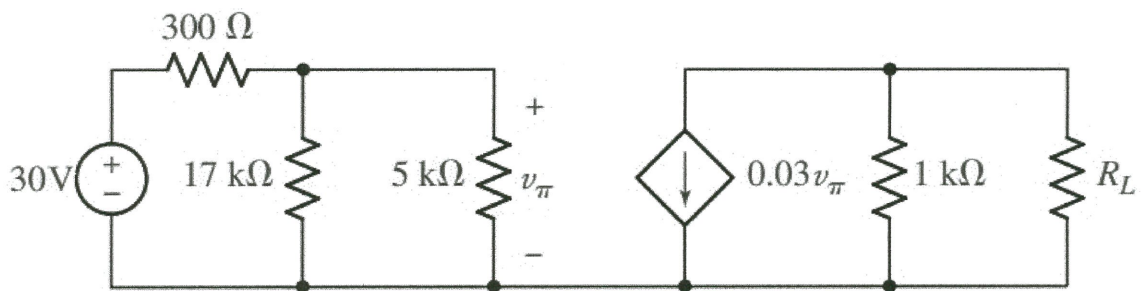


FIGURE Q3(c)

FINAL EXAMINATION

SEMESTER/SESSION	: II/ 2013/ 2014	PROGRAMME	: BEV
COURSE NAME	: ELECTRIC CIRCUIT ANALYSIS I	COURSE CODE	: BEF 12403

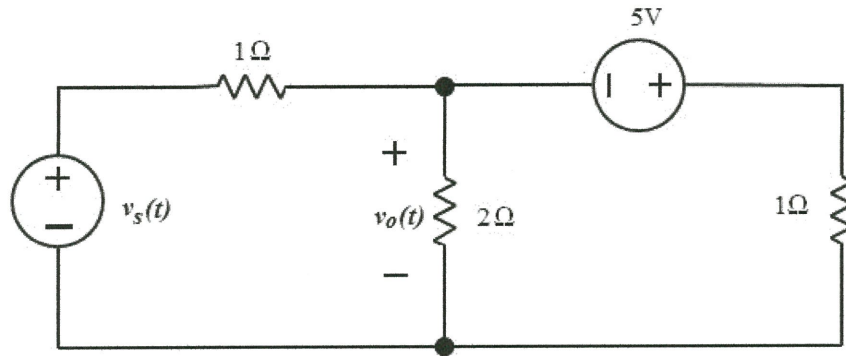


FIGURE Q4(a)

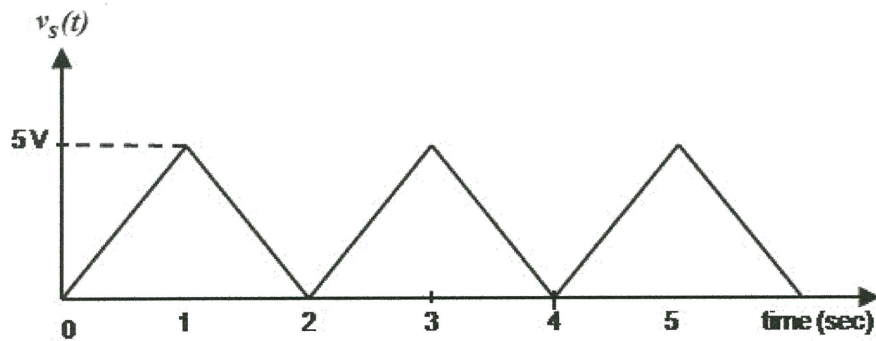


FIGURE Q4(b)