

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2013/2014**

COURSE NAME : ELECTRONIC CIRCUIT THEORY
COURSE CODE : BEF 12603
PROGRAMME : BEV
EXAMINATION DATE : JUNE 2014
DURATION : 3 HOURS
INSTRUCTION : A) ANSWER ALL FOUR (4) QUESTIONS.
B) ANSWER ONE (1) QUESTION.

THIS QUESTION PAPER CONSISTS OF TEN (10) PAGES

CONFIDENTIAL

SECTION A

- Q1** (a) Figure **Q1(a)** shows an I-V characteristics of a pn junction diode. Construct a piece wise linear (PWL) model of this pn junction diode. (3 marks)
- (b) Diodes D_1 and D_2 of the circuit shown in Figure **Q1(b)** are having the same I-V characteristics as the one indicated in Figure **Q1(a)**. Using the PWL diode model obtained in Q1(a),
- (i) Calculate the currents I_1 and I_2 , and the voltage, V_o if V_s is 5 V (8 marks)
- (ii) Calculate the currents I_1 and I_2 , and the voltage, V_o if V_s is -5 V. (4 marks)
- (c) If the I-V characteristics of diodes D_1 and D_2 are similar to those of ideal pn junction diodes, calculate the new values of I_1 , I_2 and V_o when V_s is 5 V. (5 marks)
- Q2** (For **Q2**, the voltage transfer characteristic curve, the input signal and output signal must be drawn on a **graph paper**).
The zener diode, Z_D in the regulator circuit shown in Figure **Q2** has the PWL parameters as follow:
- $$V_F = 0 \text{ V}; \quad R_F = 0 \Omega$$
- $$V_{ZK} = 6 \text{ V}; \quad R_Z = 0 \Omega$$
- (a) Modify the circuit in Figure **Q2** to include PWL model that represents the zener diode, Z_D as indicated above. (2 marks)
- (b) Analyse the circuit of Figure **Q2** to determine the transition voltages and fill-in the values in Table **Q2**. Plot the graph of the voltage transfer characteristic (V_o versus V_s for this circuit from $V_s = -10 \text{ V}$ to 10 V and label the transition voltages). (10 marks)
- (c) If the input signal, $V_s = 10 \sin(100 \pi t) \text{ V}$, draw the input waveform, V_s and output waveform, V_o for one complete cycle. (8 marks)

- Q3** (a) Explain three operation modes available for bipolar junction transistor (BJT) and the conditions required to operate in these modes. (3 marks)
- (b) Circuit in Figure **Q3** is used to control the lighting of a LED. When the input signal, V_i is at 5 V, LED is lit; else it will be turned off. Assume that the LED requires 5 mA current for full brightness and drops about 1.8 V. The controller circuit using a BJT transistor type which β is specified to be in the range of 50 to 150.
- (i) Compute the value of R_C . Calculate the voltage across R_C when the LED is lit. Also calculate the voltage across R_C when the LED is OFF. (7 marks)
- (ii) Propose the value of R_B to guarantee the circuit remains in the saturation mode. (6 marks)
- (iii) Explain how your answer in **Q2(i)** and **Q2(ii)** fulfil its operation in controlling the LED's lighting. (4 marks)
- Q4** (a) With the aid of a diagram, describe the importance of quiescent points to be in the middle of the DC load line for BJT transistor amplifier circuit. (4 marks)
- (b) The amplifier circuit shown in Figure **Q4** is used to amplify the audio signals. The three capacitors have infinite capacitances.
- (i) Draw the small-signal equivalent circuit of the amplifier circuit. (6 marks)
- (iii) Calculate the voltage gain, A_V , the current gain, A_i and the overall gain, A_{VT} . (10 marks)

SECTION B

- Q5** (a) State the assumption(s) made in modelling the ideal operational amplifiers in terms of its gain and voltage(s).
(4 marks)
- (b) Circuit in Figure **Q5** is an operational amplifier used to perform a type of mathematical operation.
- (i) Derive the expression of the output voltage, Z in terms of inputs A , B and C .
(6 marks)
- (ii) Determine the output voltage, Z for the following scenarios:
Case 1 – the values of A , B and C are 2 V, -3 V and 4 V respectively.
Case 2 – the values of A , B and C are 3 V, 3 V and 5 V respectively.
(7 marks)
- (iii) If the feedback resistor is doubled of the present value, deduce the new expression of the output, Z in terms of inputs A , B and C .
(3 marks)
- Q6** (a) State the assumption(s) made in modelling the ideal operational amplifiers in terms of its impedance values.
(4 marks)
- (b) Circuit in Figure **Q6** is an operational amplifier used to perform a type of mathematical operation.
- (i) Derive the expression of the output voltage, $v_o(t)$ in terms of input signal, $v_i(t)$.
(5 marks)
- (ii) If the input signal, $v_i(t) = 10 \sin(100\pi t)$ V, draw both the input waveform, $v_i(t)$ and output waveform, $v_o(t)$ for one complete cycle. Label the diagram clearly.
(8 marks)
- (iii) Explain the effect on the output signal, $v_o(t)$ as the frequency, ω of input signal, $v_i(t)$ is varied.
(3 marks)

- Q7** (a) State two (2) advantages of using negative feedback in the amplifier circuit design. (4 marks)
- (b) Figure **Q7** shows a series-shunt feedback network. The open-loop gain, A of this amplifier is 1×10^4 and the resistor $R_S = 1 \text{ k}\Omega$.
- (i) Derive the expression of the feedback factor, β (4 marks)
- (ii) Calculate the ratio of R_1/R_2 to obtain the closed-loop voltage gain, A_f of 5. Leave your answer in 3 decimal points (5 marks)
- (iii) If $v_s = 1 \text{ V}$, find the voltages v_o , v_f and v_i (4 marks)
- (iv) If the open loop gain decreases by 20%, deduce the corresponding decrease in the closed-loop voltage gain. (3 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014

PROGRAMME:

BEV

COURSE NAME: ELECTRONIC CIRCUIT THEORY

COURSE CODE:

BEF 12603

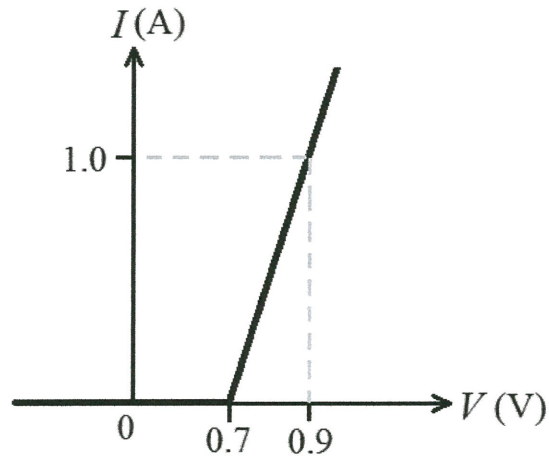


FIGURE Q1(a)

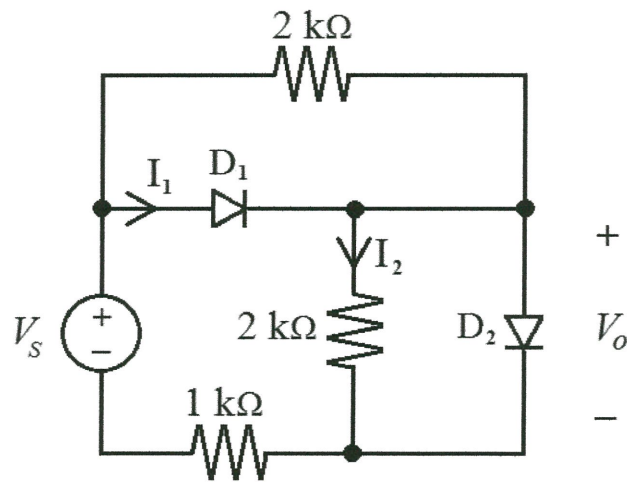


FIGURE Q1(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014

PROGRAMME:

BEV

COURSE NAME: ELECTRONIC CIRCUIT THEORY

COURSE CODE:

BEF 12603

TABLE Q2

V_s (V)	-10	0	2	5	7.5	10
V_o (V)						

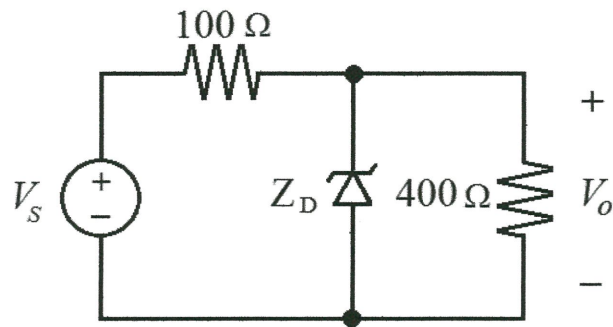


FIGURE Q2

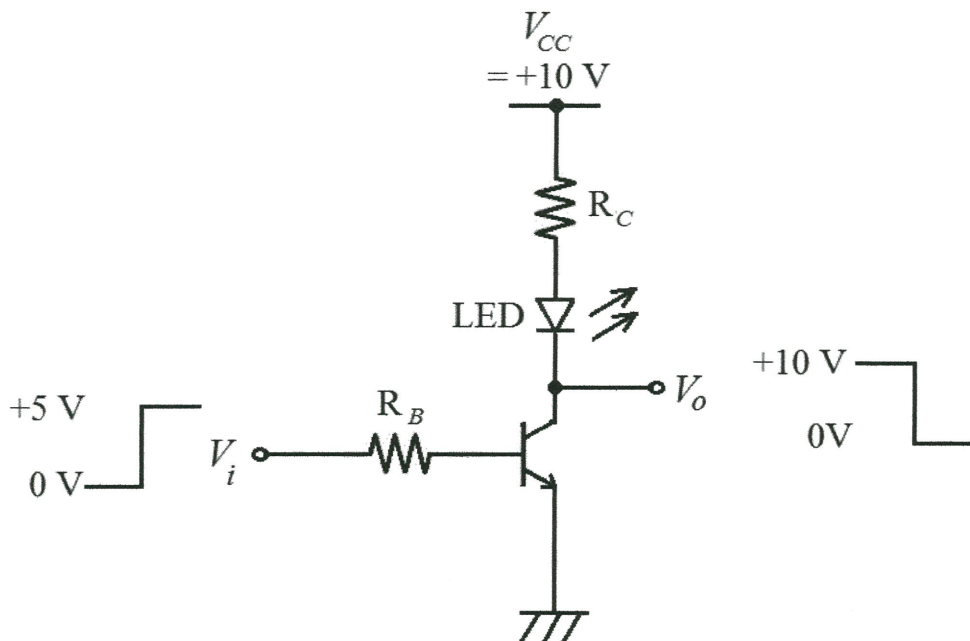


FIGURE Q3

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014

PROGRAMME:

BEV

COURSE NAME: ELECTRONIC CIRCUIT THEORY

COURSE CODE:

BEF 12603

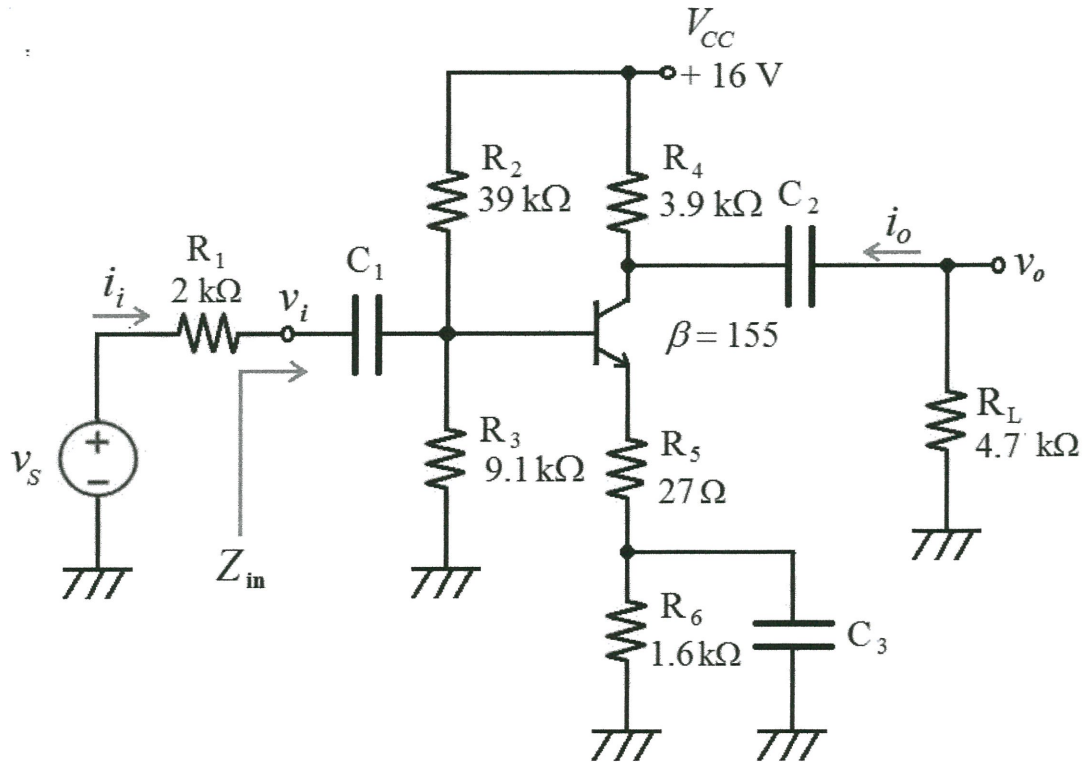


FIGURE Q4

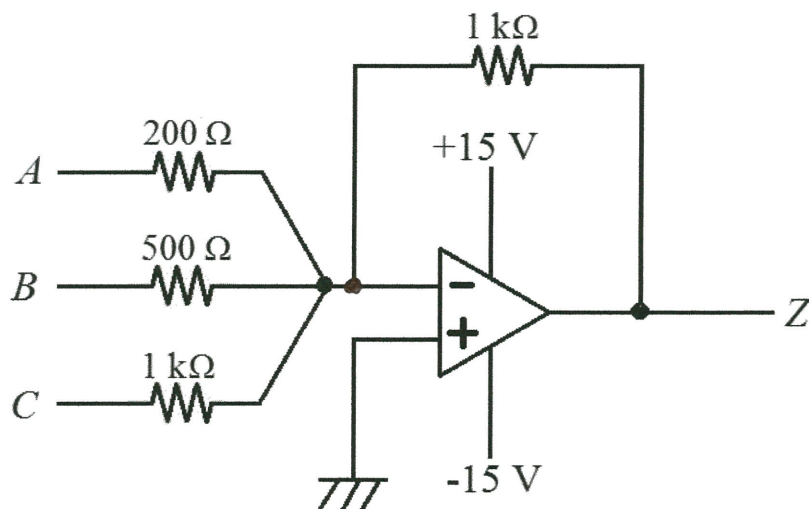


FIGURE Q5

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014

PROGRAMME:

BEV

COURSE NAME: ELECTRONIC CIRCUIT THEORY

COURSE CODE:

BEF 12603

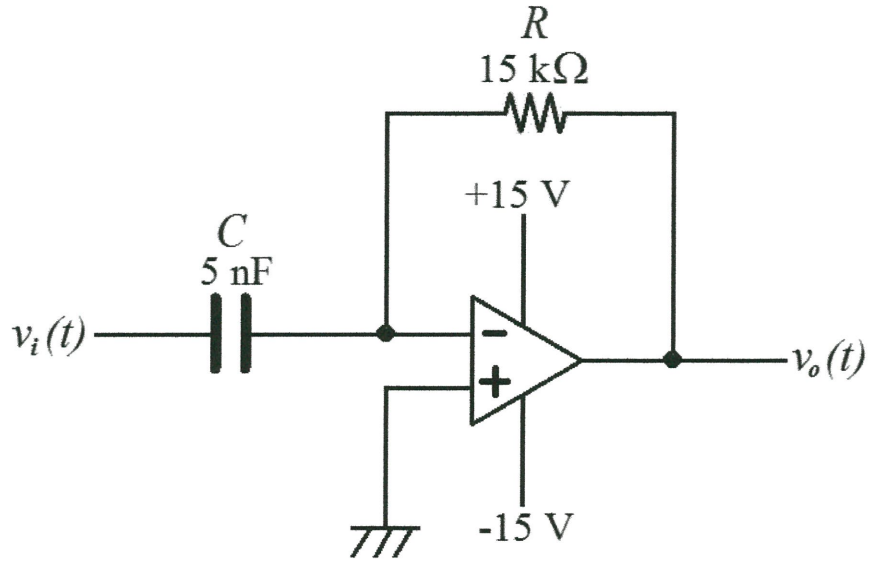


FIGURE Q6

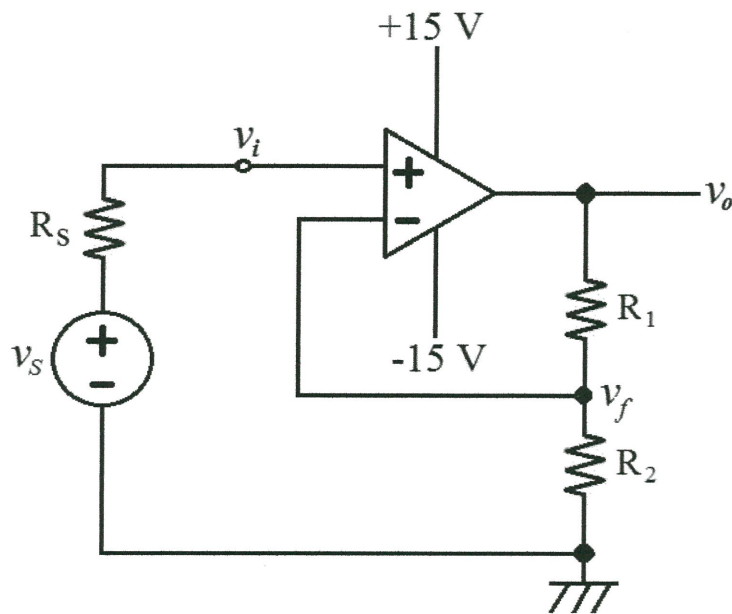


FIGURE Q7

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014

PROGRAMME:

BEV

COURSE NAME: ELECTRONIC CIRCUIT THEORY

COURSE CODE:

BEF 12603

FORMULA

Bipolar Junction Transistor (BJT)

$$\beta = \frac{I_C}{I_B}$$

$$\alpha = \frac{I_C}{I_E}$$

$$r_e = \frac{26 \text{ mV}}{I_E}$$

$$Z_{in} = R'_B \parallel \beta(r_e + R_E)$$

$$Z_{out} = R_C$$

} For common-emitter
amplifier

Amplifier Gain:

$$\text{Voltage gain, } A_v = \frac{v_o}{v_i}$$

$$\text{Current gain, } A_i = \frac{i_o}{i_i}$$

$$\text{Power gain, } A_p = \frac{p_o}{p_i}$$

$$\text{Voltage gain with feedback, } A_{vf} = \frac{A_o}{1 + A_o\beta}$$