



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2014/2015**

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I  
COURSE CODE : BEF 12403  
PROGRAMME : BACHELOR OF ELECTRICAL  
ENGINEERING WITH HONOURS  
EXAMINATION DATE : JUNE 2015 / JULY 2015  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

- Q1** (a) With the aid of appropriate mathematical expression, describe electric current, electric potential difference and energy for an element in a circuit. (6 marks)
- (b) A charge flowing in a wire is plotted in **Figure Q1(b)**. Sketch the corresponding current in the wire. (6 marks)
- (c) Calculate the power supplied or power absorbed by each element in **Figure Q1(c)**. (8 marks)
- Q2** (a) Determine the equivalent static resistance,  $R_{eq}$  and current,  $I_o$  for the circuit in **Figure Q2(a)**. (6 marks)
- (b) Solve the current flowing through the  $8\ \Omega$  resistor in **Figure Q2(b)**. (6 marks)
- (c) i) State the definition of *supernode* that is used in circuit analysis. (2 marks)
- ii) Calculate  $V_1$  and  $V_2$  in the circuit shown in **Figure Q2(c)** using nodal analysis. (6 marks)
- Q3** (a) In mesh analysis, explain the decision of using mesh currents instead of element currents as the circuit variables. (2 marks)
- (b) Evaluate currents  $I_1$ ,  $I_2$ , and  $I_3$  using mesh analysis for the circuit in **Figure Q3(b)**. (8 marks)
- (c) Establish the mesh-current equations by inspection for the circuit in by **Figure Q3(c)**. (10 marks)

- Q4** (a) By using superposition method, determine  $i_o$  for the circuit in **Figure Q4(a)**.  
(13 marks)
- (b) Establish the Norton equivalent circuit at terminal  $a-b$  for circuit in **Figure Q4(b)**.  
(7 marks)
- Q5** (a) Define the meaning of ‘*maximum power transfer*’  
(2 marks)
- (b) Find the Thevenin equivalent circuit of the circuit in **Figure Q5(b)** to the left of terminal  $a-b$ . Hence, evaluate the current through the  $R_L = 6 \Omega$  and  $R_L = 36 \Omega$   
(11 marks)
- (c) Determine the value  $R_L$  that will draw the maximum power for the circuit in **Figure Q5(c)**. Hence, calculate the maximum power.  
(7 marks)

– END OF QUESTIONS –

FINAL EXAMINATION

SEMESTER/SESSION : II/ 2014/ 2015

PROGRAMME : BEV

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I

COURSE CODE : BEF 12403

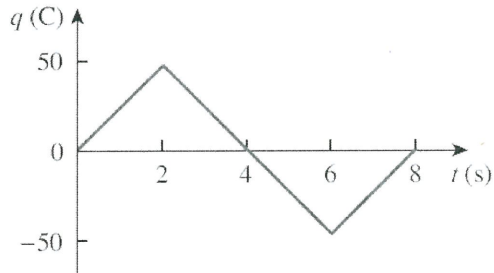


FIGURE Q1(b)

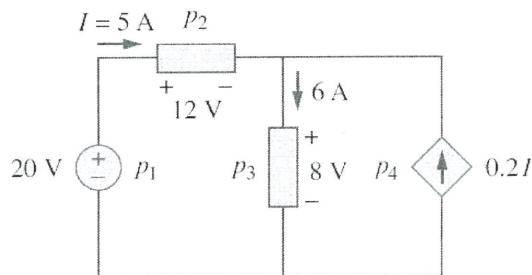


FIGURE Q1(c)

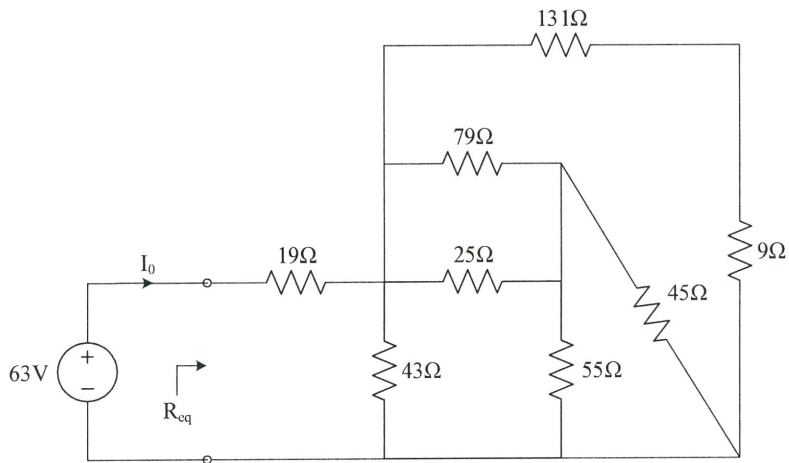


FIGURE Q2(a)


FINAL EXAMINATION

SEMESTER/SESSION : II/ 2014/ 2015


PROGRAMME : BEV

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I

COURSE CODE : BEF 12403

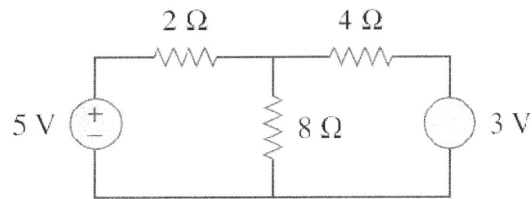

**FIGURE Q2(b)**

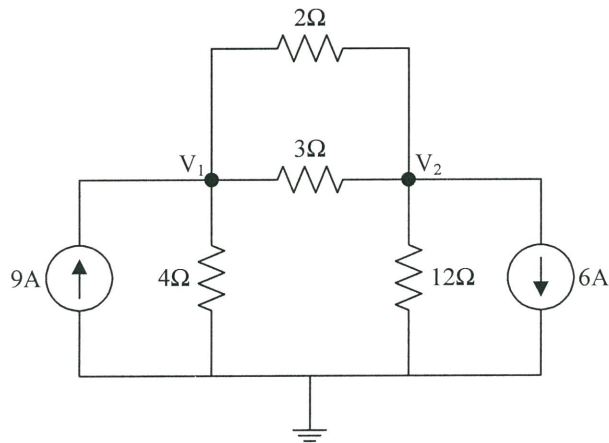

**FIGURE Q2(c)**


**FINAL EXAMINATION**

SEMESTER/SESSION : II/ 2014/ 2015


PROGRAMME : BEV

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I

COURSE CODE : BEF 12403

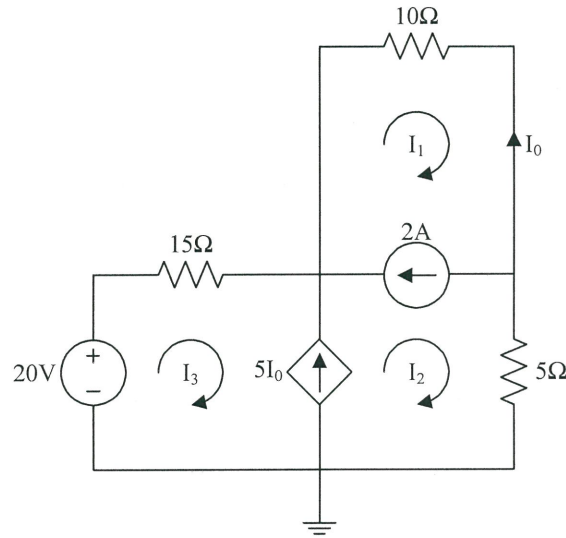

**FIGURE Q3(b)**

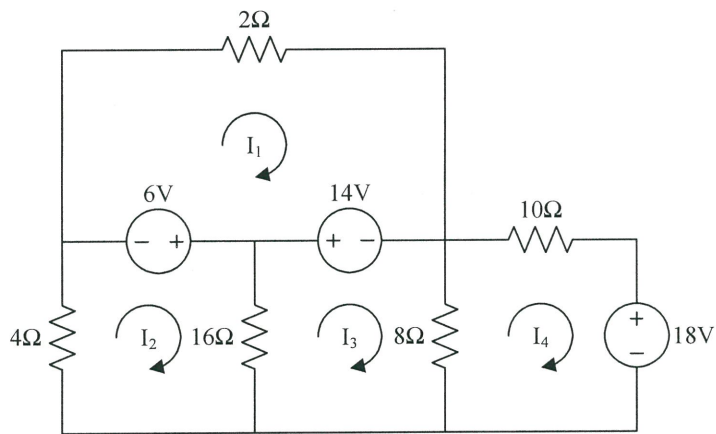

**FIGURE Q3(c)**


FINAL EXAMINATION

SEMESTER/SESSION : II/ 2014/ 2015


PROGRAMME : BEV

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I


COURSE CODE : BEF 12403

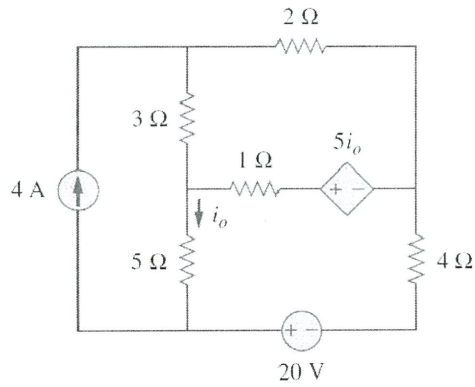

**FIGURE Q4(a)**

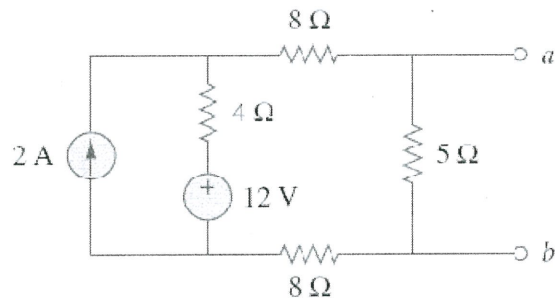

**FIGURE Q4(b)**

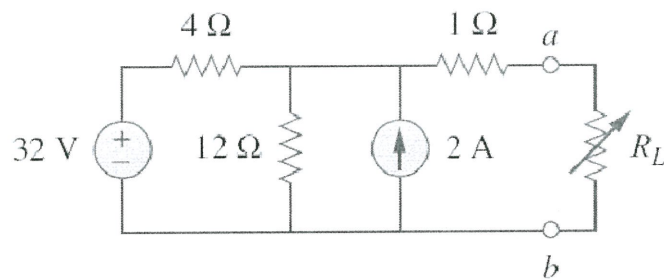

**FIGURE Q5(b)**


**FINAL EXAMINATION**

SEMESTER/SESSION : II/ 2014/ 2015

PROGRAMME : BEV

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I

COURSE CODE : BEF 12403

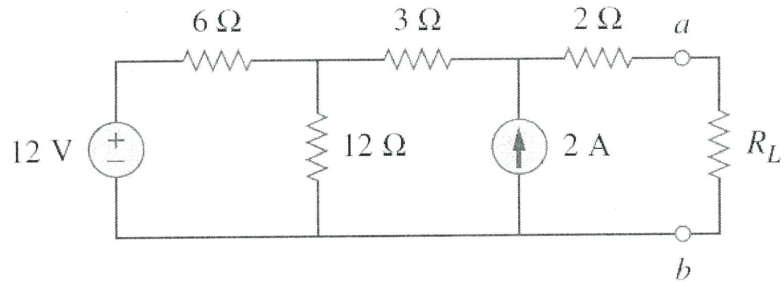

**FIGURE Q5(c)**