

**CONFIDENTIAL**



## **UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

### **FINAL EXAMINATION SEMESTER II SESSION 2014/2015**

COURSE NAME	:	ELECTRICAL AND ELECTRONIC TECHNOLOGY
COURSE CODE	:	BDA 14303 / BEX 17003
PROGRAMME	:	BACHELOR OF MECHANICAL ENGINEERING WITH HONOURS
EXAMINATION DATE	:	JUNE 2015 / JULY 2015
DURATION	:	3 HOURS
INSTRUCTION	:	<ol style="list-style-type: none"><li>1. ANSWER ALL QUESTIONS IN <b>SECTION A</b>. WRITE ANSWER IN THE ANSWER SHEET (PAGE 6).</li><li>2. ANSWER FOUR QUESTIONS ONLY IN <b>SECTION B</b>. WRITE ANSWER IN THE PROVIDED SPACE.</li><li>3. RETURN THIS QUESTION PAPER.</li></ol>

THIS QUESTION PAPER CONSISTS OF **EIGHTEEN (18) PAGES**

**CONFIDENTIAL**

**SECTION A**

**Q1** A hair dryer draws 5A from a 240V line. Find the resistance of the dryer.

- |                   |                     |
|-------------------|---------------------|
| (a) 1200 $\Omega$ | (c) 0.0208 $\Omega$ |
| (b) 48 $\Omega$   | (d) Undetermined    |

(2 marks)

**Q2** A water pump connected to a 240V line draws 0.24A. Find its power consumption.

- |           |                  |
|-----------|------------------|
| (a) 0.24W | (c) 4.167W       |
| (b) 57.6W | (d) Undetermined |

(2 marks)

**Q3** Find the total resistance for the circuit in **Figure Q3** at terminal A-C.

- |                   |                   |
|-------------------|-------------------|
| (a) 1.91 $\Omega$ | (c) 1.64 $\Omega$ |
| (b) 2.18 $\Omega$ | (d) None above    |

(2 marks)

**Q4** Find the total resistance for the circuit in **Figure Q3** at terminal D-E.

- |                   |                   |
|-------------------|-------------------|
| (a) 1.64 $\Omega$ | (c) 2.18 $\Omega$ |
| (b) 1.91 $\Omega$ | (d) None above    |

(2 marks)

**Q5** Find the total resistance for the circuit in **Figure Q3** at terminal B-C.

- |                   |                   |
|-------------------|-------------------|
| (a) 2.18 $\Omega$ | (c) 1.64 $\Omega$ |
| (b) 1.91 $\Omega$ | (d) None above    |

(2 marks)

**Q6** Solve the voltage across  $3\Omega$  resistor in **Figure Q6**.

- |            |                |
|------------|----------------|
| (a) 4.44 V | (c) 3.75 V     |
| (b) 5.56 V | (d) None above |

(2 marks)

**Q7** Solve the current through  $5\Omega$  resistor in **Figure Q6**.

- |            |                |
|------------|----------------|
| (a) 1.11 A | (c) 4.44 A     |
| (b) 0.37 A | (d) None above |

(2 marks)

**Q8** Find the power dissipated at  $5\Omega$  resistor in **Figure Q6**.

- |            |                |
|------------|----------------|
| (a) 6.16 W | (c) 98.57 W    |
| (b) 0.68 W | (d) None above |

(2 marks)

**Q9** Define the relation between  $V_{5\Omega}$ ,  $V_{6\Omega}$  and  $V_{9\Omega}$  for the circuit in **Figure Q6**.

- |   |   |
|---|---|
| (a) $V_{5\Omega} > V_{6\Omega} > V_{9\Omega}$ | (c) $V_{5\Omega} > V_{9\Omega} > V_{6\Omega}$ |
| (b) $V_{6\Omega} > V_{5\Omega} > V_{9\Omega}$ | (d) None above                                |

(2 marks)

**Q10** Solve the current through  $9\Omega$  for circuit in **Figure Q10**.

- |            |                |
|------------|----------------|
| (a) 2.73 A | (c) 4.50 A     |
| (b) 2.36 A | (d) None above |

(2 marks)

**Q11** Solve  $i_2$  for circuit in **Figure Q11**.

- |            |            |
|------------|------------|
| (a) 2.92 A | (c) 2.08 A |
| (b) 0 A    | (d) 5.00 A |

(2 marks)

**Q12** Select the correct method for obtaining Thevenin resistance.

- (a) Both voltage and current sources are ‘open’.
- (c) Voltage sources are ‘open’ and current sources are ‘shorted’.
- (b) Voltage sources are ‘shorted’ and current sources are ‘open’.
- (d) Both voltage and current sources are ‘shorted’.

(2 marks)

**Q13** Identify a dielectric material which is suitable for the construction of capacitor.

- (a) Tantalum
- (c) Copper
- (b) Aluminium
- (d) Paper

(2 marks)

**Q14** Find the total capacitance for circuit in **Figure Q14**.

- (a) 15 F
- (c) 3.33 F
- (b) 7.50 F
- (d) None above

(2 marks)

**Q15** Find the total inductance for circuit in **Figure Q15**.

- (a) 15 H
- (c) 3.33 H
- (b) 7.50 H
- (d) None above

(2 marks)

**Q16** **Figure Q16** shows a typical alternate current waveform. Identify the waveform period.

(2 marks)

**Q17** Select the parameter which CANNOT be changed by a transformer.

- (a) Voltage
- (c) Current
- (b) Power
- (d) None above

(2 marks)

**Q18** Select the electric motor which is NOT an AC motor.

- (a) Stepper motor
- (c) Synchronous motor
- (b) Induction motor
- (d) None above

(2 marks)

**Q19** Choose the logic gate for the given input and output in **Figure Q19**.

- |            |                |
|------------|----------------|
| (a) Buffer | (c) NOR        |
| (b) AND    | (d) None above |

(2 marks)

**Q20** Choose the logic gate for the given input and output in **Figure Q20**.

- |          |                |
|----------|----------------|
| (a) NAND | (c) X-NOR      |
| (b) X-OR | (d) None above |

(2 marks)

**SECTION A ANSWER SHEET**

Q1	
Q2	
Q3	
Q4	
Q5	
Q6	
Q7	
Q8	
Q9	
Q10	

Q11	
Q12	
Q13	
Q14	
Q15	
Q16	
Q17	
Q18	
Q19	
Q20	

**SECTION B**

- Q21** (a) Construct a basic transformer structure. Identify and label the core, primary winding and secondary winding.

(3 marks)

- (b) Compare between a step-up transformer and a step-down transformer.

(2 marks)

- (c) An ideal transformer is rated at 2400/120 V, 9.6 kVA, and has 50 turns on the secondary side. Calculate:

- (i) The turn ratio.

(3 marks)

- (ii) The number of turn on the primary side.

(3 marks)

- (iii) The current rating for primary and secondary winding.

(4 marks)

**Q22 (a)** Evaluate the logic circuit in **Figure Q27** and obtain the Boolean expression for Z.

(6 marks)

**(b)** Analyse the logic circuit in **Figure Q27** and fill in the truth table below.

(9 marks)

A	B	C	Z

**Q23 (a) Compare four characteristics of AC and DC motors.**

(8 marks)

**(b) Construct the general equivalent circuit of a DC motor.**

(7 marks)

**Q24 (a)** Referring to **Figure Q24**, analyse the current and power absorbed by the  $8\Omega$  resistor using source transformation method.

(8 marks)

**(b)** Illustrate and explain the concept of maximum power transfer.

(7 marks)

**Q25** **Figure Q25(a)** shows the input of AC supply voltage which is given in rms. Its signal is shown in **Figure Q25(b)**. Determine for:

- (a) period (T).
- (b) frequency (Hz).
- (c) rms current.
- (d) rms, peak and peak-peak voltages across  $500\Omega$  resistor.
- (e) sketch the current waveform and label the peak current.

(15 marks)

**Q26** (a) Construct the Norton equivalent circuit for the circuit in **Figure Q26** with referring to terminal A-B.

(9 marks)





(b) List down three factors which determine the value of capacitance.

(6 marks)

**- END OF QUESTIONS -**




**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE : BDA14303/BEX17003

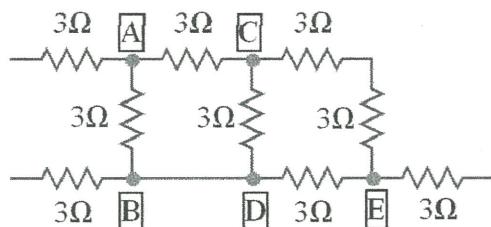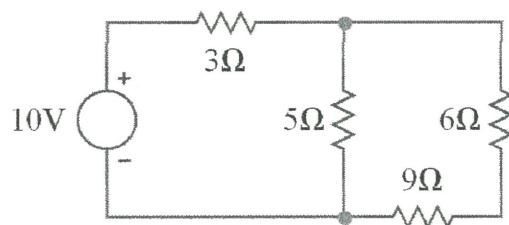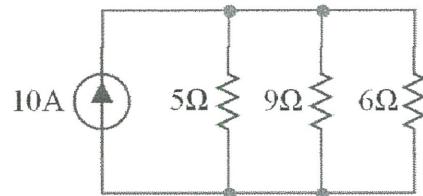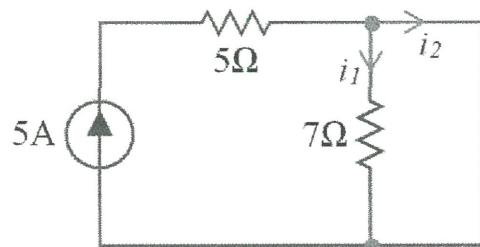**FIGURE Q3****FIGURE Q6****FIGURE Q10****FIGURE Q11**



**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE : BDA14303/BEX17003

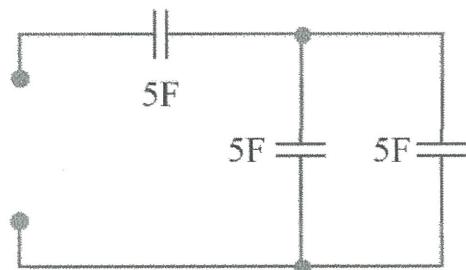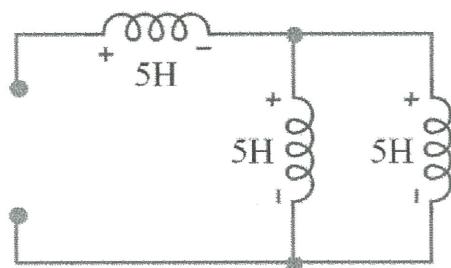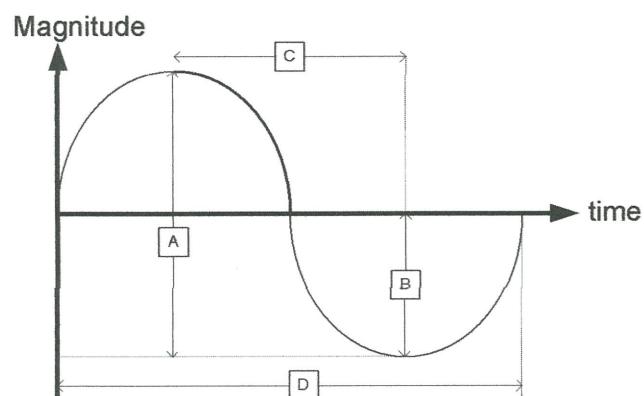**FIGURE Q14****FIGURE Q15****FIGURE Q16**



**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE : BDA14303/BEX17003

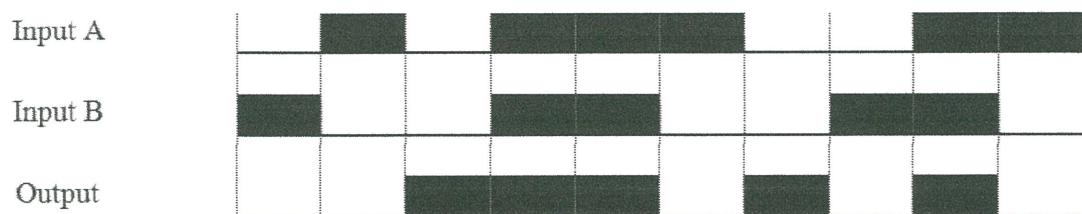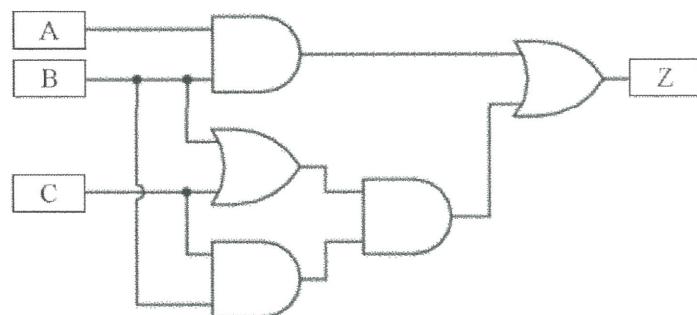**FIGURE Q19****FIGURE Q20****FIGURE Q22**


**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
 COURSE CODE : BDA14303/BEX17003

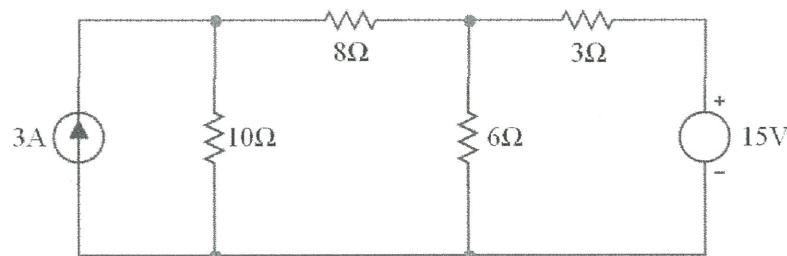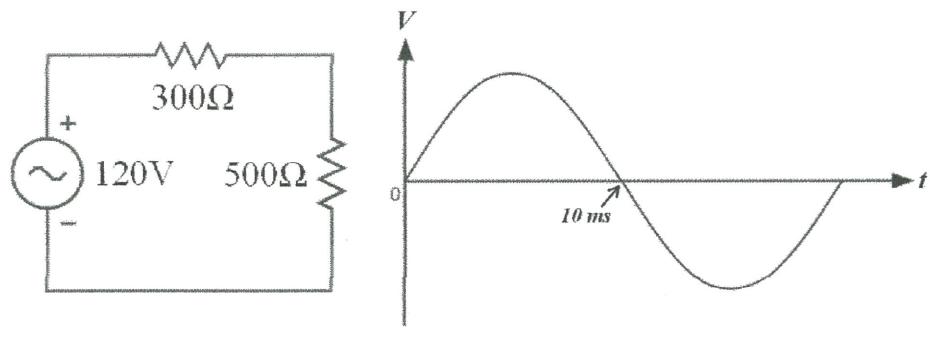**FIGURE Q24**

(a)

(b)

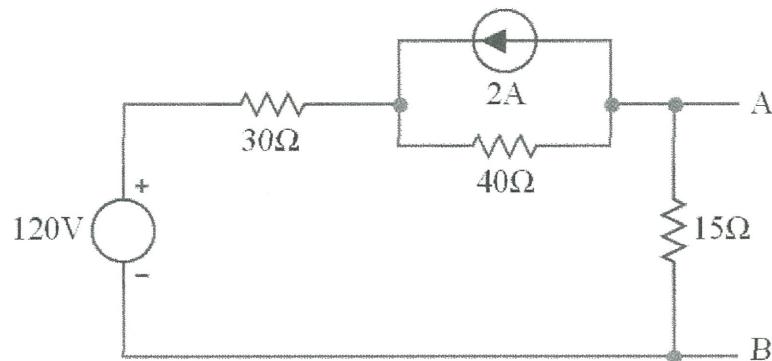**FIGURE Q25****FIGURE Q26**

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
 COURSE CODE : BDA14303/BEX17003

**LIST OF FORMULA****OHMS LAW**

$$V = IR$$


**JOULE'S LAW**

$$P = IV$$

**KIRCHHOFF LAW**

$$\sum_{k=1}^n i_k = 0$$

$$\sum_{v=1}^n v_k = 0$$

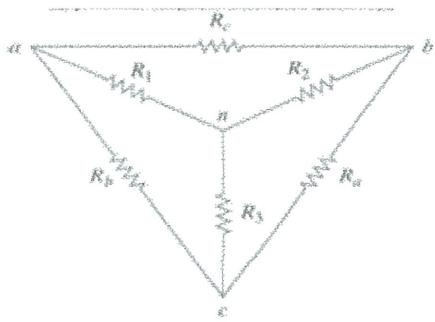**WYE-DELTA TRANSFORMATION**

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

**CAPACITOR AND INDUCTOR**

$$C = \frac{\epsilon A}{d}$$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt + v(t_0)$$

$$i = C \frac{dv}{dt}$$

$$w = \frac{1}{2} Cv^2$$

$$L = \frac{N^2 \mu A}{l}$$

$$v = L \frac{di}{dt}$$

$$i = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$w = \frac{1}{2} Li^2$$

$$\tau = RC$$

$$\tau = \frac{L}{R}$$

**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
COURSE CODE : BDA14303/BEX17003

**PHASOR REALTIONSHIP**

$$v(t+T) = v(t)$$

$$f = \frac{1}{T}$$

$$z = x + jy = r\angle\phi = r(\cos\phi + j\sin\phi)$$

**ALTERNATING CURRENT POWER CALCULATION**

$$P(t) = v(t)i(t) \quad \text{Instantaneous power}$$

$$P = \frac{1}{2} \operatorname{Re}[VI^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \text{Average power}$$

$$i_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$P_{RMS} = I_{RMS}^2 R = \frac{V_{RMS}^2}{R}$$

## FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2014/2015      PROGRAMME : 1 BDA  
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY  
 COURSE CODE : BDA14303/BEX17003

## LOGIC GATES

Name	Graphic symbol	Algebraic function	Truth table															
AND		$x = A \cdot B$ or $x = AB$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	x	0	0	0	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$x = A + B$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	1
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$x = A'$	<table border="1"> <thead> <tr> <th>A</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	x	0	1	1	0									
A	x																	
0	1																	
1	0																	
Buffer		$x = A$	<table border="1"> <thead> <tr> <th>A</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td></tr> </tbody> </table>	A	x	0	0	1	1									
A	x																	
0	0																	
1	1																	
NAND		$x = (AB)'$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	x	0	0	1	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$x = (A + B)'$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	0
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$x = A \oplus B$ or $x = A'B + AB'$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	x	0	0	0	0	1	1	1	0	1	1	1	0
A	B	x																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR or equivalence		$x = (A \oplus B)'$ or $x = A'B' + AB$	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>x</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	x	0	0	1	0	1	0	1	0	0	1	1	1
A	B	x																
0	0	1																
0	1	0																
1	0	0																
1	1	1																