



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2014/2015**

COURSE NAME : ELECTRONIC CIRCUITS  
ANALYSIS AND DESIGN

COURSE CODE : BEL 30403

PROGRAMME : BACHELOR DEGREE OF  
ELECTRONIC ENGINEERING  
WITH HONOURS

EXAMINATION DATE : JUNE 2015/JULY 2015

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **NINE (9)** PAGES

- Q1** (a) Figure **Q1(a)** shows a circuit to measure temperature. The temperature sensor in this circuit has a resistance  $R_T$  which changes with temperature according to the following equation:

$$R_T = 1000e^{-(T/25^\circ)}$$

where  $T$  is the temperature in  $^\circ\text{C}$  and  $R_T$  unit is in ohm ( $\Omega$ ).

The output voltage ( $V_o$ ) is 0 V at  $-55^\circ\text{C}$ . The meter used in the circuit will reach the full-scale deflection at  $125^\circ\text{C}$  and this is achieved when the current through the meter is at 1 mA. Design the circuit by finding the value of resistors  $R_X$ ,  $R_T$  and  $R_Y$  to fulfill the specification of the circuit as described above.

(10 marks)

- (b) Figure **Q1(b)** shows the waveforms of input voltage ( $V_i$ ) and output voltage ( $V_o$ ) of a Schmitt Trigger circuit. Based on this figure, design the Schmitt Trigger circuit that produces those waveforms using a feedback resistor of 15 k $\Omega$ . Draw the complete circuit and also the circuit transfer characteristic graph.

(10 marks)

- Q2** (a) Consider the circuit in Figure **Q2(a)**, derive the gain transfer function,  $H(s) = \frac{V_o(s)}{V_i(s)}$  of the circuit.

(8 marks)

- (b) Second-order band pass filter can be constructed by cascading a second-order high pass filter and a second-order low pass filter, as shown in Figure **Q2(b)**. For this circuit;

- (i) Determine the value of capacitor of  $C_a$  and  $C_b$  in order to have the low cut-off frequency,  $f_{c1}$  of 1026Hz and high cut-off frequency,  $f_{c2}$  of 7186Hz.

(4 marks)

- (ii) Calculate the centre frequency,  $f_o$  and quality factor,  $Q$  of the circuit.

(4 marks)

- (iii) Draw the frequency response of this filter.

(2 marks)

- (iv) If the filter is the Butterworth type, find out the needed value of  $R_F$  if the factors of polynomials  $P_n(s)$  is as below;

$$s^2 + 1.414s + 1$$

(2 marks)

- Q3** (a) For the circuit shown in Figure **Q3(a)**:
- (i) Determine the amplifier type and feedback topology (2 marks)
  - (ii) Derive the input impedance with feedback,  $Z_{if}$  and state whether it is increased or decreased from that without feedback. (5 marks)
  - (iii) If  $A_f = 10$ ,  $Z_{if} = 500\text{k}\Omega$ ,  $Z_o = 2\text{k}\Omega$ , and  $Z_{of} = 25\text{k}\Omega$ , calculate  $Z_i$ ,  $A_{ic}$  and  $\beta$ . (6 marks)
- (b) An amplifier without feedback network has a gain of 200 and the gain bandwidth product (GBP) of 30 MHz. A negative feedback amplifier is imposed on this amplifier with the following feedback factor of  $1+A\beta = 23.33$ .
- (i) Calculate the gain and the GBP for the amplifier with the feedback. (3 marks)
  - (ii) If the low and high cut-off frequency without feedback is 3.5 kHz and 153.5 kHz respectively, compute the new low and high cut-off frequency with feedback. (4 marks)
- Q4** (a) State the name of the oscillator in Figure **Q4(a)** and draw the output waveform  $V_o$ . Design the oscillator circuit such that the output waveform  $V_o$  has a frequency of oscillation at 10 kHz. (10 marks)
- (b) A one-shot multivibrator circuit that uses a 555 timer generates a pulse waveform ( $V_o$ ) at pin 3, when it receives an input trigger ( $V_T$ ) at pin 2, as shown in Figure **Q4(b)**.
- (i) Use a 555 timer IC as in Figure **Q4(b)(i)** to design the circuit. Draw and completely label the circuit. Use a 1 nF capacitor for the design. (7 marks)
  - (ii) Explain why the trigger voltage  $V_T$  must be as shown in Figure **Q4(b)** to trigger the output. (3 marks)

**Q5** Figure **Q5** is a voltage regulator circuit.


- (a) Briefly describe how the circuit operates when there is a slight increase in the regulated output voltage. (4 marks)
- (b) Find the value of the regulated output voltage. (3 marks)
- (c) Calculate the power dissipated by the transistor. (9 marks)
- (d) Obtain the range for  $R_S$  that can be used in the circuit to ensure the Zener diode is in the breakdown region. Given parameter:  $P_{Zmax} = 60\text{mW}$  and  $I_{Zmin} = 2\text{mA}$ . (4 marks)

**– END OF QUESTION –**


**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015  
 COURSE NAME : ELECTRONIC CIRCUIT  
 ANALYSIS AND DESIGN

PROGRAM : 3 BEJ  
 KOD KURSUS : BEL30403

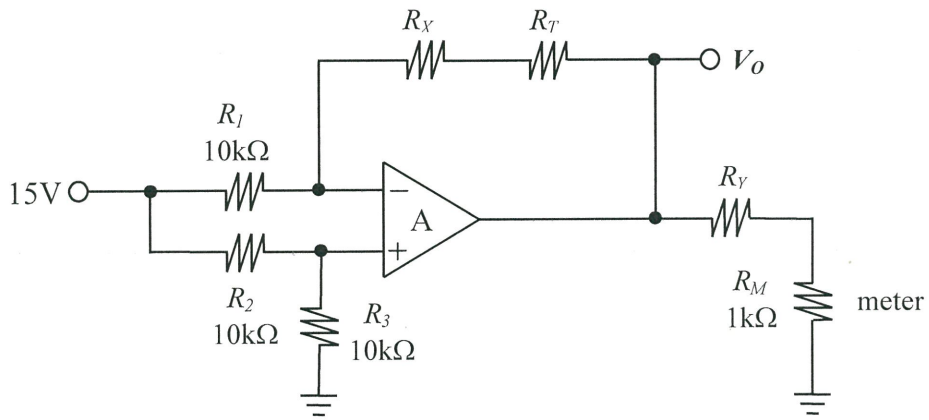

**FIGURE Q1(a)**

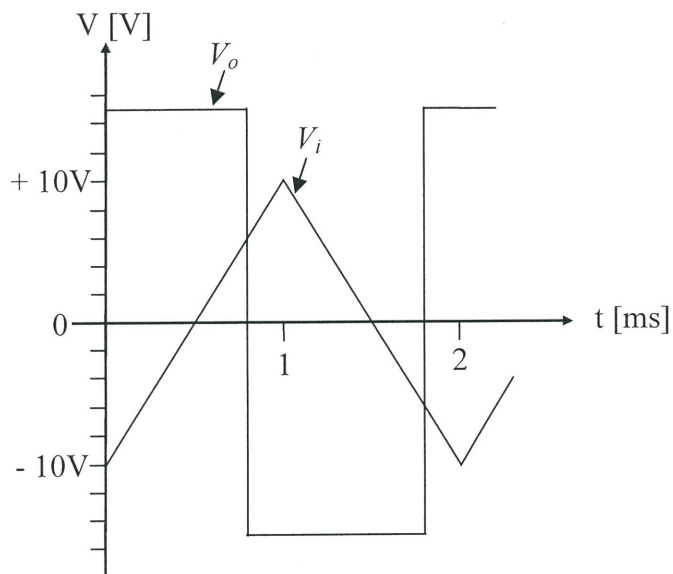

**FIGURE Q1(b)**

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2014/2015  
COURSE NAME : ELECTRONIC CIRCUIT  
ANALYSIS AND DESIGN

PROGRAM : 3 BEJ  
KOD KURSUS : BEL30403

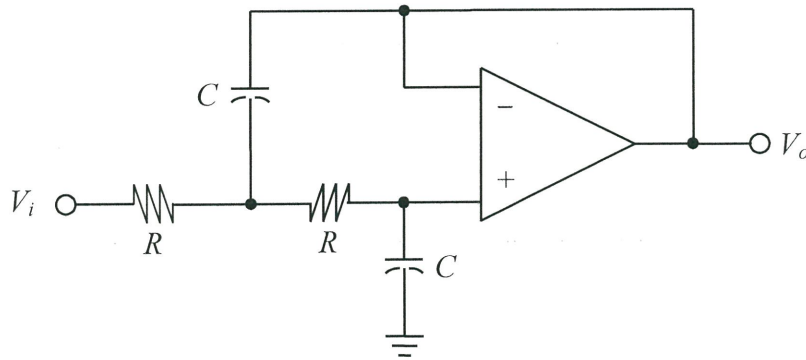


FIGURE Q2(a)

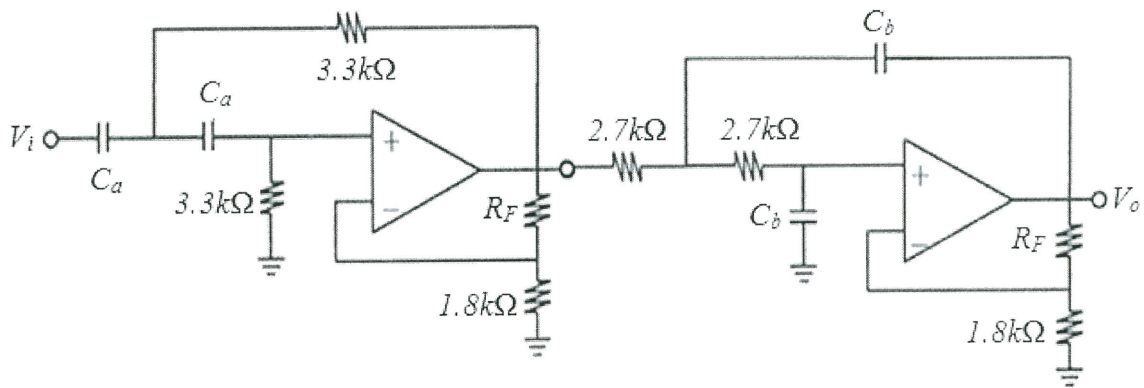



FIGURE Q2(b)




**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015  
 COURSE NAME : ELECTRONIC CIRCUIT  
 ANALYSIS AND DESIGN

PROGRAM : 3 BEJ  
 KOD KURSUS : BEL30403

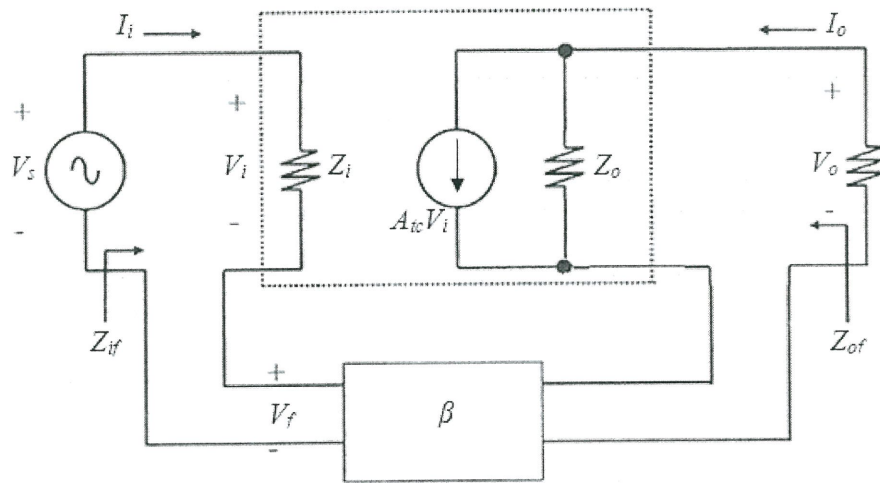

**FIGURE Q3(a)**

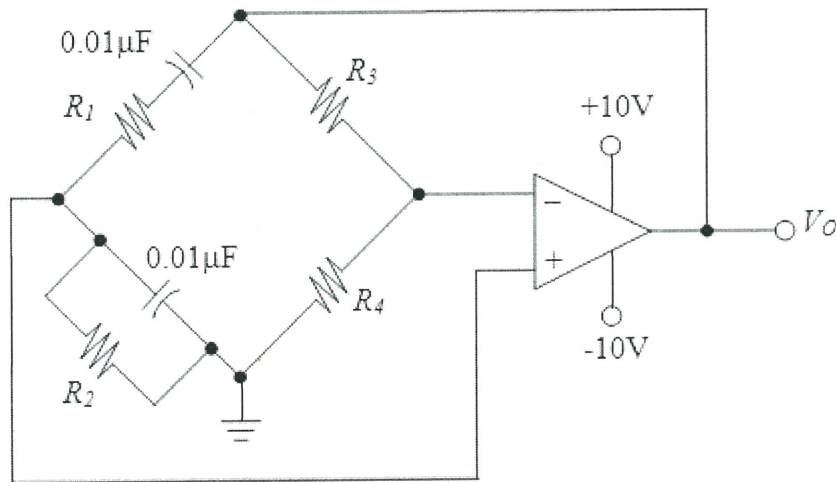


**FIGURE Q4(a)**


**FINAL EXAMINATION**

SEMESTER / SESSION : SEM II / 2014/2015  
 COURSE NAME : ELECTRONIC CIRCUIT  
 ANALYSIS AND DESIGN

PROGRAM : 3 BEJ  
 KOD KURSUS : BEL30403

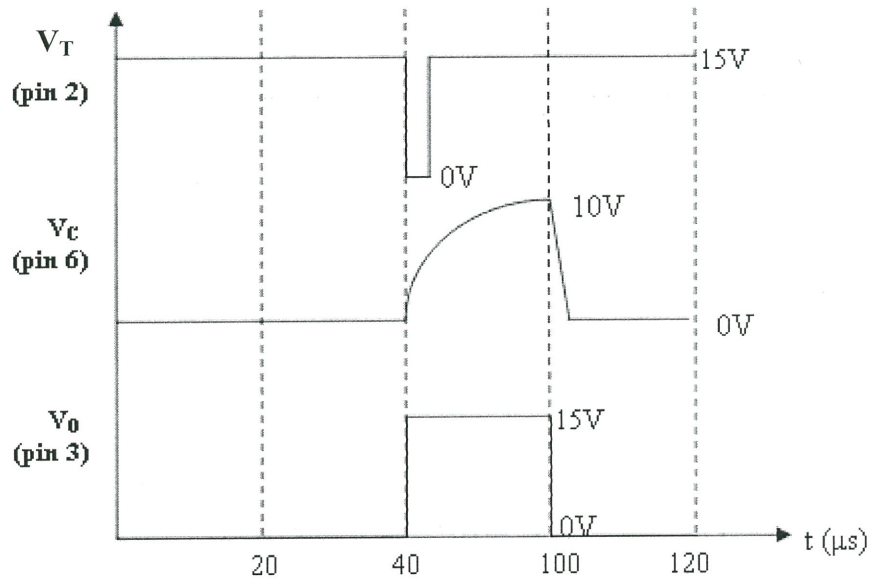

**FIGURE Q4(b)**

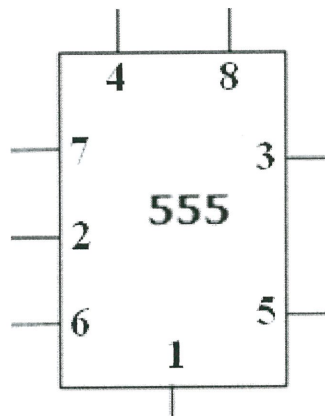

**FIGURE Q4(b)(i)**



FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2014/2015  
COURSE NAME : ELECTRONIC CIRCUIT  
ANALYSIS AND DESIGN

PROGRAM : 3 BEJ  
KOD KURSUS : BEL30403

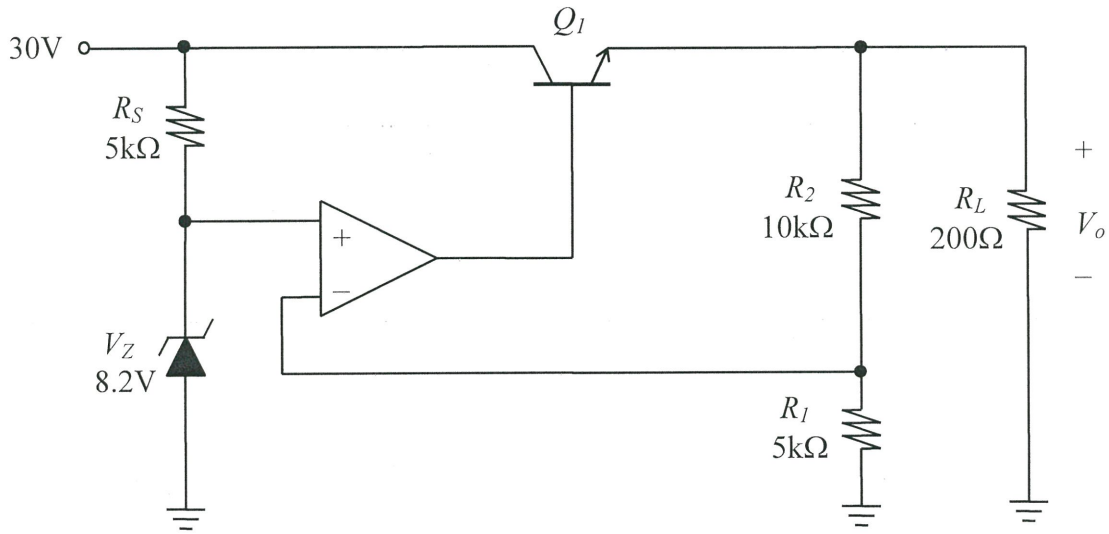


FIGURE Q5