

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2015/2016**

COURSE NAME : DIGITAL SYSTEM DESIGN
COURSE CODE : BEC 30503
PROGRAMME : BACHELOR OF ELECTRONIC
ENGINEERING WITH HONOURS
EXAMINATION DATE : DECEMBER 2015 / JANUARY 2016
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **FOUR (4)** PAGES.

CONFIDENTIAL

CONFIDENTIAL

BEC 30503

- Q1**
- (a) State TWO (2) predominant hardware description languages. (2 marks)
 - (b) Discuss a difference between FPGA devices and ASIC devices. (2 marks)
 - (c) Sketch a typical design flow chart of CAD tools to implement a design into FPGA chip. (6 marks)
 - (d) Briefly discuss the flow chart in **Q1(c)**. (10 marks)

- Q2** **Figure Q2** shows a combination of three 2x1 multiplexers to create a 4x1 multiplexer.
- (a) Clearly explain the difference between a structural HDL description and a behavioral HDL description. (5 marks)
 - (b) Create a behavioral HDL description of a 2x1 multiplexer described in **Figure Q2**. (5 marks)
 - (c) Create a structural HDL description of a 4x1 multiplexer that combines three 2x1 multiplexers in **Figure Q2**. (10 marks)

 


Figure Q2

Q3 Table 3.1 lists the desired operations for a multifunction calculator to perform various basic Boolean operations.

TABLE 3.1: Desired operations.

Inputs			Operation
x	y	z	
0	0	0	$S = A + B$
0	0	1	$S = A \text{ AND } B$ (bitwise AND)
0	1	0	$S = A \text{ NAND } B$ (bitwise NAND)
0	1	1	$S = A \text{ OR } B$ (bitwise OR)
1	0	0	$S = A \text{ NOR } B$ (bitwise NOR)
1	0	1	$S = A \text{ XOR } B$ (bitwise XOR)
1	1	0	$S = A \text{ XNOR}$ (bitwise XNOR)
1	1	1	$S = \text{NOT } A$ (bitwise complement)

- (a) Create a block diagram for a multifunction calculator without using an arithmetic logic unit. The calculator has two 8-bit inputs A and B , and control inputs x , y and z .
(10 marks)
- (b) Build a simple logic calculator using dual in-line package (DIP) switches for input and LEDs for output. The logic calculator should have three DIP switch inputs to select which logic operation to perform. A register is used to block output changes as the user configures the switches. The LEDs will display the value after a button e is pressed by user.
(4 marks)
- (c) Explain and justify TWO (2) weaknesses of the design without arithmetic logic unit.
(6 marks)

Q4 Register-transfer level (RTL) design involves transferring data from registers, through other datapath components like adders, and back to register.

- (a) Describe the steps of the RTL design process.
(8 marks)
- (b) Create a datapath for the desired behavior to perform computations on input data shown in **Figure Q4**.
(12 marks)

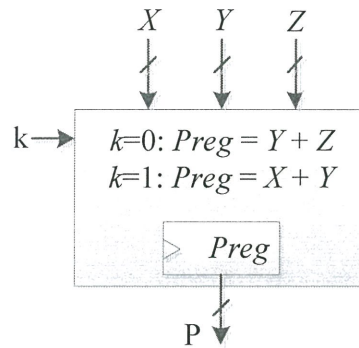


Figure Q4

- Q5 (a) List all single faults in the circuit in **Figure Q5(a)** that can be detected using each of the test $w_1w_2w_3w_4 = 1100$ and 0110 . (8 marks)
- (b) For the circuit shown in **Figure Q5(b)**, sensitize each path in this circuit to obtain a complete test set that comprises a minimum number of tests. (13 marks)

 


Figure Q5(a)

 


Figure Q5(b)

- END OF QUESTIONS -