

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2015/2016**

**COURSE NAME** : INSTRUMENTATION AND MEASUREMENT  
**COURSE CODE** : BEH 10102  
**PROGRAMME CODE** : BEJ  
**EXAMINATION DATE** : JUNE/JULY 2016  
**DURATION** : 2 HOURS 30 MINUTES  
**INSTRUCTION** : ANSWER ALL QUESTIONS

**THIS PAPER CONSISTS OF EIGHT (8) PAGES**

**CONFIDENTIAL**

- Q1** (a) Draw the block diagram of the instrumentation system. (2 marks)
- (b) Explain the meaning of measurement, resolution and sensitivity. (3 marks)
- (c) Three resistors that are connected to each other are shown in **Figure Q1(c)**. Each resistor has a nominal resistance value of  $270 \Omega$  with tolerance of  $\pm 10 \%$  for  $R_1$ ,  $\pm 5 \%$  for  $R_2$  and  $\pm 15 \%$  for  $R_3$ . These resistors are specified at  $25^\circ\text{C}$  and their temperature coefficient is  $500 \text{ ppm}/^\circ\text{C}$ . By applying appropriate measurement error combination formula, calculate the total resistance,  $R_T$  of the circuit and its tolerance. (10 marks)
- (d) **Table Q1(d)** shows one set of recorded voltage measurements obtained after 8 times repetition measurement. Calculate the precision of the 4<sup>th</sup> measurement. (5 marks)
- Q2** (a) The strain gauge is an example of a passive transducer that uses electrical resistance variation in wires to sense the strain produced by a force on the wires. With the help of diagram, explain the 2 types of strain gauge in terms of their advantageous and disadvantageous. (5 marks)
- (b) **Figure Q2(b)** shows a strain gauge applied in a bridge circuit. All resistors including the strain gauge have a resistance of  $250 \Omega$ . During a load test, the strain gauge undergoes a change of  $1.02 \Omega$ . If the applied tensile strain is  $1450\mu$ , determine:
- (i) The gauge factor. (2 marks)
- (ii) The bridge offset voltage,  $V_{out}$  if  $V_S$  is 12 V. (3 marks)
- (c) A parallel-plate capacitor has plates with area of  $4 \times 10^{-3} \text{ m}^2$ . The distance between the plates is  $5 \times 10^{-4} \text{ m}$ . Determine the capacitance (in nF) if the dielectric is ceramic ( $k=1000$ ) and the permittivity,  $\epsilon$  is  $8.854 \times 10^{-12} \text{ F/m}$ . (2 marks)
- (d) **Figure Q2(c)** shows a photoconductive cell circuit with its corresponding illumination characteristics. The photoconductive cell is used to control the relay. When the cell is illuminated at  $50 \text{ lm/m}^2$ , the circuit delivers 1 mA at 25 V setting whereas the circuit becomes deenergized when the cell is dark. By referring to the illumination characteristics graph, calculate:
- (i) The required series resistance. (4 marks)
- (ii) The level of the dark current. (4 marks)

- Q3** (a) **Figure Q3(a)** shows the Wheatstone bridge circuit. The resistance values for  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  are  $1\text{ k}\Omega$ ,  $1.6\text{ k}\Omega$ ,  $3.5\text{ k}\Omega$  and  $7.5\text{ k}\Omega$  respectively.
- (i) With a clear justification, analyse whether or not the bridge is balanced. (2 marks)
  - (ii) If the internal resistance of the galvanometer is  $200\ \Omega$ , determine the current through the galvanometer using Thevenin equivalent circuit. (10 marks)
  - (iii) Determine the deflection (mm) of the galvanometer's pointer if the sensitivity of the detector is  $2.5\text{ mm}/\mu\text{A}$ . (2 marks)
- (b) A Kelvin double bridge is shown in **Figure Q3(b)**. Compute the value of  $R_x$  when  $R_a$  is  $1200\ \Omega$ ,  $R_b$  is  $1600R_b$ ,  $R_1$  is  $800R_b$  and  $R_2$  is  $1.25R_2$ . (6 marks)
- Q4** (a) An instrumentation engineer has decided to use a potentiometric sensor to measure the bumpiness of a roadway by moving it to the right as shown in **Figure Q4(a)**. The potentiometric sensor, which consists of a resistive position transducer (resistance of  $10\text{ k}\Omega$ ) and a shaft stroke (movable arm) of  $8\text{ cm}$ , is connected to a bridge circuit. Assuming the initial position is when the shaft is at the mid stroke:
- (i) Derive the formula for  $V_{out}$  in terms of the value of the resistors in the circuit. (2 marks)
  - (ii) Calculate the  $V_{out}$  when the shaft of the transducer is at initial position. (2 marks)
  - (iii) Determine the  $V_{out}$  when the shaft has reached point A. (6 marks)
- (b) A numerical control (NC) worktable as shown in **Figure Q4(b)** is scheduled for a preventive maintenance of its incremental optical encoder. During the preventive maintenance procedure, the appointed engineer has to ensure that the control system should receive  $6000$  pulses when the table is moved by  $300\text{ mm}$ . If the lead screw has a pitch of  $30\text{ mm}$  and is coupled to the motor shaft with a gear ratio of  $12:1$  (twelve turns of drive motor for each turn of the screw), calculate:
- (i) The pulses/rev that the incremental encoder can generate of its output shaft. (2 marks)
  - (ii) The resolution (in mm/pulses) of the NC worktable. (2 marks)
  - (iii) The encoder pulse rate (pulses/sec) if the table is moved at  $600\text{ mm}/\text{min}$ . (2 marks)
  - (iv) The drive motor speed in terms of revolution per minute (RPM) if the table is moved at the speed as specified in **Q4(b)(iii)**. (4 marks)

- Q5** (a) Draw the logic NOR gate and its truth table. (2 marks)
- (b) A first year student is assigned to design an interface circuit of a temperature sensor to an 8-bit of Analog to Digital Converter (ADC). This sensor is able to sense from 5 °C to 125 °C using a single positive supply. Meanwhile, the output voltage of temperature sensor has a linear scale factor of + 5.5 mV/°C. If 5 V is used as voltage reference:
- (i) Determine the sensor output (in voltage) at minimum and maximum temperature that the sensor can sense. (3 marks)
- (ii) Calculate required gain at 125 °C. (4 marks)
- (iii) Determine the temperature resolution at 125 °C. (6 marks)
- (c) A sensor signal is converted to a frequency that varies from 2 kHz to 20 kHz.
- (i) If this signal is to be converted into 6-bit digital signal, determine the count time,  $T_c$  in second when the frequency is at maximum. (2.5 marks)
- (ii) Determine the pulses count output when the frequency is at minimum in 6-bit binary form. (2.5 marks)

**- END OF QUESTIONS -**

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2015/2016      PROGRAMME : 1 BEJ  
COURSE NAME : INSTRUMENTATION & MEASUREMENT      COURSE CODE : BEH10102

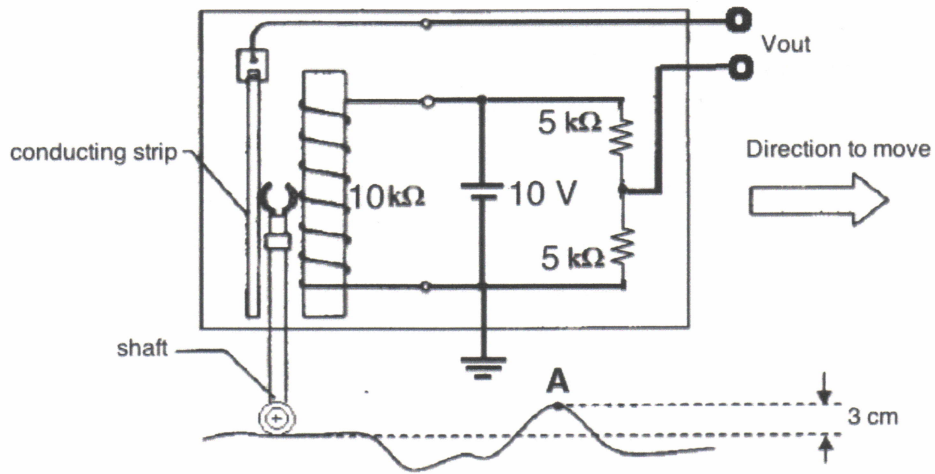


Figure Q4 (a)

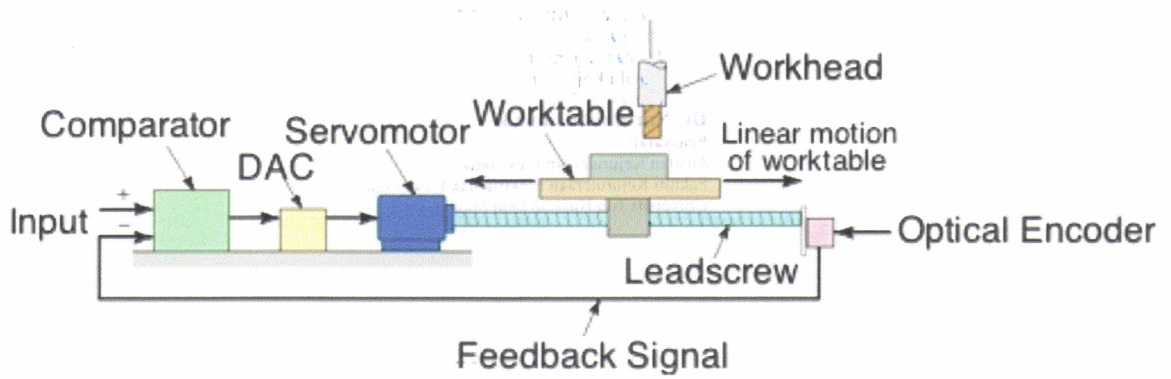


Figure Q4 (b)