

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2015/2016**

COURSE NAME : POWER SYSTEMS  
COURSE CODE : BEF 25503  
PROGRAMME : BEJ  
EXAMINATION DATE : JUNE / JULY 2016  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER **ALL** QUESTIONS

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

**CONFIDENTIAL**

- Q1** (a) Summarize **three (3)** main features available in the primary distribution substation. (3 marks)
- (b) Justify the purpose for the size and shape of the metal conductor to be among important elements to be considered in designing the busbars. (5 marks)
- (c) Typically at the entrance point of utilization, the distribution electrical power lines are carried either a three-phase or single-phase AC live voltage, together with a ground or neutral line used for protection purposes.
- (i) Construct the schematic diagram of three-phase four wires system referred from the source. (5 marks)
- (ii) Construct the typical system and equipment grounding connections inside a premise being supplied with single-phase two wires AC lines. (7 marks)
- Q2** (a) Summarize a general working concept of the voltage and the current transformers. (4 marks)
- (b) Propose the appropriate circuit breaker placements and the zone of protections for a power system network shown in **Figure Q2(b)**. (7 marks)
- (c) Consider a three-phase, 50 MVA power transformer is connected with a current transformer based on the differential protection style. Their rating data is stated in **Table Q2(c)**.
- (i) Analyze the circuit by providing a full schematic diagram of the equipment connections. (3 marks)
- (ii) Analyze the relay current level at full load capacity. (5 marks)
- (iii) Analyze the minimum relay current setting to allow 1.3p.u overload condition. (1 mark)

- Q3** (a) Calculate the ABCD constant for transmission line model that is 50 km long and operates at 50 Hz. Series resistance and inductance of the transmission line is  $0.2 \Omega/\text{km}$  and  $0.3183 \text{ mH}/\text{km}$ . (5 marks)

- (b) A 220 kV, 200 MVA and 50 Hz, three-phase transmission line is 150 km long completely transposed transmission line has the following positive-sequence impedance and admittance:

$$r = 0.11 \Omega/\text{km}$$

$$x = 0.90 \Omega/\text{km}$$

$$y = 5.0 \times 10^{-6} \text{ S}/\text{km}$$

Given the voltage at the receiving end of the transmission line is 200 kV;

- (i) Calculate the values of series impedance and shunt admittance of the transmission line. (2 marks)
- (ii) Calculate the sending end line to line voltage if the transmission line is supplying rated apparent power at unity power factor. (8 marks)
- (iii) Calculate the efficiency of the transmission line. (5 marks)

- Q4** (a) Determine the daily average load demand of Factory X having its daily load profiling as in **Table Q4(a)**. (5 marks)

- (b) Calculate the mass of uranium fissioned per hour when an atomic reactor delivers 300 MW power if due to fission of each atom  ${}_{92}\text{U}^{235}$ , the energy released is 200 MeV. Given  $1 \text{ MeV} = 1.6 \times 10^{-19} \text{ J}$ . (5 marks)

- (c) (i) Differentiate between the horizontal-axis and vertical-axis type wind turbine systems. (4 marks)
- (ii) Explain briefly the operation of binary cycle (geothermal) energy generation system with the aid of appropriate diagram. (6 marks)

- Q5** (a) By referring to the circuit shown in **Figure Q5(a)**, two parallel loads of  $Z_1=120 \Omega$  and  $Z_2=15 + j20 \Omega$  are connected across  $250 V_{\text{rms}}$ , 50 Hz source.
- (i) Calculate the total real and reactive power, the power factor at the source and the total current. (6 marks)
- (ii) Propose a suitable capacitance value for the capacitor that will be connected across the loads in order to improve the overall power factor to 0.9 lagging. (4 marks)
- (b) A Y connected synchronous generator rated 100 MVA, 13.2 kV has a rated impedance of  $R = 5\%$  and  $X_s = 80\%$ . It is connected to a  $j10 \Omega$  transmission line through a 100 MVA, 13.8/120 kV,  $\Delta - Y$  three phase transformer. The rated impedance for the three phase transformer is  $R = 2\%$  and  $X = 8\%$ .
- (i) Construct the one line diagram of this system. (1 mark)
- (ii) Outline the new impedance diagram for this system by using 200 MVA and 120 kV at the transmission line as base. (9 marks)


- END OF QUESTIONS -

**CONFIDENTIAL**

**FINAL EXAMINATION**

SEMESTER/SESSION : II/ 2015/2016  
 COURSE NAME : POWER SYSTEMS

PROGRAMME : 2 BEJ  
 COURSE CODE : BEF 25503

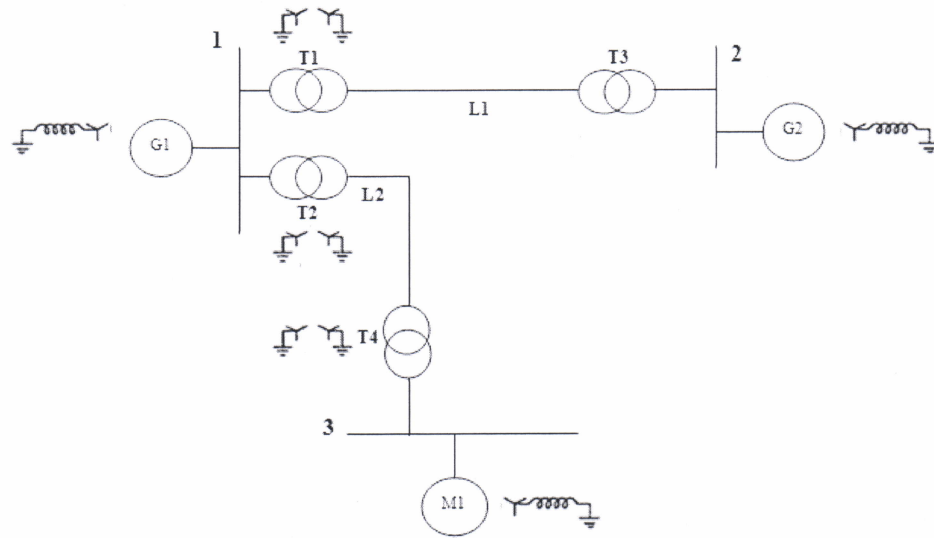

**FIGURE Q2(b)**

**TABLE Q2(c)**

Equipments	Primary Circuit	Secondary Circuit
Three-phase Transformer (T1)	132 kV / $\Delta$	11 kV / Y
Current Transformer (CT)	500 A / 5 A / Y	5000 A / 5 A / $\Delta$

**CONFIDENTIAL****FINAL EXAMINATION**

SEMESTER/SESSION : II/ 2015/2016


PROGRAMME : 2 BEJ

COURSE NAME : POWER SYSTEMS

COURSE CODE : BEF 25503

**TABLE Q4(a)**

TIME	POWER, P (kW PER HOUR)
9 am – 11 am	200
11 am – 3 pm	100
3 pm – 6 pm	300
6 pm – 10 pm	500
10 pm – 1 am	50
1 am – 6 am	250
6 am – 9 am	100

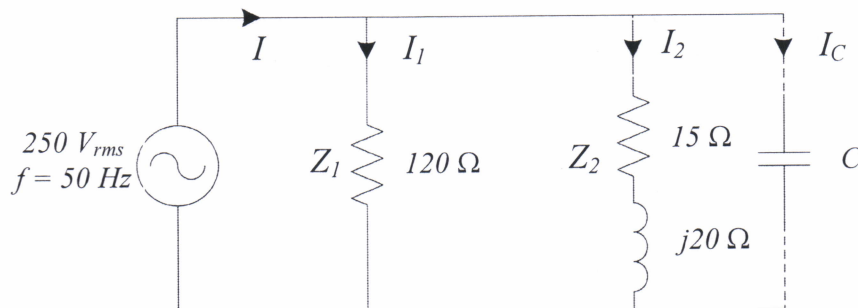**FIGURE Q5(a)****CONFIDENTIAL**