

CONFIDENTIAL



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2015/2016**

COURSE NAME : VLSI DESIGN
COURSE CODE : BED 30303
PROGRAMME : BEJ
EXAMINATION DATE : JUNE / JULY 2016
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

CONFIDENTIAL

- Q1** (a) Timing Analysis, Extraction and Verification are among the steps in the VLSI design flow. Describe clearly each of these steps. (6 marks)
- (b) Analyse the stick diagram illustrated in **Figure Q1**.
- (i) Draw the electrically equivalent transistor level schematic of the stick diagram. (10 marks)
- (ii) Deduce the logic equation for the output Y . (4 marks)
- Q2** (a) Find the output Y of the circuit shown in **Figure Q2** by analyzing which transistors on the circuit will be ON when the input $C = 0$, and then when the input $C = 1$. Determine the Boolean equation for the output Y . (7 marks)
- (b) Design a dynamic logic circuit with minimum number of transistors to realize the logic function of $F = \overline{WZ + X(Y + V)}$. The circuit must be able to eliminate a contention problem. (8 marks)
- (c) Construct a pass transistor circuit using only pMOS transistor to implement AND gate function. (5 marks)
- Q3** (a) Define logical effort in VLSI circuit design. (2 marks)
- (b) Calculate the logical effort for input A and B to the output for the circuit as shown in **Figure Q3(a)**. (5 marks)

- (c) In VLSI design, power consumption by the integrated circuit is always the main issues to be addressed by the designer besides the silicon area and speed or performance of the circuit.
- (i) Discuss factors that contribute to the power consumption and loss due to the static and dynamic power. (4 marks)
- (ii) Propose and deliberate methods to minimize the power consumption. (3 marks)
- (d) Calculate the size for all PMOS transistors of the circuit illustrated in **Figure Q3(b)** such that the circuit will have an equivalent driving capability on an inverter. Given the minimum transistor length (L) is 2λ and the width (W) is 3λ ; and the mobility of the electron is 3 times of the hole's mobility. (6 marks)
- Q4** (a) Edge-triggered flip-flop may experience hold-time failures or problems if the system has too much clock skew. State the meaning of clock skew and recommend **THREE (3)** techniques to eliminate or reduce these problems. (5 marks)
- (b) A positive-level sensitive (positive triggered) D latch circuit can be designed using a circuit as shown in **Figure Q4**.
- (i) Examine and describe the operation of the circuit. (4 marks)
- (ii) Modify the circuit to produce a negative-level sensitive (negative triggered) D latch. Draw and clearly label the new circuit. (3 marks)
- (c) Design at full transistor level a negative edge or falling edge triggered D flip-flop using minimum number of transistors. Draw and completely label the circuit. (8 marks)

- Q5** (a) **Figure Q5(a)** is a 1-to-2 demultiplexer. Employ a pseudo-nMOS logic method to transform the circuit into a transistor level circuit with minimum number of transistors. (4 marks)
- (b) A block diagram of a 2-to-4 decoder is shown in **Figure Q5(b)**.
- (i) Construct a truth table for the decoder and obtain the equation for each output. (8 marks)
- (ii) Design a dynamic 2-to-4 NOR decoder and draw the full circuit at transistor level with minimum number of transistors. (8 marks)

– END OF QUESTIONS –

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2015/2016
 COURSE NAME : VLSI DESIGN

PROGRAMME : BEJ
 COURSE CODE : BED 30303

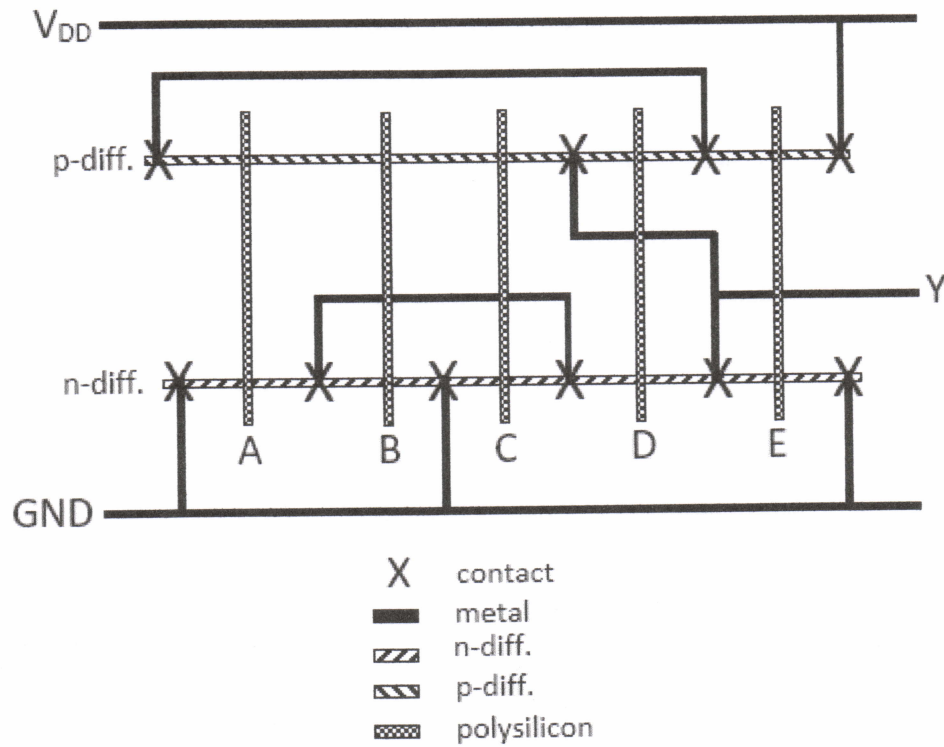


Figure Q1

 


Figure Q2

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2015/2016
COURSE NAME : VLSI DESIGN

PROGRAMME : BEJ
COURSE CODE : BED 30303

 


Figure Q3(a)

 


Figure Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II/2015/2016
COURSE NAME : VLSI DESIGN

PROGRAMME : BEJ
COURSE CODE : BED 30303

 


Figure Q4

 


Figure Q5(a)

 


Figure Q5(b)