

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2016/2017**

**TERBUKA**

**COURSE NAME : DIGITAL TECHNIQUES**

**COURSE CODE : BEF12302**

**PROGRAMME CODE : BEV**

**EXAMINATION DATE : DECEMBER 2016/ JANUARY 2017**

**DURATION : 2 HOURS**

**INSTRUCTION : 1. ANSWER ALL QUESTIONS**

**2. ATTACH APPENDIX A AND B WITH YOUR ANSWER BOOKLET**

**THIS QUESTION PAPER CONSISTS OF ELEVEN (11) PAGES**

**CONFIDENTIAL**

- Q1**
- (a) List **one (1)** disadvantage of series and parallel digital data transmission.  
(2 marks)
  
  - (b) Identify why digital data transmission is preferred over analogue data transmission?  
(4 marks)
  
  - (c) Convert the Gray code 111011000110 to BCD number.  
(6 marks)
  
  - (d) Convert  $324.253_{10}$  to octal.  
(6 marks)
  
  - (e) A 4-bit binary number is represent by  $A_3 A_2 A_1 A_0$  with  $A_3 A_2 A_1$  and  $A_0$  are the individual bits and  $A_0$  is the LSB. Draw a combinational logic circuit which produce an output HIGH when the binary number  $A_3 A_2 A_1 A_0$  should be at least  $5_{10}$  and above and less than  $12_{10}$ .  
(7 marks)

**TERBUKA**  
**CONFIDENTIAL**

**Q2** (a) Simplify using Boolean Algebra:

(i)  $\overline{AB + AC + ABC}$ . (3 marks)

(ii)  $(A + C)(A + \overline{B})$ . (3 marks)

(b) **Table 2 (b)** shows a truth table of a four-input and two-output logic function. Use Karnaugh maps, formulate:

(i) the minimal sum-of-product (MSOP) of expression for Y. (5 marks)

(ii) the minimal product-of-sum (MPOS) of expression for Z. (5 marks)

(c) A NAND gate is known as a universal gate as it can be configured into any basic logic gate.

i) Illustrate how a NAND gate can be used as OR gate. (3 marks)

ii) Implement the function  $Z = P\overline{Q} + \overline{S} + P\overline{R}$  using only a 2-input NAND gates. (6 marks)

TERBUKA

CONFIDENTIAL

- Q3** (a) Explain the operation of the following functional combinational logic circuit. You may use appropriate diagram to aid your explanation.
- i) Decoder. (2 marks)
  - ii) Comparator (2 marks)
- (b) Analyze the 16 inputs multiplexer shown in **Figure Q3 (b)**.
- i) Give brief explanation of the system. (4 marks)
  - ii) Find the Boolean expression for the output Z (6 marks)
- (c) Implement the following Boolean expression using IC 74LS138 (3-to-8 decoder) in **APPENDIX A**. Symbol for IC 74LS138 is shown in **APPENDIX A** for the internal circuitry and pins assignment of 74LS138 (3-to-8 decoder).
- $$Z = (\overline{A.B}) + (\overline{B + C})$$
- (6 marks)
- (d) Analyze the flip-flop circuit in **Figure Q3 (d)** and sketch output waveform. Assume both SET and CLR are inactive. Complete the timing diagram for Q in **APPENDIX B** and write down the operation (e.g. HOLD) that takes place in each clock pulse as illustrated in the diagram. (5 marks)

TERBUKA

CONFIDENTIAL

- Q4** (a) Explain **one (1)** advantage and **two (2)** disadvantages of a synchronous counter compared to asynchronous counter. (3 marks)
- (b) **Figure Q4 (b)** shows the state transition diagram of a state machine.
- (i) Build the excitation table for this state machine. Use JK flip-flops. (10 marks)
- (ii) Express the simplest Boolean expression for the circuit using Karnaugh map. (6 marks)
- (iii) Draw the circuit. (4 marks)
- (d) Explain the operation of the Parallel In Serial Out register (PISO) register. You may use appropriate diagram to aid your explanation. (2 marks)

**-END OF QUESTION-**

**TERBUKA**

**CONFIDENTIAL**

**FINAL EXAMINATION**SEMESTER/SESSION: SEM I/2016/2017  
COURSE :DIGITAL TECHNIQUESPROGRAMME CODE: BEV  
COURSE CODE: BEF12302**Table 2 (b)**

INPUT				OUTPUT	
A	B	C	D	Y	Z
0	0	0	0	1	1
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	1	0
0	1	0	1	X	0
0	1	1	0	1	0
0	1	1	1	0	0
1	0	0	0	0	X
1	0	0	1	X	0
1	0	1	0	X	1
1	0	1	1	1	0
1	1	0	0	1	1
1	1	0	1	1	X
1	1	1	0	X	0
1	1	1	1	X	1

**TERBUKA****CONFIDENTIAL**

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017  
COURSE :DIGITAL TECHNIQUES

PROGRAMME CODE: BEV  
COURSE CODE: BEF12302

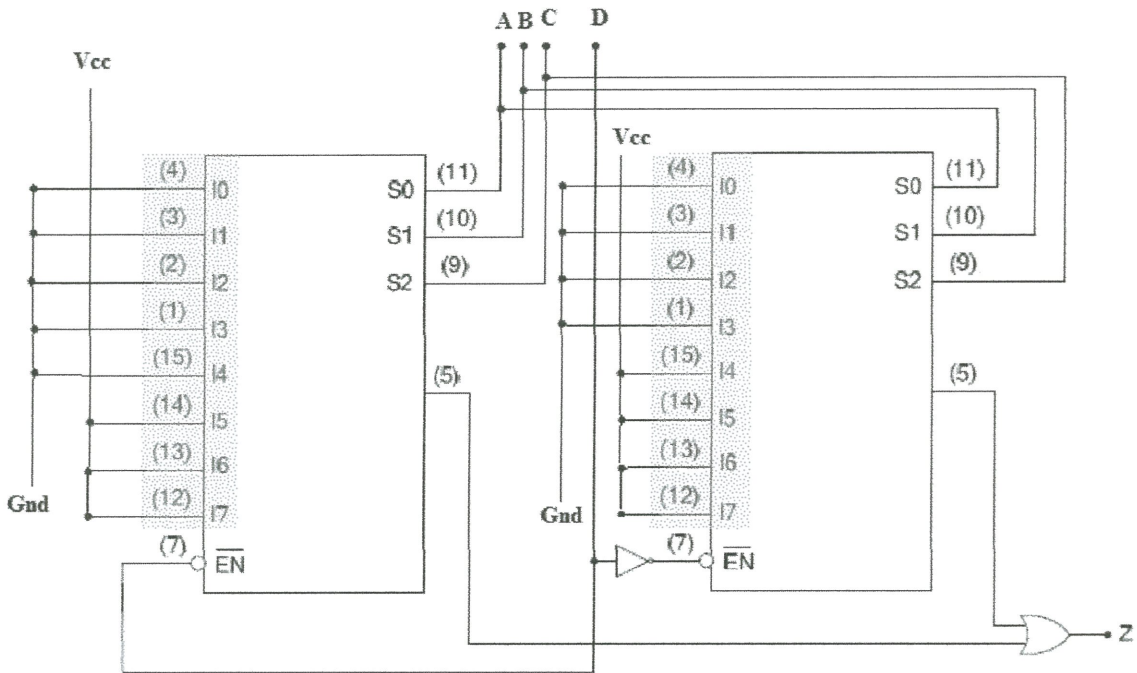


FIGURE Q3 (b)

TERBUKA

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2016/2017	PROGRAMME CODE: BEV
COURSE :DIGITAL TECHNIQUES	COURSE CODE: BEF12302


 


FIGURE Q3 (d)

**TERBUKA**


**CONFIDENTIAL**

 

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2016/2017  
COURSE :DIGITAL TECHNIQUES

PROGRAMME CODE: BEV  
COURSE CODE: BEF12302

 

**FIGURE Q4 (b)**

**TERBUKA**  
**CONFIDENTIAL**

FINAL EXAMINATION



SEMESTER/SESSION: SEM I/2016/2017  
 COURSE :DIGITAL TECHNIQUES

PROGRAMME CODE: BEV  
 COURSE CODE: BEF12302

APPENDIX A

PIN ASSIGNMENT AND INTERNAL CIRCUITRY

74LS138 (3-to-8 Decoder)

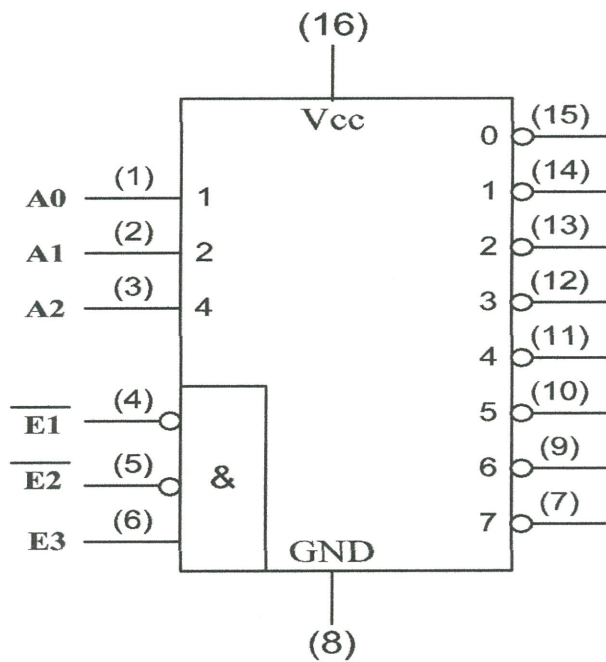 

**TERBUKA**


CONFIDENTIAL

**FINAL EXAMINATION**

SEMESTER/SESSION: SEM I/2016/2017  
COURSE :DIGITAL TECHNIQUES

PROGRAMME CODE: BEV  
COURSE CODE: BEF12302

**APPENDIX B**

 

**TERBUKA**

**CONFIDENTIAL**