

**CONFIDENTIAL**



**UTHM**

Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2016/2017**

COURSE NAME : ELECTRICAL MEASUREMENTS  
COURSE CODE : BEF 20903 / BEF 23903  
PROGRAMME CODE : BEV  
EXAMINATION DATE : DECEMBER 2016 / JANUARY 2017  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **EIGHT (8)** PAGES

**CONFIDENTIAL**

DR. MOHAMMAD...  
Pusat Penyelidikan Elektrik dan Elektronik  
Fakulti Kejuruteraan Elektrik dan Elektronik  
Universiti Tun Hussein Onn Malaysia

# CONFIDENTIAL

BEF 20903/ BEF 23903

- Q1** (a) It is important to know the performance characteristics of the instrument before performing the measurement. Discuss **two (2)** main performance characteristics that should be considered in measurements. (4 marks)
- (b) The voltmeter and ammeter are connected in parallel and series respectively in order to determine the value of unknown resistor as shown in **Figure Q1(b)**. It is found that the voltmeter reads 100 V on the 150 V scale while the ammeter reads 10 mA. The voltmeter has sensitivity of 1 k $\Omega$ /V and the internal resistance of ammeter is neglected. From the circuit, determine:
- (i) The apparent resistance of the resistor. (2 marks)
- (ii) The actual resistance of the resistor. (4 marks)
- (iii) The percentage error due to loading effect of the voltmeter. (2 marks)
- (c) The Permanent Magnet Moving Coil (PMMC) can be modified to measure the DC and AC voltage.
- (i) Construct the AC voltmeter by using full wave rectifier circuit. (4 marks)
- (ii) Illustrate the input and output of the AC voltmeter based on **Q1(c)(i)**. (2 marks)
- (iii) Justify the effectiveness of the full wave rectifier AC voltmeter compared to half wave rectifier circuit. (2 marks)
- Q2** (a) Wheatstone bridge is the basic DC bridges for measuring the medium resistance.
- (i) The wheatstone bridge shows in **Figure Q2(a)(i)** is under unbalanced condition. By using appropriate theorem, calculate the total current through the galvanometer if  $V=8$  V,  $R_1=15$  k $\Omega$ ,  $R_2=15$  k $\Omega$ ,  $R_3=2$  k $\Omega$ ,  $R_4=2.2$  k $\Omega$  and  $R_G=200$   $\Omega$ . (6 marks)
- (ii) Identify the limitations of wheatstone bridge. (4 marks)

**TERBUKA**

(b) The Maxwell Bridge is used to measure the unknown inductance in term of a known capacitor as shown in **Figure Q2(b)**.

(i) Under balanced condition, show that the unknown inductance,  $L_x$  and resistance,  $R_x$  are as follows:

(Hint: the general equation for balance condition is  $Z_1Z_x=Z_2Z_3$ )

$$R_x = \frac{R_2R_3}{R_1}; \quad L_x = C_1R_2R_3$$

(5 marks)

(ii) Define the equation of quality factor,  $Q$  of the unknown inductance in **Q2(b)(i)**. (3 marks)

(iii) Maxwell Bridge is limited to the measurement of material with low quality factor,  $Q$  (1-10). Justify this limitation. (2 marks)

**Q3** (a) The high current AC can be measured by using combination of a current transformer and a low range ammeter. Determine the main function of current transformer in high current measurement. (2 marks)

(b) The turn of primary and secondary windings of current transformer are 1 and 200 respectively. The secondary winding supplies current of 5 A to a non-inductive burden of  $1 \Omega$  resistance. The requisite flux is set up in the core by a magnetomotive force (mmf) of 80 AT. The frequency is 50 Hz and the net cross-section of the core is  $1000 \text{ mm}^2$ . By neglecting the effects of magnetic leakage and iron losses:

(i) Draw the equivalent circuit the current transformer (3 marks)

(ii) Calculate the actual transformation ratio,  $K_{act}$ . (6 marks)

(iii) Sketch the phasor diagram. (2 marks)

(iv) Determine the phase angle. (3 marks)

(v) Calculate the maximum flux density in the core. (4 marks)

**TERBUKA**

# CONFIDENTIAL

BEF 20903/ BEF 23903

- Q4** (a) (i) Explain the main feature of Capacitive Voltage Transformer (CVT). (2 marks)
- (ii) Setup a connection of Electromagnetic Voltage Transformer (EVT) for measuring high voltage line . (4 marks)
- (b) A potential transformer rated 14.4 KV/115 V and a current transformer rated 75A/5A are used to measure the voltage and current in a transmission line as shown in **Figure Q4(b)**. The voltmeter and ammeter indicate 101 V and 3 A respectively. Calculate the line voltage and current. (4 marks)
- (c) (i) Compare the **two (2)** main features of dynamometer wattmeter and induction wattmeter. (4 marks)
- (ii) Select a suitable method for measuring the total power in unbalanced load condition. (2 marks)
- (d) There are various methods can be used to measure the power in single phase AC circuit. Construct a measurement circuit for measuring power without using wattmeter. (4 marks)
- Q5** (a) The resistance can be classified into three categories. Distinguish the **three (3)** categories of resistance by using appropriate examples. (6 marks)
- (b) There are several approaches can be used to measure the low resistance.
- (i) Demonstrate the electrical connection of ammeter-voltmeter method. (3 marks)
- (ii) Describe the related formulas that can be used to calculate the unknown resistance based on the ammeter-voltmeter method in **Q5(b)(i)**. (2 marks)
- (iii) Identify an error that contribute in low resistance measurements and propose a solution in order to significantly minimize this error. (3 marks)

**TERBUKA**

(c) The insulation resistance of a metal-sheath electrical cable shown in **Figure Q5(c)** is tested using 20 kV supply and a micro ammeter. A current of 5  $\mu\text{A}$  is measured when the components are connected without guard wire. When the circuit is connected with a guard wire, the current is 1.5  $\mu\text{A}$ . Calculate:

(i) The volume resistance of the cable insulation,  $R_v$ . (2 marks)

(ii) The surface leakage resistance,  $R_l$ . (4 marks)

- END OF QUESTIONS -

**TERBUKA**



FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2016/2017  
COURSE : ELECTRICAL MEASUREMENTS

PROGRAMME CODE : BEV  
COURSE CODE : BEF20903/  
BEF23903


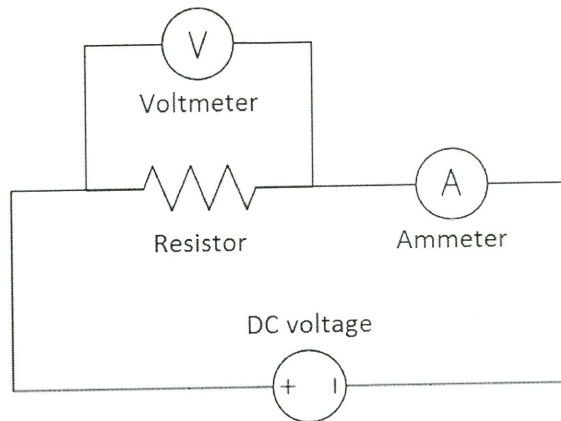


Figure Q1(b)

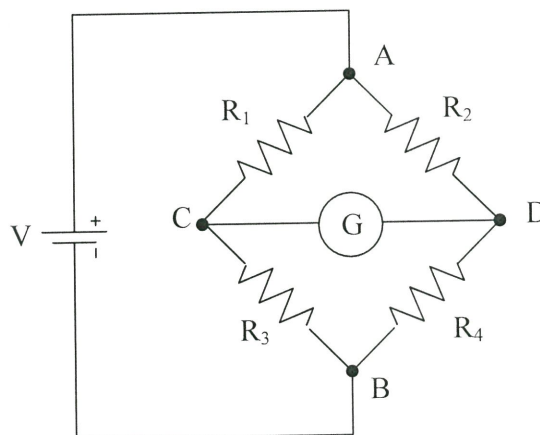

- $V = 8\text{ V}$
- $R_1 = 15\text{ k}\Omega$
- $R_2 = 15\text{ k}\Omega$
- $R_3 = 2\text{ k}\Omega$
- $R_4 = 2.2\text{ k}\Omega$
- $R_G = 200\ \Omega$

Figure Q2(a)(i)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I 2016/2017 PROGRAMME CODE : BEV  
COURSE : ELECTRICAL MEASUREMENTS COURSE CODE : BEF20903/  
BEF23903

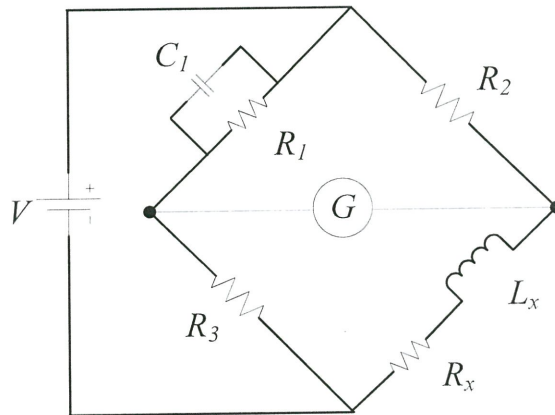


Figure Q2(b)

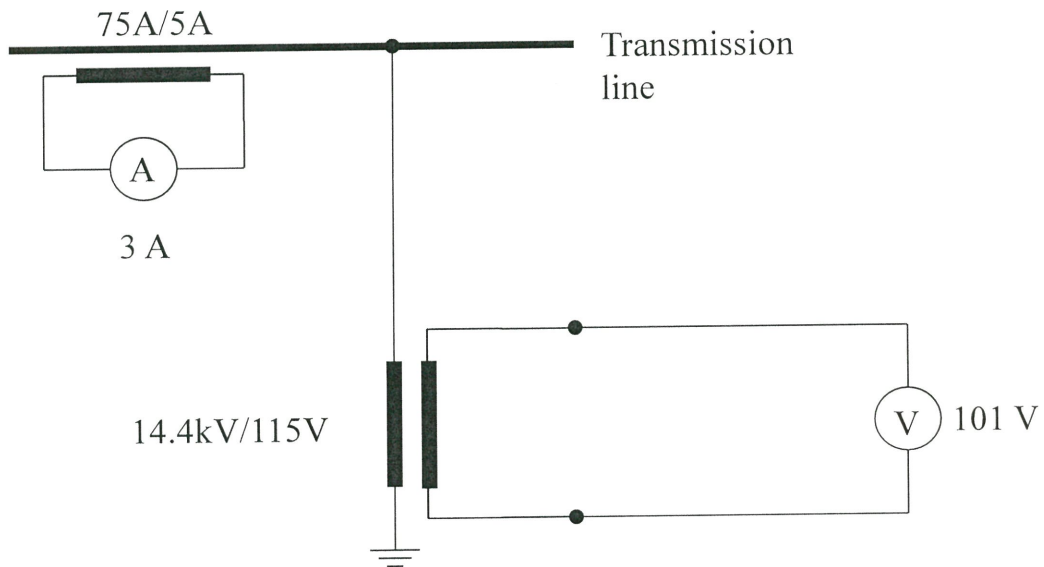


Figure Q4(b)

**TERBUKA**

