



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2016/2017**

TERBUKA

COURSE NAME : POWER SYSTEMS
COURSE CODE : BEF 25503
PROGRAMME : BEJ
EXAMINATION DATE : DECEMBER 2016 / JANUARY 2017
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF FOUR (4) PAGES

- Q1**
- (a) Describe electric power system. (4 marks)
 - (b) Outline how distribution systems are being classified. (8 marks)
 - (c) List out **four (4)** functions of distribution substation. (4 marks)
 - (d) Illustrate **two (2)** ways the primary distribution lines can be laid. (4 marks)
- Q2** A Y-connected synchronous generator rated 100 MVA, 13.2 kV has a rated impedance of $R = 5\%$ and $X_s = 80\%$. It is connected to a $j10 \Omega$ transmission line through a 100 MVA, 13.8/120 kV, $\Delta - Y$ three phase transformer. The rated impedance for the three phase transformer is $R = 2\%$ and $X = 8\%$.
- (a) Construct the one line diagram of this system. (2 marks)
 - (b) Outline the new impedance diagram for this system when 200 MVA and 120 kV at the transmission line are used as base. (18 marks)
- Q3**
- (a) Give **four (4)** advantages of the thermal generation system. (4 marks)
 - (b) Compare the differences between high-head development and low-head development of hydropower station. (8 marks)
 - (c) Calculate the mass of uranium fissioned per hour if an atomic power reactor can deliver 400 MW. Given that, due to fission reaction of each atom ${}_{92}\text{U}^{235}$, the energy released is 200 MeV. (8 marks)

TERBUKA**CONFIDENTIAL**

- Q4 (a)** **Figure Q4(a)** shows an equivalent circuit of a medium length line for nominal π model which the total series impedance, $Z = R + jX$ and shunt reactance, $\frac{Y}{2}$.
Generate the equation for $ABCD$ constant of the nominal π model.

(5 marks)

- (b)** A 220 kV, 200 MVA and 50 Hz, three-phase transmission line that is 150 km long has the following positive-sequence impedance and admittance:

$$\begin{aligned} r &= 0.11 \Omega/\text{km} \\ x &= 0.90 \Omega/\text{km} \\ y &= 5.0 \times 10^{-6} \text{ S/km} \end{aligned}$$

The voltage at the receiving end of the transmission line is 200 kV, analyse:

- (i)** The values of series impedance and shunt admittance of the transmission line.

(2 marks)

- (ii)** The value of sending end voltage if the line supplying rated voltage and rated apparent power at 0.85 PF lagging.

(8 marks)

- (iii)** The efficiency of the line.

(5 marks)

- Q5 (a)** Outline the operation of the protection scheme of the radial system shown in **Figure Q5(a)**.

(7 marks)

- (b)** Consider a Δ/Y -connected, 15 MVA, 33/11 kV transformer shown in **Figure Q5(b)** with differential protection applied. The CT ratio at the secondary side is 2000/5 A and at the primary side is $X/5$ A. The minimum relay current setting is $i_r = 1.206$ A with 125% overload.

- (i)** Calculate the relay current when the system is 125% overload.

(2 marks)

- (ii)** Calculate the CT current on the primary side when the current on the secondary side is 3.41 A.

(3 marks)

- (iii)** Determine the ratio of the CT at primary side.

(8 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER/SESSION : SEM I / 2016 / 2017
 COURSE : POWER SYSTEM

PROGRAMME : BEJ
 COURSE CODE : BEF 25503

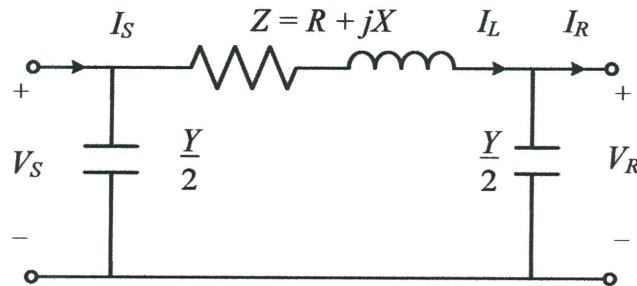


Figure Q4(a)

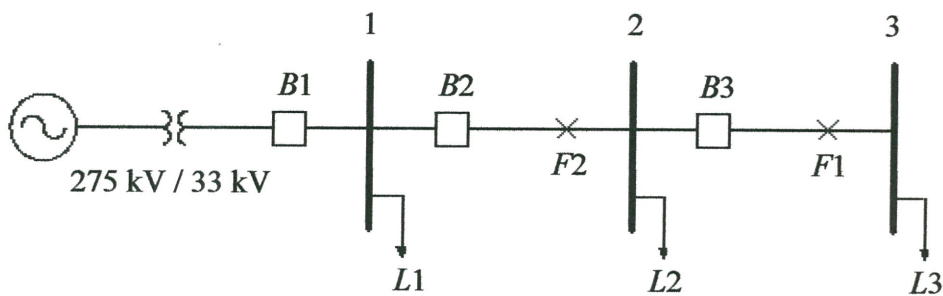


Figure Q5(a)

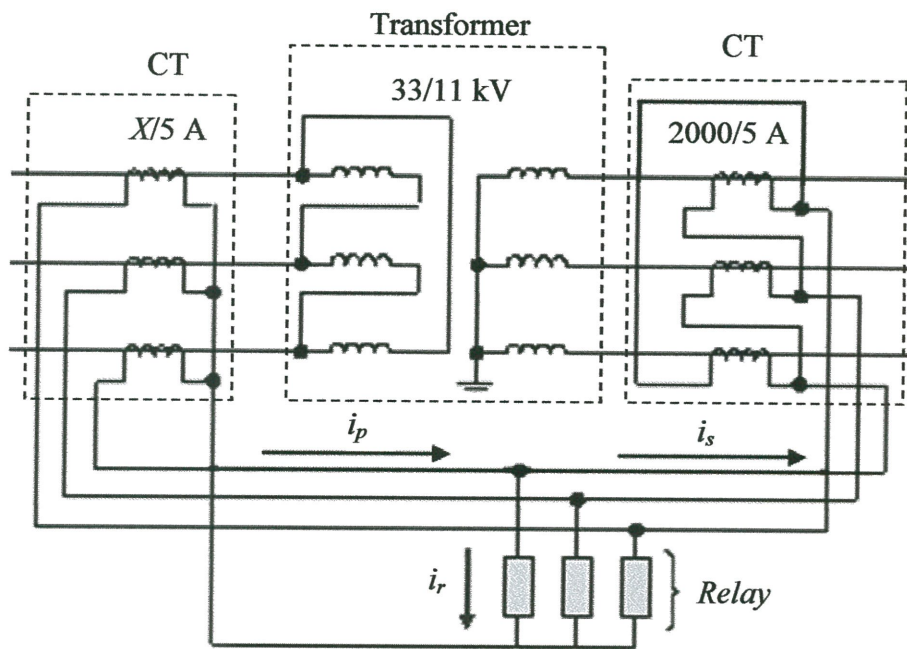


Figure Q5(b)

TERBUKA
CONFIDENTIAL

Program Studi Teknik Elektro
 Fakultas Teknik dan Ilmu Komputer
 Universitas Kristen Indonesia