

CONFIDENTIAL



UTHM
Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2016/2017**

TERBUKA

COURSE NAME : VLSI DESIGN
COURSE CODE : BED 30303
PROGRAMME : BEJ
EXAMINATION DATE : DECEMBER 2016/JANUARY 2017
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

CONFIDENTIAL

- Q1** (a) State and elaborate **THREE (3)** design metrics that are used to evaluate the overall performance of VLSI design. (6 marks)
- (b) **Figure Q1** shows a stick diagram of logical circuit using fully complementary static CMOS.
- (i) Analyse the figure and draw the electrically equivalent transistor level schematic of the stick diagram. (10 marks)
- (ii) Determine the logic equation for the output Y . (4 marks)
- Q2** (a) Discuss **ONE (1)** advantage and **ONE (1)** disadvantage of designing a logic circuit at transistor level using pseudo-nMOS method. (4 marks)
- (b) Describe the monotonicity requirement when designing a circuit using dynamic logic method. (4 marks)
- (c) Construct a NOR gate function by using pass transistor method. (5 marks)
- (d) Analyse the circuit in **Figure Q2** and determine the equation for the output. (7 marks)
- Q3** (a) List **TWO (2)** sources of leakage current in CMOS transistor and explain clearly the reason why leakage current increases with the advancement of technology scaling in CMOS transistor. (4 marks)

TERBUKA**CONFIDENTIAL**

- (b) A logic function is given by equation $Y = \overline{A(B+C) + DE}$
- Design a transistor level circuit utilising fully complementary static CMOS logic method to implement the function using minimum number of transistor. The circuit need to have a minimum parasitic delay. (6 marks)
 - Determine the size of each transistor to be used in the design such that the circuit will have an equivalent driving capability of an inverter. Also calculate the minimum parasitic delay. Assume that the minimum length for the transistor is 2λ and the mobility ratio of electron and holes is 2. (10 marks)
- Q4** (a) A negative-level sensitive (negative triggered) D latch circuit can be designed using a circuit as shown in **Figure Q4**.
- Obtain the equation for the output of the circuit, Q . (2 marks)
 - Analyse the circuit and determine when the circuit is in 'transparent' form and 'opaque' form with regards to the clock input. Assess the output at these two forms. (6 marks)
 - Modify the circuit to produce a positive-level sensitive (positive triggered) D latch. Draw and clearly label the new circuit and state the new equation for the output. (4 marks)
- (b) Create a positive or rising edge triggered D flip-flop using minimum number of transistors. Draw and completely label the circuit. (8 marks)

TERBUKA**CONFIDENTIAL**

- Q5** (a) **Figure Q5(a)** is a block diagram of 2-to-1 multiplexer. Employ a tri-state logic method to implement the multiplexer at transistor level. (8 marks)
- (b) A block diagram of 8-to-3 (octal-to-binary) encoder is shown in **Figure Q5(b)**.
- (i) Construct a truth table for the encoder and obtain the equation for each output. (8 marks)
- (ii) Illustrate at transistor level the circuit for the output D_1 of the encoder using dynamic logic with minimum number of transistors. (4 marks)

– END OF QUESTIONS –

TERBUKA

CONFIDENTIAL

2011/2012
Program Kurikulum
Fakultas Teknik
Universiti Teknikal Malaysia Melaka

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2016/2017
 COURSE NAME : VLSI DESIGN

PROGRAMME : BEJ
 COURSE CODE : BED 30303

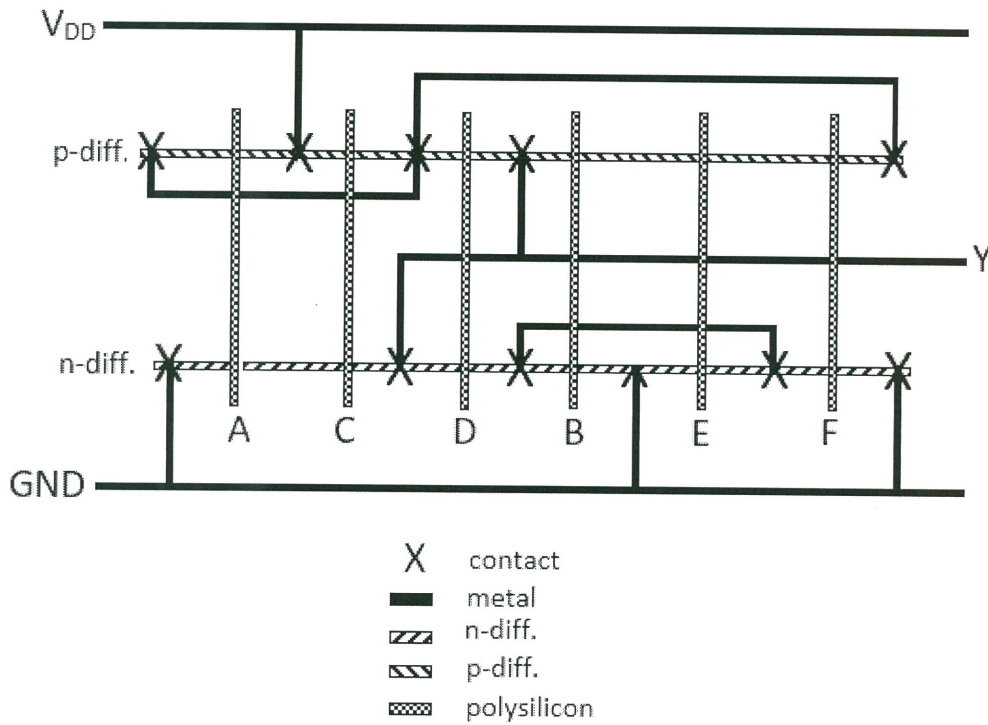


Figure Q1

 


Figure Q2

TERBUKA

CONFIDENTIAL

This document is the property of the University of Kuala Lumpur. It is to be used only for the purpose of the examination. It is not to be distributed, copied, or reproduced in any form without the prior written consent of the University of Kuala Lumpur.

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2016/2017
COURSE NAME : VLSI DESIGN

PROGRAMME : BEJ
COURSE CODE : BED 30303

 


Figure Q4

 


Figure Q5(a)

 


Figure Q5(b)

TERBUKA
CONFIDENTIAL