

CONFIDENTIAL



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER 2
SESSION 2016/2017**

COURSE NAME : ANALOG ELECTRONICS
COURSE CODE : BEL 10203
PROGRAMME : BEJ / BEV
TEST DATE : JUNE 2017
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS.

TERBUKA

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

CONFIDENTIAL

Q1 (a) A P-N (positive-negative) junction is a boundary or interface between two types of semiconductor material, p-type and n-type, inside a single crystal of semiconductor. In your own words and with the aid of diagram,

(i) discuss the formation of depletion region in a P-N junction (4 marks)

(ii) explain the effect if forward biased voltage is applied across a silicon P-N diode. (3 marks)

(b) **Figure Q1 (b)** showed an example of a clipper circuit designed to prevent the output of a circuit from exceeding a predetermined voltage level. Given that the input voltage, V_i , is a triangular wave with $V_{p-p} = 20\text{ V}$.

(i) With the aid of diagrams, determine the output of this circuit assuming that D_1 and D_2 are silicon diode. (5 marks)

(ii) Label your input and output waveform accordingly. (4 marks)

 


Figure Q1 (b)

TERBUKA

- (c) Based on the zener diode circuit shown in **Figure Q1 (c)**, the knee current, I_K , of this ideal zener diode is given by 10 mA. Using the information provided in this diagram, and with the voltage drop maintained at 5 volts across the load, R_L ,

 


Figure Q1 (c)

- (i) Determine the minimum resistance value of load, R_L . (5 marks)
- (ii) Calculate the minimum power rating of the zener diode. (4 marks)

Q2 (a) With the help of an output characteristic diagram (I_C versus V_{CE}), explain how to determine the DC Load Line in fixed biased BJT circuit. (3 marks)

(b) In **Figure Q2 (b)**, another $9.1\text{ k}\Omega$ resistor is added at the base terminal to the ground. Other specifications for this biasing circuit are: $R_C = 3.9\text{ k}\Omega$, $R_E = 0.68\text{ k}\Omega$, $R = 62\text{ k}\Omega$, $V_{CC} = 16\text{ V}$ and $\beta = 80$.

- (i) Draw the new circuit and state the name of the circuit. (2 marks)

- (ii) Determine suitable method to analyse this circuit. (2 marks)
- (iii) Estimate I_B and I_E currents. (5 marks)
- (iv) Determine V_{CE} voltage. (2 marks)

 


Figure Q2 (b)

TERBUKA

- (c) Based on the new circuit that you have drawn in Q2 (b) (i) above, if r_o is $50\text{ k}\Omega$, determine following parameters:
 - (i) Draw the r_e model AC equivalent circuit. (3 marks)
 - (ii) Find r_e value. (1 mark)
 - (iii) Determine Z_i and Z_o . (5 marks)
 - (iv) Calculate A_v . (2 marks)

- Q3** (a) Briefly discuss the significant differences between a p-channel JFET and p-channel E-MOSFET in terms of the construction and operation. (6 marks)
- (b) Design a self-bias amplifier circuit using a JFET transistor with $I_{DSS} = 8 \text{ mA}$ and $V_P = -6 \text{ V}$ to have a Q-point at $I_{DQ} = 4 \text{ mA}$ using a supply of 14V. Assume that $R_D = 3R_S$. (10 marks)
- (c) The major advantage of FETs is their very high input resistance, which makes them very useful in amplifier circuit. Based on the amplifier circuit with common-source voltage divider configuration shown in **Figure Q3(c)**,

 


Figure Q3 (c)

TERBUKA

- (i) sketch the ac equivalent circuit (2 marks)
- (ii) determine the Z_i , Z_o and A_v if the resulting $V_{GSQ} = +0.35\text{V}$ and $I_{DQ} = 7.6\text{mA}$ (7 marks)

Q4 (a) Figure Q4 (a) shows a BJT amplifier. At low frequency response, Coupling capacitors (C_s , C_c) and Bypass capacitor (C_E) will have capacitive reactance X_c that will affect the circuit impedance.

- (i) Derive the cutoff frequency (f_{LS}, f_{LC}, f_{LE}) due to each capacitor (C_s, C_c, C_E). (6 marks)
- (ii) Draw the resultant bode plot for this circuit. (4 marks)

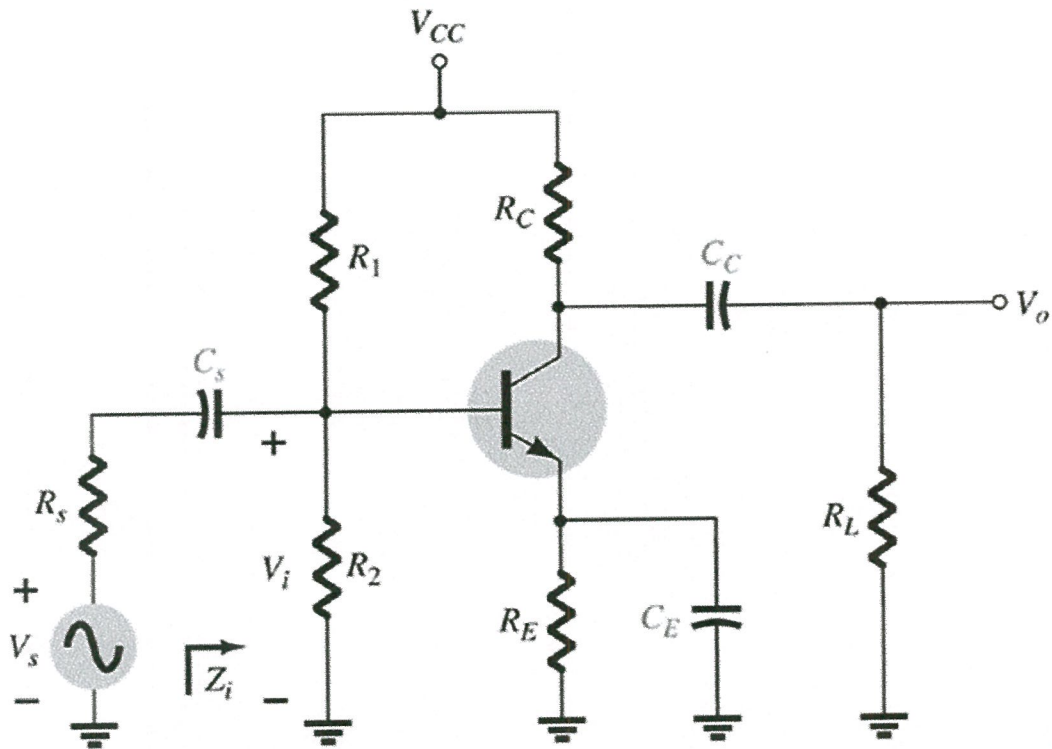


Figure Q4 (a)

TERBUKA

- (b) Explain the Miller Effect Capacitance. (3 marks)
- (c) Figure Q4 (c) shows a biased-class B amplifier:
 - (i) Explain with the aid of a diagram how cross-over distortion problem occur for class B amplifier. (6 marks)

DR. ALIYAH HUNG
 Lecturer in Electronic Engineering
 Faculty of Electrical and Electronic Engineering
 Universiti Teknikal Malaysia Melaka

- (ii) Determine the value of resistor R_2 to provide trickle current for distortion free output. Given $R_1=300\ \Omega$, $R_L=16\ \Omega$ and $V_{cc} = 30V$. V_{BE} for each transistor is 0.7 V.

(6 marks)

 


Figure Q4 (c)

- END OF QUESTION -

TERBUKA