

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER II SESSION 2016/2017

COURSE NAME

MEASUREMENT AND

INSTRUMENTATION

COURSE CODE

BEH 20403

PROGRAMME CODE :

BEJ

EXAMINATION DATE : JUNE 2017

DURATION

3 HOURS

INSTRUCTION

: ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

CONFIDENTIAL

Q3

(a)

BEH 20403

Draw the block diagram of an instrumentation system. **Q1** (a) (4 marks) Differentiate between analog and digital instruments by providing three (3) factors (b) each. (4 marks) Explain the meaning of the terms; instrument, measurement, accuracy, resolution, (c) precision, expected value, error and sensitivity which referred to an instrumentation system. (4 marks) Calculate the precision of the 7th measurement of the 12 sets the resistance value as (d) given in Table Q1(d). (4 marks) The two (2) voltage measurement are as below: (e) The first measurement voltage is V₁=120±1.5% The second measurement voltage is $V_2 = 67 \pm 10\%$ Determine the sum of two voltage measurements and the difference of the two voltage measurements. (4 marks) Briefly describe the basic operation of a typical electrical transducer. Q2 (a) (5 marks) Describe the working principle of a strain gauge. (i) (b) (3 marks) Draw the schematic diagram (with proper labeling) of a typical strain (ii) measurement circuit with temperature variation compensation. (5 marks) A strain gauge with GF = 2.03 and active gauge, $R_I = 350\Omega$ is used in the bridge of (c) Figure Q2(c). The bridge resistors are $R_1=R_2=350\Omega$, and the dummy gauge has R_D =350 Ω . If a tensile strain of 1450 μ m/m is applied, figure the bridge offset voltage if $V_s=10$ V. (7 marks)

> is 100Ω with its measuring sensitivity is $100 \text{ mm/}\mu\text{A}$. niversiti Tun Hussein Onn Malaysta

For a Wheatstone Bridge as in Figure Q3(a), $R_1 = 1000 \Omega$, $R_2 = 4000 \Omega$, $R_3 = 100\Omega$

and $R_4 = 400 \Omega$ when the bridge is balanced. Internal resistance of the galvanometer

CONFIDENTIAL

BEH 20403

- (i) Find the current through the galvanometer using thevenin equivalent circuit (10 marks)
- (ii) Analyze the deflection (mm) of the galvanometer caused by an additional resistor, $R_4=1$ Ω . (Hint: Use Thevenin's theorem due to imbalance in R_4)

(5 marks)

(b) (i) Name three (3) applications for capacitive transducers.

(3 marks)

(ii) An electrode-diaphragm pressure transducer has plates whose area is $5x10^{-3}$ m² and distance between plates is $1x10^{-3}$. Calculate its capacitance if it measures air pressure,

with k=1. [hint: $C = \frac{kA\varepsilon_o}{d}$]

(2 marks)

- A numerical control (NC) worktable operates by closed-loop positioning as shown in **Figure Q4**. The lead screw has a pitch of 25mm and is coupled to the motor shaft with a gear ratio of 10:1 (Ten turns of drive motor for each turn of the screw). An incremental optical encoder generates 500 pulses/rev of its output shaft. Figure out:
 - (i) The resolution of the NC worktable.

(2 marks)

(ii) Number of encoder pulses should be received by the control system to verify if the table has moved exactly 250mm.

(2 marks)

(iii) The encoder pulse rate if the table is to move at 500mm/min.

(2 marks)

(iv) The drive motor speed in terms of revolution per minute (RPM) if the table is moved at the speed as specified at Q4(a)(iii).

(4 marks)

- (b) An engineer has decided to replace the incremental encoder as shown in **Figure Q4** with a linear absolute encoder along the shaft. Given the specification of the absolute encoder as stroke length 500mm, 12 bits, Gray code. The origin is defined when the table is at the most left and the encoder reads 0000 0000 1100 Gray Code. The encoder value increases as the table moves to the right.
 - (i) Explain Gray Code using 4-bits binary.

TERBUKA (2 marks)

CONFIDENTIAL

CONFIDENTIAL

BEH 20403

		(ii)	Explain the reason of using Gray Code.	(2 marks)
		(iii)	Calculate the minimum travel distance possible.	(2 marks)
		(iv)	If the table is to move 250mm away from the origin, calculate t value in Gray Code.	he encoder
			, and an end, electrical and an end of the e	(4 marks)
Q5	(a)	A measurement of temperature using a sensor that outputs 6.5mV temperature from 0 to 100°C. A 6-bit Analog to Digital Converter 10V reference is used.		
		(i)	Develop a circuit to interface the sensor and the ADC.	(10 marks)
		(ii)	Figure out the temperature resolution.	(6 marks)
	(b)	A sensor signal is converted to a frequency that varies from 2.0kl signal is to be converted into an 8-bit digital signal.		20kHz. This
		(i)	Specify the count time T _c .	(2 marks)
		(ii)	Determine the range of count output for the sensor signal's freq	uency range?
				(2 marks)

END OF QUESTIONS -



BEH 20403

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2016/2017

COURSE

PROGRAMME : MEASUREMENT AND INSTRUMENTATION COURSE CODE : BEJ

: BEH20403

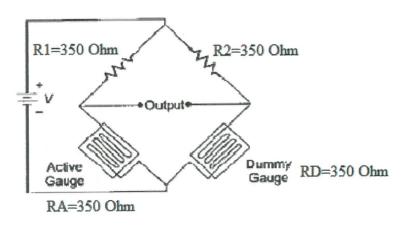


Figure Q2(c)

Table Q1(d)

Measure Number	Measurement Value	
1	202 Ω	
2	198 Ω	
3	201 Ω	
4	190 Ω	
5	200 Ω	
6	188 Ω	
7	203 Ω	
8	199 Ω	
9	192 Ω	
10	191 Ω	
11	201 Ω	
12	199 Ω	

FINAL EXAMINATION

SEMESTER / SESSION

: SEM II / 2016/2017

PROGRAMME

: BEJ

COURSE

: MEASUREMENT AND INSTRUMENTATION COURSE CODE

: BEH20403

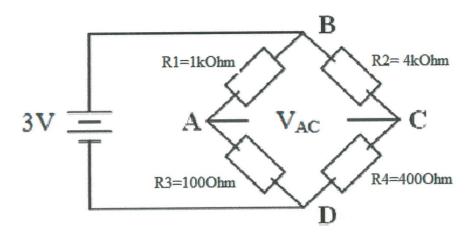


Figure Q3(a)

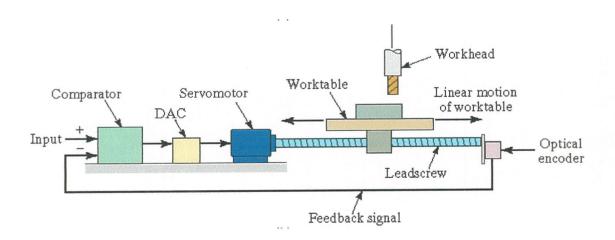


Figure Q4

