



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2017/2018**

COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I  
COURSE CODE : BEF12403  
PROGRAMME CODE : BEV  
EXAMINATION DATE : DECEMBER 2017/JANUARY 2018  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

- Q1** Differentiate the following concepts. Use an appropriate diagram or equation to support your explanation.
- (a) Active and passive elements. (5 marks)
- (b) Kirchhoff current and voltage laws. (5 marks)
- Q2** Configuration of a resistance array for a black box is given in **Figure Q2**. Calculate the equivalent resistance between the following terminals.
- (a) *A* and *B*. (4 marks)
- (b) *A* and *C*. (4 marks)
- (c) *B* and *D*. (4 marks)
- Q3** Device 1 and 2 are rated as shown in **Figure Q3**. Find the values of  $R_1$  and  $R_2$  to power the devices using a 20 V battery. (15 marks)
- Q4** A typical transistor amplifier is shown in **Figure Q4**. Determine the amplifier gain, which is the ratio of the output voltage,  $v_o$  to the input voltage,  $v_i$ . (15 marks)
- Q5** With mesh analysis, prove that the value of  $i = -5.33\text{mA}$  for the circuit in **Figure Q5**. (10 marks)

TERBUKA

- Q6** The variable resistor,  $R_L$  in the circuit of **Figure Q6** is adjusted to achieve maximum power transfer to  $R_L$ .
- (a) Calculate the value of  $R_L$ . (19 marks)
- (b) Find the maximum power transferred,  $P_{max}$  to  $R_L$ . (3 marks)
- Q7** Explain the superposition theorem. Justify why superposition principle can be applied to passive direct current (DC) circuits. (6 marks)
- Q8** Three (3) devices and each with  $P1$ ,  $P2$  and  $P3$  watts are connected in parallel to a voltage source. Prove that the total power,  $P_T = P1 + P2 + P3$ . (10 marks)




**TERBUKA**

- END OF QUESTIONS -


**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/ 2017/2018      PROGRAMME CODE : BEV  
 COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I      COURSE CODE : BEF12403

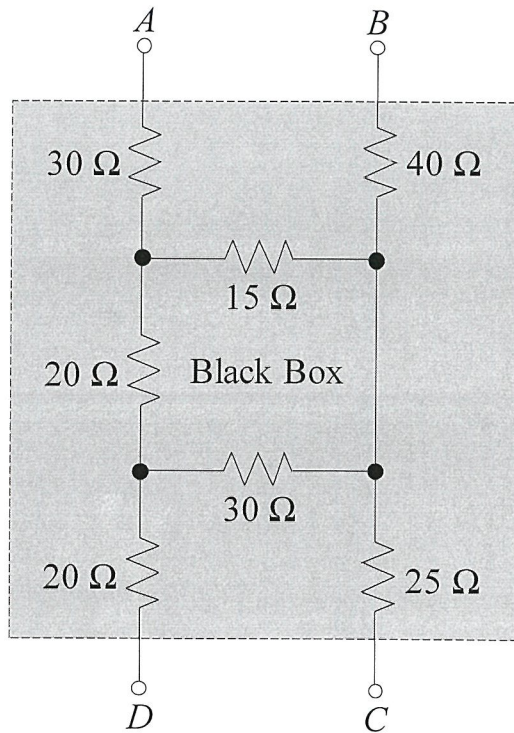

**Figure Q2**


**TERBUKA**

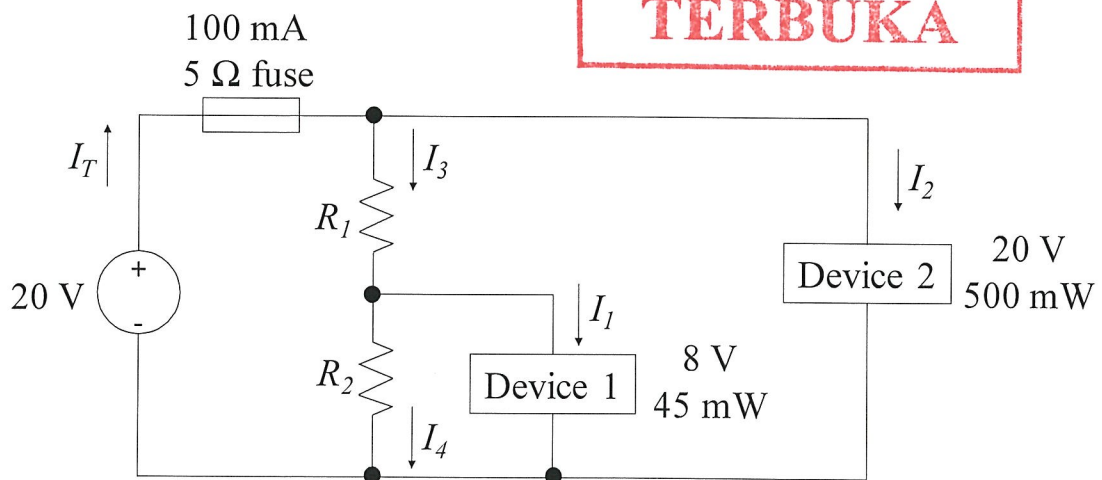


**Figure Q3**

**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/ 2017/2018      PROGRAMME CODE : BEV  
 COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I      COURSE CODE : BEF12403

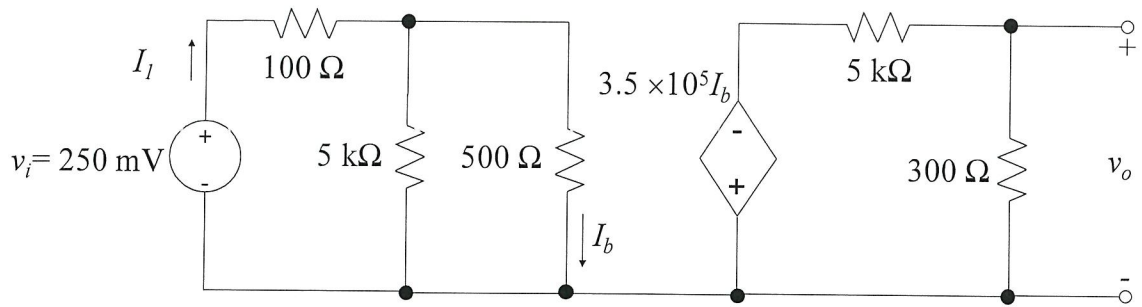

**Figure Q4**

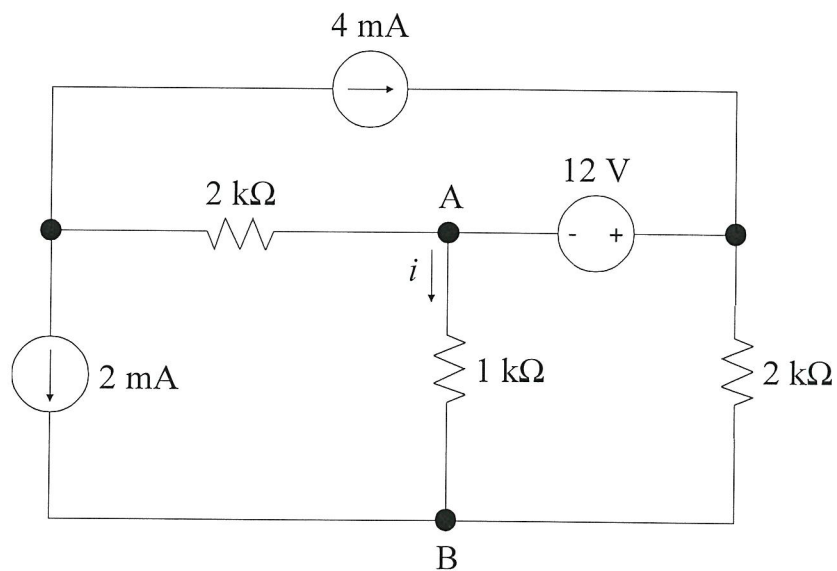

**Figure Q5**

**TERBUKA**

*Subanga*

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/ 2017/2018  
COURSE NAME : ELECTRIC CIRCUIT ANALYSIS I

PROGRAMME CODE : BEV  
COURSE CODE : BEF12403

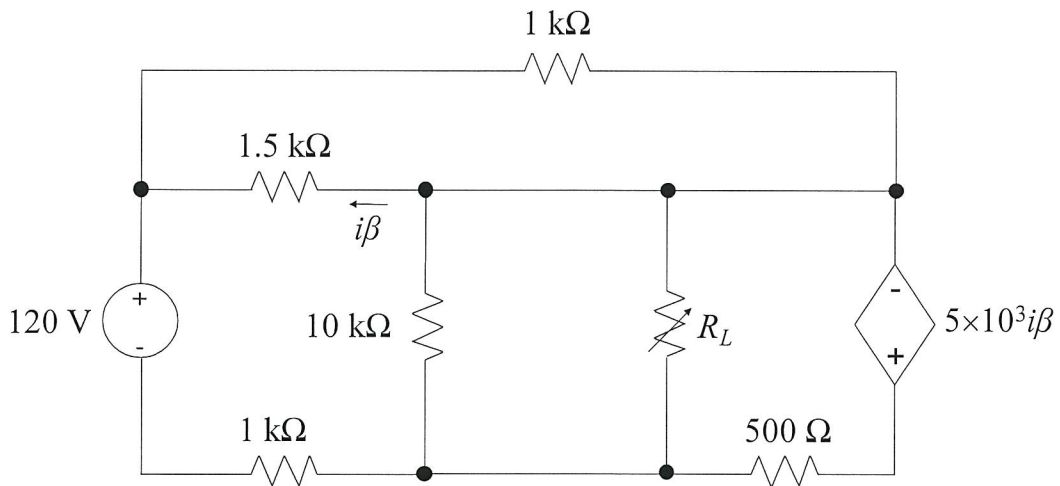


Figure Q6

TERBUKA

*Terbuka*