



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2017/2018**

**TERBUKA**

COURSE NAME : ELECTRICAL TECHNOLOGY  
COURSE CODE : BEE 10403  
PROGRAMME CODE : BEJ  
EXAMINATION DATE : DECEMBER 2017/JANUARY 2018  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF SIX (6) PAGES

Q1 (a) Explain the relation between line voltage,  $V_L$  and phase voltage,  $V_P$ ; and between line current,  $I_L$  and phase current,  $I_P$  in Wye-Y and Delta- $\Delta$  connected load. Draw 3-phase phasor diagram for the voltages and currents.

(10 marks)

(b) For a  $\Delta - \Delta$  balanced system, a line to line voltage of  $V_{ab} = 173$  V and a load of  $Z_a = 30 + j10 \Omega$ . If the source voltage are in positive sequence, determine

(i) The phase and line currents.

(6 marks)

(ii) The average power, total reactive power and total complex power at the source.

(4 marks)

Q2 (a) Describe the two conditions of 'the right hand rule' using a simple diagram.

(3 marks)

(b) A coil of 300 turns is wound uniformly on a ring of non-magnetic material. The ring has a mean circumference of 40 cm and a uniform cross sectional area of  $4 \text{ cm}^2$ . If the current in the coil is 5 A and the relative permeability of non-magnetic material is 1, calculate

(i) The magnetic field strength,  $H$

(3 marks)

(ii) The flux density,  $\beta$

**TERBUKA**

(2 marks)

(iii) The total magnetic flux in the ring,  $\Phi$

(2 marks)

(c) A closed magnetic circuit of cast steel contains a 7 cm long path of cross-sectional area  $1.5 \text{ cm}^2$  and a 2 cm path of cross-sectional area of  $0.5 \text{ cm}^2$ . A coil of 300 turns is wound around the 7 cm length of the circuit and a current of 0.5 A flows. If the relative permeability of the cast steel is 750, determine the flux density in the 7 cm path of the cast steel.

(10 marks)

**Q3** (a) A 5 kVA, 200 V / 100 V, 50 Hz, single phase ideal two winding transformer is used to step up a voltage of 200 V to 300 V by connecting it as an auto transformer.

(i) Show the connection diagram of the auto transformer that is used to step up a voltage of 200 V to 300 V with all important labels of  $V_L$ ,  $I_L$ ,  $V_{SE}$ ,  $V_C$ ,  $I_H$ , and  $V_H$ .

(4 marks)

(ii) Recommend the maximum value of kVA that can be handled by the autotransformer (without over loading any of coil).

(4 marks)

(iii) Determine the value of kVA that is transferred magnetically and the kVA that is transferred by electrical conduction.

(2 marks)

(b) A 500 kVA 30 kV/240V transformer has the following parameters:

$$R_p = 0.5 \Omega \qquad X_p = 0.4 \Omega \qquad R_c = 20 k\Omega$$

$$R_s = 2 m\Omega \qquad X_s = 4 m\Omega \qquad X_m = 5 k\Omega$$

By using the equivalent circuit referred to the primary as that illustrated in **Figure Q3(b)**, compute the  $V_{Rc}$  (i.e. the voltage across the resistor,  $R_c$ ) of the transformer at the rated load with 0.85 lagging power factor.

(10 marks)

TERBUKA

**Q4** (a) (i) Explain two main power losses in a Direct Current (DC) machine. (3 marks)

(ii) Suggest two (2) methods to increase the turning force (or torque) of a DC motor. (3 marks)

(iii) Differentiate between DC motors and DC generators. (2 marks)

(b) A 12 V shunt DC machine in **Figure Q4(b)** has an armature resistance of  $0.5 \Omega$  and a field resistance of  $100 \Omega$ . The line current at full load is 2 A. At no load, the DC machine takes a line current of 0.5 A while running at 2500 rpm.

(i) Classify the DC machine with an explanation. (2 marks)

- (ii) Find the field current and the induced voltage when there is no load. (5 marks)
- (iii) Find the full load speed and the speed regulation of the DC motor. (5 marks)

**Q5** (a) Briefly explain the followings:

- (i) The working principle of a three-phase synchronous motor. (5 marks)
- (ii) The differences between a synchronous motor and an induction motor. (3 marks)

(b) A synchronous motor that is connected to 4000 V, 3-phase line develops an excitation voltage  $E_o$  of 1500 V (line to neutral) when the DC exciting current is 25 A as illustrated in **Figure Q5(b)**. The synchronous reactance is  $22 \Omega$  and the torque angle is  $30^\circ$ . Show the answers of the following questions in polar forms with **two (2)** decimal places.

- (i) Compute the voltage across the synchronous reactance,  $E_x$ . (4 marks)
- (ii) Compute the AC line current,  $I$ . (2 marks)
- (iii) Compute the power factor of the motor,  $p.f$ . (3 marks)
- (iv) Draw the phasor diagram. (3 marks)

**- END OF QUESTIONS -**

**TERBUKA**

UNIVERSITÄT DUISBURG ESSEN  
FACHBEREICH ELEKTROTECHNIK  
LEHRGEBIET ELEKTROMOTOREN UND ANTRIEBE  
VERGLEICHENDE MASCHINENLEHRE  
PROF. DR.-ING. habil. RUDOLF DIERKS  
LEHRSTUHL FÜR ELEKTROMOTOREN UND ANTRIEBE



FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 20172018  
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BEJ  
COURSE CODE : BEE 10403

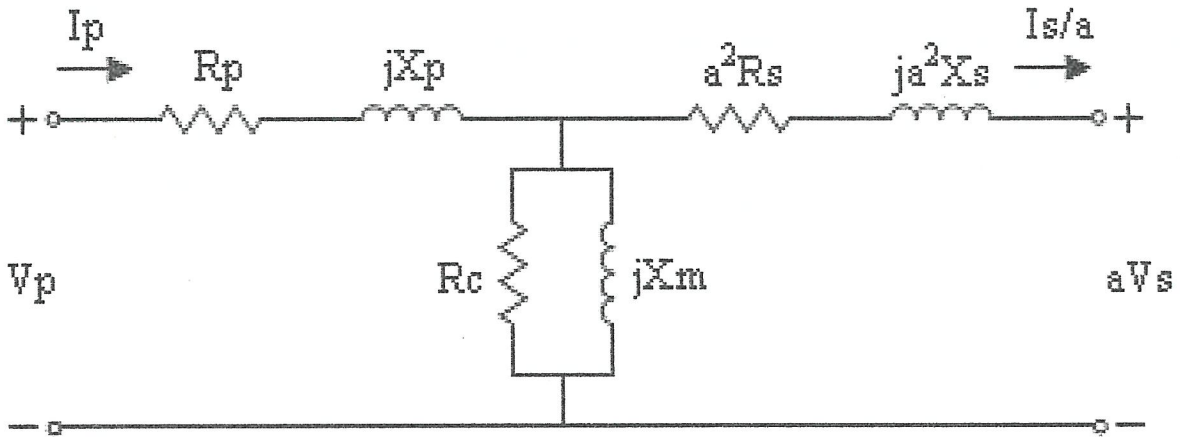


Figure Q3(b)

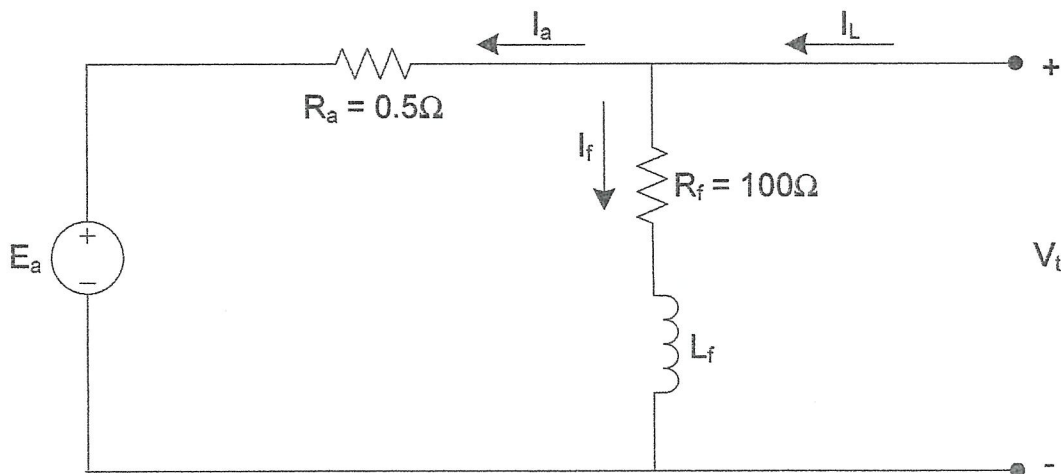


Figure Q4(b)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 20172018  
 COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BEJ  
 COURSE CODE : BEE 10403

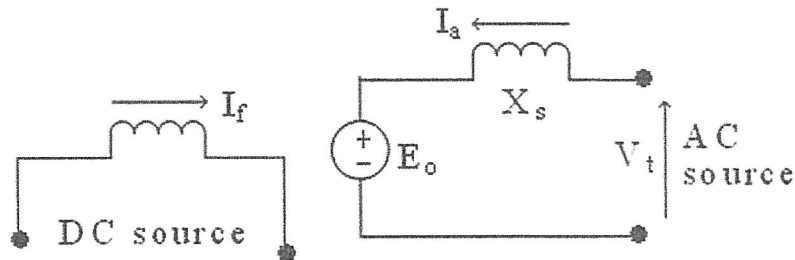


Figure Q5(b)

**TERBUKA**

List of Formulae and Constant

1.  $\beta = \mu H$  (unit: Tesla, T)
2. mmf (or  $F_m$ ) =  $NI = Hl$  (unit: Ampere-turns, At)
3.  $S$  (or  $R$ ) =  $l/\mu A = \text{mmf}/\phi$  (unit: Ampere-turns/weber, At/Wb)
4.  $\phi_{\max} = B_{\max} a_{\text{area}}$  (unit: Weber, Wb)
5.  $E = 4.44 f N \phi_m$  (unit: Volt, V)
6.  $a = \frac{v_p}{v_e} = \frac{e_p}{e_s} = \frac{N_p}{N_s}$  (unit: -)
7. Permeability of vacuum,  $\mu_0 = 4\pi \times 10^{-7} \text{ Wb/At.m}$  (or H/m)