

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2017/2018**

TERBUKA

**COURSE NAME : ELECTRONIC CIRCUITS
ANALYSIS AND DESIGN**

COURSE CODE : BEL 30403

PROGRAMME CODE : BEJ

EXAMINATION DATE : DECEMBER 2017 / JANUARY 2018

DURATION : 3 HOURS

INSTRUCTION : ANSWERS ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF TEN (10) PAGES

CONFIDENTIAL

Q1 Based on input signal, V_{in} in **Figure Q1(a)**:

- (i) Name the function of each op-amp in **Figure Q1(b)**. (3 marks)
- (ii) Draw and label completely the output waveforms V_{01} , V_{02} and V_{03} by analysing the circuit in **Figure Q1(b)**. (17 marks)

Q2 (a) **Figure Q2** shows an oscillator circuit using two 555 timers. Assume that the reset pin is active low. When the switch is opened:

- (i) Draw the output waveform (V_{01}) of Timer A indicating clearly the ON and OFF time, and calculate the frequency of oscillation of Timer A. (4 marks)
 - (ii) Obtain the duty cycle of Timer B. (3 marks)
- (b) Explain the operation of the oscillator when the switch in **Figure Q2** is closed and draw the output waveform of both timers (V_{01} and V_0) for **two (2)** cycles of V_{01} . Indicate clearly the relationship between those two waveforms by drawing them parallel at time axis. (8 marks)
- (c) Redesign the Timer A to be a one shot or monostable multivibrator with a high output of similar time to t_{ON} in **Q2(a)(i)**. State the condition on the input to the monostable multivibrator in order to produce the output. (5 marks)



Q3 (a) **Figure Q3(a)** shows an Op-Amp amplifier circuit which employs a negative feedback.

- (i) Classify the feedback topology used and the type of amplifier in the circuit. (4 marks)
 - (ii) Formulate the feedback network (β) and the overall gain of the amplifier with feedback (A_F). (10 marks)
- (b) A current amplifier with an input impedance (z_i) of $5k\Omega$ has an open loop gain (A) of $100k$ and a high cut-off frequency (f_H) at 15 kHz . The amplifier is connected to a feedback network as shown in **Figure Q3(b)** and the close loop gain (A_F) is 100 .

- (i) Obtain the closed-loop high cut-off frequency (f_{HF}) for this system. (4 marks)
- (ii) Based on your answer in Q3(b)(i), point out the advantage of having a negative feedback (2 marks)

Q4 The circuit in **Figure Q4** is an active filter. For this circuit

- (i) Derive the expression for the voltage transfer function of the circuit

$$H(s) = \frac{V_o(s)}{V_i(s)}$$
 (9 marks)
- (ii) Determine the gain of the circuit at DC ($f= 0$ Hz). (3 marks)
- (iii) Find the cut-off frequency for the circuit. (3 marks)
- (iv) Draw the frequency response and then determine the filter type and order. (5 marks)

TERBUKA

- Q5** (a) Design a shunt regulator circuit that meets these requirements:
- voltage regulation is achieved by drawing large current from load through a transistor
 - the regulated output voltage is 9V
 - the input voltage is 15V
 - input current shall be twice the load current

Show a complete circuit configuration with values of all required components. (12 marks)

- (b) Analyse the effect to circuit operation if the load resistor is larger than its designed value in Q5(a). Support your analysis with the appropriate examples. (8 marks)

- END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2017/2018
 COURSE NAME : ELECTRONIC CIRCUITS
 ANALYSIS AND DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEL 30403

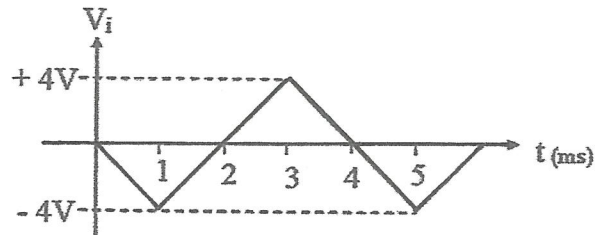


Figure Q1(a)

TERBUKA

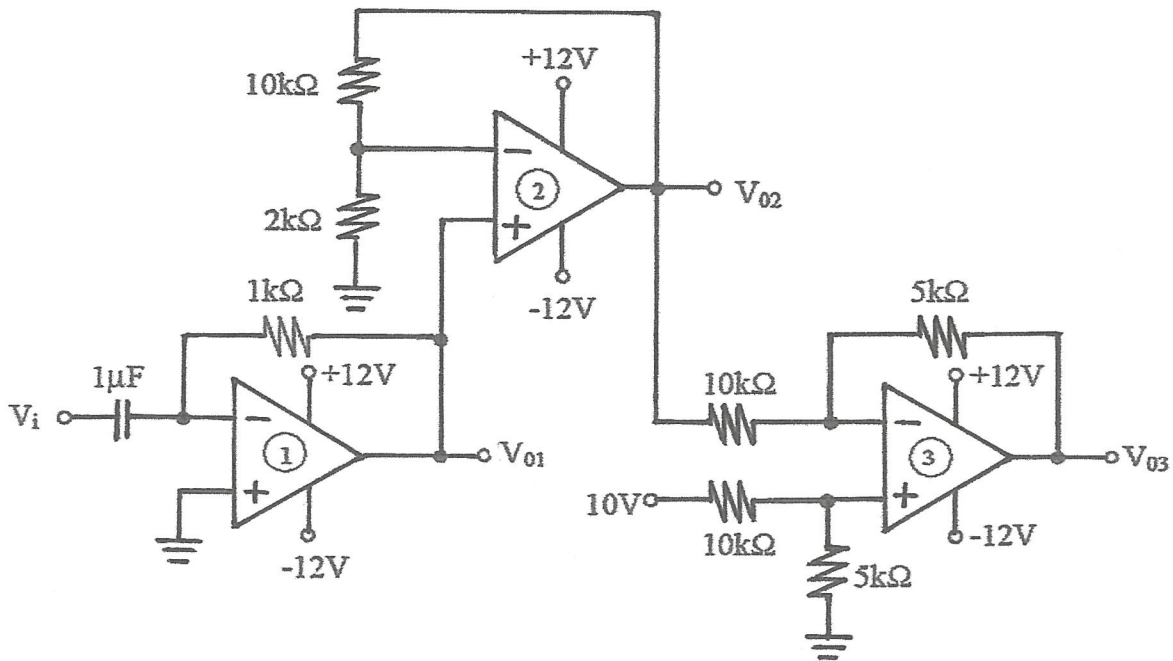


Figure Q1(b)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2017/2018
 COURSE NAME : ELECTRONIC CIRCUITS
 ANALYSIS AND DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEL 30403

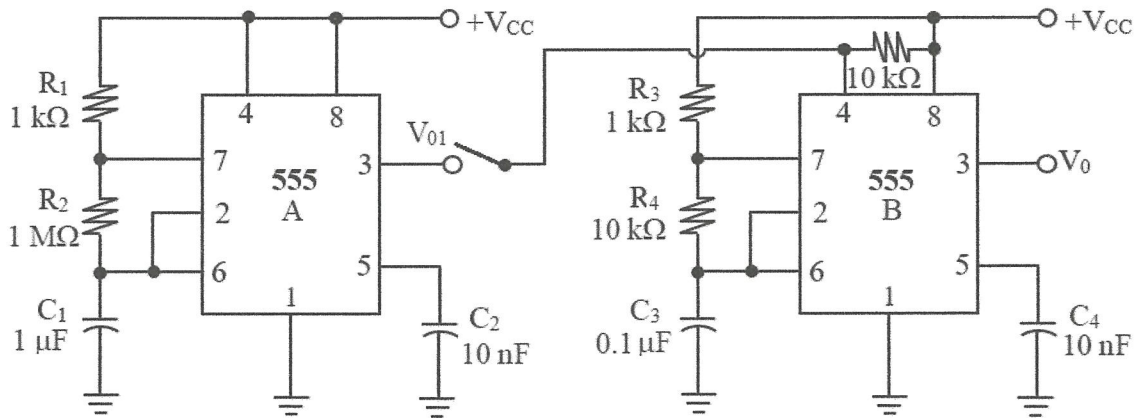


Figure Q2

TERBUKA

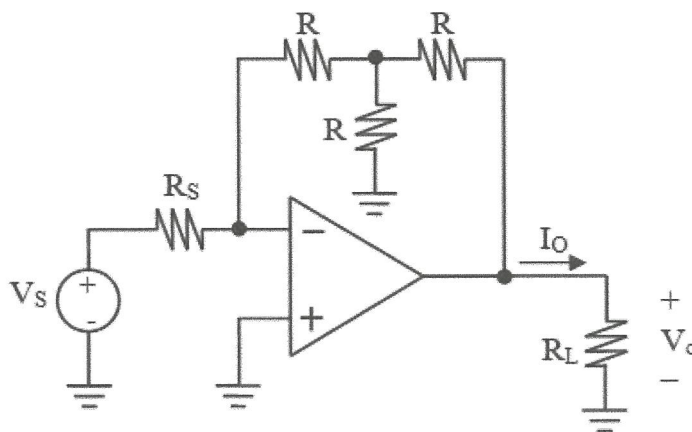


Figure Q3(a)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2017/2018
COURSE NAME : ELECTRONIC CIRCUITS
ANALYSIS AND DESIGN

PROGRAMME CODE : BEJ
COURSE CODE : BEL 30403

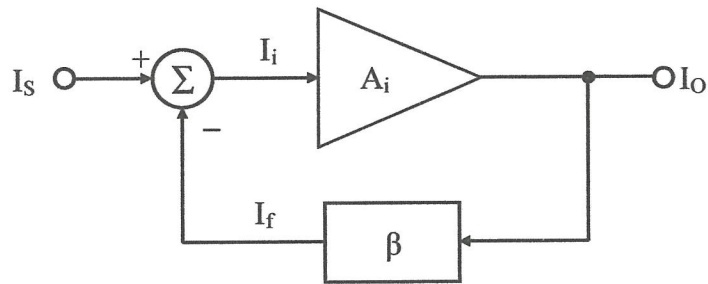


Figure Q3(b)

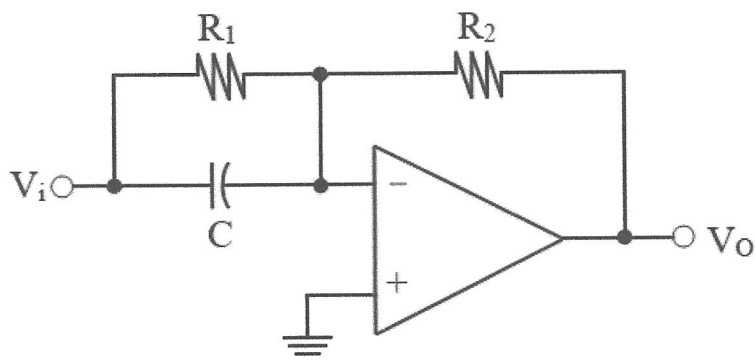


Figure Q4

TERBUKA

FINAL EXAMINATION	
SEMESTER / SESSION : SEM I / 2017/2018	PROGRAMME CODE : BEJ
COURSE NAME : ELECTRONIC CIRCUITS ANALYSIS AND DESIGN	COURSE CODE : BEL 30403

Table 1 List of formula

Inverting Amplifier	$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$
Non-Inverting Amplifier	$A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$
Inverting Summing Amplifier	$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$
Non-Inverting Summing Amplifier	$V_o = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{R_B}{R_A + R_B} V_A + \frac{R_A}{R_A + R_B} V_B \right)$
Subtracting Amplifier	$V_o = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} V_2 - \frac{R_f}{R_1 + R_f} V_1 \right)$
Instrumentation Amplifier	$A_T = A_1 A_2 = \frac{v_o}{v_{in}} = \left(1 + \frac{2R}{R_x} \right) \left(\frac{R_4}{R_3} \right)$
Integrator	$V_o(t) = -\frac{1}{RC} \int_{t_0}^t V_i(t) dt + V_o(t_0)$
Differentiator	$V_o(t) = -RC \frac{dV_i(t)}{dt}$
Schmitt Trigger	$V_{UTP \text{ or } LTP} = \frac{R_2}{R_1 + R_2} (\pm V_{out(max)}) + \frac{R_1}{R_1 + R_2} (V_{REF})$
Cut-off frequency for a filter	$f_c = \frac{1}{2\pi RC}$
1 st order Low Pass Filter	$A_v(s) = \frac{V_o}{V_i} = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{1}{1 + sRC} \right)$
2 nd order Low pass filter	$A_v(s) = \frac{V_o}{V_i}(s) = \frac{A_{vo}}{(RCs)^2 + (3 - A_{vo})RCs + 1}$
1 st order High Pass Filter	$A_v(s) = \frac{V_o}{V_i} = \left(1 + \frac{R_f}{R_1} \right) \left(\frac{1}{1 + \frac{1}{sRC}} \right)$

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017
 COURSE NAME : ELECTRONIC CIRCUITS
 ANALYSIS AND DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEL 30403

Table 1 List of formula (Cont..)

2 nd order High Pass Filter	$A_v(s) = \frac{V_o}{V_i}(s) = \frac{A_{vo}}{\frac{1}{(sRC)^2} + \frac{3-A_{vo}}{sRC} + 1}$
Negative feedback – Gain	$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$
Positive feedback – Gain	$A_f = \frac{A}{1 - \beta A}$
Phase shift oscillator	$\beta = \frac{V_F}{V_o} = \frac{1}{\left(1 - \frac{5}{\omega^2 R^2 C^2}\right) + j\left(\frac{1}{\omega^3 R^3 C^3} - \frac{6}{\omega RC}\right)}$ or $\beta = \frac{V_F}{V_o} = \frac{1}{(1 - 5\omega^2 R^2 C^2) + j(6\omega RC - \omega^3 R^3 C^3)}$
Wien bridge oscillator	$f_o = \frac{1}{2\pi RC\sqrt{6}} \quad \text{or} \quad f_o = \frac{\sqrt{6}}{2\pi RC}$
Wien bridge oscillator	$f_o = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$
Colpitts Oscillator	$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$
Hartley Oscillator	$f_o = \frac{1}{2\pi\sqrt{CL_{eq}}} \quad L_{eq} = L_1 + L_2$
UJT relaxation oscillator	$f_o = \frac{1}{R_T C_T \ln[1/(1-\eta)]}$

TERBUKA

FINAL EXAMINATION	
SEMESTER / SESSION : SEM I / 2016/2017 COURSE NAME : ELECTRONIC CIRCUITS ANALYSIS AND DESIGN PROGRAMME CODE : BEJ COURSE CODE : BEL 30403	
Table 1 List of formula (Cont..)	
Square-wave Oscillator	$f = \frac{1}{T} = \frac{1}{2RC \ln \left(\frac{1+\beta}{1-\beta} \right)}$ $\beta = \frac{R_3}{R_3 + R_2}$
Triangular-wave Oscillator	$f = \frac{1}{4R_1C} \frac{R_2}{R_3}$
Capacitor voltage	$v_c(t) = v_c(0) + (v_c(\infty) - v_c(0)) \left(1 - e^{-t/\tau} \right)$ $= v_c(\infty) + (v_c(0) - v_c(\infty)) e^{-t/\tau}$
Astable Multivibrator	$T_m = t_1 = \tau_2 \ln 2 = 0.693(R_1 + R_2)C_1$ $T_s = t_2 = \tau_2 \ln 2 = 0.693R_2C_1$ $T = T_m + T_s$ $f = \frac{1.44}{(R_1 + 2R_2)C_1}$ $D = \frac{T_m}{T_m + T_s} \times 100\% = \frac{R_1 + R_2}{R_1 + 2R_2} \times 100\%$
Monostable Multivibrator	$T = 1.1 R_1 C_1$
Ripple Factor	$\% r = \frac{\text{ripple voltage (rms)}}{\text{dc voltage}} = \frac{V_{r(rms)}}{V_{dc}} \times 100$
Half-wave rectifier with a filter	$V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}} \approx \frac{V_{o(p)}}{2\sqrt{3} f C R_L}$ <div style="border: 2px solid red; padding: 5px; display: inline-block; margin: 10px 0;">TERBUKA</div> $V_{o(DC)} = V_{o(p)} - \frac{V_{r(p-p)}}{2}$ $V_{r(p-p)} \approx \frac{V_{o(p)}}{f C R_L} = \frac{I_{o(DC)}}{f C}$ $r = \frac{V_{r(rms)}}{V_{DC}} \approx \frac{1}{2\sqrt{3} f C R_L}$

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017
 COURSE NAME : ELECTRONIC CIRCUITS
 ANALYSIS AND DESIGN

PROGRAMME CODE : BEJ
 COURSE CODE : BEL 30403

Table 1 List of formula (Cont..)

<p>Full-wave rectifier with a filter</p>	$V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}} \approx \frac{V_{o(p)}}{4\sqrt{3}fCR_L} = \frac{I_{DC}}{4\sqrt{3}fC}$ $V_{o(DC)} = V_{o(p)} - \frac{V_{r(p-p)}}{2} \qquad V_{r(p-p)} = \frac{I_{o(DC)}}{2fC} \approx \frac{V_{o(p)}}{2fCR_L}$ $r = \frac{V_{r(rms)}}{V_{DC}} \approx \frac{1}{4\sqrt{3}fCR_L}$
<p>Rectifier with Additional RC filter</p>	$V'_{r(rms)} \approx \frac{X_C}{R} V_{r(rms)}$
<p>Inductor Filter</p>	$r = \frac{R_L}{3\sqrt{2}\omega L}$
<p>Shunt regulator</p>	$V_o \cong V_B \left(\frac{R_1 + R_2}{R_2} \right) \qquad V_B = V_Z + V_{BE}$ $V_o \cong \left(\frac{R_1 + R_2}{R_2} \right) (V_Z)$
<p>Series regulator</p>	$V_o = \frac{R_1 + R_2}{R_1} (V_Z + V_{BE}) \qquad V_o = V_Z \left(\frac{R_1 + R_2}{R_1} \right)$
<p>Adjustable IC regulator</p>	$V_o = V_{ref} \left(1 + \frac{R_2}{R_1} \right) + I_{adj} R_2$

TERBUKA