

CONFIDENTIAL



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER I SESSION 2017/2018

COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

COURSE CODE : BEF 22803

PROGRAMME CODE : BEV

EXAMINATION DATE : DECEMBER 2017 / JANUARY 2018

DURATION : 3 HOURS

INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

CONFIDENTIAL

Q1 (a) Sketch the waveform of the following functions:

(i) $x(t) = \begin{cases} 0 & t < 2 \\ t + 2 & t \geq 2 \end{cases}$ (2 marks)

(ii) $f(t) = 2u(t - 2) + 3u(t - 4) - 6u(t - 6)$ (3 marks)

(b) Determine the mathematical function $f(t)$ as shown in **Figure Q1(b)**.
(hint: **not** the piecewise function)

(3 marks)

(c) System $h(t)$ is given with an input signal of $y_i(t)$. Determine the piecewise function of signal output $y_o(t) = h(t) * y_i(t)$ using convolution method. The signals are given in **Figure Q1(c)**. Fold the input signal to solve this question.

(12 marks)

Q2 (a) Find the Laplace transformation of following functions by referring to the Laplace Transform Table:

(i) $y_1(t) = 2e^{8t}u(t)$ (2 marks)

(ii) $y_2(t) = 2u(t - 3) - 4u(t - 6)$ (4 marks)

(iii) $y_3(t) = \cos 2(t - 4)u(t - 4)$ (4 marks)

(b) Find the inverse Laplace transformation of the following function by referring to Laplace Transform tables:

(i) $F_1(s) = 3 + \frac{6}{s+6} - \frac{7s}{s^2+16}$ (5 marks)

(ii) $F_2(s) = \frac{s+10}{s^2-8s-20}$ (5 marks)

TERBUKA

Q3 (a) Consider the circuit for **Figure Q3(a)**. Assume the circuit is in steady state prior to $t = 0$, determine $i(t)$ for $t > 0$ s. (hint: switch is closed at $t = 0$). (10 marks)

(b) The input. A circuit with the parallel RLC load is shown in **Figure Q3(b)**. Given the input current is $i_s(t) = 4u(t)$ A, $v(0) = 5V$ and $i(0) = -2A$. Determine the function of $v(t)$ and $i(t)$ for C and L loads. (10 marks)

Q4 (a) The input voltage for **Figure Q4(a)** is $v_i(t) = 2e^{-3t}u(t)$. Determine the output voltage of the capacitor, $v_o(t)$ (6 marks)

(b) The input current of the circuit in **Figure Q4(b)** is $i_i(t) = 10 \sin 2t$ A. Using the Fourier transform method, determine the output current of the circuit, $i_o(t)$ (14 marks)

Q5 The input voltage $v(t)$ for **Figure Q5** is given in Fourier series expansion:

$$v(t) = 1 + \sum_{n=1}^{\infty} \frac{2(-1)^n}{1+n^2} (\cos(nt) - n \cdot \sin(nt))$$

- (a) Determine the total impedance of the circuit, Z_{total} (3 marks)
- (b) Calculate the output current for the inductor in time domain, $i_0(t)$ (10 marks)
- (c) Calculate the rms value of the input voltage, V_{rms} (7 marks)





-END OF QUESTIONS-

TERBUKA

FINAL EXAMINATION




SEMESTER/SESSION : SEMESTER I/ SESSION 2017/2018
 COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEV
 COURSE CODE : BEF 22803

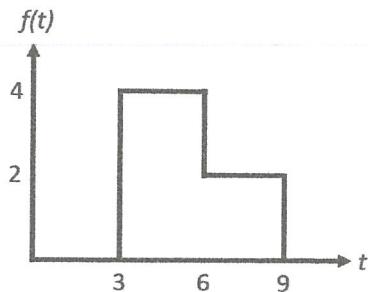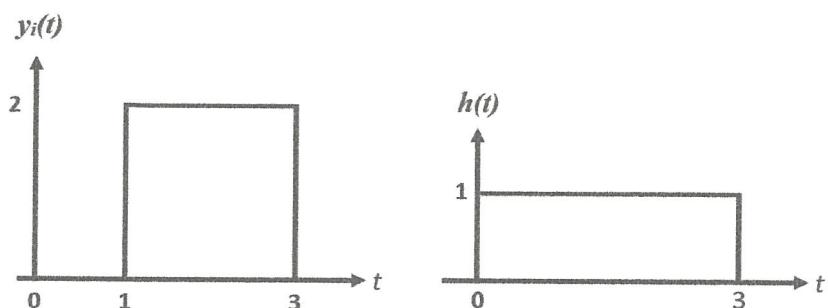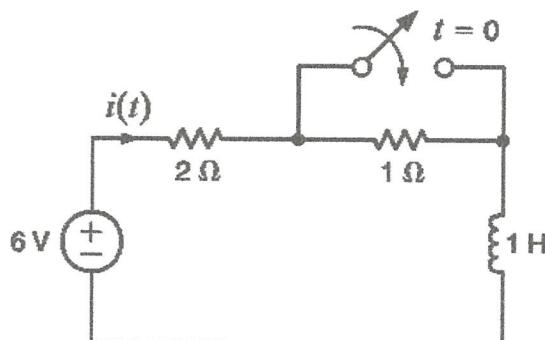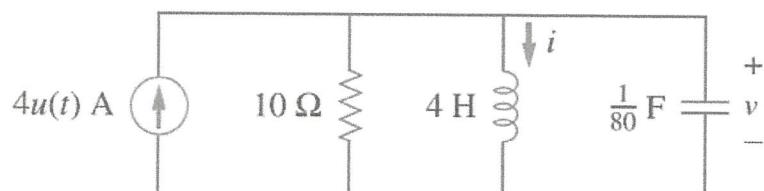Figure Q1(b)Figure Q1(c)Figure Q3(a)Figure Q3(b)

TERBUKA⁴

CONFIDENTIAL

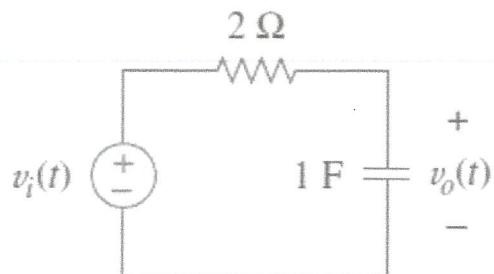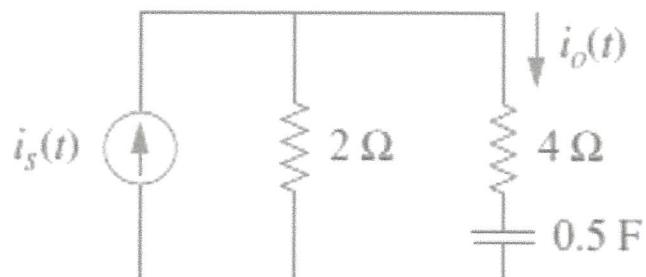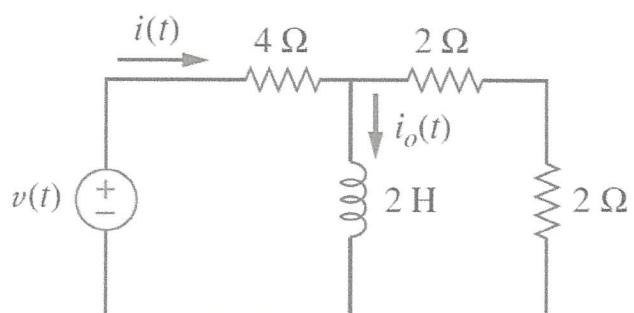FINAL EXAMINATIONSEMESTER/SESSION : SEMESTER I/ SESSION 2016/2017
COURSE NAME : TRANSFORM CIRCUIT ANALYSISPROGRAMME : BEV
COURSE CODE : BEF 22803**Figure Q4(a)****Figure Q4(b)****Figure Q5****TERBUKA**

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER I/ SESSION 2017/2018
 COURSE NAME : TRANSFORM CIRCUIT ANALYSIS

PROGRAMME : BEV
 COURSE CODE : BEF 22803

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$f(t) = a_0 + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t + \phi_n)$$

$$A_n = \sqrt{a_n^2 + b_n^2}, \quad \phi_n = -\tan^{-1} \frac{b_n}{a_n}$$

$$A_n/\phi_n = a_n - jb_n$$

TABLE 1: LAPLACE TRANSFORM PAIRS

$f(t)$	$F(s)$	$f(t)$	$F(s)$
$\delta(t)$	1		
$u(t)$	$\frac{1}{s}$	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
e^{-at}	$\frac{1}{s+a}$	$\sin(\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
t	$\frac{1}{s^2}$	$\cos(\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$
t^n	$\frac{n!}{s^{n+1}}$	$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
te^{-at}	$\frac{1}{(s+a)^2}$	$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$t^n e^{-at}$	$\frac{n!}{(s+a)^{n+1}}$		
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$		

*Defined for $t \geq 0$; $f(t) = 0$, for $t < 0$.

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : SEMESTER I/ SESSION 2017/2018
COURSE NAME : TRANSFORM CIRCUIT ANALYSISPROGRAMME : BEV
COURSE CODE : BEF 22803

TABLE 2: LAPLACE TRANSFORM PROPERTIES

Property	$f(t)$	$F(s)$
Linearity	$a_1f_1(t) + a_2f_2(t)$	$a_1F_1(s) + a_2F_2(s)$
Scaling	$f(at)$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
Time shift	$f(t - a)u(t - a)$	$e^{-as}F(s)$
Frequency shift	$e^{-at}f(t)$	$F(s + a)$
Time differentiation	$\frac{df}{dt}$ $\frac{d^2f}{dt^2}$ $\frac{d^3f}{dt^3}$ $\frac{d^n f}{dt^n}$	$sF(s) - f(0^-)$ $s^2F(s) - sf(0^-) - f'(0^-)$ $s^3F(s) - s^2f(0^-) - sf'(0^-)$ $-f''(0^-)$ $s^n F(s) - s^{n-1}f(0^-) - s^{n-2}f'(0^-)$ $- \dots - f^{(n-1)}(0^-)$
Time integration	$\int_0^t f(x) dx$	$\frac{1}{s}F(s)$
Frequency differentiation	$tf(t)$	$-\frac{d}{ds}F(s)$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^\infty F(s) ds$
Time periodicity	$f(t) = f(t + nT)$	$\frac{F_1(s)}{1 - e^{-sT}}$
Initial value	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$

TERBUKA