



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2017/2018**

COURSE NAME : DIGITAL DESIGN
COURSE CODE : BEC 30503
PROGRAMME CODE : BEJ
EXAMINATION DATE : JUNE/JULY 2018
DURATION : 3 HOURS
INSTRUCTION : ANSWER ALL QUESTIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF **FOUR (4)** PAGES

- Q1** (a) Explain the similarities between VHDL and Verilog? (6 marks)
- (b) Sketch and explain the digital design flow for logic circuits. (10 marks)
- (c) Explain the difference between Combinational digital circuit and Sequential digital circuit. (10 marks)
- Q2** (a) By referring to the **Table Q2(a)**, construct the PAL logic circuit. The three variables, *a*, *b*, and *c*, are input signals, and the two variables, *x* and *y*, are output signals. (7 marks)

Table Q2(a) Truth Table

<i>a</i>	<i>b</i>	<i>c</i>	<i>x</i>	<i>y</i>
0	0	0	1	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	1
1	1	0	1	0
1	1	1	0	0

- (b) List the differences of the hardware properties between FPGAs and microcontrollers. (5 marks)
- (c) Construct a 4-to-1 multiplexer by using a 2-to-4 decoder and other necessary gates. (4 marks)

- Q3** (a) By referring to the VHDL code in **Listing Q3(a)**, write the suitable code for the **Entity** part. (3 marks)

```

architecture gates of two_gates is
Signal    C: bit
begin
    C <= A and B; --concurrent
    E <= C or D;  --statement
End gates;
    
```

Listing Q3(a)

- (b) Convert the Data Flow modeling in **Listing Q3(a)** to the Behavior modeling description. (5 marks)



Q4 (a) Derive the excitation equations for D1 and D0 in **Figure Q4(a)**.

(2 marks)

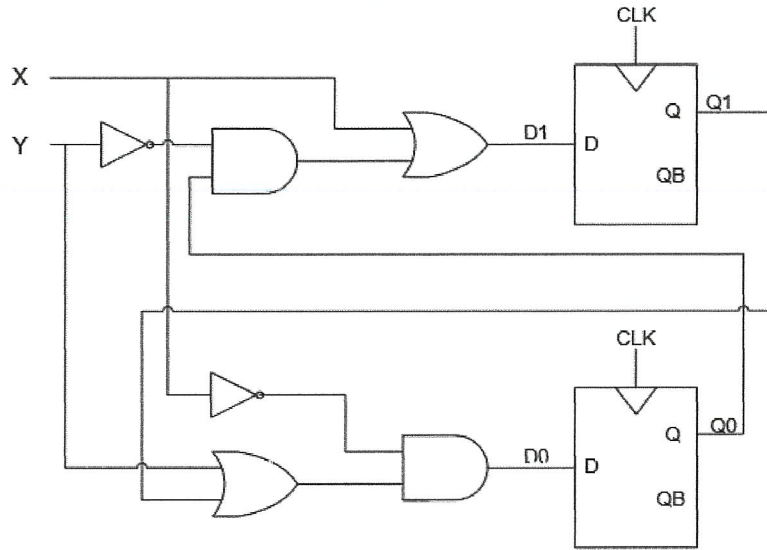


Figure Q4(a): Finite State Machine Analysis

(b) Given the state assignments in **Table Q4(b)**, Create the respective transition table and the state table.

(8 marks)

Table Q4(b): State Assignments:

S	Q1	Q0
A	0	1
B	1	0
U1	0	0
U2	1	1

(c) Based on **Table Q4(b)**, a used state will be reached in one clock cycle under all possible input conditions. For unused states U1 = 00 and U2 = 11, determine the input combinations for which this state machine is unsafe (if any).

(4 marks)

Q5 (a) Write the VHDL code for finite state machine in **Figure Q5(a)**.

(11 marks)

 


Figure Q5(a): Finite state machine

TEPBUKA