



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER II  
SESSION 2017/2018**

COURSE NAME : DIGITAL ELECTRONICS  
COURSE CODE : BEL 20303  
PROGRAMME : BEV/ BEJ  
EXAMINATION DATE : JUNE/ JULY 2018  
DURATION : 3 HOURS  
INSTRUCTION : 1. ANSWER ALL QUESTIONS IN THIS BOOKLET.  
2. **NO CALCULATOR IS ALLOWED.**

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF TWELVE (12) PAGES

- Q1** (a) Assuming that all numbers can be represented using 8 bit binary, complete the missing entries which are not shaded in the Table **Q1 (a)**. Also assume two's complement numbering system is used where necessary. (No mark will be awarded for this question unless you show how the solutions are derived).

(8 marks)

**TABLE Q1(a)**

Binary	Hexadecimal	Decimal	BCD	Gray
(i)		81		(ii)
	F4	(iii)	(iv)	

TERBUKA

(b) Given the Boolean expression:

$$Y = (a + b + c)(b + c + d)(\bar{a} + \bar{b} + \bar{d})(\bar{b} + \bar{c} + \bar{d})$$

(i) Construct a truth table for output Y

(8 marks)

(ii) Derive the minimal sum-of-product of expression Y using Karnaugh map.  
(6 marks)

(iii) Implement the circuit for the simplest Boolean expression.  
(3 marks)

TERBUKA

**Q2** (a) A combinational circuit has three inputs X, Y, and Z. Its output are 2-bit binary number which are F1 and F0. This circuit will counts the number of 1 present in the inputs.

(i) Obtain the truth table for this combinational circuit.

(4 marks)


(ii) Derive the minimal sum-of-product of expression F1 and F0.

(6 marks)

TERBUKA

- (b) Design a system, which has three inputs (A2, A1 and A0) and produces two outputs, X and Y. The output X is HIGH (1) whenever A2 and A0 are HIGH. Output Y is HIGH when X and A2 are both HIGH OR X and A1 are both LOW (0). Using the logic symbol of IC 74LS138 (3-to-8 line decoder) shown in **Figure Q2(b)**, implement this system together with the external logic gates. Show all the steps and wiring of the IC 74LS138.

(10 marks)

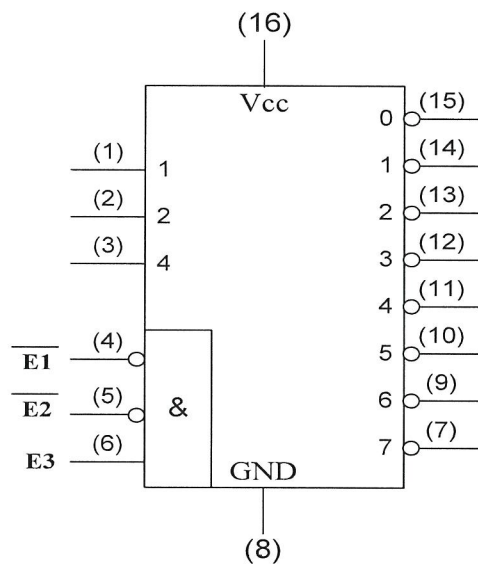


**Figure Q2(b)**

TERBUKA

- (c) Show how a 74LS151 IC (8-to-1 multiplexer) in **Figure Q2(c)** is used to implement the function:

$$F = A.B.\bar{C} + \bar{A}.B.C + A.\bar{B}.\bar{C} + A.B.C$$

(5 marks)

 

**Figure Q2(c)**

TERBUKA

Q3 (a) Explain the differences in S-R and J-K flip flop.

(4 marks)

(b) **Figure Q3(b)(i)** is a logic circuit that comprises of a JK, SC and D flip-flop. **Figure Q3(b)(ii)** shows the waveforms for signal CLK, X, Y,  $\overline{CLR}$  and  $\overline{PRE}$ . Complete the timing diagram for  $Q_A$ ,  $Q_B$  and  $Q_C$  in **Figure Q3(b)(ii)** Assume that  $Q_A$ ,  $Q_B$  and  $Q_C$  are at high level initially.

(12 marks)

 


Figure Q3(b)(i)

TERBUKA

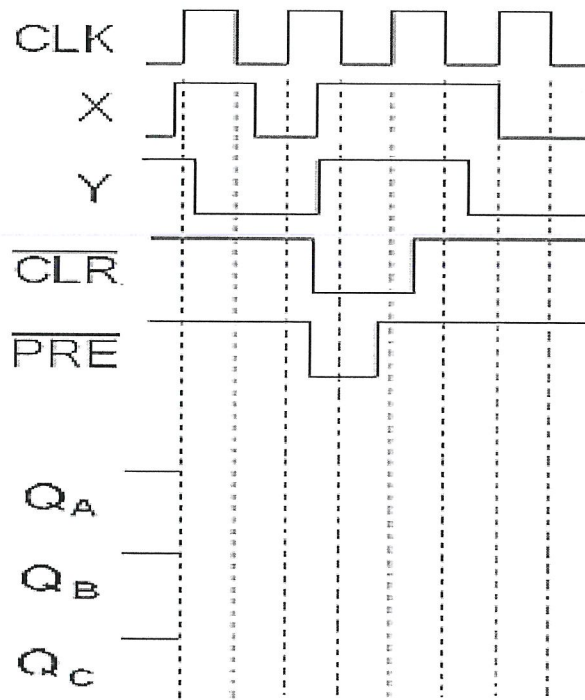


Figure Q3(b)(ii)

- (c) Given the circuit diagram in **Figure Q3(c)(i)**, determine the timing diagram for S, C and Q in **Figure Q3(c)(ii)**. Assume that Q is in high state initially.

(9 marks)

 


Figure Q3(c)(i)

TERBUKA



 


Figure Q3(c)(ii)

**Q4** Figure Q4(a)(i) shows a register and Figure Q4(a)(ii) shows the input waveforms (CLOCK and Data in) to the circuit.

(a) Analyse the circuit and draw the output waveforms for  $Q_{U1}$ ,  $Q_{U2}$ ,  $Q_{U3}$  and  $Q_{U4}$  in Figure Q4(b)(ii).

(8 marks)

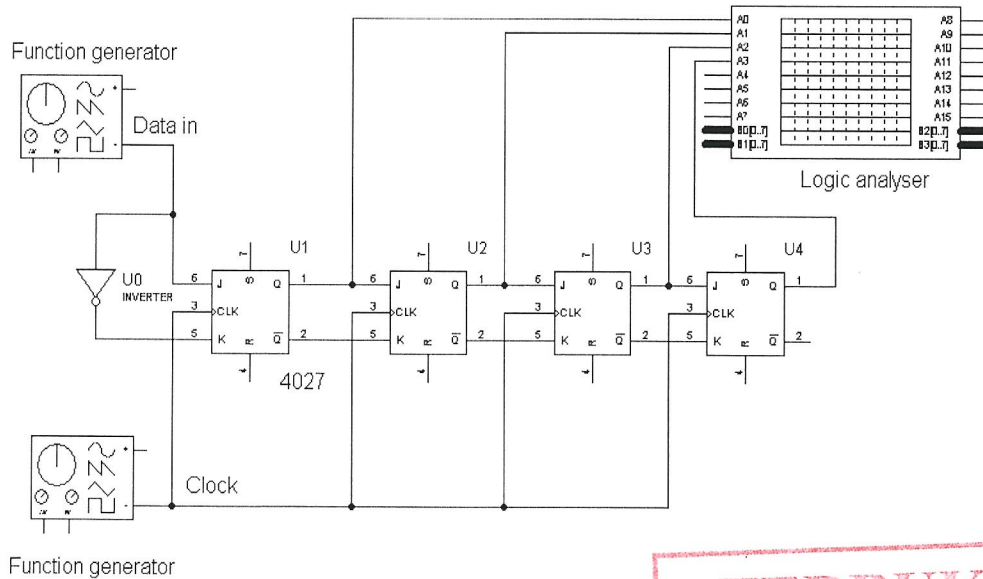


Figure Q4(a)(i)



 


Figure Q4(b)(ii)

a) Analyse and state the type of register as shown in **Figure Q4 (a)(i)**.

(2 marks)

(c) **Figure Q4(c)** shows the state transition diagram of a state machine.

 


Figure Q4(c)

TERBUKA

- (i) Build the excitation table for this state machine.

(5 marks)

- (ii) Find the simplest Boolean expression for the circuit using Karnaugh map.

(6 marks)

(iii) Implement the circuit diagram

(4 marks)

- END OF QUESTIONS -

**TERBUKA**