

**CONFIDENTIAL**



**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2018/2019**

COURSE NAME : ANALOG ELECTRONICS  
COURSE CODE : BEL 10203  
PROGRAMME : BEV/ BEJ  
EXAMINATION DATE : DECEMBER 2018/JANUARY 2019  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS


THIS QUESTION PAPER CONSISTS OF EIGHT (8) PAGES

DR. ADZIL ZUBIR / ZUBIR / ZUBIR  
Pensyarah Kanan

**CONFIDENTIAL**

Universiti Tun Hussein Onn Malaysia  
**TERBUKA**


- Q1** (a) State the definition of unbiased, forward-biased and reverse-biased a p-n junction. (3 marks)
- (b) The Shockley equation gives the relationship between the voltage across a semiconductor p-n junction diode and the current through it.
- (i) By using a diagram, describe the current-voltage characteristics of a silicon diode. (3 marks)
- (ii) When a voltage of 0.7 V is applied, the current through a diode is 18.3 mA. Calculate saturation current ( $I_S$ ) for that diode. Given that, emission coefficient ( $n$ ) is 1 and thermal voltage ( $V_T$ ) is 25 mV. (2 marks)
- (c) **Figure Q1(c)** shows an ideal diode circuit with  $R_1 = 3 \text{ k}\Omega$ ,  $R_2 = 3 \text{ k}\Omega$  and  $R_3 = 6 \text{ k}\Omega$ .

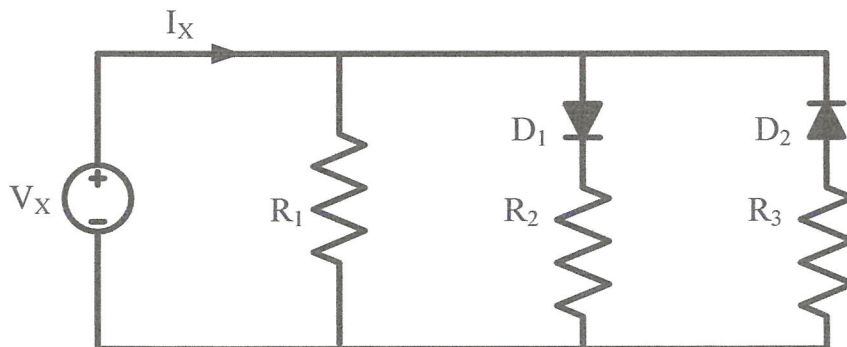

**Figure Q1(c)**


- (i) Calculate the input current ( $I_X$ ) by verifying for both condition where the diode is ON and OFF. (3 marks)
- (ii) Plot the  $I_X$ - $V_X$  characteristics. (2 marks)

- (d) **Figure Q1(d)** shows an ideal diode with  $R_1 = 10\text{ k}\Omega$  and  $R_2 = 20\text{ k}\Omega$ .

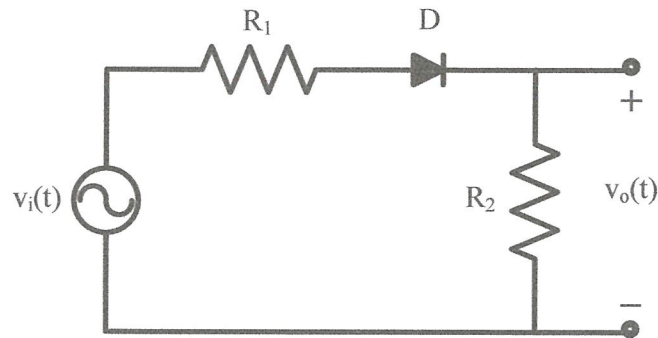

**Figure Q1(d)**

- (i) Determine the range of input voltage ( $v_i$ ) where the diode is ON and the range where the diode is OFF. (3 marks)
  - (ii) Plot the output voltage  $v_o(t)$  waveform if  $v_i = 12 \sin 2\pi \cdot 50t$  V is applied at input voltage. (2 marks)
  - (iii) State an advantage of the circuit shown in **Figure Q1(d)**. (1 marks)
- (e) **Figure Q1(e)** shows a block diagram of Circuit A which produces an output waveform  $v_o(t)$  obtained from a given input waveform  $v_i(t)$ .

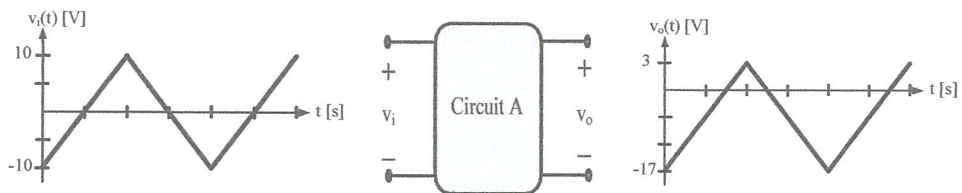


**Figure Q1(e)**

- (i) By comparing both the input and output waveforms, analyze the operation of Circuit A. (3 marks)

- (ii) Draw the schematic of Circuit A. (2 marks)
- (iii) Indicate the name of Circuit A. (1 marks)

**Q2** (a) The biasing circuit shown in **Figure Q2(a)** has the values of  $R_1 = 56 \text{ k}\Omega$ ,  $R_2 = 12.2 \text{ k}\Omega$ ,  $R_C = 2 \text{ k}\Omega$ ,  $R_E = 0.4 \text{ k}\Omega$ ,  $V_{CC} = 12 \text{ V}$  and  $\beta = 100$ .

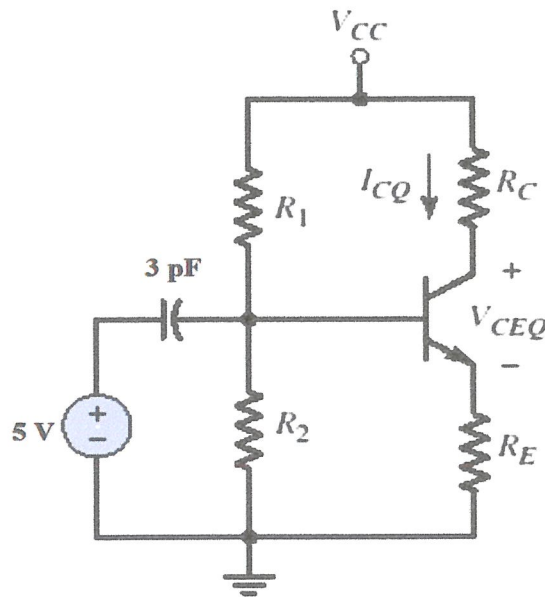


**Figure Q2(a)**

Using exact analysis,

- (i) draw the Thevenin's equivalent of the circuit. (3 marks)
- (ii) estimate,  $V_E$ . (5 marks)
- (iii) determine  $I_{CQ}$  and  $V_{CEQ}$  for the circuit. (3 marks)
- (iv) predict the operation mode of this circuit. (1 mark)

- (b) The emitter-stabilized bias configuration shown in **Figure Q2(b)** has the specifications of  $V_{CC} = 24 \text{ V}$ ,  $V_E = 2.4 \text{ V}$ ,  $I_{CQ} = 0.5 I_{CSat}$ ,  $I_{CSat} = 4.4 \text{ mA}$ ,  $V_{CEQ} = 10 \text{ V}$ ,  $C_1 = C_2 = 1 \mu\text{F}$ ,  $C_E = 10 \mu\text{F}$  and  $\beta = 90$ .

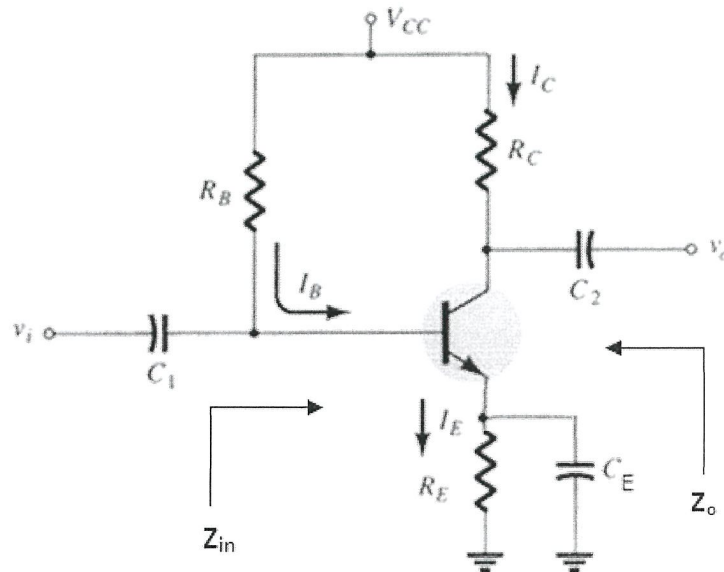


**Figure Q2(b)**

- (i) Determine the values for  $R_C$ ,  $R_E$  and  $R_B$ . (6 marks)
- (ii) If the amplifier in **Figure Q2(b)** is connected to a load of  $1 \text{ k}\Omega$  and source resistance of  $200 \Omega$ , draw the resultant small-signal equivalent circuit (AC equivalent). (3 marks)
- (iii) By using the AC equivalent circuit obtained from Q2(b)(ii), calculate the values for input and output impedances. (3 marks)
- (iv) Determine the voltage gain ( $A_v$ ). (1 mark)
- Q3** (a) Sketch and label clearly the transfer characteristics curve of a Depletion Mode Metal Oxide Semiconductor Field Effect Transistor (D-MOSFET) and Enhancement Mode Metal Oxide Semiconductor Field Effect Transistor (E-MOSFET). (*Hint: Use Shockley's equation*). (4 marks)



- (i) Determine  $I_{DQ}$  and  $V_{GSQ}$  using graphical method. (5 marks)
  - (ii) Determine the  $V_{DS}$ . (2 marks)
- (d) A common source FET amplifier circuit is shown in **Figure Q3(d)**. Given the values of  $I_{DSS} = 9 \text{ mA}$ ,  $V_p = -4.5 \text{ V}$ ,  $g_m = 60$ , and  $r_d = 30 \text{ k}\Omega$ .

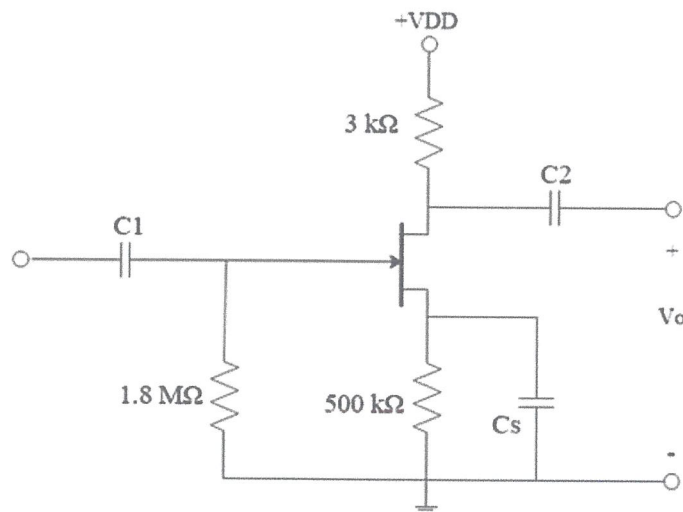

**Figure Q3(d)**

- (i) Draw the AC equivalent circuit. (4 marks)
  - (ii) Calculate the value of voltage gain,  $A_v$ . (4 marks)
  - (iii) Determine the values of input impedance,  $Z_i$  and output impedance,  $Z_o$ . (4 marks)
- Q4** (a) Bode plot indicates the frequency response of an amplifier. It is a graph of amplifier gain versus the frequency.
- (i) Sketch a bode plot of a bandpass filter complete with labels. (5 marks)

- (ii) Define a bandwidth and state the equation used. (2 marks)
- (iii) Define the roll-off gain. (1 mark)
- (iv) Differentiate between dB/decade and dB/octave. (2 marks)
- (b) Bipolar Junction Transistor (BJT)/ Field Effect Transistor (FET) amplifier reacts differently at low and high frequency resulting in different frequency response (bode plot).
- (i) Explain why the above condition happen. (2 marks)
- (ii) By using a table, list the capacitors which are affected at low frequency and high frequency for both BJT and FET amplifier. (6 marks)
- (c) By using a suitable diagram, elaborate how does Class AB amplifier configuration can be used to eliminate crossover distortion. (7 marks)

- END OF QUESTIONS -