



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2018/2019**

**COURSE NAME** : POWER ELECTRONICS  
**COURSE CODE** : BEF 34503  
**PROGRAMME** : BEV  
**EXAMINATION DATE** : DECEMBER 2018 / JANUARY 2019  
**DURATION** : 3 HOURS  
**INSTRUCTION** : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

- Q1** (a) Demonstrate power electronics system by drawing a suitable block diagram. Then, explain the function of each block. (7 marks)
- (b) Explain diode reverse recovery time ( $t_{rr}$ ) condition. You may consider suitable diagrams to support your answer. (5 marks)
- (c) A power switching device has maximum voltage and current of 280 V and 120 A, respectively. It takes 1.5  $\mu\text{s}$  to fully turn-ON and 3.3  $\mu\text{s}$  to fully turn-OFF. The switching period is 40  $\mu\text{s}$ .
- (i) Calculate the switching frequency. (1 mark)
- (ii) If the switching device is a MOSFET, sketch and label drain-source voltage ( $V_{DS}$ ) and drain-source current ( $I_{DS}$ ) waveforms with rise time ( $t_r$ ) and fall time ( $t_f$ ). (6 marks)
- (iii) Calculate average power dissipation of the switching device based on the parameters given in Q1(c). (6 marks)
- Q2** (a) Explain the operation of the rectifier circuit shown in **Figure Q2(a)** (4 marks)
- (b) **Figure Q2 (b)** shows a single phase half-wave controlled rectifier has a resistive load of  $R = 10 \Omega$ , the voltage at the secondary transformer is 230 V with ratio 2:1, and the firing angle of thyristor is  $60^\circ$ .
- (i) Calculate the average and rms load voltage. (5 marks)
- (ii) Determine the average and rms load current. (4 marks)
- (iii) Analyse the average output power. (2 marks)
- (iv) Determine the new firing angle,  $\alpha$ , if the rectifier is connected to the load which consumes 75% less than maximum possible average output voltage. (4 marks)
- (v) Draw the input voltage ( $V_s$ ), output voltage ( $V_o$ ), and current waveforms ( $I_o$ ) for the new firing angle ( $\alpha$ ). (6 marks)

TERBUKA

**Q3** A single-phase full-bridge inverter has  $RLC$  loads with  $R = 10 \Omega$ ,  $L = 31.5 \text{ mH}$  and  $C = 112 \mu\text{F}$  is shown in **Figure Q3**. The inverter frequency is 50 Hz and the DC input voltage is 240 V. Determine,

- (i) the instantaneous load current expressed as a Fourier series up to the 9<sup>th</sup>-order harmonic. (16 marks)
- (ii) the rms load current at the fundamental frequency. (2 marks)
- (iii) the %THD of the load current. (3 marks)
- (iv) the power absorbed by the load and the fundamental power. (3 marks)
- (v) the average DC supply current. (1 mark)

**Q4** (a) With adding the both Continuous Current Mode (CCM) and Discontinuous Current Mode (DCM) waveforms, explain briefly operation of the converter. (6 marks)

(b) Design a boost converter to provide an output of 36 V from 24 V source for continuous current mode. The load is 50 W and the output voltage ripple must be less than 0.5%. The maximum inductor current should be 3 A. The converter circuit is shown in **Figure Q4(b)**. Assuming for the ideal components and the switching frequency is 40 kHz.

- (i) Specify the duty cycle of the converter. (2 marks)
- (ii) Determine the capacitor size. (4 marks)
- (iii) Analyse the average inductor current. (2 marks)
- (iv) Derive and determine minimum inductor  $L_{min}$ , for Continuous Current Mode (CCM) operation. (4 marks)

(c) **Figure Q4(c)** shows a single phase full wave AC voltage controller with resistor load. If the firing angle,  $\alpha = 90^\circ$ , plot the waveform (in one period) of  $V_{sw}$ ,  $I_o$ , and  $V_o$ . (7 marks)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : SEM I / 2018 / 2019  
COURSE NAME : POWER ELECTRONICS

PROGRAMME : 3 BEV  
COURSE CODE : BEF 34503

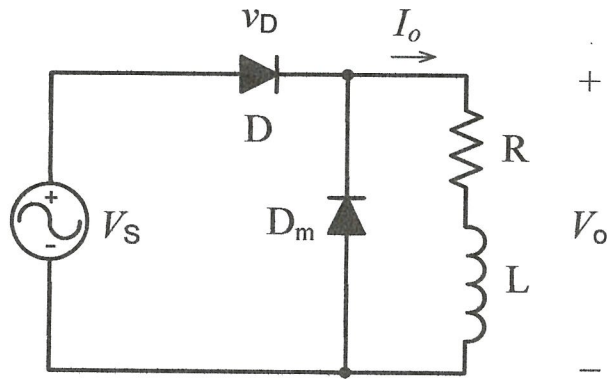


Figure Q2(a)

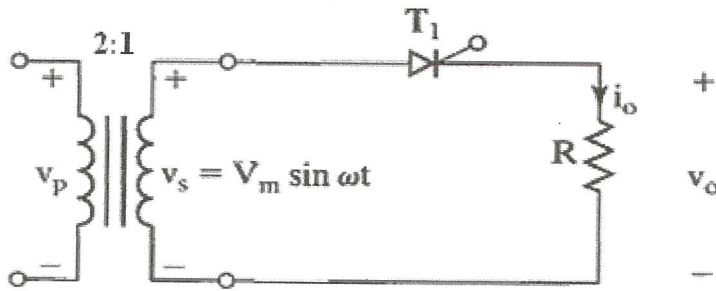



Figure Q2(b)

TERBUKA


**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I / 2018 / 2019  
 COURSE NAME : POWER ELECTRONICS


PROGRAMME : 3 BEV  
 COURSE CODE : BEF 34503

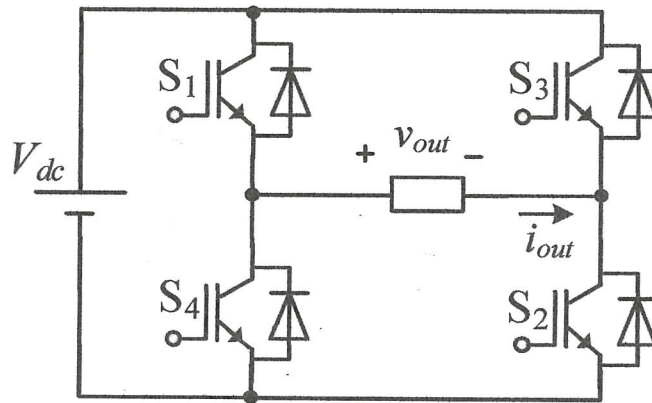

**Figure Q3**

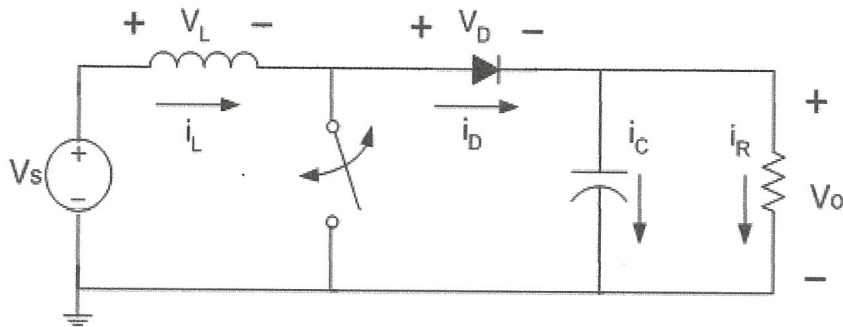

**Figure Q4(b)**

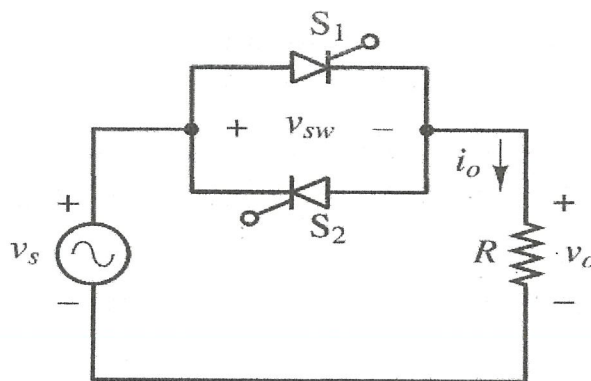

**Figure Q4(c)**

**TERBUKA**

DR. ASMARASHID BIN BUNYAN  
 Lecturer in Power Electronics  
 Faculty of Electrical Engineering  
 Universiti Teknikal Malaysia Melaka  
 76100 Durian Tunggal, Melaka

## FINAL EXAMINATION

SEMESTER/SESSION : SEM I / 2018 / 2019  
 COURSE NAME : POWER ELECTRONICS

PROGRAMME  
 COURSE CODE

: 3 BEV  
 : BEF 34503

## FORMULAE

Half-wave controlled rectifier rms voltage

$$V_{rms} = \frac{V_m}{2} \left[ \frac{1}{\pi} \left( \pi - \alpha + \frac{1}{2} \sin 2\alpha \right) \right]^{\frac{1}{2}}$$

Instantaneous output voltage

$$v_o = \sum_{n=1,3,5,\dots} \frac{4V_{DC}}{n\pi} \sin n\omega t$$

Instantaneous load current

$$i_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{DC}}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n)$$

Impedance for the  $n$ th harmonic

$$|Z| = \sqrt{R^2 + \left( n\omega L - \frac{1}{n\omega C} \right)^2}$$

TERBUKA