

CONFIDENTIAL



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2018/2019**

COURSE NAME	: POWER GENERATION, TRANSMISSION AND DISTRIBUTION
COURSE CODE	: BEF 36003
PROGRAMME CODE	: BEV
EXAMINATION DATE	: DECEMBER 2018 / JANUARY 2019
DURATION	: 3 HOURS
INSTRUCTION	: ANSWER ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF FIVE (5) PAGES

CONFIDENTIAL

TERBUKA

- Q1** (a) Explain **TWO (2)** important desirable properties which the insulators should have and list **TWO (2)** types of insulators that are commonly used. (6 marks)
- (b) The towers of height 30 m and 70 m, respectively support a transmission line conductor at water crossing. Base of the towers can be considered to be at water level. The horizontal distance between the towers is 400 m and weight of conductor is 1.5 kg/m. If the tension in the conductor is 1500 kg, analyse:
- (i) The minimum clearance of the conductor and water. (10 marks)
- (i) The clearance mid-way between the supports. (4 marks)
- (c) A 220 kV, 50 Hz, 200 km long 3-phase line has its conductors at the corners of a triangle with sides 6 m, 6 m and 12 m. The conductor radius is 1.81 cm. Determine:
- (i) The capacitance per phase per km. (3 marks)
- (ii) The capacitive reactance per phase. (1 mark)
- (iii) The charging current. (1 mark)
- Q2** (a) List **THREE (3)** transmission voltage levels in Malaysia. (3 marks)
- (b) Compare the short and medium transmission lines in terms of the range of length and the model. (6 marks)
- (c) A 220 kV, 200 MVA and 50 Hz, three-phase transmission line completely transposed for a length of 150 km has the following positive-sequence impedance and admittance:
- $$r = 0.11 \Omega/\text{km}$$
- $$x = 0.90 \Omega/\text{km}$$
- $$y = 5.0 \times 10^{-6} \text{ S}/\text{km}$$
- The voltage at the receiving end of the transmission line is 200 kV, determine:

- (i) The values of series impedance and shunt admittance of the transmission line. (2 marks)
- (ii) The value of sending end voltage if the line supplying rated voltage and rated apparent power at p.f. of 0.85 lagging. (8 marks)
- (iii) The voltage regulation of the transmission line. (2 marks)
- (iv) The efficiency of the transmission line when it is supplying rated apparent power at p.f. of 0.85 lagging. (4 marks)

- Q3** (a) Define power factor and describe the characteristic of current-voltage in capacitive circuit. Include the respective power triangle diagram and labels. (5 marks)
- (b) A water pump (single phase motor) connected to 400 V, 50 Hz supply takes 35.8 A at a power factor of 0.75 lagging.
- (i) Propose one simple approach to increase the power factor. (2 marks)
 - (ii) Sketch a simple circuit representation and the respective phasor diagram for the answer in **Q3(b)(i)**. (4 marks)
 - (iii) Determine the required capacitance in order to increase the power factor up to 0.95 lagging. (8 marks)
- (c) Highlight and discuss **THREE (3)** importance of power factor improvement to the consumers and power generating stations. (6 marks)

- Q4** (a) Describe **THREE (3)** general roles of distribution substation in power distribution network. (3 marks)
- (b) Explain **THREE (3)** types of primary distribution lines circuits. Include appropriate illustration for the respective type. (6 marks)
- (c) A 1000 m long, single phase distributor as shown in **Figure Q4(c)**, has resistance and reactance per conductor of 0.1 and 0.15 ohm respectively. At the far end point B, the voltage $V_B = 200$ V and the current is 100 A at p.f. of 0.8 lagging. At mid-point M of the distributor, a current of 100 A is tapped at p.f. of 0.6 lagging with reference to the voltage V_M at the mid-point. Analyse:
- (i) The voltage at mid-point. (7 marks)
- (ii) The sending end voltage. (6 marks)
- (iii) The phase angle between V_A and V_B . (3 marks)

END OF QUESTIONS –

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2018/2019
COURSE : POWER GENERATION,
TRANSMISSION AND
DISTRIBUTION

PROGRAMME CODE : BEV
COURSE CODE : BEF 36003

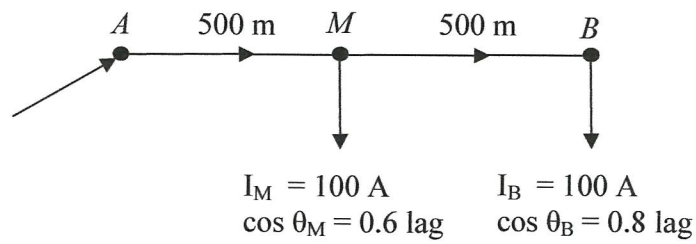


Figure Q4(c)