

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2018/2019**

COURSE NAME : RF AND MICROWAVE
ENGINEERING
COURSE CODE : BEB 40803
PROGRAMME CODE : BEJ
EXAMINATION DATE : DECEMBER 2018 / JANUARY
2019
DURATION : 3 HOURS
INSTRUCTION : ANSWER FIVE (5) QUESTIONS

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

DR. SAMSUJ HAIMI BIN DAHLAN
Fakulti Kejuruteraan Komunikasi
& Elektronik
Universiti Tun Hussein Onn Malaysia

CONFIDENTIAL
TERBUKA

CONFIDENTIAL

Q1 A transmission line is a distributed parameter network, where voltages and currents can vary in magnitude and phase over its length.

(a) Sketch and label the lumped-element equivalent circuit of a transmission line. (4 marks)

(b) Show that, for a transmission line terminated with Z_L , characteristic impedance of Z_0 and length $l = \frac{\lambda}{4}$, the input impedance Z_{in} is,

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

(4 marks)

(c) **Figure Q1(c)** shows frequency response of an antenna. At the frequency of 9.75 GHz, calculate :

(i) the reflection coefficient

(3 marks)

(ii) the signal to wave ratio

(3 marks)

(iii) the return loss, and

(3 marks)

(iv) the percentage of power transmitted

(3 marks)

Q2 (a) Show that the S-parameter for the circuit in **Figure Q2(a)** is

$$\begin{bmatrix} \frac{Z}{2Z_0+Z} & \frac{2Z_0}{2Z_0+Z} \\ \frac{2Z_0}{2Z_0+Z} & \frac{Z}{2Z_0+Z} \end{bmatrix}$$

(5 marks)

(b) Consider a two-port network as illustrated in **Figure Q2(b)**. Determine the S-Parameter of the system.

(15 marks)

CONFIDENTIAL

- Q3** Microwave and radio frequency (RF) system relied on transmission lines for low loss transmission of power at high frequency.
- a) Sketch the field pattern of the propagating fields in a coaxial cable, stripline and microstrip line. Label the fields accordingly. (6 marks)
 - b) Design a microstrip line on a 0.5 mm alumina substrate ($\epsilon_r = 9.9$, $\text{Tan } \delta = 0.001$) for a 50Ω characteristic impedance. The line is to be operated at 10 GHz range. (10 marks)
 - c) The frequency response of the microstrip line in **Q3(b)** is measured using a network analyzer. Construct the expected transmission coefficient and the reflection coefficient response if the measurement is performed from 7 GHz to 11 GHz frequency range. Label the graph accordingly. (4 marks)
- Q4**
- (a) Briefly describe the properties of filter characteristics in (i) to (iii) and sketch the corresponding frequency response. Label them clearly.
 - (i) Butterworth filter (2 marks)
 - (ii) Chebyshev filter (2 marks)
 - (iii) Bessel filter (2 marks)
 - (b) A microstrip low-pass filter with cut-off frequency of 2 GHz and 30 dB attenuation at 3.5 GHz is to be designed. The filter have Chebyshev response characteristic with 0.5 dB ripple. The filter is to be implemented on a microstrip board with a relative permittivity, $\epsilon_r = 9.9$, thickness, $h = 0.63$ mm and loss tangent, $\text{Tan } \delta = 0.001$.
 - (i) Draw the lump element prototype of the filter and determine the element values. (5 marks)
 - (ii) Using the stepped impedance technique, calculate the value of series and shunt reactance components, if the high impedance transmission line value of, $Z_{High} = 100 \Omega$ and low impedance transmission line value of $Z_{Low} = 30 \Omega$ are used to realized the filter practically. (9 marks)

TERBUKA

CONFIDENTIAL

- Q5** (a) Doppler radar can be used for the detection of moving objects and determine its velocity. A simple Doppler radar can be designed using components listed in Table 2. Draw the schematic diagram of a Doppler radar using only the component listed. (10 marks)
- (b) The parabolic reflector antenna used in **Q5(a)** is 50 cm in diameter and operates at 12.4 GHz. Calculate the far field distance of this antenna. (5 marks)
- (c) An object is detected from a distance.
- (i) Calculate the distance of the detected object if the time travel of the wave is $\Delta t = 0.1$ ms. (2 marks)
- (ii) If the object is moving with a velocity of $v_0 = 60$ km/h towards the radar, calculate the Doppler frequency shift. (3 marks)
- Q6** (a) For an amplifier, give brief description for the three types of gain below:
- (i) transducer gain (1 mark)
- (ii) power gain (1 mark)
- (iii) available gain (1 mark)
- (b) The S-parameter for HP HFET-102 GaAs FET at 2 GHz with a bias voltage $V_{gs} = 0$ are given as follows ($Z_0 = 50 \Omega$).
- $$S_{11} = 0.38 \angle -158^\circ, S_{12} = 0.11 \angle 54^\circ$$
- $$S_{21} = 3.50 \angle 80^\circ, S_{22} = 0.40 \angle -43^\circ$$
- The source impedance is $Z_s = 25 \Omega$ and the load impedance is $Z_L = 40 \Omega$.
- (i) Compute the power gain, available gain and the transducer gain. (12 marks)
- (ii) Determine the stability of this transistor. (5 marks)

- END OF QUESTION -

TERBUKA

CONFIDENTIAL

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2018/2019
COURSE NAME : RF AND MICROWAVE ENGINEERING

PROGRAMME : BEJ
COURSE CODE: BEB 40803

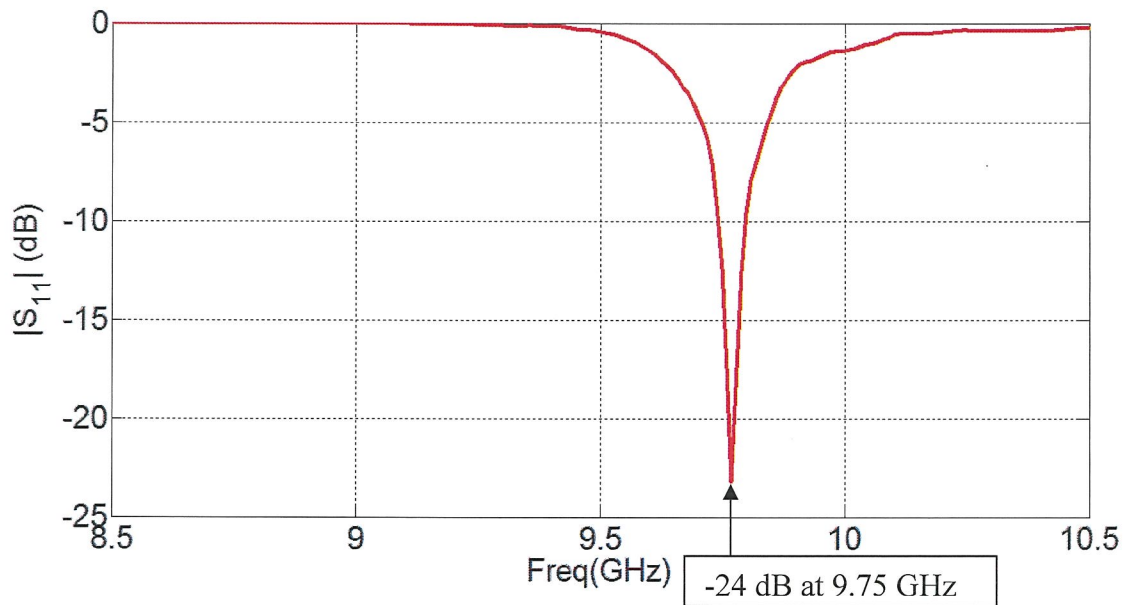


Figure Q1 (c)

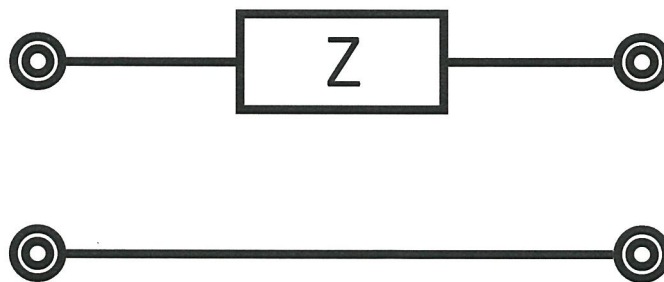


Figure Q2 (a)

TERBUKA

CONFIDENTIAL**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/2018/2019

PROGRAMME : BEJ

COURSE NAME : RF AND MICROWAVE ENGINEERING

COURSE CODE: BEB 40803

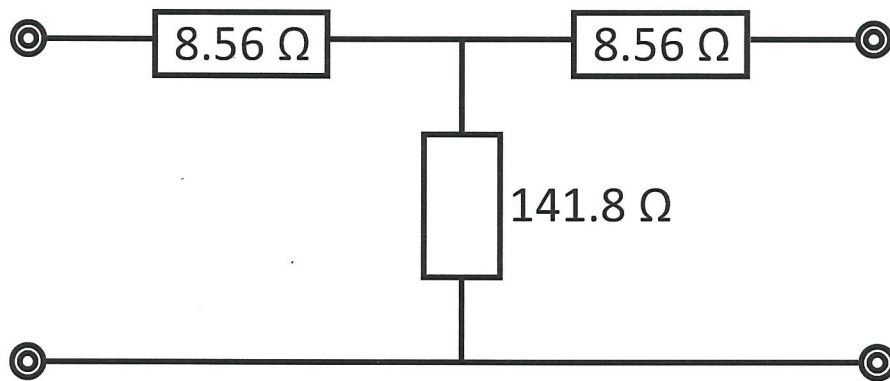


Figure Q2 (b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2018/2019
 COURSE NAME : RF AND MICROWAVE ENGINEERING

PROGRAMME : BEJ
 COURSE CODE: BEB 40803

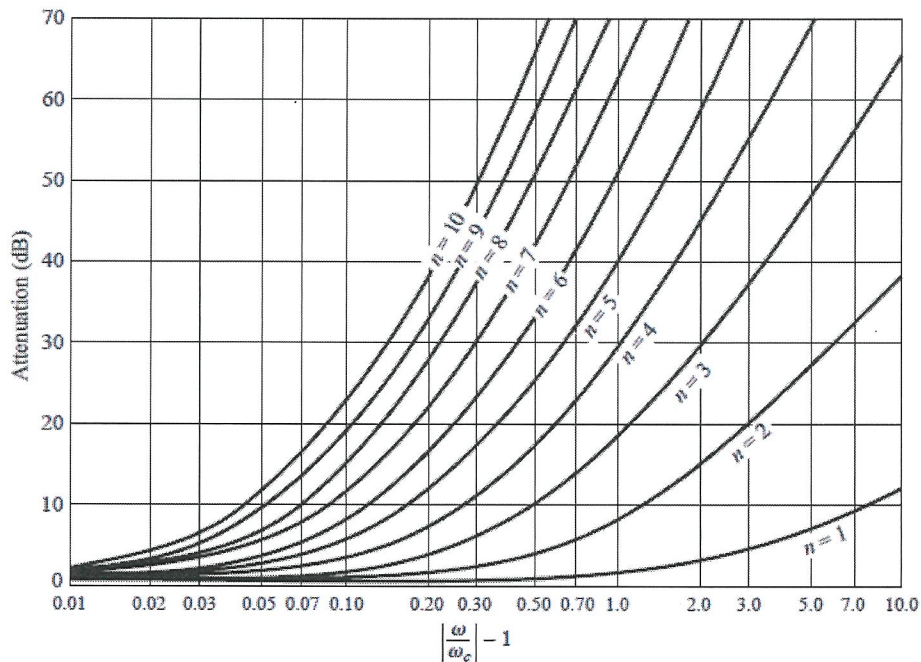


Figure Q4 (b)

TABLE 1

0.5 dB Ripple											
N	g1	g2	g3	g4	g5	g6	g7	g8	g9	g10	g11
1	0.6986	1.0000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.0000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.0000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.0000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6678	1.2690	1.7504	1.0000	
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

DR. SAMSUL HAIMI BIN DAHLAN
 Ketua Jurusan Teknik Elektronika
 Fakultas Teknik Universitas Kebangsaan Malaysia
 Kampus UI Depok



CONFIDENTIAL**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/2018/2019

PROGRAMME : BEJ

COURSE NAME : RF AND MICROWAVE ENGINEERING

COURSE CODE: BEB 40803

TABLE 2

Item	Quantity
Frequency modulator	1
Oscillator	1
Low Noise Amplifier	1
Power Amplifier	1
Splitter	1
Mixer	1
Reflector antenna	2

CONFIDENTIAL**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/2018/2019

PROGRAMME : BEJ

COURSE NAME : RF AND MICROWAVE ENGINEERING

COURSE CODE: BEB 40803

$$\varepsilon_e = \frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{2} \frac{1}{\sqrt{1 + 12d/W}}$$

$$Z_o = \begin{cases} \frac{60}{\sqrt{\varepsilon_e}} \ln \left(\frac{8d}{W} + \frac{W}{4d} \right) & \text{for } W/d \leq 1 \\ \frac{120\pi}{\sqrt{\varepsilon_e} [W/d + 1.393 + 0.667 \ln(W/d + 1.444)]} & \text{for } W/d \geq 1 \end{cases}$$

$$\frac{W}{d} = \begin{cases} \frac{8\varepsilon^A}{e^{2A} - 2} & \text{for } W/d < 2 \\ \frac{2}{\pi} \left[B - 1 - \ln(2B - 1) + \frac{\varepsilon_r - 1}{2\varepsilon_r} \left\{ \ln(B - 1) + 0.39 - \frac{0.61}{\varepsilon_r} \right\} \right] & \text{for } W/d > 2 \end{cases}$$

$$A = \frac{Z_o}{60} \sqrt{\frac{\varepsilon_r + 1}{2} + \frac{\varepsilon_r - 1}{\varepsilon_r + 1} \left(0.23 + \frac{0.11}{\varepsilon_r} \right)}$$

$$B = \frac{377\pi}{2Z_o\sqrt{\varepsilon_r}}$$

TERBUKA