



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : DIGITAL ELECTRONICS
COURSE CODE : BEJ 10603
PROGRAMME CODE : BEV/ BEJ
EXAMINATION DATE : DECEMBER 2019 / JANUARY 2020
DURATION : 3 HOURS
INSTRUCTION : 1. ANSWER ALL QUESTIONS IN THIS BOOKLET.
2. NO CALCULATOR IS ALLOWED.

TERBUKA

THIS QUESTION PAPER CONSISTS OF **FOURTEEN (14)** PAGES

Q1 (a) Describe **THREE (3)** technique to convert decimal number to binary conversion.
(3 marks)

(b) Convert a negative decimal number, **-35** in binary number, 1's and 2's complement form using 8-bit binary.

(6 marks)

TERBUKA

(c) Consider a 4-bit binary number function, $F(A B C D)$ is represented in **4-bit signed number format**.

(i) Write out the truth table for the Boolean function of F where the absolute value of F is **greater than 2**.

(6 marks)

(ii) Analyze the truth table and write out the **minimum sum-of-product (SOP)** of the Boolean function.

(5 marks)

TERBUKA

- Q2** (a) Design a circuit that counts the number of 1's present in 3 inputs A, B and C. Its output is a two-bit number which are X_1 and X_0 , representing that count in binary.
- (i) Construct the truth table for this circuit. (5 marks)
- (ii) Find the minimize logic equations for output X_1 and X_0 . Use the Karnaugh map and Boolean algebra to simplify the expressions. (5 marks)

TERBUKA

(b) Given the Boolean expression:

$$y = (a + b)(b + c)(\bar{a} + \bar{b})(\bar{b} + \bar{c})$$

(i) Construct a truth table for the output, y .

(4 marks)

TERBUKA

(ii) Derive the **minimal product-of-sum (MPOS)** for the output, y . (4 marks)

(iii) Implement the simplest Boolean expression for the output, y . (2 marks)

TERBUKA

Q3 (a) Describe the operation of the following functional combinational logic circuit. Use an appropriate diagram and a truth table to aid your explanation.

(i) Comparator.

(4 marks)

(ii) Demultiplexer.

(4 marks)

TERBUKA

- (b) System A, which has three inputs (A3, A2, A1) is designed to produce two outputs, M and N. The output M is **HIGH** whenever A1 and A2 are **HIGH**. Output N is **HIGH** when M and A3 are both **HIGH** or A1 and M are both **LOW**.

A 3 to 8 line decoder shown in **Figure Q3(b)** is used to employ this system together with the external logic gates. Show all the steps to design system A including truth table.

(6 marks)

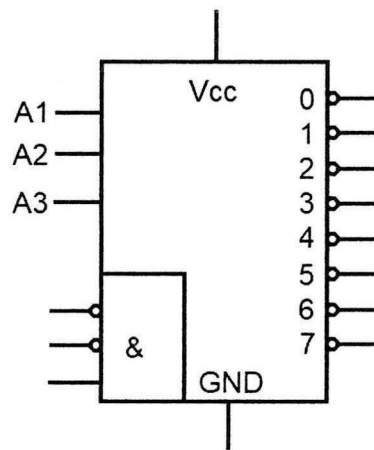


Figure Q3(b)

TERBUKA

- (c) Evaluate the output for a 4-bit compactor (74LS85) in **Figure Q3(c)** using given inputs of A0, A1, A2, A3, B0, B1, B2 and B3 below. The outputs are active-HIGH.

(6 marks)


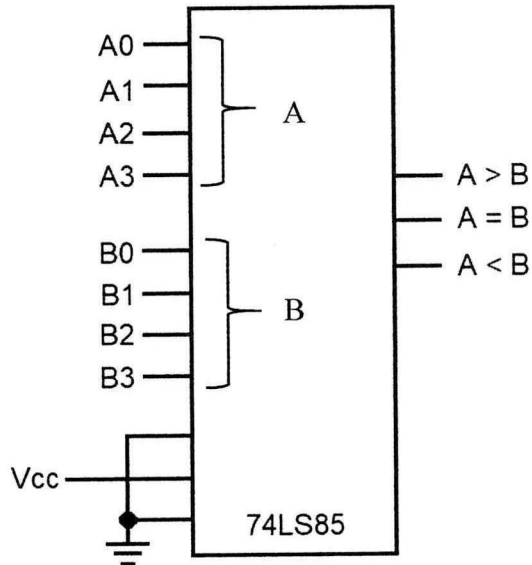


Figure Q3(c)

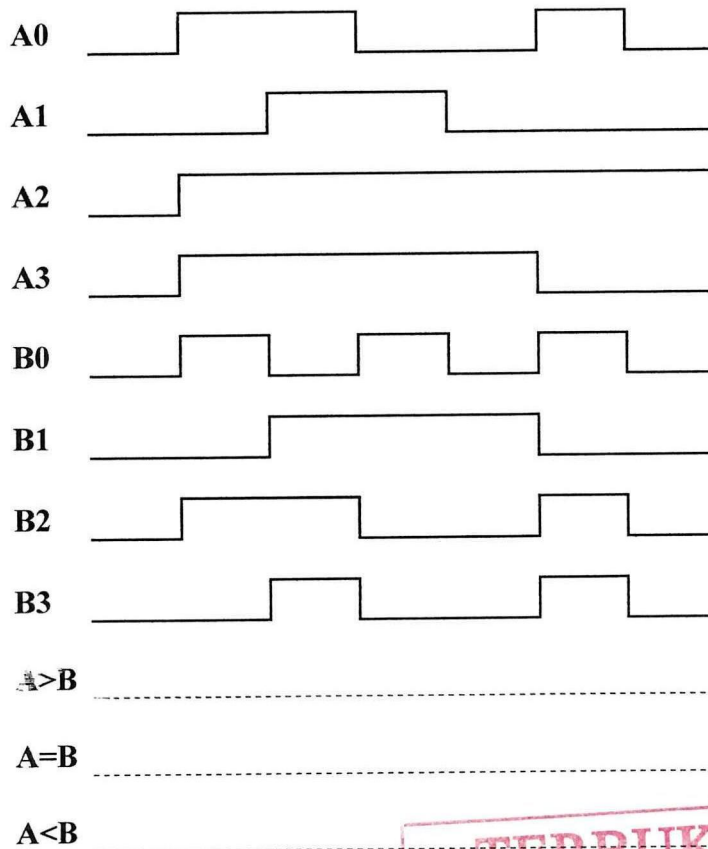

TERBUKA

- Q4 (a) Complete the missing entries (i) to (vii) in **Table Q4(a)** of flip-flop excitation values required to produce the indicated flip-flop state changes. X indicates the present state and Y is the desired next state of the flip-flop.

(7 marks)

Table Q4(a)

Present state X	Next State Y	J-K Flip flop		SC Flip flop		D Flip flop
		J	K	S	C	D
0	0	(i)	(ii)			(iii)
(iv)	0	1	1			
0	1			(v)	(vi)	
1	(vii)	1	0			

- (b) A clock generator has an output frequency of 112 kHz. The system is required to generate two frequencies, 28 kHz and 7 kHz at the outputs. Design a circuit that will generate the two output frequencies by using JK flip-flops.

(4 marks)

TERBUKA

- (c) **Figure Q4(c)(i)** shows a register and **Figure Q4(c)(ii)** shows the input waveforms (CLOCK and Data in) to the circuit.

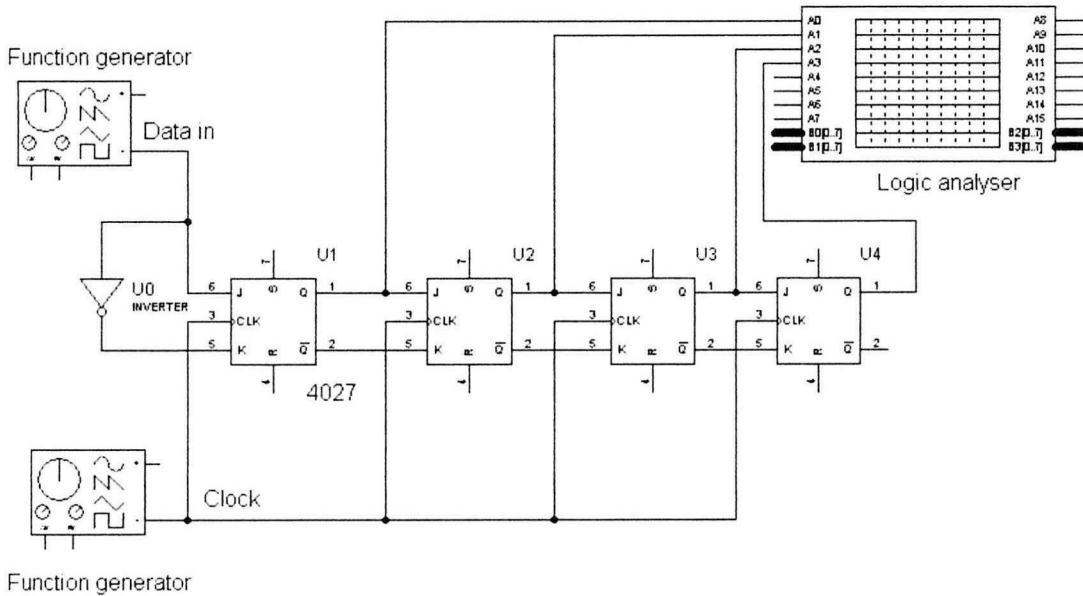


Figure Q4(c)(i)

- (i) State the type of register as shown in **Figure Q4(c)(i)**. (1 marks)
- (ii) Analyze the circuit and draw the output waveforms for Q_{U1} , Q_{U2} , Q_{U3} and Q_{U4} in **Figure Q4(c)(ii)**. (8 marks)

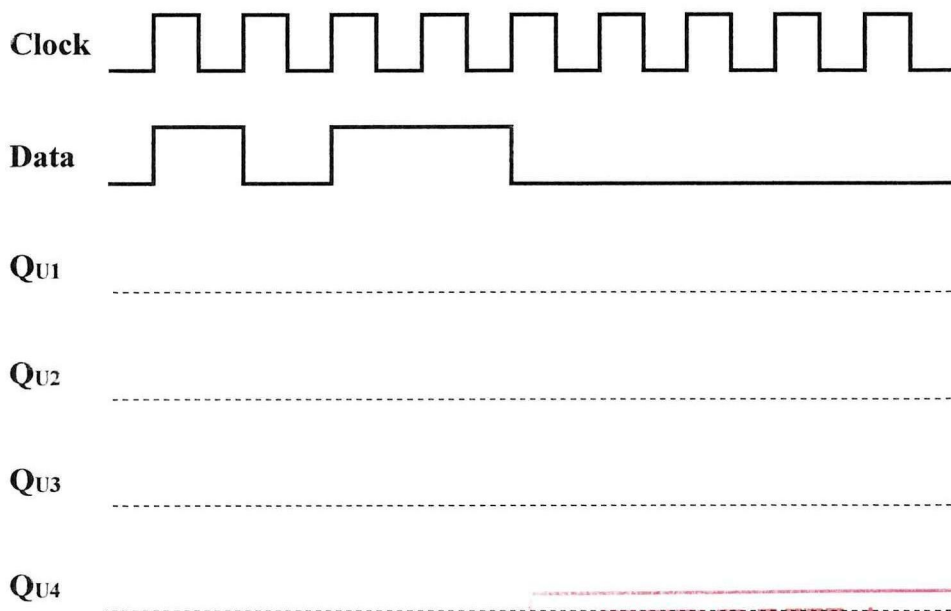


Figure Q4(c)(ii)

TERBUKA

Q5 (a) **Figure Q5(a)** shows the state transition diagram of a state machine.

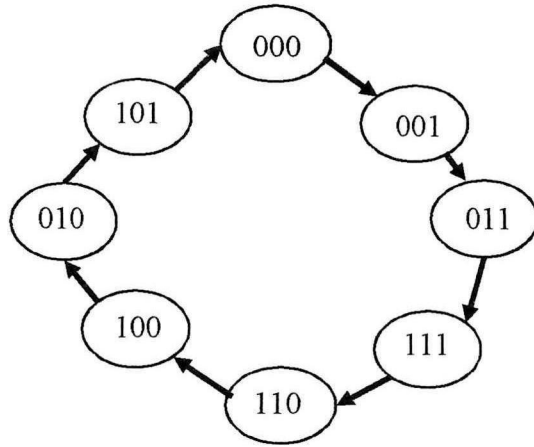


Figure Q5(a)

(i) Build the excitation table for this state machine.

(5 marks)

TERBUKA

- (ii) Find the simplest Boolean expression for the circuit using Karnaugh map.
(10 marks)

TERBUKA

- (iii) Implement the circuit diagram based on the result in Q5(a)(ii). (5 marks)

TERBUKA

- END OF QUESTIONS -