



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2019/2020**

COURSE NAME : ELECTRIC CIRCUIT II
COURSE CODE : BEJ 10403
PROGRAMME CODE : BEJ
EXAMINATION DATE : DECEMBER 2019/JANUARY 2020
DURATION : 3 HOURS
INSTRUCTION :
1. ANSWER ALL QUESTIONS
2. SHOW ALL CALCULATIONS

TERBUKA

THIS QUESTION PAPER CONSISTS OF SEVEN (7) PAGES

Q1 (a) Explain the method to store energy in capacitor. (2 marks)

(b) The voltage across a $5 \mu\text{F}$ capacitor is shown in **Figure Q1(b)**.

(i) Draw the current waveform through the capacitor. (6 marks)

(ii) Calculate the energy is stored in the capacitor at $t = 4 \text{ ms}$. (2 marks)

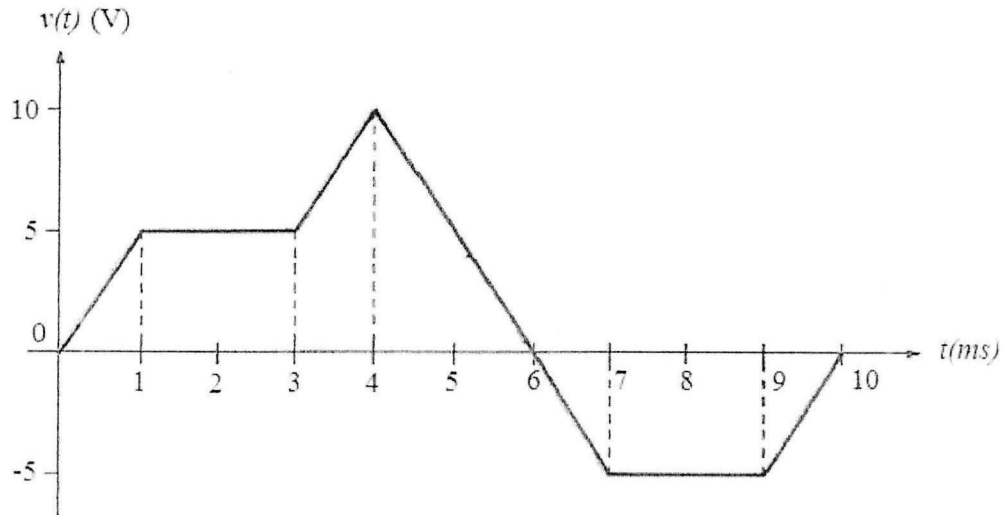


Figure Q1 (b)

(c) The circuit in **Figure Q1(c)** has reached steady state at $t = 0^-$ (switch at position a). At $t = 0 \text{ s}$, the switch is moved to position b.

(i) Determine the current across inductor, $i(t)$ for $t > 0 \text{ s}$. (6 marks)

(ii) Sketch the complete current response, $i(t)$ from initial value to final value. (4 marks)

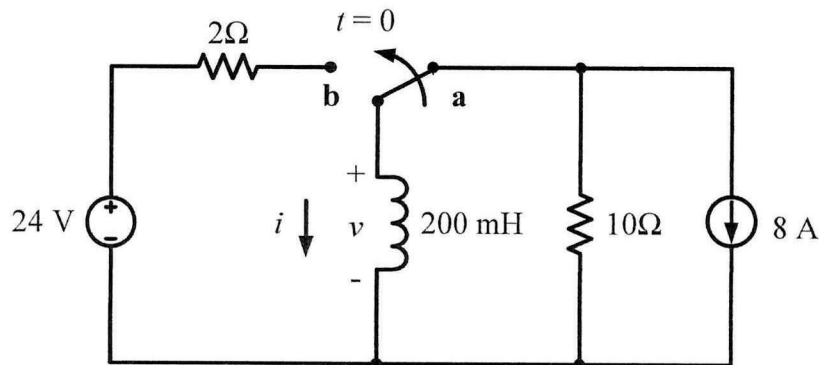


Figure Q1(c)

TERBUKA
2

Q2 (a) The switch in **Figure Q2(a)** was opened for a long time but closed at $t = 0$ s. Determine the following:

(i) $i(0^+)$ and $v(0^+)$ (3 marks)

(ii) $\frac{di(0^+)}{dt}$ and $\frac{dv(0^+)}{dt}$ (4 marks)

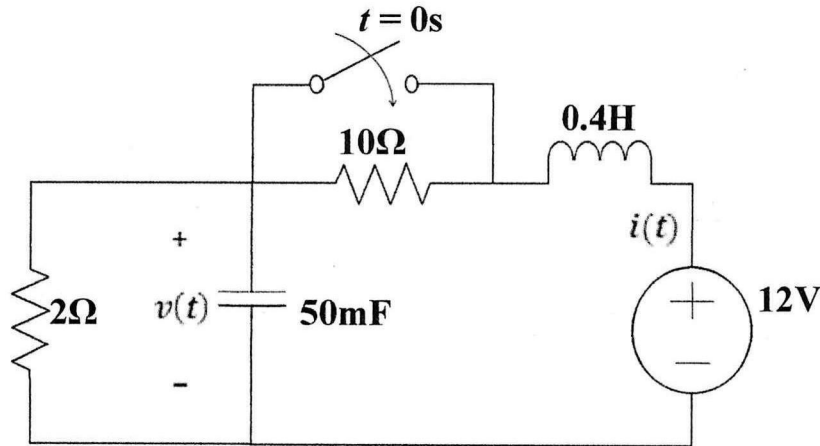


Figure Q2(a)

(b) The switch in **Figure Q2(b)** has been opened for a long time, and it is closed at $t = 0$ s.

(i) Determine the roots of the characteristic equation and the type of damping response. (5 marks)

(ii) Find current response, $i(t)$ for $t > 0$ s. (8 marks)

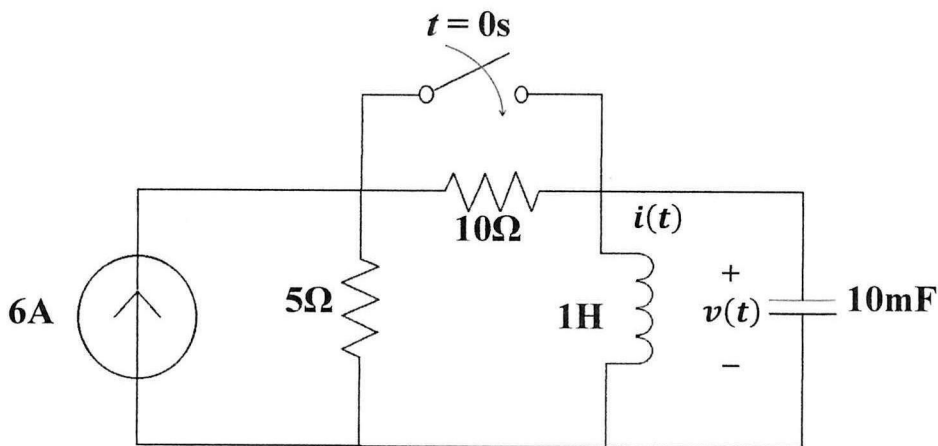


Figure Q2(b) TERBUKA

Q3 (a) Source transformation methods are used for circuit simplification to modify the complex circuits by transforming independent current sources into independent voltage sources and vice-versa.

(i) Illustrate the conversion of voltage source into current source using the source transformation method.

(3 marks)

(ii) In **Figure Q3(a)**, given that the voltage across the resistor $10\ \Omega$, $V_o = 5.519\angle -28^\circ\text{ V}$. Find the impedance, Z .

(8 marks)

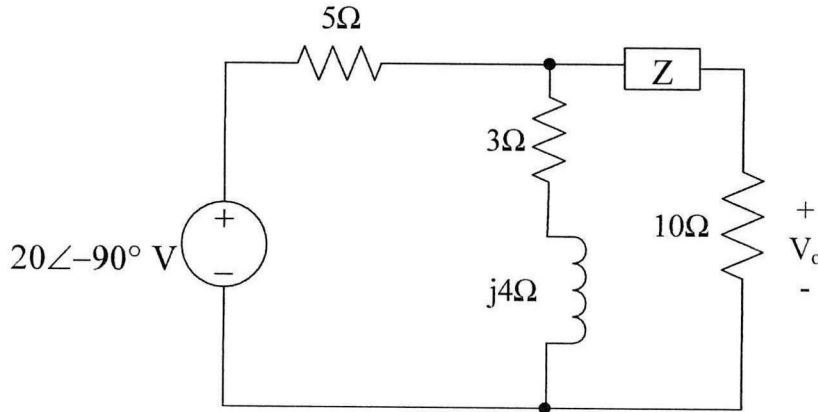


Figure Q3(a)

(b) For the circuit in **Figure Q3(b)**,

(i) draw the Thevenin equivalent circuit at terminal a-b.

(1 mark)

(ii) determine the Thevenin Voltage, V_{TH} .

(4 marks)

(iii) determine the Thevenin Impedance, Z_{TH} .

(4 marks)

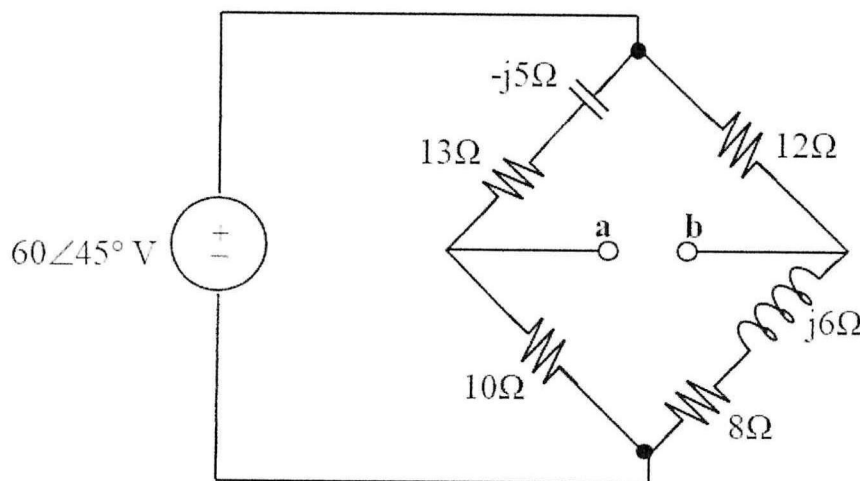


Figure Q3(b)

TERBUKA

Q4 (a) Power is the most important quantity in electric utilities, electronic, and communication systems. Such systems involve transmission of power from one point to another. Given a circuit shown in **Figure Q4(a)**,

- (i) describe the technique to achieve maximum power transfer. (2 marks)
- (ii) determine the impedance R_L for maximum average power transfer. (4 marks)
- (iii) find the value of the maximum average power absorbed by the load. (4 marks)

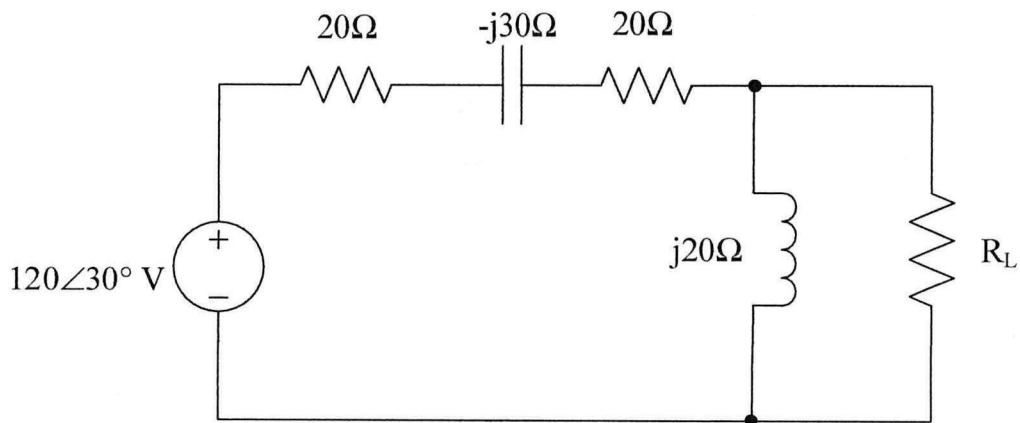


Figure Q4(a)

(b) A small industrial plant with a supply of 1000 V at 60 Hz has a 20 kVA inductive load due to a bank of induction motors. The induction motors have a lagging power factor, pf of 0.7.

- (i) Determine the capacitive element, X_C required to raise the power factor, pf to 0.95. (5 marks)
- (ii) Based on part **Q4(b)(i)**, compare the levels of current drawn from the supply at $pf = 0.95$ and $pf = 0.7$. (3 marks)
- (iii) Sketch the power triangle. (2 marks)

TERBUKA

Q5 (a) Differentiate between one port network and two port network by defining and drawing those two networks respectively.

(4 marks)

(b) For **Figure Q5(b)**, obtain the impedance parameter of the circuit.

(8 marks)

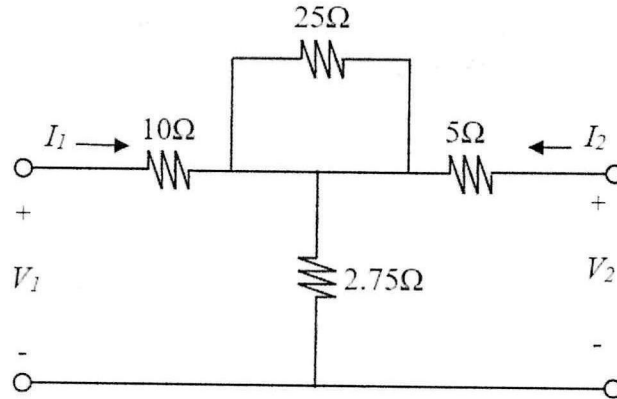


Figure Q5(b)

(c) By using **Figure Q5(c)**, calculate the admittance parameter of the circuit.

(8 marks)

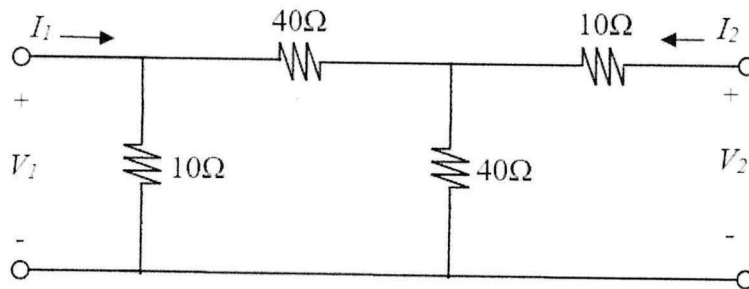


Figure Q5(c)

~END OF QUESTIONS~

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2019/2020
 COURSE NAME : ELECTRIC CIRCUIT II

PROGRAMME CODE : BEJ
 COURSE CODE : BEJ 10403

APPENDIX A

TRIGONOMETRIC EQUATIONS

$$\sin(-x) = -\sin(x)$$

$$\cos(-x) = \cos(x)$$

$$\tan(-x) = -\tan(x)$$

$$\sec x = \frac{1}{\cos x}, \quad \csc x = \frac{1}{\sin x}$$

$$\tan x = \frac{\sin x}{\cos x}, \quad \cot x = \frac{1}{\tan x}$$

$$\sin 2x + \cos 2x = 1$$

$$\sin(2x) = 2 \sin x \cos x$$

$$\cos(2x) = \cos^2 x - \sin^2 x$$

$$\cos(2x) = 2 \cos^2 x - 1 = 1 - 2 \sin^2 x$$

$$\sin(x \pm 90^\circ) = \pm \cos x$$

$$\cos(x \pm 90^\circ) = \mp \sin x$$

$$\sin(x \pm 180^\circ) = \mp \sin x$$

$$\cos(x \pm 180^\circ) = \mp \cos x$$

$$\cos^2 x + \sin^2 x = 1$$

$$\sin(x \pm y) = \sin x \cos y \pm \cos x \sin y$$

$$\cos(x \pm y) = \cos x \cos y \mp \sin x \sin y$$

$$\tan(x \pm y) = \frac{\tan x \pm \tan y}{1 \mp \tan x \tan y}$$

$$2 \sin x \sin y = \cos(x - y) - \cos(x + y)$$

$$2 \sin x \cos y = \sin(x + y) + \sin(x - y)$$

$$2 \cos x \cos y = \cos(x + y) + \cos(x - y)$$

$$\cos x \cos y = \frac{1}{2} [\cos(x + y) + \cos(x - y)]$$

TERBUKA