

**CONFIDENTIAL**



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2019/2020**

COURSE NAME : ELECTRONIC CIRCUIT  
ANALYSIS AND DESIGN  
COURSE CODE : BEL 30403  
PROGRAMME CODE : BEJ  
EXAMINATION DATE : DECEMBER 2019/JANUARY 2020  
DURATION : 3 HOURS  
INSTRUCTION : ANSWER ALL QUESTIONS

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **TWELVE (12)** PAGES

**CONFIDENTIAL**

- Q1** (a) The circuit in **Figure Q1(a)** is used to drive an LED with a voltage source. The circuit can also be thought of as a current amplifier with a proper design where  $I_D > I_I$ .
- (i) Based on the circuit given, derive the expression for  $I_D$  in terms of  $I_I$  and the resistors. (7 marks)
- (ii) Design the circuit to have  $I_D = 8$  mA, and  $I_I = 1.2$  mA for  $V_I = 7$  V. Use  $R_F = 56$  k $\Omega$ . (4 marks)
- (b) A Schmitt Trigger circuit is shown in **Figure Q1(b)**.
- (i) Determine the upper threshold voltage,  $V_{UT}$ , and lower threshold voltage,  $V_{LT}$ , of the circuit. (4 marks)
- (ii) Sketch the output waveform if the input waveform  $V_{in}$  is as shown in **Figure Q1(b)(ii)**. Label clearly the output waveform. (5 marks)
- Q2** (a) (i) Design an active filter using non-inverting amplifier that will produce a frequency response as shown in **Figure Q2(a)**. The bandwidth of the filter is 30 kHz. Use a capacitor value of 10 nF. (9 marks)
- (ii) Draw the circuit and clearly label it. (5 marks)
- (b) Derive the transfer function of the filter in **Q2(b)**. (6 marks)

TERBUKA

**Q3** (a) **Figure Q3(a)** is a block diagram of an amplifier (dotted box) utilizing a negative feedback. For this figure:

- (i) Determine the type of the amplifier and the feedback topology used. (2 marks)
- (ii) Derive the relationship between the output impedance without feedback ( $Z_O$ ) and the output impedance with feedback ( $Z_{OF}$ ). (8 marks)
- (iii) Discuss how the negative feedback can improved the output impedance of the amplifier. (2 marks)

(b) An amplifier system without feedback has the following specifications:

*Open loop gain: 120*  
*Input impedance: 60kΩ*  
*Output impedance: 3kΩ*

- (i) If the amplifier system employs a negative feedback and the close loop gain is 9.2, calculate the with system feedback factor,  $\beta$ . (2 marks)
- (ii) Suppose the negative feedback topology used for the amplifier system in **Q3(b)(i)** is a current shunt feedback, determine the amplifier, input impedance and output impedance of the amplifier with feedback. (6 marks)

**Q4** (a) Explain a Barkhusen criteria that must be fulfilled by an oscillator. (4 marks)

(b) Refer to the circuit shown in **Figure Q4(b)**.

- (i) Calculate the period, frequency of oscillation and duty cycle for the output waveform ( $V_O$ ). (6 marks)
- (ii) Draw and clearly label the output waveform ( $V_O$ ). (4 marks)

(c) Design the oscillator shown in **Figure Q4(c)** by finding the value of the capacitors  $C_D$  and  $C_F$  to achieve a gain of 20 and oscillating frequency of 20 Hz. Assume the inductor  $L = 10 \text{ mH}$ . (6 marks)

**TERBUKA** (6 marks)

- Q5** (a) A centre-tapped rectifier with transformer coupled is supplied by  $200 \sin \omega t$  V input voltage. The turn ratio of the transformer used is 4:1. The diodes used are silicon IN4001 and connected to a load resistor of  $100 \Omega$  at the output.
- (i) Determine the voltage at secondary winding parallel with primary winding and the dc voltage across the load resistor.  
(4 marks)
- (ii) A capacitor filter is connected to the circuit in **Q5(a)(i)** to eliminate the fluctuations in the output voltage of the centre-tapped rectifier. Draw the new circuit from the input section at the primary up until the load resistor. Sketch and label the ripple of the output voltage and show clearly the dc voltage level. Determine the values if  $f = 120$  Hz and capacitor of  $1000 \mu\text{F}$  is used. Show all calculations.  
(8 marks)
- (iii) Find the ripple factor for the circuit in **Q5(a)(ii)**.  
(3 marks)
- (b) For the circuit in **Figure Q5(b)**, calculate the approximate values of output voltage  $V_O$ , input current  $I_{R2}$ , load current  $I_L$  and collector current  $I_{SH}$ . Given:  $R_2 = 10\Omega$ ,  $V_Z = 6.8\text{V}$ ,  $R_3 = 2.5 \text{ k}\Omega$ ,  $R_4 = 7.5 \text{ k}\Omega$  and  $R_L = 50 \Omega$ .  
(5 marks)

– END OF QUESTIONS –

TERBUKA

**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/2019/2020  
 COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
 AND DESIGN

PROGRAMME CODE : BEJ  
 COURSE CODE : BEL 30403

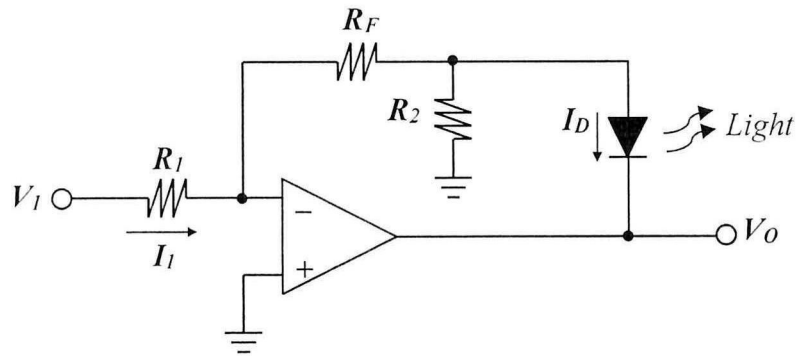


Figure Q1(a)

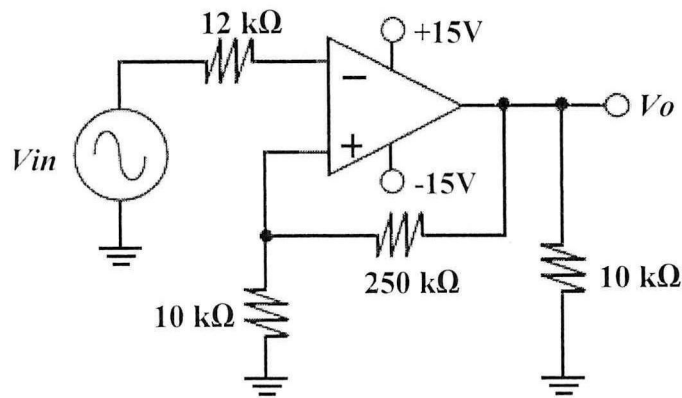


Figure Q1(b)

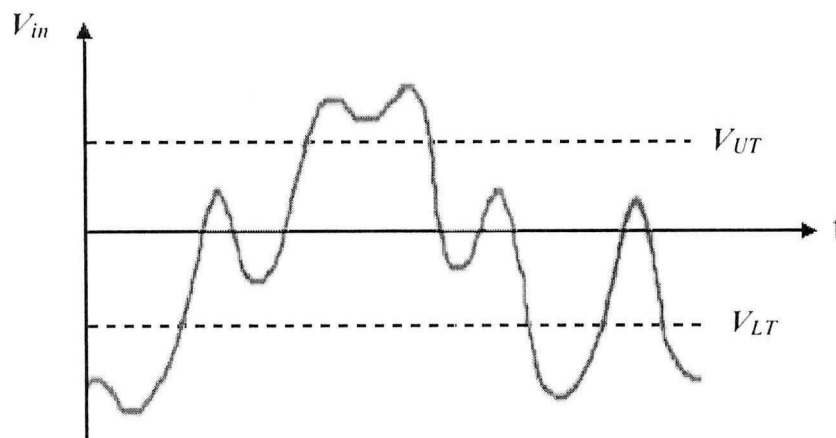


Figure Q1(b)(ii)

**TERBUKA**



FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2019/2020  
COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
AND DESIGN

PROGRAMME CODE : BEJ  
COURSE CODE : BEL 30403

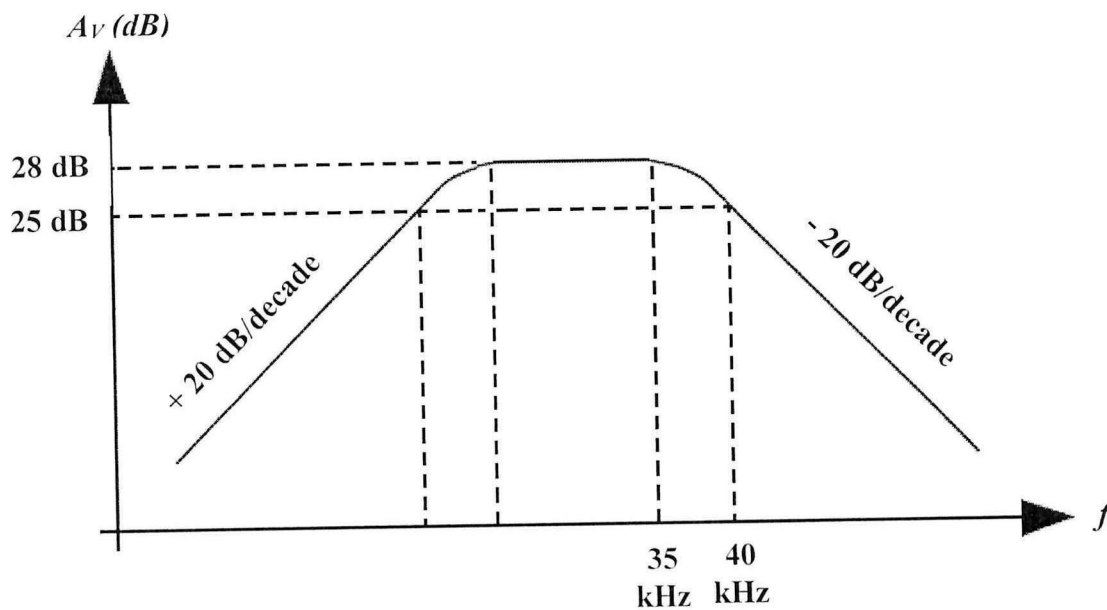


Figure Q2(a)

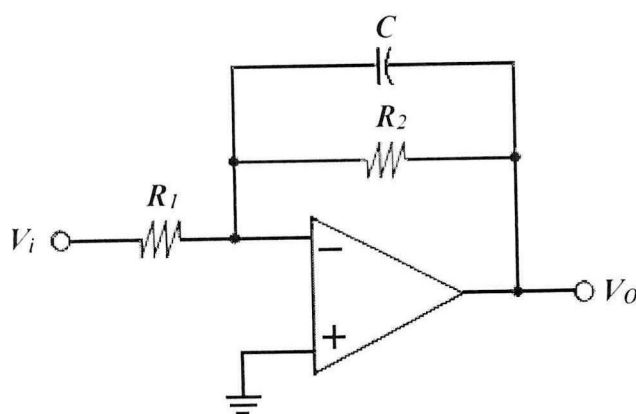


Figure Q2(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : SEM I/2019/2020

PROGRAMME CODE : BEJ

COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
AND DESIGN

COURSE CODE : BEL 30403

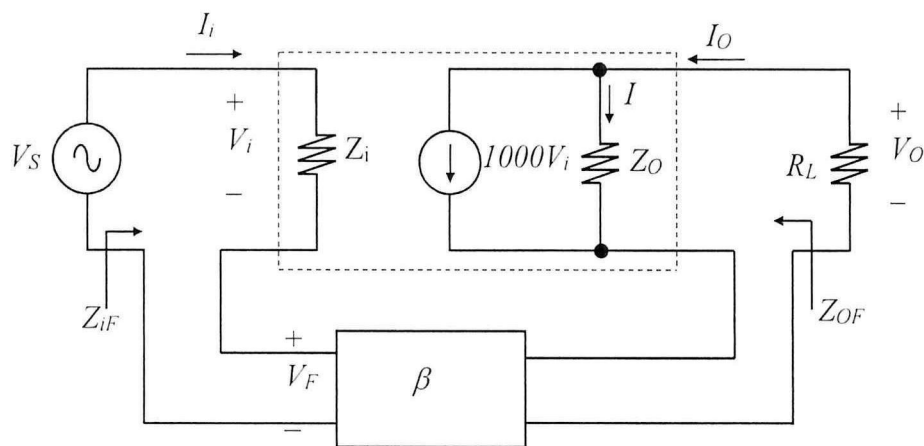


Figure Q3(a)

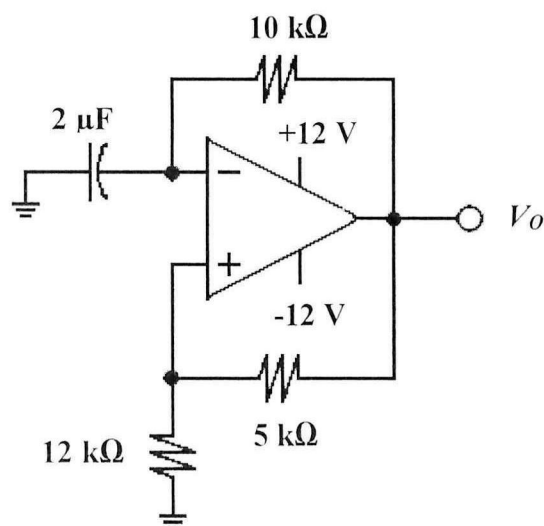


Figure Q4(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION : SEM 1/2019/2020  
COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
AND DESIGN

PROGRAMME CODE : BEJ  
COURSE CODE : BEL 30403

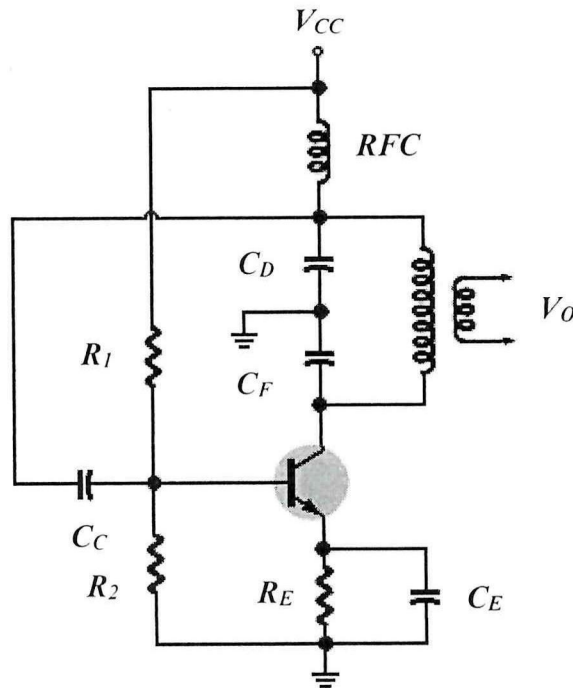


Figure Q4(c)

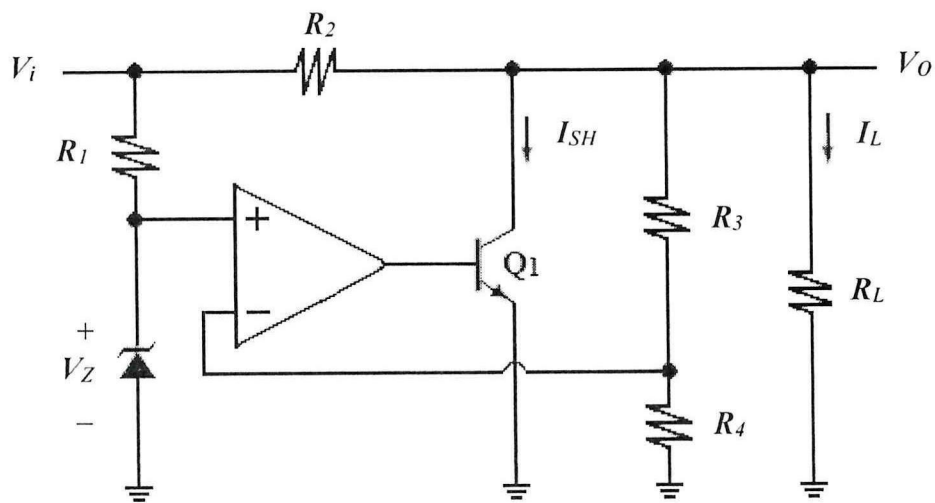


Figure Q5(b)

TERBUKA



<b>FINAL EXAMINATION</b>	
SEMESTER/SESSION : SEM I/2019/2020	PROGRAMME CODE : BEJ
COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS AND DESIGN	COURSE CODE : BEL 30403

**Table 1 : List of formula**

Inverting Amplifier	$A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$
Non-Inverting Amplifier	$A_v = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_1}$
Inverting Summing Amplifier	$V_o = -\left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$
Non-Inverting Summing Amplifier	$V_o = \left( 1 + \frac{R_f}{R_1} \right) \left( \frac{R_B}{R_A + R_B} V_A + \frac{R_A}{R_A + R_B} V_B \right)$
Subtracting Amplifier	$V_o = \left( 1 + \frac{R_f}{R_1} \right) \left( \frac{R_3}{R_2 + R_3} V_2 - \frac{R_f}{R_1 + R_f} V_1 \right)$
Instrumentation Amplifier	$A_v = A_1 A_2 = \frac{v_o}{v_m} = \left( 1 + \frac{2R}{R_x} \right) \left( \frac{R_4}{R_3} \right)$
Integrator	$V_o(t) = -\frac{1}{RC} \int_{t_0}^t V_i(t) dt + V_o(t_0)$
Differentiator	$V_o(t) = -RC \frac{dV_i(t)}{dt}$
Schmitt Trigger	$V_{UTP \text{ or } LTP} = \frac{R_2}{R_1 + R_2} (\pm V_{out(max)}) + \frac{R_1}{R_1 + R_2} (V_{REF})$
Cut-off frequency for a filter	$f_c = \frac{1}{2\pi RC}$
1 <sup>st</sup> order Low Pass Filter	$A_v(s) = \frac{V_o}{V_i} = \left( 1 + \frac{R_f}{R_1} \right) \left( \frac{1}{1 + sRC} \right)$
2 <sup>nd</sup> order Low pass filter	$A_v(s) = \frac{V_o}{V_i}(s) = \frac{A_{1\omega}}{(RCs)^2 + (3 - A_{1\omega})RCs + 1}$
1 <sup>st</sup> order High Pass Filter	$A_v(s) = \frac{V_o}{V_i} = \left( 1 + \frac{R_f}{R_1} \right) \left( \frac{1}{1 + \frac{1}{sRC}} \right)$

TERBUKA

**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/2019/2020

PROGRAMME CODE : BEJ

COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
AND DESIGN

COURSE CODE : BEL 30403

**Table 1 : List of formula (cont.)**

2 <sup>nd</sup> order High Pass Filter	$A_v(s) = \frac{V_o}{V_i}(s) = \frac{A_{vO}}{(sRC)^2 + \frac{3-A_{vO}}{sRC} + 1}$
Negative feedback – Gain	$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$
Positive feedback – Gain	$A_f = \frac{A}{1 - \beta A}$
Phase shift oscillator	$\beta = \frac{V_f}{V_o} = \frac{1}{\left(1 - \frac{5}{\omega^2 R^2 C^2}\right) + j\left(\frac{1}{\omega^3 R^3 C^3} - \frac{6}{\omega RC}\right)}$ or $\beta = \frac{V_f}{V_o} = \frac{1}{\left(1 - 5\omega^2 R^2 C^2\right) + j\left(6\omega RC - \omega^3 R^3 C^3\right)}$ $f_o = \frac{1}{2\pi RC\sqrt{6}} \quad \text{or} \quad f_o = \frac{\sqrt{6}}{2\pi RC}$
Wien bridge oscillator	$f_o = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$
Colpitts Oscillator	$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$
Hartley Oscillator	$f_o = \frac{1}{2\pi\sqrt{CL_{eq}}} \quad L_{eq} = L_1 + L_2$
UJT relaxation oscillator	$f_o = \frac{1}{R_f C_f \ln[1(1-\eta)]}$
Triangular-wave Oscillator	$f = \frac{1}{4R_1 C} \frac{R_2}{R_3}$

**TERBUKA**

**FINAL EXAMINATION**

SEMESTER/SESSION : SEM 1/2019/2020  
 COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
 AND DESIGN

PROGRAMME CODE : BEJ  
 COURSE CODE : BEL 30403

**Table 1 : List of formula (cont.)**

Square-wave Oscillator	$f = \frac{1}{T} = \frac{1}{2RC \ln \left( \frac{1+\beta}{1-\beta} \right)} \quad \beta = \frac{R_3}{R_3 + R_2}$
Capacitor voltage	$v_c(t) = v_c(0) + (v_c(\infty) - v_c(0)) \left( 1 - e^{-t/\tau} \right)$ $= v_c(\infty) + (v_c(0) - v_c(\infty)) e^{-t/\tau}$
Astable Multivibrator	$T_m = t_1 = \tau_2 \ln 2 = 0.693(R_1 + R_2)C_1$ $T_s = t_2 = \tau_2 \ln 2 = 0.693R_2C_1$ $T = T_m + T_s$ $f = \frac{1.44}{(R_1 + 2R_2)C_1}$ $D = \frac{T_m}{T_m + T_s} \times 100\% = \frac{R_1 + R_2}{R_1 + 2R_2} \times 100\%$
Monostable Multivibrator	$T = 1.1 R_1 C_1$
Ripple Factor	$\% r = \frac{\text{ripple voltage (rms)}}{\text{dc voltage}} = \frac{V_{r(rms)}}{V_{dc}} \times 100$
Half-wave rectifier with a filter	$V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}} \approx \frac{V_{o(p)}}{2\sqrt{3} f C R_L}$ $V_{o(DC)} = V_{o(p)} - \frac{V_{r(p-p)}}{2} \quad V_{r(p-p)} \approx \frac{V_{o(p)}}{f C R_L} = \frac{I_{o(DC)}}{f C}$ $r = \frac{V_{r(rms)}}{V_{DC}} \approx \frac{1}{2\sqrt{3} f C R_L} \quad I_{o(DC)} = \frac{V_{o(DC)}}{R_L} \approx \frac{V_{o(p)}}{R_L}$

**TERBUKA**

**CONFIDENTIAL**

**FINAL EXAMINATION**

SEMESTER/SESSION : SEM I/2019/2020

PROGRAMME CODE : BEJ

COURSE NAME : ELECTRONIC CIRCUIT ANALYSIS  
AND DESIGN

COURSE CODE : BEL 30403

**Table 1 : List of formula (cont.)**

<p>Full-wave rectifier with a filter</p>	$V_{r(rms)} = \frac{V_{r(p-p)}}{2\sqrt{3}} \approx \frac{V_{o(p)}}{4\sqrt{3}fCR_L} = \frac{I_{o(DC)}}{4\sqrt{3}fC}$ $V_{o(DC)} = V_{o(p)} - \frac{V_{r(p-p)}}{2}$ $V_{r(p-p)} = \frac{I_{o(DC)}}{2fC} \approx \frac{V_{o(p)}}{2fCR_L}$ $r = \frac{V_{r(rms)}}{V_{DC}} \approx \frac{1}{4\sqrt{3}fCR_L} \qquad I_{o(DC)} = \frac{V_{o(DC)}}{R_L} \approx \frac{V_{o(p)}}{R_L}$
<p>Rectifier with Additional RC filter</p>	$V'_{r(rms)} \approx \frac{X_C}{R} V_{r(rms)}$
<p>Inductor Filter</p>	$r = \frac{R_L}{3\sqrt{2}\omega L}$
<p>Shunt regulator</p>	$V_o \cong V_B \left( \frac{R_1 + R_2}{R_2} \right) \qquad V_B = V_Z + V_{BE}$ $V_o \cong \left( \frac{R_1 + R_2}{R_2} \right) (V_Z)$
<p>Series regulator</p>	$V_o = \frac{R_1 + R_2}{R_1} (V_Z + V_{BE}) \qquad V_o = V_Z \left( \frac{R_1 + R_2}{R_1} \right)$
<p>Adjustable IC regulator</p>	$V_o = V_{ref} \left( 1 + \frac{R_2}{R_1} \right) + I_{adj} R_2$

**TERBUKA**