



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE NAME : ELECTRICAL AND ELECTRONIC
TECHNOLOGY

COURSE CODE : BNJ10903

PROGRAMME : 1BNH/ 1BNK

EXAMINATION DATE : JUNE 2013

DURATION : 3 HOURS

INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY
FROM SIX (6) QUESTIONS PROVIDED

THIS QUESTION PAPER CONSISTS OF ELEVEN (11) PAGES

- Q1**
- (a) Draw the symbolic representation of the dependent voltage source and independent current source. (1 mark)
- (b) What is the difference between active and passive elements? (1 mark)
- (c) A 1.2kW electric heater has a resistance of 6Ω .
- (i) How much current does it draw? (3 marks)
- (ii) Determine the total energy used for 45 minutes heater operation. (3 marks)
- (d) (i) When the voltage across a resistor is 120V, the current through it is 2.5mA. Calculate its conductance. (2 marks)
- (ii) The voltage across a $5k\Omega$ resistor is 16V. Find the current through the resistor. (2 marks)
- (e) A 20V source is applied to a resistor with colour bands brown, black, red, and silver. Calculate the minimum and maximum currents based on the tolerance of the resistor. (3 marks)
- (f) Two electric bulbs are connected in series across a 24V battery. The specification of the bulbs are as follows:
– Bulb 1: 24V, 10W,
– Bulb 2: 24V, 4W.
By drawing the circuit and making calculation on the power dissipated by each bulb, determine which bulb will glow brighter. (10 marks)

- Q2** (a) Consider the circuit of **Figure Q2(a)**.
- (i) Determine the total circuit resistance, R_T . (3 marks)
- (ii) Determine the current I_T through the voltage sources. (2 marks)
- (iii) Solve for the currents I_1 and I_2 . (4 marks)
- (iv) Calculate the voltage V_{ab} . (2 marks)
- (b) Determine the voltage across each of the resistors in the circuit shown in **Figure Q2(b)**. (3 marks)
- (c) Derive the Thevenin equivalent circuits for the circuit in **Figure Q2(c)**. (11 marks)
- Q3** (a) **Figure Q3(a)** shows the basic structure of a parallel plate capacitor. Given the area of the plates is 0.6cm^2 and the distance between the plates is 4mm . Determine the relative permittivity of the dielectric material in order to have 10pF capacitor if the permittivity of vacuum is $8.85 \times 10^{-12}\text{F/m}$. (4 marks)
- (b) Determine the equivalent capacitance for the circuit in **Figure Q3(b)**. (5 marks)
- (c) Calculate the inductance of 3cm length solenoid without a core with 200 turns and 2.5cm^2 cross sectional area. Given the permeability of air is $1.257 \times 10^{-6}\text{H/m}$. (3 marks)

- (d) Determine the equivalent inductance for the circuit in **Figure Q3(d)**.
(7 marks)
- (e) If the flux density in a certain magnetic material is 2.3T and the area of the material is 300mm^2 , calculate is the flux through the material?
(2 marks)
- (f) Draw the construction of a permanent-magnet speaker and explain its operation.
(4 marks)

- Q4**
- (a) (i) Define frequency and state its unit.
(3 marks)
- (ii) Which sine wave in **Figure Q4(a)(ii)** has the higher frequency? Determine the frequency and the period of both waveforms.
(6 marks)
- (b) The output waveform A of an AC system is as shown in **Figure Q4(b)** with the V_{RMS} is 150V. Calculate:
- (i) Amplitude (V_{max}).
- (ii) The angular frequency, ω .
- (iii) The phase angle.
- (iv) Considering waveform A as the reference, write the equation of waveform B in the form of $v = V_m \sin(\omega t \pm \phi)$.
(8 marks)
- (c) The current in an a.c. circuit at any time t seconds is given by: $I = 120\sin(100\pi t + 0.36)$ A. Find:
- (i) The peak value, the periodic time, the frequency and phase angle relative to $120\sin 100\pi t$.
- (ii) The value of the current when $t = 0$.
- (iii) The value of the current when $t = 8\text{ms}$.
- (iv) The time when the current first reaches 60A.
(8 marks)

- Q5**
- (a) (i) Sketch the symbol of diode and its basic structure. (3 marks)
- (ii) Sketch the connection of a diode to a DC source when it is in reverse biased state. (2 marks)
- (b) (i) Two common types of relays are Normally Closed (NC) and Normally Opened (NO). Describe briefly about the two relays using a relevant diagram. (5 marks)
- (ii) Explain the function of rectifier and filter in the block diagram of DC power supply system as illustrated in **Figure Q5(b)(ii)**. (5 marks)
- (c) A 5kVA single-phase transformer has a turns ratio of 10:1 and is fed from a 2.5kV supply. By neglecting losses, determine:
- (i) The full-load secondary current. (5 marks)
- (ii) The minimum load resistance which can be connected across the secondary winding to give full load kVA. (3 marks)
- (iii) The primary current at full load kVA. (2 marks)
- Q6**
- (a) (i) Write the Boolean expression and the truth table for the logic diagrams in **FigureQ6(a)(i)**. (6 marks)
- (ii) Draw a logic diagram circuit for the Boolean expression $\bar{A} \cdot \bar{B} + A \cdot B = Y$. Use inverters, AND gates and OR gates. (4 marks)

- (b) The truth table in **Table Q6(b)**, shows the operation of the four inputs of a logic circuit and its resulting outputs. Obtain the simplest Boolean expression of this logic circuit using Karnaugh map.

(6 marks)

- (c) (i) Using block diagrams show the differences between motor and generator.

(4 marks)

- (ii) State three advantages of AC induction motor.

(3 marks)

- (iii) A three-phase two-pole induction motor is connected to a 50 Hz supply. Determine the synchronous speed of the motor in rev/min.



(2 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 20122013
 COURSE : ELECTRICAL AND ELECTRONIC
 TECHNOLOGY

PROGRAMME : 1BNH / 1BNK
 COURSE CODE : BNJ10903

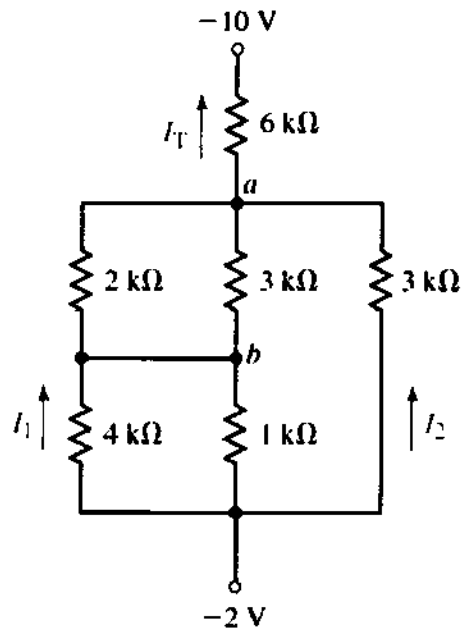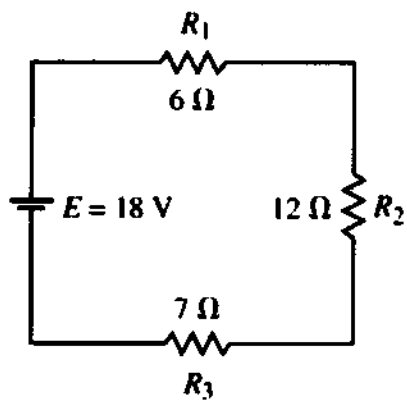**FIGURE Q2(a)****FIGURE Q2(b)**

FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 20122013
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME : 1BNH / 1BNK
 COURSE CODE : BNJ10903

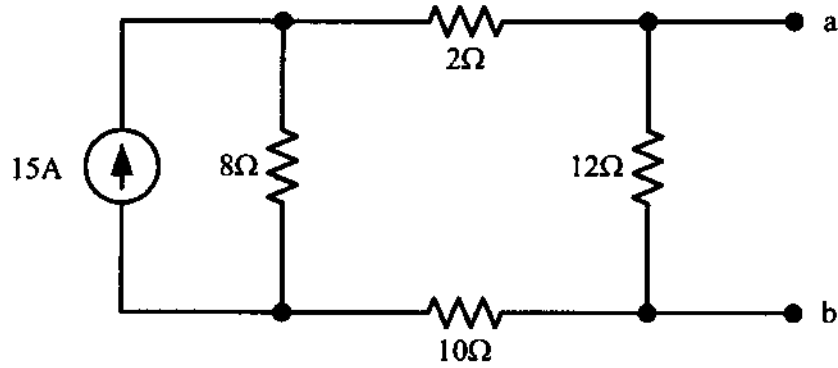


FIGURE Q2(c)

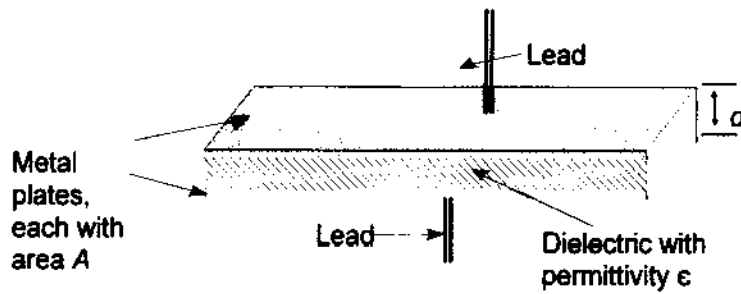


FIGURE Q3(a)

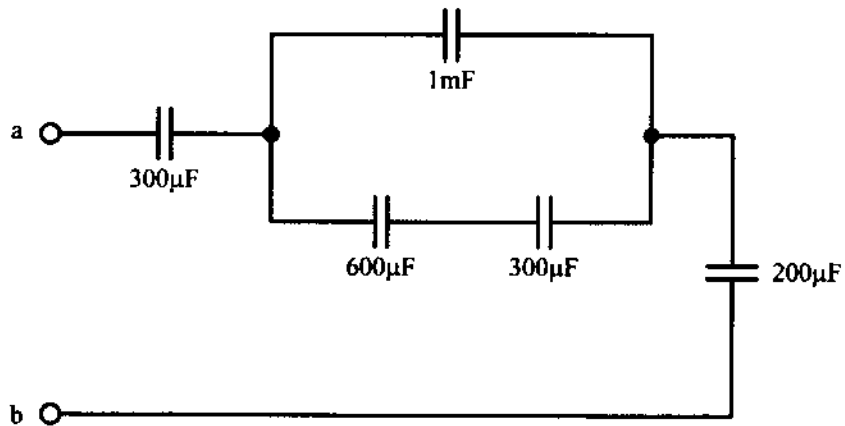


FIGURE Q3(b)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 20122013
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME : 1BNH / 1BNK
 COURSE CODE : BNJ10903

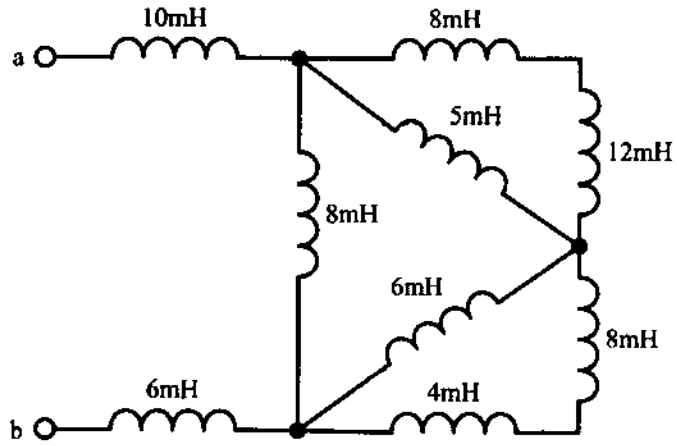


FIGURE Q3(d)

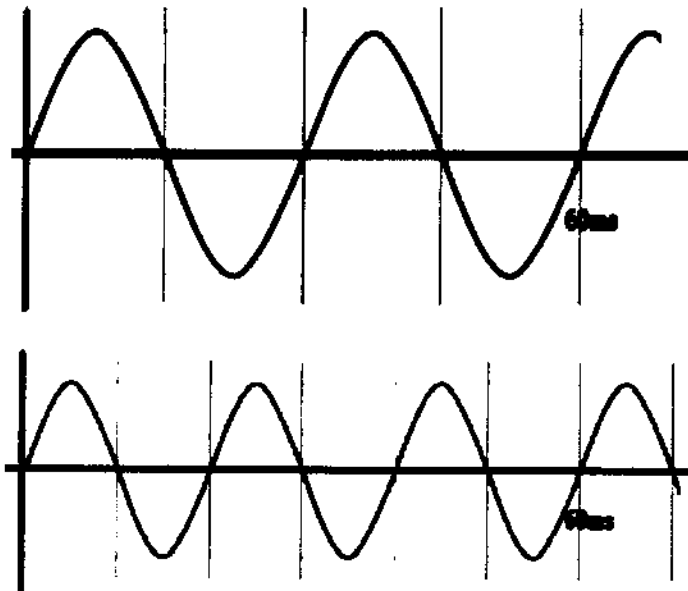


FIGURE Q4(a)(ii)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 20122013
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME : 1BNH / 1BNK
 COURSE CODE : BNJ10903

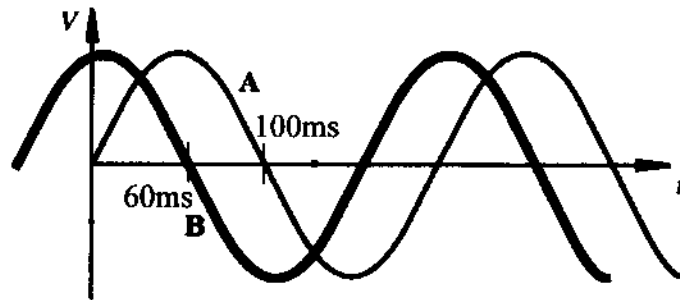


FIGURE Q4(b)

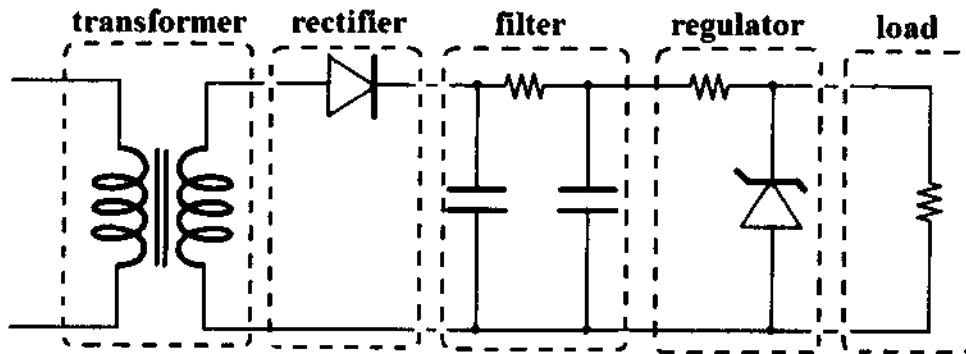


FIGURE Q5(b)(ii)

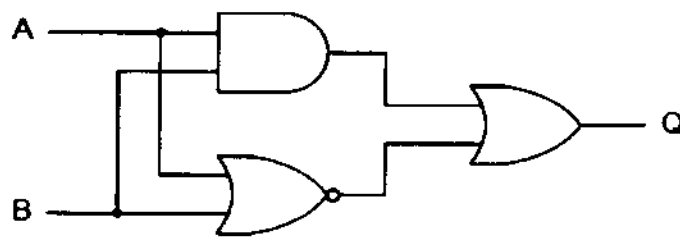


FIGURE Q6(a)(i)

FINAL EXAMINATION

SEMESTER/SESSION : SEM II / 20122013
 COURSE : ELECTRICAL AND ELECTRONIC TECHNOLOGY

PROGRAMME : 1BNH / 1BNK
 COURSE CODE : BNJ10903

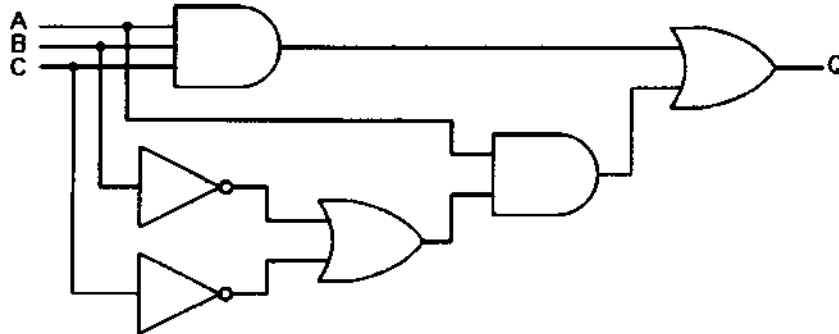


FIGURE Q6(a)(ii)

TABLE Q6(b)

A	B	C	D	Y2
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0