



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2012/2013**

COURSE : ELECTRICAL PRINCIPLES II
COURSE CODE : BNR 10303
PROGRAMME : 1 BND
EXAMINATION DATE : JUNE 2013
DURATION : 3 HOURS
INSTRUCTION : ANSWER FIVE (5) QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF TEN (17) PAGES

Q1 (a) Given a sinusoid, $5 \sin(4\pi t - 60^\circ)$, calculate:

- (i) phase,
- (ii) angular frequency,
- (iii) period, and
- (iv) frequency.

(3 marks)

(b) Identify the phase angle between $i_1 = -4 \sin(377t + 25^\circ)$ and $i_2 = 5 \cos(377t - 40^\circ)$. Does i_1 lead or lag i_2 ?

(3 marks)

(c) Show the steps to your solution to evaluate the following complex numbers:

$$\frac{10 + j5 + 3 \angle 40^\circ}{3 + j4} + 10 \angle 30^\circ + j5$$

(6 marks)

(d) Determine the input impedance of the circuit in **Figure Q1 (d)** at $\omega = 10$ rad/s.

(8 marks)

Q2 (a) Use the superposition theorem to determine v_o in the circuit as shown in **Figure Q2 (a)**.

(12 marks)

(b) Find I_o in the circuit of **Figure Q2 (b)** using the concept of source transformation.

(8 marks)

Q3 (a) For circuit in **Figure Q3 (a)**, determine the maximum power delivered to the load Z_L .

(14 marks)

(b) Calculate the *effective value* of the current waveform in **Figure Q3 (b)** and the *average power* delivered to a $12\text{-}\Omega$ resistor when the current runs through the resistor.

(6 marks)

Q4 (a) If $V_{ab} = 400\text{V}$ in a balanced Y-connected three-phase generator, identify the phase voltages, assuming the phase sequence is:

- (i) abc
- (ii) acb

(5 marks)

(b) In a balanced three-phase wye-wye system, the source is an abc -sequence of voltages and $V_{an} = 220\angle 20^\circ \text{ V rms}$. The line impedance per phase is $0.6 + j1.2\Omega$, while the per phase impedance of the load is $10 + j14\Omega$. Calculate the line currents and the load voltages.

(7 marks)

(c) In the balanced three-phase wye-delta system in **Figure Q4 (c)**, calculate the line current I_L and the average power delivered to the load.

(8 marks)

Q5 (a) Determine the real power absorbed by the load in **Figure Q5 (a)**,

(14 marks)

(b) Consider the delta-delta system shown in **Figure Q5 (b)**. Take $Z_1 = 8 + j6 \Omega$, $Z_2 = 4.2 - j2.2 \Omega$, $Z_3 = 10 + j0 \Omega$.

- (i) Find the phase current I_{AB} , I_{BC} , and I_{CA} .
- (ii) Calculate line currents I_{aA} , I_{bB} , and I_{cC} .

(6 marks)

Q6 (a) For the coupled coils in **Figure Q6 (a)**, show that

$$L_{\text{eq}} = L_1 + L_2 + 2M$$

(3 marks)

(b) For the coupled coils in **Figure Q6 (b)**, show that

$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 L_2 - 2M^2}$$

(7 marks)

(c) Consider the circuit in **Figure Q6 (c)**.

- (i) Determine the coupling coefficient.
- (ii) Calculate the energy stored in the coupled inductors at time $t = 1\text{ s}$ if $v = 60\cos(4t + 30^\circ) \text{ V}$.

(10 marks)

-END OF QUESTION-

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013 PROGRAMME : 1 BND
 COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

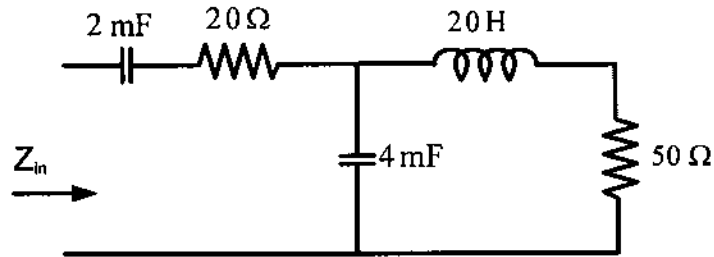


FIGURE Q1 (d)

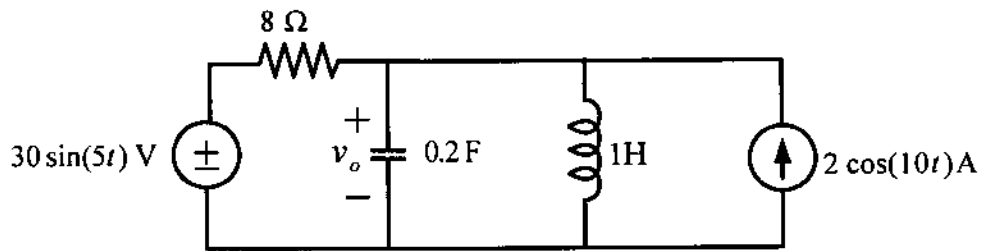


FIGURE Q2 (a)

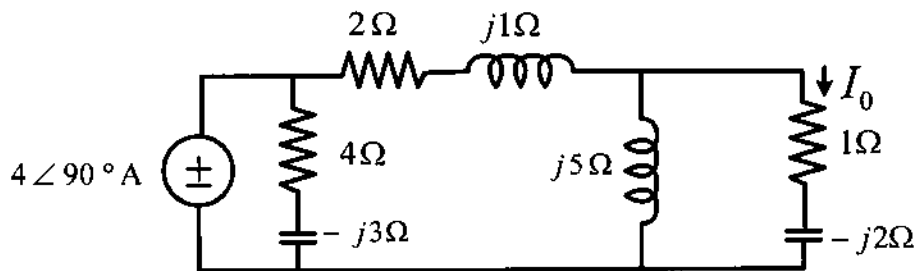


FIGURE Q2 (b)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : I BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

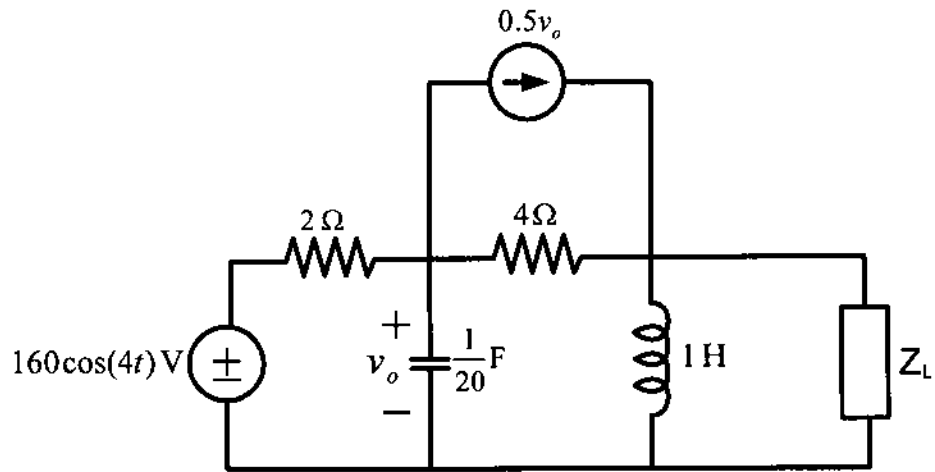


FIGURE Q3 (a)

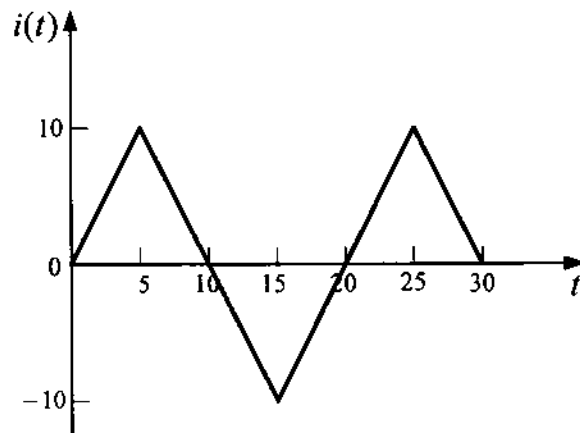


FIGURE Q3 (b)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND
 COURSE CODE : BNR 10303

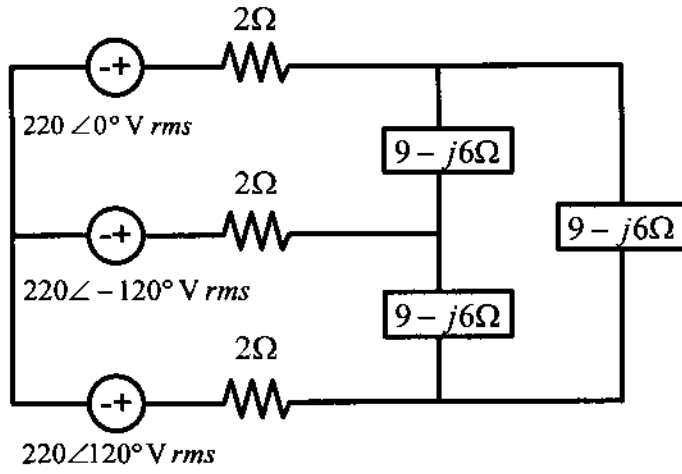


FIGURE Q4 (c)

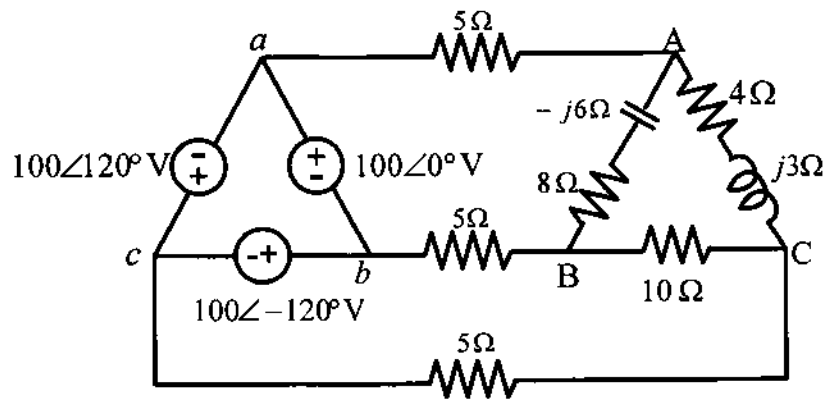


FIGURE Q5 (a)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

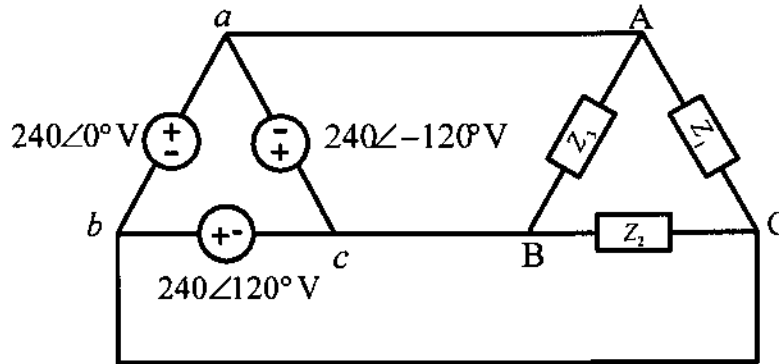


FIGURE Q5 (b)

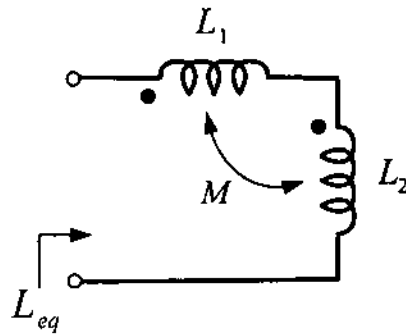


FIGURE Q6 (a)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : I BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

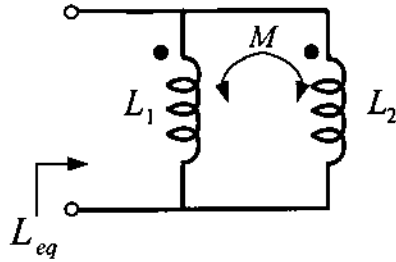


FIGURE Q6 (b)

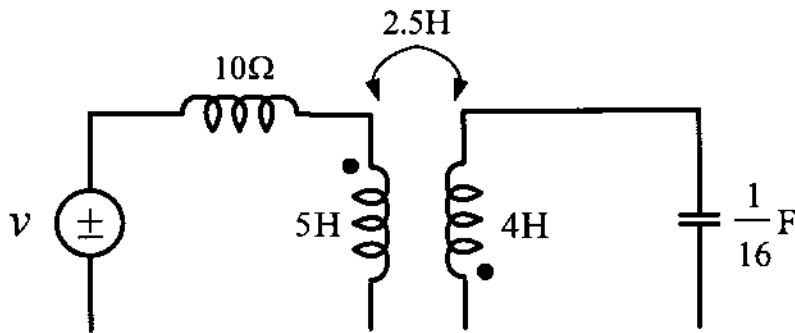


FIGURE Q6 (c)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Chapter 1***A general expression for the sinusoid***

Frequency: $f = \frac{1}{T} \text{ Hz}$

Angular frequency: $\omega = 2\pi f \text{ Hz}$

Trigonometric identities

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

Mathematic operation of complex number

Addition: $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

Subtraction: $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

Multiplication: $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

Division: $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

Reciprocal: $\frac{1}{z} = \frac{1}{r} \angle -\phi$

Square root: $\sqrt{z} = \sqrt{r} \angle \phi/2$

Complex conjugate: $z^* = x - jy = r \angle -\phi = r e^{-j\phi}$

Euler's identity: $e^{\pm j\phi} = \cos \phi \pm j \sin \phi$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Summary of voltage-current relationship		
Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Impedances and admittances of passive elements		
Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

Relationship between differential, integral operation in phasor listed as follow:

$$v(t) \rightarrow V = V \angle \phi$$

$$\frac{dv}{dt} \rightarrow j\omega V$$

$$\int v dt \rightarrow \frac{V}{j\omega}$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303


Chapter 2

Superposition Theorem


When a circuit has sources operating at different frequencies,

- *The separate phasor circuit for each frequency must be solved independently,*
- *The total response is the sum of time-domain responses of all the individual phasor circuits.*

Thevenin and Norton Equivalent Circuits

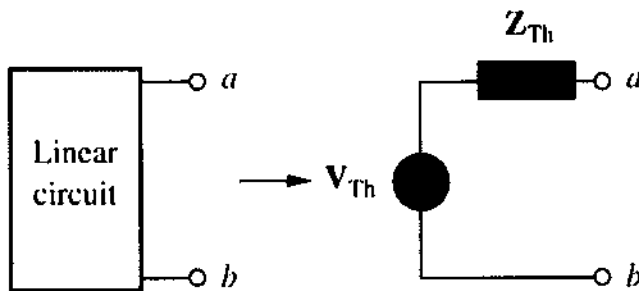

Thevenin transform

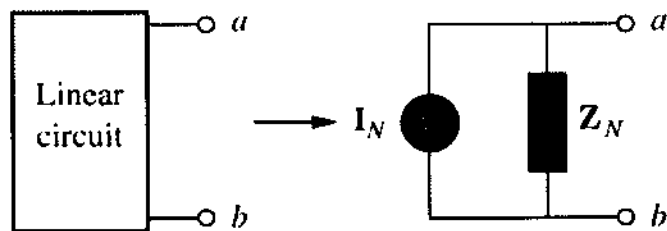

Norton transform

FINAL EXAMINATION


SEMESTER/SESSION : II / 2012/2013

PROGRAMME : I BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Source Transformation

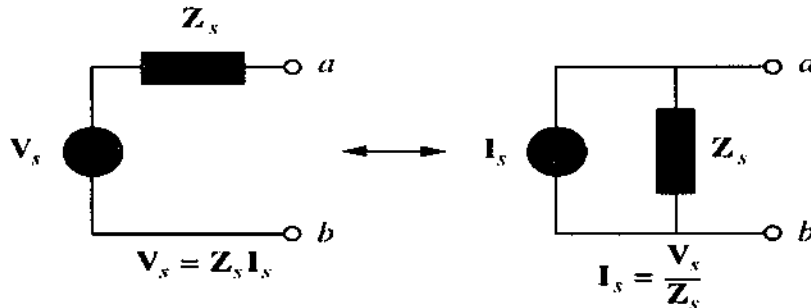

Chapter 3

Average Power:
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Load Impedance:
$$Z_L = Z_{TH} = R_{TH} + jX_{TH}$$

$$Z_{TH}^* = R_{TH} - jX_{TH}$$

Maximum Average Power:
$$P_{\max} = \frac{|V_{TH}|^2}{8 R_{TH}}$$

If the load is purely real:
$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$$

Effective Current:
$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{\text{rms}}$$

The rms value of a sinusoid $i(t) = I_m \cos(\omega t)$ is given by:
$$I_{\text{rms}}^2 = \frac{I_m^2}{2}$$

The average power can be written in terms of the rms values:

$$I_{\text{eff}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II


COURSE CODE : BNR 10303

Apparent Power and Power Factor:

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

Apparent Power, S
Power Factor, pf

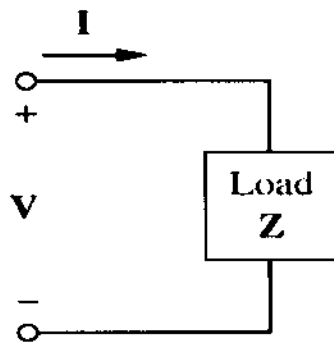Complex power S is the product of the voltage and the complex conjugate of the current:



$$V = V_m \angle \theta_v \quad I = I_m \angle \theta_i$$

$$\frac{1}{2} V I^* = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$S = \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_{+j Q}$$

P: is the average power in watts delivered to a load and it is the only useful power.

Q: is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- $Q = 0$ for *resistive loads* (unity pf).
- $Q < 0$ for *capacitive loads* (leading pf).
- $Q > 0$ for *inductive loads* (lagging pf).

Power Absorbed:
$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

$$\text{Conservation of AC Power : } \bar{S} = \frac{1}{2} \bar{V} \bar{I}^* = \frac{1}{2} \bar{V} (\bar{I}_1^* + \bar{I}_2^*) = \frac{1}{2} \bar{V} \bar{I}_1^* + \frac{1}{2} \bar{V} \bar{I}_2^* = \bar{S}_1 + \bar{S}_2$$

$$\text{Power Factor Correction : } C = \frac{Q_c}{\omega V_{\text{rms}}^2} = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2}$$

$$Q_c = Q_1 - Q_2, \quad Q_1 = S_1 \sin \theta_1 = P \tan \theta_1, \quad Q_2 = P \tan \theta_2$$

Chapter 4**The voltages can be expressed in phasor form as**

$$V_{an} = 200 \angle 10^\circ \text{V}$$

$$V_{bn} = 200 \angle -230^\circ \text{V}$$

$$V_{cn} = 200 \angle -110^\circ \text{V}$$

A balanced Y-Y system

$$V_L = \sqrt{3} V_p, \text{ where}$$

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

A balanced Y-Δ system

$$I_L = \sqrt{3} I_p, \text{ where}$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

$$\text{Power loss in a single-phase system: } P'_{\text{loss}} = 2R \frac{P_L^2}{V_L^2}$$

$$\text{Power loss in a three-phase system: } P'_{\text{loss}} = R' \frac{P_L^2}{V_L^2}$$

Unbalanced Three-Phase Systems:

$$I_a = \frac{V_{AN}}{Z_A}, \quad I_b = \frac{V_{BN}}{Z_B}, \quad I_c = \frac{V_{CN}}{Z_C},$$

$$I_n = -(I_a + I_b + I_c)$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : I BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Summary of phase and line voltages/currents for balanced three-phase system

Connecti on	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ <p style="text-align: center;">Same as line currents</p>	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = \frac{V_{an}}{Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y-Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{AB}}{Z_\Delta}$ $I_{BC} = \frac{V_{BC}}{Z_\Delta}$ $I_{CA} = \frac{V_{CA}}{Z_\Delta}$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{ab}}{Z_\Delta}$ $I_{BC} = \frac{V_{bc}}{Z_\Delta}$ $I_{CA} = \frac{V_{ca}}{Z_\Delta}$	<p style="text-align: center;">Same as phase voltages</p> $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$


FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013
 COURSE NAME : ELECTRICAL PRINCIPLES II


PROGRAMME : 1 BND
 COURSE CODE : BNR 10303

Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ <p style="text-align: center;">Same as line currents</p>	<p style="text-align: center;">Same as phase voltages</p> $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
-------------	--	--

Chapter 5

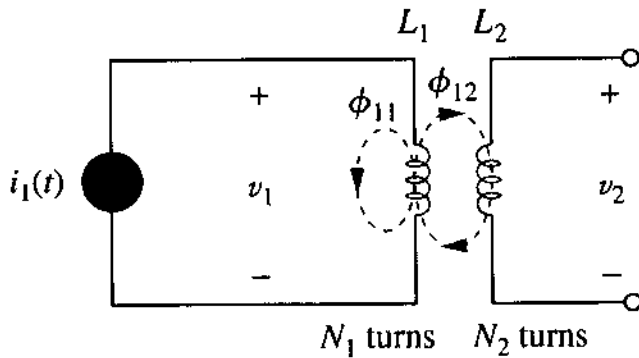

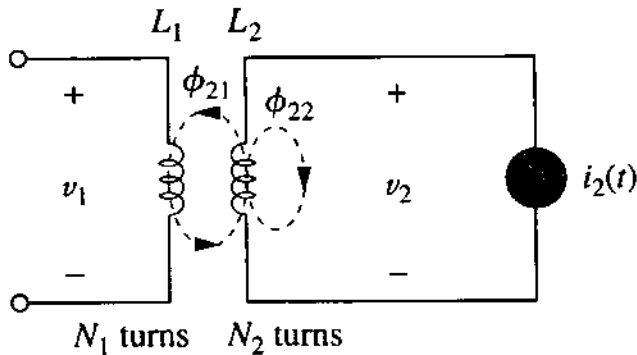The open-circuit mutual voltage across coil 2: $v_2 = M_{21} \frac{di_1}{dt}$



The open-circuit mutual voltage across coil 1: $v_1 = M_{12} \frac{di_2}{dt}$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2012/2013

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Series-Aiding Connection: $L = L_1 + L_2 + 2M$ **Series-Opposing Connection** $L = L_1 + L_2 - 2M$ **Coefficient of Coupling k :** $M = k\sqrt{L_1L_2}$ **Instantaneous Energy Stored:** $w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 \pm MI_1I_2$