

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2014/2015**

COURSE NAME : ELECTRICAL PRINCIPLES II
COURSE CODE : BNR 10303
PROGRAMME : 1 BND
EXAMINATION DATE : JUNE 2015 / JULY 2015
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF **EIGHTEEN (18)** PAGES

CONFIDENTIAL

- Q1 (a) Given a sinusoidal voltage $v(t) = 50\cos(30t + 10^\circ)$ V, compute:
- the amplitude $v(t)$,
 - the period T ,
 - the frequency f
 - $v(t)$ at $t = 10\text{ms}$
- (3 marks)
- (b) Calculate these complex numbers and express your results in rectangular form.
- $\frac{15 \angle 45^\circ}{3 - j4} + j2$
 - $\frac{8 \angle -20^\circ}{(2 + j)(3 - j4)}$
 - $10 + (8 \angle 50^\circ)(5 - j12)$
- (7 marks)
- (c) A voltage $v(t) = 100\cos(60t + 20^\circ)$ V is applied to a parallel combination of a $40\text{ k}\Omega$ resistor and a $50\text{ }\mu\text{F}$ capacitor. Compute the steady-state currents through the resistor and the capacitor?
- (3 marks)
- (d) Calculate current i in the circuit of **Figure Q1 (d)**, when $v_s(t) = 50\cos(200t)$ V
- (5 marks)
- (e) Calculate current I in the circuit of **Figure Q1 (e)**.
- (7 marks)
- Q2 (a) Determine V_x in the circuit of **Figure Q2 (a)**.
- (5 marks)
- (b) Use mesh analysis to find i_o current in the circuit of **Figure Q2 (b)**.
- (6 marks)
- (c) Using the superposition principle, compute i_x in the circuit of **Figure Q2 (c)**.
- (6 marks)
- (d) Calculate the Thevenin equivalent at terminals $a-b$ of the circuit in **Figure Q2 (d)**.
- (8 marks)

- Q3** (a) If $v(t) = 160\cos(50t)V$ and $i(t) = -20\sin(50t - 30^\circ)A$, compute the instantaneous power and the average power. (3 marks)
- (b) The Thevenin impedance of a source is $Z_{TH} = 120 + j60\Omega$, while the peak Thevenin voltage is $V_{TH} = 110 + j0V$. Determine the maximum available average power from the source. (3 marks)
- (c) Calculate the effective value of the voltage waveform in **Figure Q3 (c)**. (4 marks)
- (d) For the entire circuit in **Figure Q3 (d)**, calculate
 (i) the power factor
 (ii) the average power delivered by the source
 (iii) the reactive power
 (iv) the apparent power
 (v) the complex power (6 marks)
- (e) Determine the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging **pf** to unity **pf**. Assume that the load is supplied by a 110-V (rms), 60-Hz line. (9 marks)
- Q4** (a) Provide two advantages of a three phase circuit? (2 marks)
- (b) If $V_{ab} = 4000V$ in a balanced Y-connected three-phase generator, identify the phase voltages, assuming the phase sequence is:
 (i) abc
 (ii) acb (5 marks)
- (c) A positive-sequence, balanced Δ -connected source supplies a balanced Δ -connected load. If the impedance per phase of load is $18 + j12\Omega$ and $I_a = 19.202 \angle 35^\circ A$, calculate I_{AB} and V_{AB} . (6 marks)
- (d) Refer to the circuit in **Figure Q4 (d)**. Determine the total average power, reactive power and complex power at the source and at the load. (6 marks)
- (e) The unbalanced Y-load of **Figure Q4 (e)** has balanced voltages of 100 V and the acb sequence. Calculate the line currents and the neutral current. Take $Z_A = 15\Omega$, $Z_B = 10 + j5\Omega$ and $Z_C = 6 - j8\Omega$. (6 marks)

- Q5** (a) Determine the voltage V_o in the circuit of **Figure Q5 (a)**.
(5 marks)
- (b) Consider the circuit in **Figure Q5 (b)**. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1\text{ s}$ if $v(t) = 60\cos(4t + 30^\circ)\text{ V}$
(10 marks)
- (c) Compute the input impedance of the circuit in **Figure Q5 (c)** and the current from voltage source.
(5 marks)
- (d) The primary current to an ideal transformer rated at 3300/110 V is a 5 A. Calculate
(i) the turns ratio
(ii) the kVA rating
(iii) the secondary current.
(5 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND
 COURSE CODE : BNR 10303

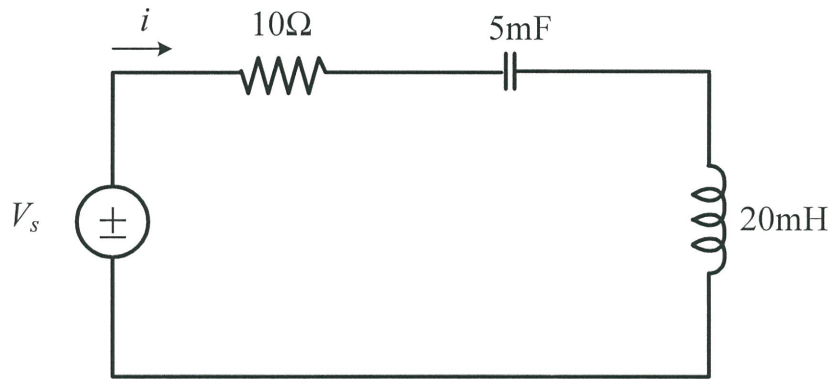


FIGURE Q1 (d)

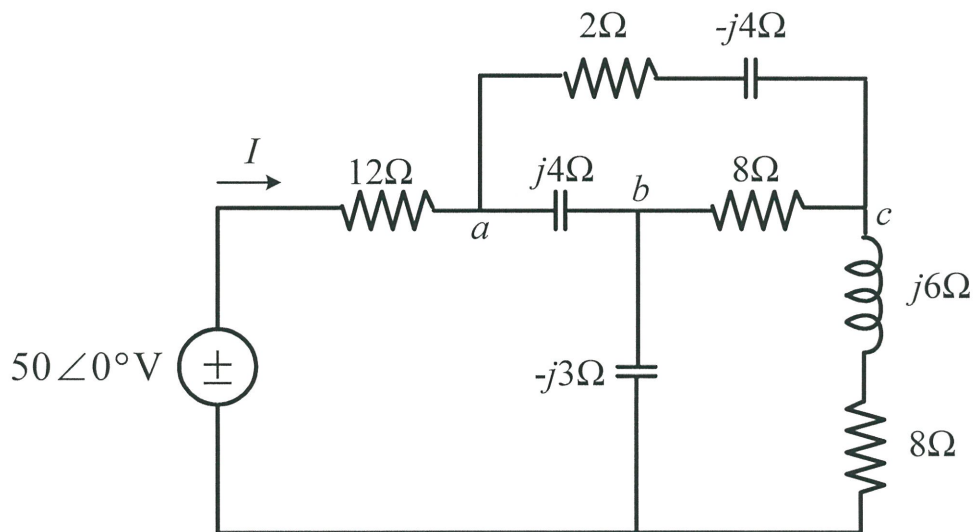


FIGURE Q1 (e)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

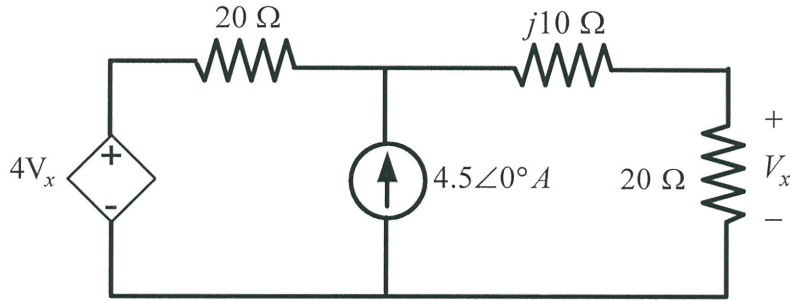


FIGURE Q2 (a)

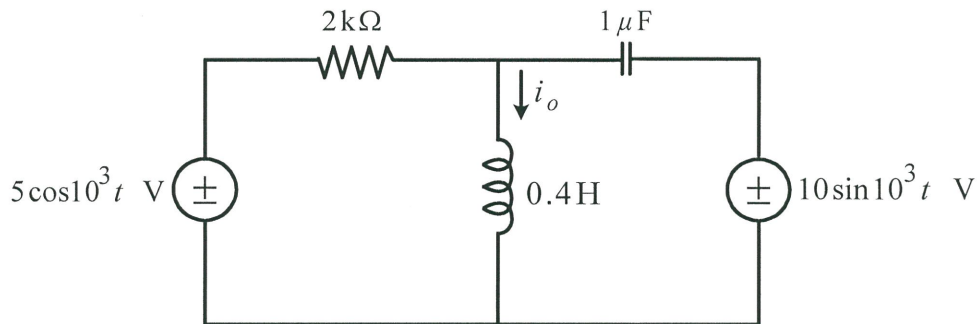


FIGURE Q2 (b)

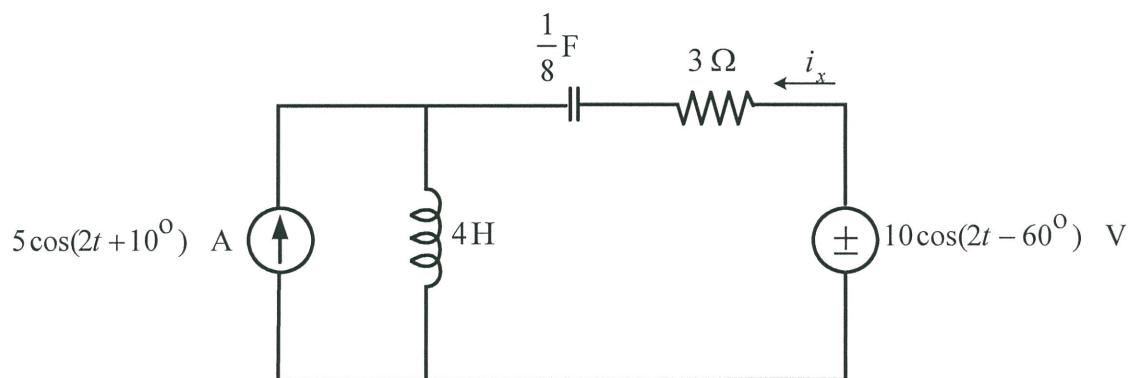


FIGURE Q2 (c)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015 PROGRAMME : 1 BND
 COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

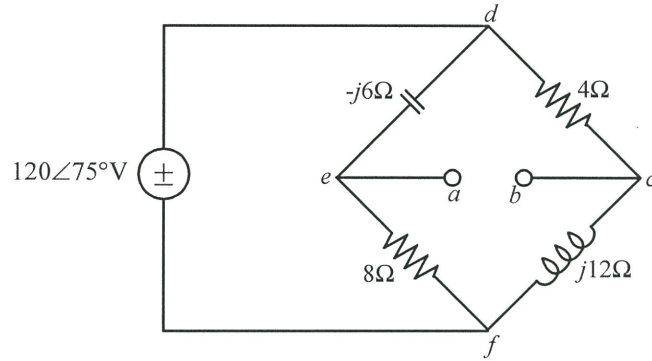


FIGURE Q2 (d)

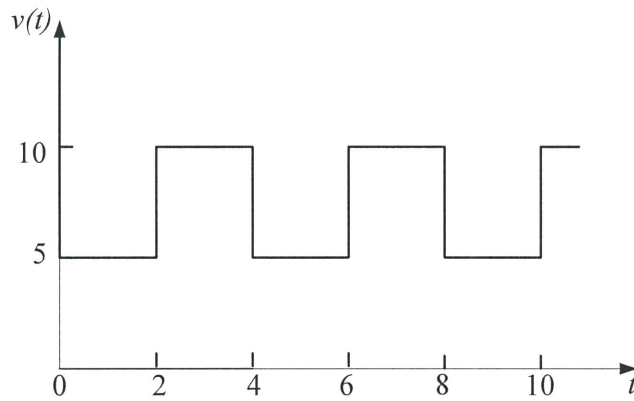


FIGURE Q3 (c)

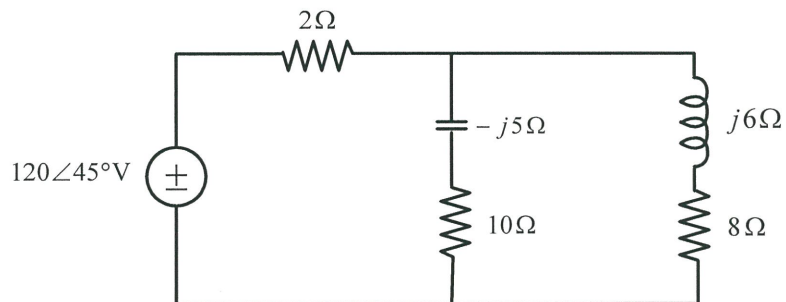


FIGURE Q3 (d)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015 PROGRAMME : 1 BND
COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

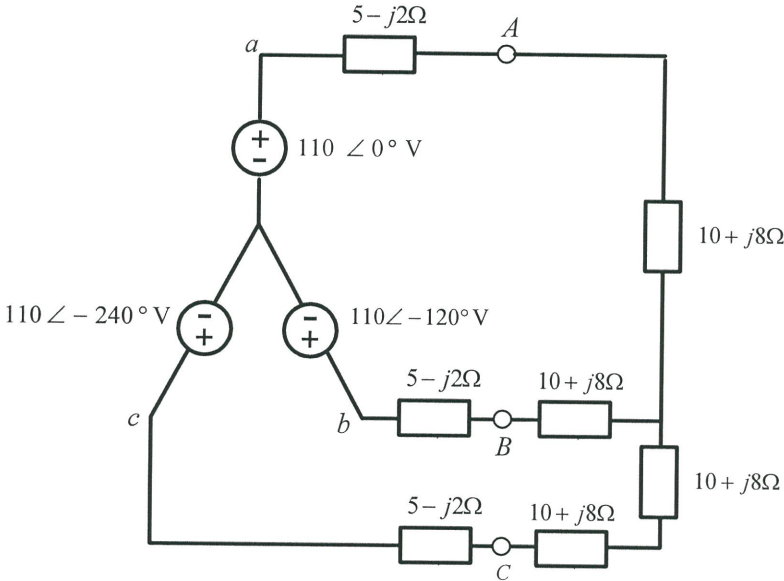


FIGURE Q4 (d)

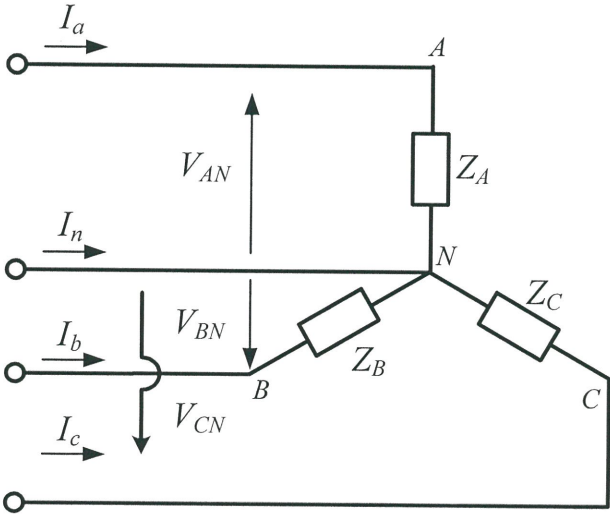


FIGURE Q4 (e)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

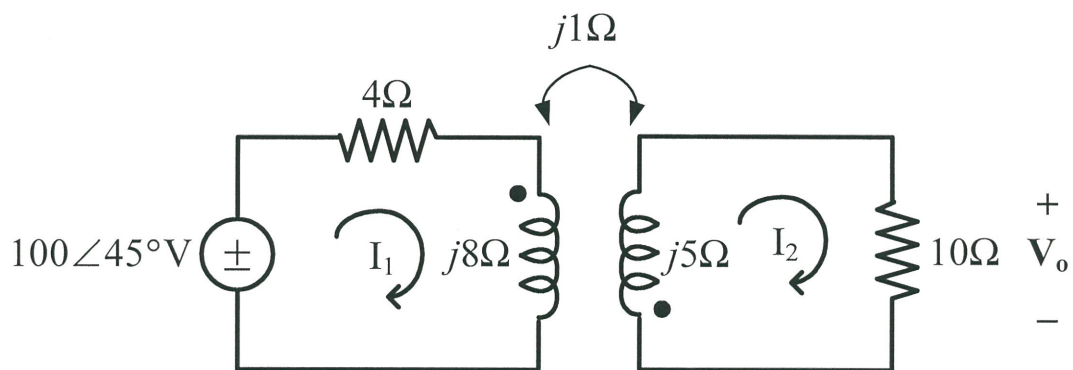


FIGURE Q5 (a)

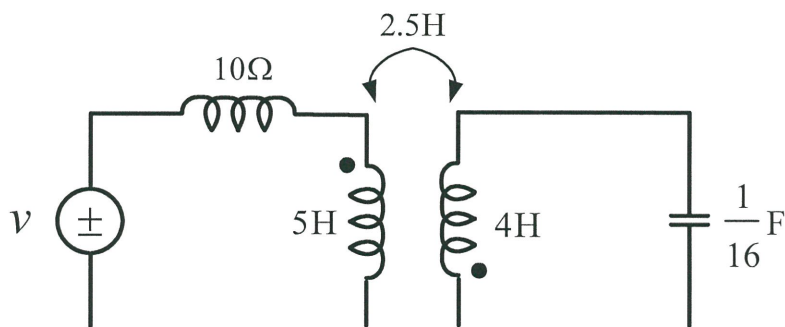


FIGURE Q5 (b)

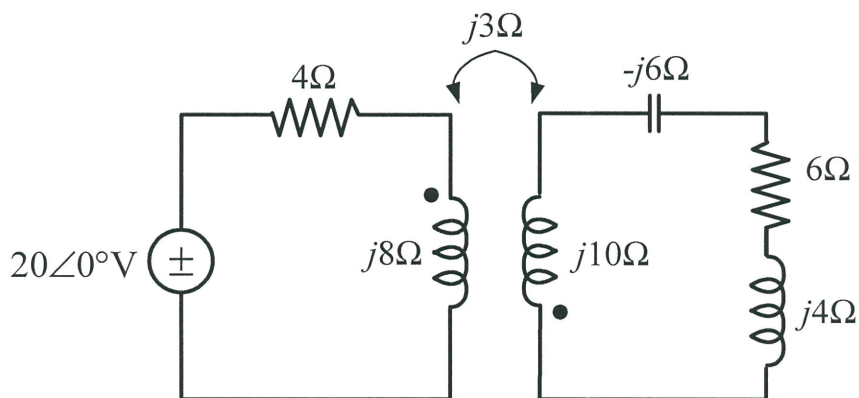


FIGURE Q5 (c)

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Chapter 1*A general expression for the sinusoid*

Frequency: $f = \frac{1}{T} \text{ Hz}$

Angular frequency: $\omega = 2\pi f \text{ Hz}$

Trigonometric identities

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

Mathematic operation of complex number

Addition: $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

Subtraction: $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

Multiplication: $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

Division: $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

Reciprocal: $\frac{1}{z} = \frac{1}{r} \angle -\phi$

Square root: $\sqrt{z} = \sqrt{r} \angle \phi/2$

Complex conjugate: $z^* = x - jy = r \angle -\phi = r e^{-j\phi}$

Euler's identity: $e^{\pm j\phi} = \cos \phi \pm j \sin \phi$

FINAL EXAMINATION


SEMESTER/SESSION : II / 2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

Source Transformation

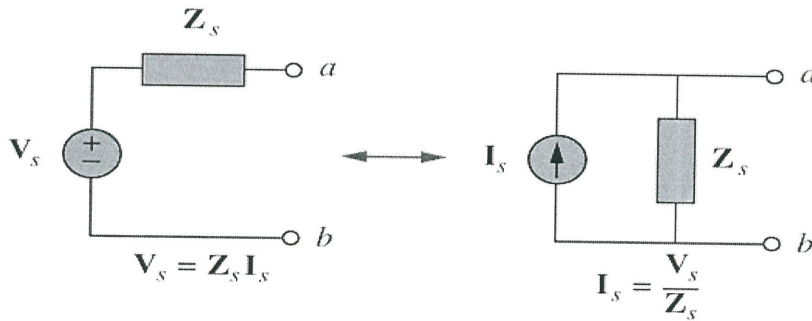

Chapter 3

Average Power:
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Load Impedance:
$$Z_L = Z_{TH} = R_{TH} + jX_{TH}$$

$$Z_{TH}^* = R_{TH} - jX_{TH}$$

Maximum Average Power:
$$P_{max} = \frac{|V_{TH}|^2}{8 R_{TH}}$$

If the load is purely real:
$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$$

Effective Current:
$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{rms}$$

The rms value of a sinusoid $i(t) = I_m \cos(\omega t)$ is given by:
$$I_{rms}^2 = \frac{I_m}{\sqrt{2}}$$

The average power can be written in terms of the rms values:

$$I_{eff} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

FINAL EXAMINATION


SEMESTER/SESSION : II / 2014/2015 PROGRAMME : 1 BND
 COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

Apparent Power and Power Factor:

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$

Apparent Power, S Power Factor, pf

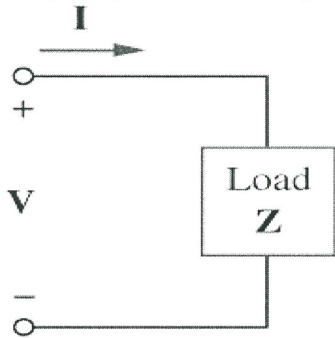Complex power S is the product of the voltage and the complex conjugate of the current:



$$V = V_m \angle \theta_v \quad I = I_m \angle \theta_i$$

$$\frac{1}{2} V I^* = V_{rms} I_{rms} \angle \theta_v - \theta_i$$

$$S = \underbrace{V_{rms} I_{rms} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{rms} I_{rms} \sin(\theta_v - \theta_i)}_Q$$

S = P +j Q

P: is the average power in watts delivered to a load and it is the only useful power.
 Q: is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- Q = 0 for *resistive loads* (unity pf).
- Q < 0 for *capacitive loads* (leading pf).
- Q > 0 for *inductive loads* (lagging pf).

Power Absorbed: $P = I_{rms}^2 R = \frac{V_{rms}^2}{R}$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015

PROGRAMME : 1 BND

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

$$\text{Conservation of AC Power: } \bar{S} = \frac{1}{2} \overline{V I^*} = \frac{1}{2} \overline{V (I_1^* + I_2^*)} = \frac{1}{2} \overline{V I_1^*} + \frac{1}{2} \overline{V I_2^*} = \bar{S}_1 + \bar{S}_2$$

$$\text{Power Factor Correction: } C = \frac{Q_c}{\omega V_{\text{rms}}^2} = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2}$$

$$Q_c = Q_1 - Q_2, \quad Q_1 = S_1 \sin \Theta_1 = P \tan \Theta_1, \quad Q_2 = P \tan \Theta_2$$

Chapter 4**The voltages can be expressed in phasor form as**

$$V_{an} = 200 \angle 10^\circ V$$

$$V_{bn} = 200 \angle -230^\circ V$$

$$V_{cn} = 200 \angle -110^\circ V$$

A balanced Y-Y system

$$V_L = \sqrt{3} V_p, \text{ where}$$

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

A balanced Y-Δ system

$$I_L = \sqrt{3} I_p, \text{ where}$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

$$\text{Power loss in a single-phase system: } P'_{\text{loss}} = 2R \frac{P_L^2}{V_L^2}$$

$$\text{Power loss in a three-phase system: } P'_{\text{loss}} = R' \frac{P_L^2}{V_L^2}$$

Unbalanced Three-Phase Systems:

$$I_a = \frac{V_{AN}}{Z_A}, \quad I_b = \frac{V_{BN}}{Z_B}, \quad I_c = \frac{V_{CN}}{Z_C},$$

$$I_n = -(I_a + I_b + I_c)$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015 PROGRAMME : 1 BND
 COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

Summary of phase and line voltages/currents for balanced three-phase system


Connecti on	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ <p style="text-align: center;">Same as line currents</p>	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = \frac{V_{an}}{Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y-Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{AB}}{Z_\Delta}$ $I_{BC} = \frac{V_{BC}}{Z_\Delta}$ $I_{CA} = \frac{V_{CA}}{Z_\Delta}$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{ab}}{Z_\Delta}$ $I_{BC} = \frac{V_{bc}}{Z_\Delta}$ $I_{CA} = \frac{V_{ca}}{Z_\Delta}$	<p style="text-align: center;">Same as phase voltages</p> $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

FINAL EXAMINATION


SEMESTER/SESSION : II / 2014/2015 PROGRAMME : 1 BND
 COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ Same as line currents	Same as phase voltages $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
-------------	--	--

Chapter 5

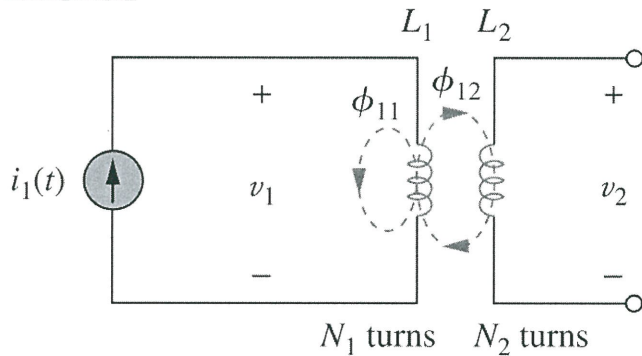

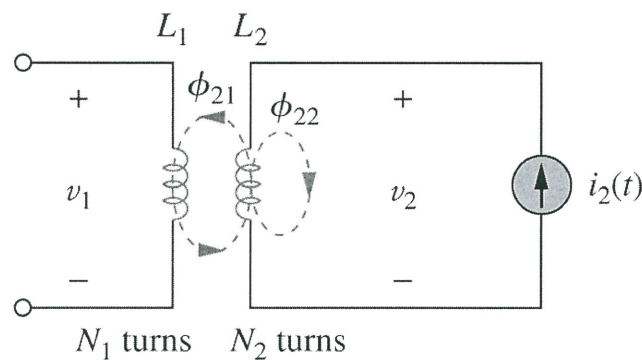The open-circuit mutual voltage across coil 2: $v_2 = M_{21} \frac{di_1}{dt}$



The open-circuit mutual voltage across coil 1: $v_1 = M_{12} \frac{di_2}{dt}$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2014/2015 PROGRAMME : 1 BND
 COURSE NAME : ELECTRICAL PRINCIPLES II COURSE CODE : BNR 10303

<p>Series-Aiding Connection: $L = L_1 + L_2 + 2M$</p>	<p>Series-Opposing Connection $L = L_1 + L_2 - 2M$</p>
<p>Coefficient of Coupling k: $M = k\sqrt{L_1L_2}$</p>	<p>Instantaneous Energy Stored: $w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 \pm MI_1I_2$</p>
<p>Reflected impedance $Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$</p>	<p>Voltage-current relationships for the primary and secondary coils $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$</p>
<p>Transforming to the II network the inductors are: $L_A = \frac{L_1L_2 - M^2}{L_2 - M} \quad L_B = \frac{L_1L_2 - M^2}{L_1 - M}$ $L_C = \frac{L_1L_2 - M^2}{M}$</p>	<p>The voltages are related to each other by the turns ration n: $\frac{V_1}{V_2} = \frac{N_2}{N_1} = n$</p>
<p>The current is related as: $\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$</p>	<p>The complex power in the primary winding is: $S_1 = V_1I_1^* = \frac{V_2}{n}(nI_2)^* = V_2I_2^* = S_2$</p>
<p>The input impedance that appears at the source is: $Z_{in} = \frac{Z_L}{n^2}$</p>	<p>The voltage relationship for an auto transformer is: $\frac{V_1}{V_2} = \frac{N_1}{N_1 + N_2}$</p>