

CONFIDENTIAL



UTHM

Universiti Tun Hussein Onn Malaysia

UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2013/2014**

COURSE NAME : ELECTRICAL PRINCIPLES II
COURSE CODE : BNR10303
PROGRAMME : 1 BND/BNF
EXAMINATION DATE : JUN 2014
DURATION : 3 HOURS
INSTRUCTION : ANSWER **FIVE (5)** QUESTIONS
ONLY

THIS QUESTION PAPER CONSISTS OF **SEVENTEEN (17)** PAGES

CONFIDENTIAL

- Q1** (a) A current source in a linear circuit has
 $i_s = 8 \cos(500\pi t - 25^\circ)$ A
- (i) Determine the amplitude of the current?
(ii) Determine the angular frequency?
(iii) Determine the frequency of the current.
(iv) Calculate i_s at $t = 2$ ms.
- (5 marks)
- (b) Two voltages v_1 and v_2 appear in series so that their sum is $v = v_1 + v_2$. If
 $v_1 = 10 \cos(50t - \pi/3)$ V and $v_2 = 12 \cos(50t + 30^\circ)$ V. Calculate total of voltage, v .
- (4 marks)
- (c) A linear network has a current input $4 \cos(\omega t + 20^\circ)$ A and a voltage output
 $10 \cos(\omega t + 110^\circ)$ V. Calculate the associated impedance.
- (3 marks)
- (d) By analyzing the circuit shown in Figure **Q1(d)**, determine the value of Z_T .
- (8 marks)
- Q2** (a) Using Nodal analysis, calculate V_1 and V_2 in the circuit shown in Figure **Q2(a)**.
- (10 marks)
- (b) Calculate current I_0 in the circuit of Figure **Q2(b)** using mesh analysis.
- (10 marks)
- Q3** (a) Calculate the rms value of the current waveform in Figure **Q3(a)**. If the current is
passed through a resistor, determine the average power absorbed by the resistor.
- (7 marks)
- (b) For the circuit in Figure **Q3(b)**, discover the wattmeter reading.
- (6 marks)
- (c) The variable resistor R in the circuit of Figure **Q3(c)** is adjusted until it absorbs
the maximum average power. Calculate R and the maximum average power
absorbed.
- (7 marks)

- Q4** (a) A 110-V rms, 60-Hz source is applied to a load impedance Z . The apparent power entering the load is 120 VA at a power factor of 0.707 lagging.
- (i) Calculate the complex power. (3 marks)
 - (ii) Calculate the rms current supplied to the load. (2 marks)
 - (iii) Calculate the impedance, Z . (2 marks)
 - (iv) Assuming that $Z = R + j\omega L$, identified the values of R and L . (3 marks)
- (b) Three loads are connected in parallel to a $120\angle 0^\circ$ V rms source. Load 1 absorbs 60 kVAR at $\text{pf} = 0.85$ lagging; load 2 absorbs 90 kW and 50 kVAR leading; and load 3 absorbs 100 kW at $\text{pf} = 1$.
- (i) Find the equivalent impedance. (7 marks)
 - (ii) Calculate the power factor of the parallel combination. (1 mark)
 - (iii) Determine the current supplied by the source. (2 marks)
- Q5** For the unbalanced circuit in Figure **Q5**, calculate:
- (a) the line currents, (10 marks)
 - (b) the total complex power absorbed by the load, and (5 marks)
 - (c) the total complex power absorbed by the source. (5 marks)
- Q6** (a) By Analyzing the circuit of Figure **Q6(a)**, determine the phasor currents I_1 and I_2 (7 marks)
- (b) For the circuit in Figure **Q6(b)**, calculate the coupling coefficient and the energy stored in the coupled inductors at $t = 1.5$ s. (13 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014

PROGRAMME : 1 BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE: BNR10303

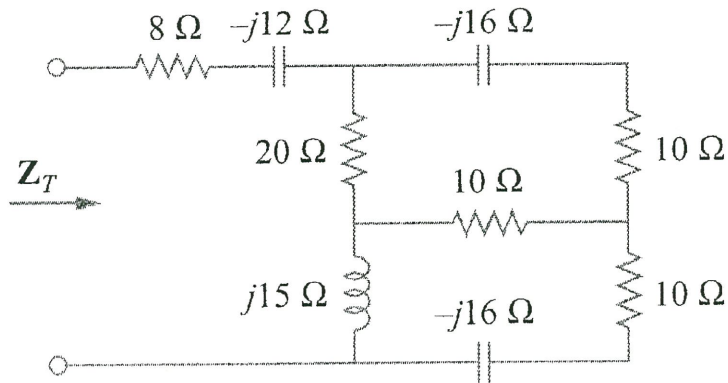


FIGURE Q1(d)

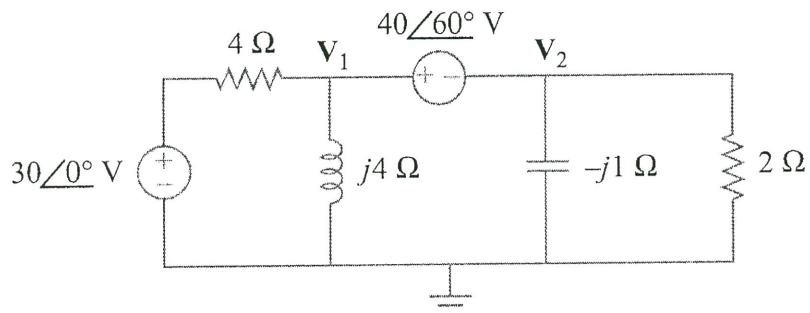


FIGURE Q2(a)

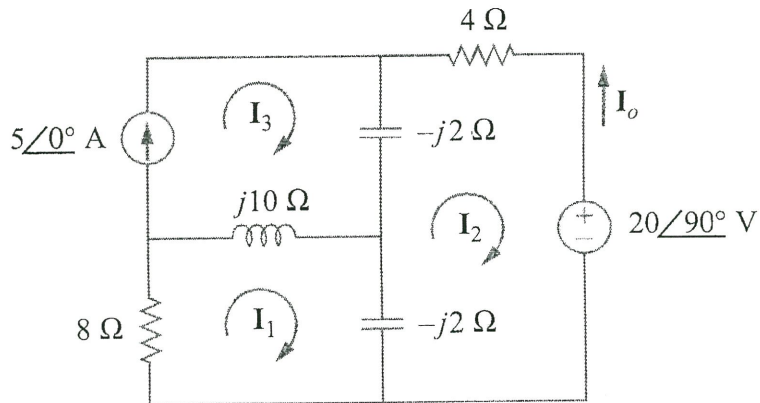


FIGURE Q2(b)

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND/BNF
 COURSE CODE: BNR10303

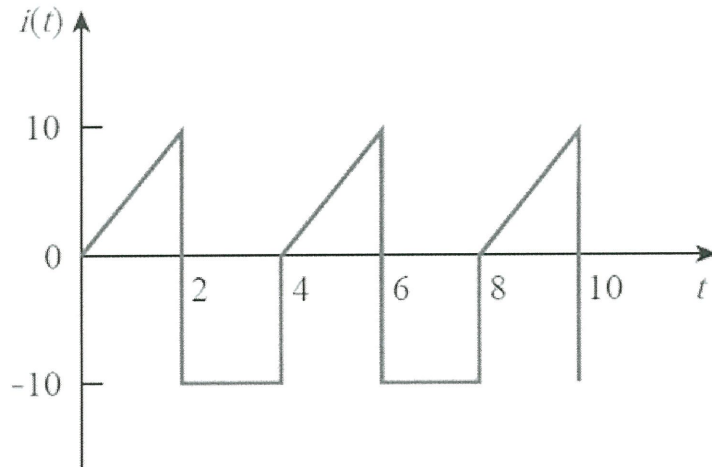


FIGURE Q3(a)

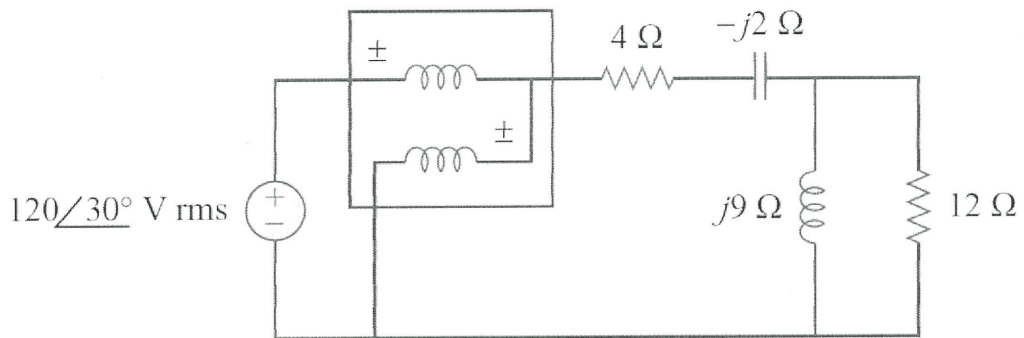


FIGURE Q3(b)

UNIVERSITI TEKNIK MALAYSIA
 INSTITUT TEKNIK MALAYSIA
 UNIVERSITI TEKNIK MALAYSIA
 INSTITUT TEKNIK MALAYSIA

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND/BNF
 COURSE CODE: BNR10303

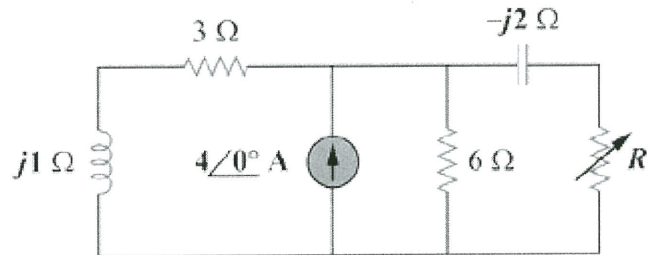


FIGURE Q3(c)

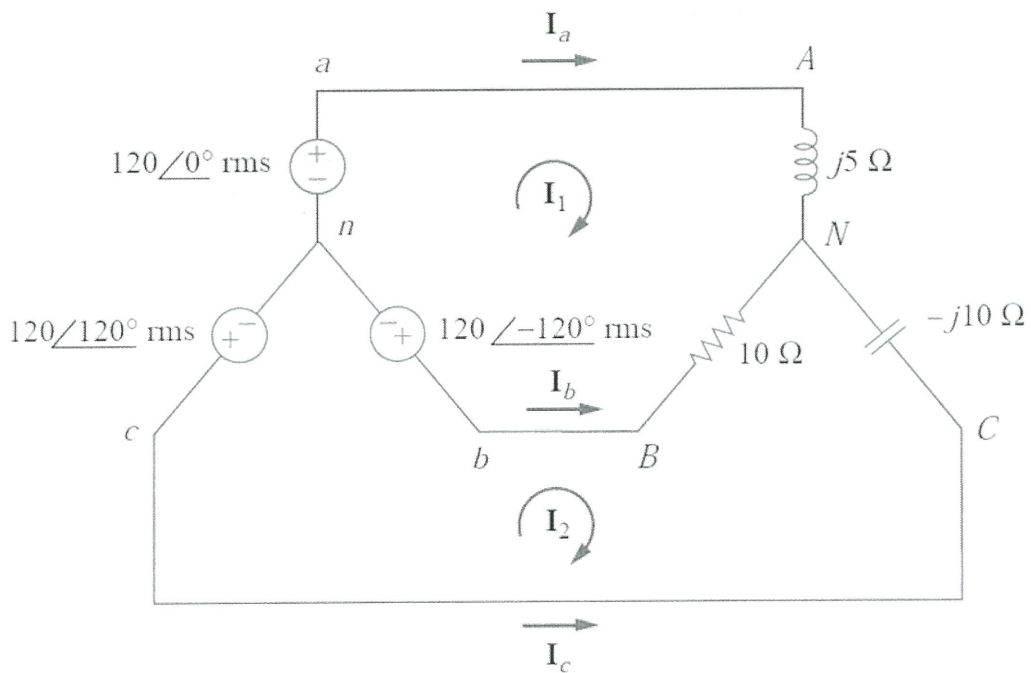


FIGURE Q5

FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND/BNF
 COURSE CODE: BNR10303

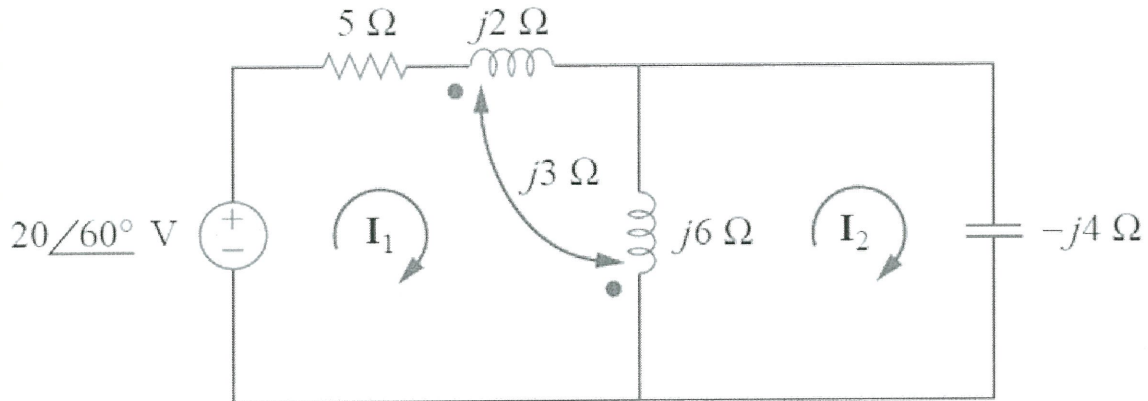


FIGURE Q6(a)

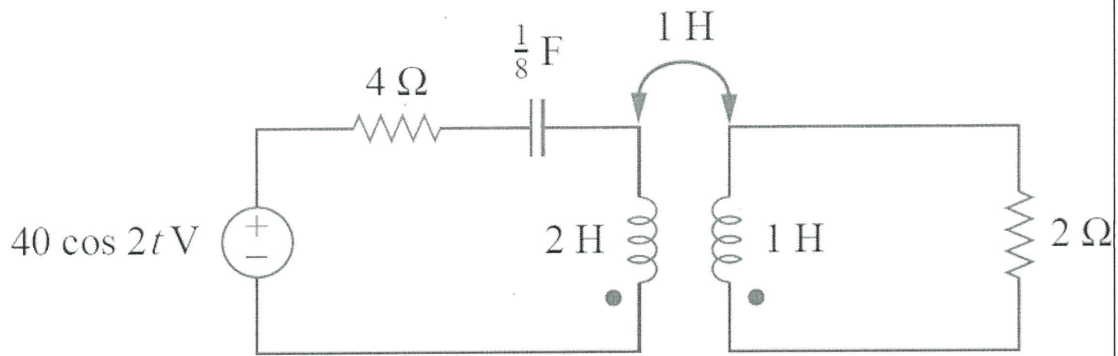


FIGURE Q6(b)


FINAL EXAMINATION

SEMESTER/SESSION: SEM II/2013/2014
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND/BNF
 COURSE CODE: BNR10303

APPENDIX

Chapter 1

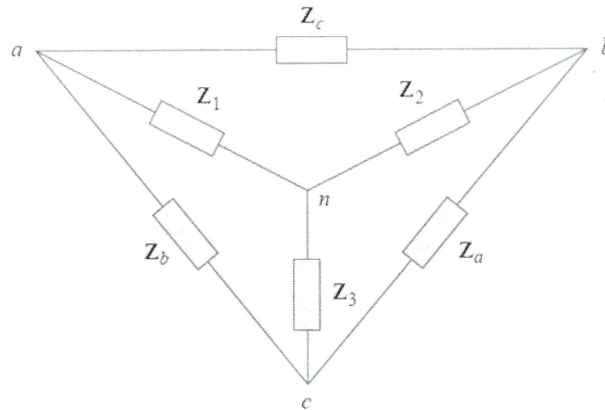

Y – Delta
Conversion

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

Delta – Y
Conversion

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014

PROGRAMME : 1 BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

APPENDIX

A general expression for the sinusoid

$$\text{Frequency: } f = \frac{1}{T} \text{ Hz}$$

$$\text{Angular frequency: } \omega = 2\pi f \text{ Hz}$$

Trigonometric identities

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

Mathematic operation of complex number

$$\text{Addition: } z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$\text{Subtraction: } z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

$$\text{Multiplication: } z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$$

$$\text{Division: } \frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$$

$$\text{Reciprocal: } \frac{1}{z} = \frac{1}{r} \angle -\phi$$

$$\text{Square root: } \sqrt{z} = \sqrt{r} \angle \phi/2$$

$$\text{Complex conjugate: } z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

$$\text{Euler's identity: } e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND/BNF
 COURSE CODE : BNR 10303

APPENDIX

Summary of voltage-current relationship		
Element	Time domain	Frequency domain
R	$v = Ri$	$V = RI$
L	$v = L \frac{di}{dt}$	$V = j\omega LI$
C	$i = C \frac{dv}{dt}$	$V = \frac{I}{j\omega C}$

Impedances and admittances of passive elements		
Element	Impedance	Admittance
R	$Z = R$	$Y = \frac{1}{R}$
L	$Z = j\omega L$	$Y = \frac{1}{j\omega L}$
C	$Z = \frac{1}{j\omega C}$	$Y = j\omega C$

Relationship between differential, integral operation in phasor listed as follow:

$$v(t) \rightarrow V = V \angle \phi$$

$$\frac{dv}{dt} \rightarrow j\omega V$$

$$\int v dt \rightarrow \frac{V}{j\omega}$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014

PROGRAMME : 1 BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

APPENDIX


Chapter 2

Superposition Theorem


When a circuit has sources operating at different frequencies,

- *The separate phasor circuit for each frequency must be solved independently,*
- *The total response is the sum of time-domain responses of all the individual phasor circuits.*

Thevenin and Norton Equivalent Circuits

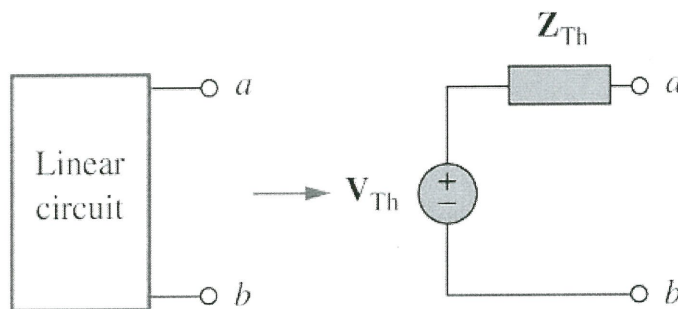

Thevenin transform

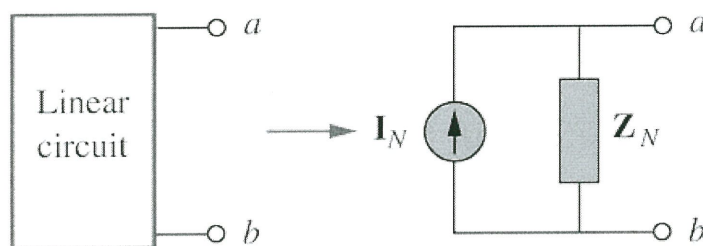

Norton transform

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014


PROGRAMME : I BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

APPENDIX

Source Transformation

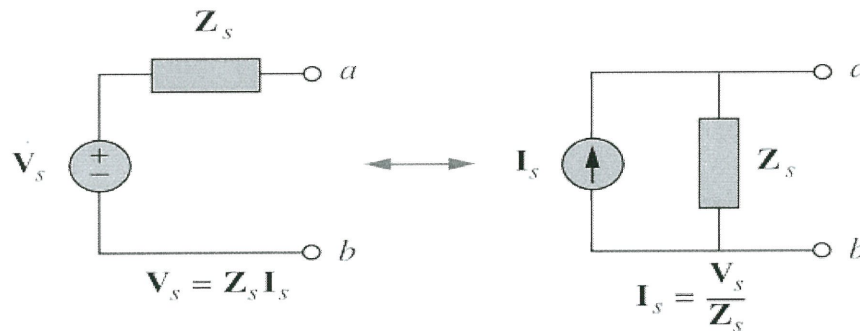

Chapter 3

Average Power:
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

Load Impedance:
$$Z_L = Z_{TH} = R_{TH} + jX_{TH}$$

$$Z_{TH}^* = R_{TH} - jX_{TH}$$

Maximum Average Power:
$$P_{\max} = \frac{|V_{TH}|^2}{8 R_{TH}}$$

If the load is purely real:
$$R_L = \sqrt{R_{TH}^2 + X_{TH}^2} = |Z_{TH}|$$

Effective Current:
$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} = I_{\text{rms}}$$

The rms value of a sinusoid $i(t) = I_m \cos(\omega t)$ is given by:
$$I_{\text{rms}}^2 = \frac{I_m}{\sqrt{2}}$$

The average power can be written in terms of the rms values:

$$I_{\text{eff}} = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014
 COURSE NAME : ELECTRICAL PRINCIPLES II

PROGRAMME : 1 BND/BNF
 COURSE CODE : BNR 10303

APPENDIX


Apparent Power and Power Factor:

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i) = S \cos(\theta_v - \theta_i)$$



Apparent Power, S Power Factor, pf

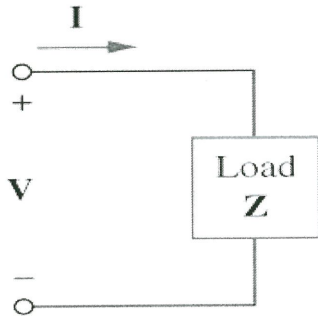Complex power S is the product of the voltage and the complex conjugate of the current:



$$\mathbf{V} = V_m \angle \theta_v \quad \mathbf{I} = I_m \angle \theta_i$$

$$\frac{1}{2} \mathbf{V} \mathbf{I}^* = V_{\text{rms}} I_{\text{rms}} \angle \theta_v - \theta_i$$

$$S = \underbrace{V_{\text{rms}} I_{\text{rms}} \cos(\theta_v - \theta_i)}_P + j \underbrace{V_{\text{rms}} I_{\text{rms}} \sin(\theta_v - \theta_i)}_Q$$

$$S = P + jQ$$

P: is the average power in watts delivered to a load and it is the only useful power.

Q: is the reactive power exchange between the source and the reactive part of the load. It is measured in VAR.

- $Q = 0$ for *resistive loads* (unity pf).
- $Q < 0$ for *capacitive loads* (leading pf).
- $Q > 0$ for *inductive loads* (lagging pf).

Power Absorbed: $P = I_{\text{rms}}^2 R = \frac{V_{\text{rms}}^2}{R}$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014

PROGRAMME : 1 BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

APPENDIX

Conservation of AC Power : $\bar{S} = \frac{1}{2} \bar{V} \bar{I}^* = \frac{1}{2} \bar{V} (\bar{I}_1^* + \bar{I}_2^*) = \frac{1}{2} \bar{V} \bar{I}_1^* + \frac{1}{2} \bar{V} \bar{I}_2^* = \bar{S}_1 + \bar{S}_2$

Power Factor Correction : $C = \frac{Q_c}{\omega V_{\text{rms}}^2} = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2}$

$Q_c = Q_1 - Q_2$, $Q_1 = S_1 \sin \Theta_1 = P \tan \Theta_1$, $Q_2 = P \tan \Theta_2$

Chapter 4

The voltages can be expressed in phasor form as

$$V_{an} = 200 \angle 10^\circ V$$

$$V_{bn} = 200 \angle -230^\circ V$$

$$V_{cn} = 200 \angle -110^\circ V$$

A balanced Y-Y system

$$V_L = \sqrt{3} V_p, \text{ where}$$

$$V_p = |V_{an}| = |V_{bn}| = |V_{cn}|$$

$$V_L = |V_{ab}| = |V_{bc}| = |V_{ca}|$$

A balanced Y-Δ system

$$I_L = \sqrt{3} I_p, \text{ where}$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

Power loss in a single-phase system: $P'_{\text{loss}} = 2R \frac{P_L^2}{V_L^2}$

Power loss in a three-phase system: $P'_{\text{loss}} = R' \frac{P_L^2}{V_L^2}$

Unbalanced Three-Phase Systems:

$$I_a = \frac{V_{AN}}{Z_A}, I_b = \frac{V_{BN}}{Z_B}, I_c = \frac{V_{CN}}{Z_C},$$

$$I_n = -(I_a + I_b + I_c)$$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014

PROGRAMME : 1 BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

APPENDIX

Summary of phase and line voltages/currents for balanced three-phase system

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ <p style="text-align: center;">Same as line currents</p>	$V_{ab} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{ab} \angle +120^\circ$ $I_a = \frac{V_{an}}{Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Y-Δ	$V_{an} = V_p \angle 0^\circ$ $V_{bn} = V_p \angle -120^\circ$ $V_{cn} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{AB}}{Z_\Delta}$ $I_{BC} = \frac{V_{BC}}{Z_\Delta}$ $I_{CA} = \frac{V_{CA}}{Z_\Delta}$	$V_{ab} = V_{AB} = \sqrt{3}V_p \angle 30^\circ$ $V_{bc} = V_{BC} = V_{ab} \angle -120^\circ$ $V_{ca} = V_{CA} = V_{ab} \angle +120^\circ$ $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
Δ-Δ	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ $I_{AB} = \frac{V_{ab}}{Z_\Delta}$ $I_{BC} = \frac{V_{bc}}{Z_\Delta}$ $I_{CA} = \frac{V_{ca}}{Z_\Delta}$	<p style="text-align: center;">Same as phase voltages</p> $I_a = I_{AB} \sqrt{3} \angle -30^\circ$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014

PROGRAMME : 1 BND/BNF


COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303


APPENDIX

Δ -Y	$V_{ab} = V_p \angle 0^\circ$ $V_{bc} = V_p \angle -120^\circ$ $V_{ca} = V_p \angle +120^\circ$ <p style="text-align: center;">Same as line currents</p>	<p style="text-align: center;">Same as phase voltages</p> $I_a = \frac{V_p \angle -30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a \angle -120^\circ$ $I_c = I_a \angle +120^\circ$
-------------	--	--

Chapter 5

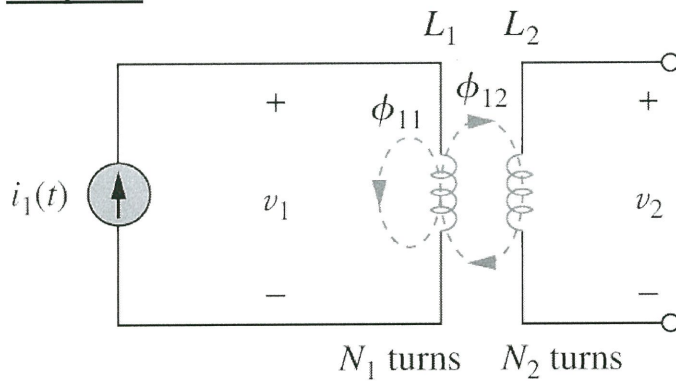

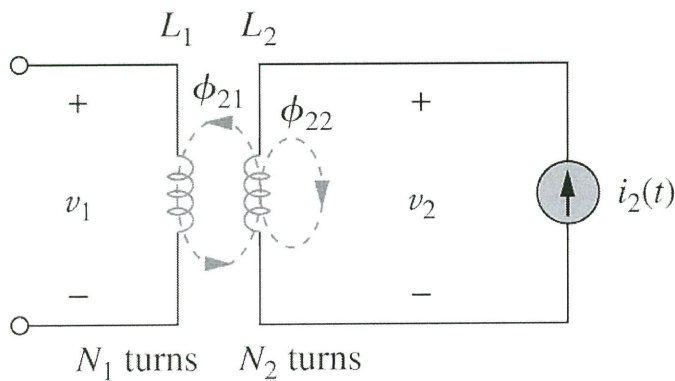The open-circuit mutual voltage across coil 2: $v_2 = M_{21} \frac{di_1}{dt}$



The open-circuit mutual voltage across coil 1: $v_1 = M_{12} \frac{di_2}{dt}$

FINAL EXAMINATION

SEMESTER/SESSION : II / 2013/2014

PROGRAMME : 1 BND/BNF

COURSE NAME : ELECTRICAL PRINCIPLES II

COURSE CODE : BNR 10303

APPENDIX**Series-Aiding Connection:** $L = L_1 + L_2 + 2M$ **Series-Opposing Connection** $L = L_1 + L_2 - 2M$ **Coefficient of Coupling k :** $M = k\sqrt{L_1L_2}$ **Instantaneous Energy Stored:** $w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 \pm MI_1I_2$