



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

FINAL EXAMINATION SEMESTER I SESSION 2010/2011

COURSE NAME : BASIC ELECTRIC AND ELECTRONICS

COURSE CODE : DKE 3273

PROGRAMME : 3 DDT

EXAMINATION DATE : NOVEMBER/DECEMBER 2010

DURATION : 3 HOURS

INSTRUCTIONS : ANSWER FIVE (5) QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF TEN (10) PAGES

Q1 Refer to Figure Q1, show all the calculation to find the value for;

- a) Total resistance R_T (4 marks)
- b) The voltage drop across resistance R_2 (V_{R2}), resistance R_3 (V_{R3}), resistance R_4 (V_{R4}) and resistance R_6 (V_{R6}) (8 marks)
- c) The current flow through resistance R_2 (I_{R2}), resistance R_3 (I_{R3}), resistance R_4 (I_{R4}) and resistance R_6 (I_{R6}) (8 marks)

- Q2** a) An electromagnet produces a magnetic flux of $900\mu\text{Wb}$. Determine the magnetic field lines. (10 marks)
- b) Calculate the flux density, in gauss units for a flux, Φ , of $200\mu\text{Wb}$ in a cross sectional area of $5 \times 10^{-4} \text{ m}^2$. (10marks)

- Q3** a) Determine the amount of charge, Q , stored by a capacitor if
- i) $C = 10\mu\text{F}$ and $V = 5\text{V}$
 ii) $C = 680 \text{ pF}$ and $V = 200\text{V}$
 iii) $C = 0.22 \mu\text{F}$ and $V = 50 \text{ V}$ (6 marks)
- b) Determine the voltage, V , across a capacitor if
- i) $Q = 2.5 \mu\text{C}$ and $C = 0.01 \mu\text{F}$
 ii) $Q = 10 \text{ mC}$ and $C = 1000 \mu\text{F}$
 iii) $Q = 188 \text{ nC}$ and $C = 0.0047 \mu\text{F}$ (6 marks)
- c) Calculate the capacitance, C , of a capacitor for each set of physical characteristics listed below;
- i) $A = 0.1 \text{ cm}^2$, $d = 0.005 \text{ cm}$, $K\epsilon = 1$
 ii) $A = 1 \text{ cm}^2$, $d = 5 \times 10^{-6} \text{ cm}$, $K\epsilon = 6$ (8 marks)

- Q4** Refer to Figure Q4, assume a charging current of 2.4 mA flows for 1 ms, determine;
- a) Total equivalent capacitance, C_{EQ} (4 marks)
 - b) The charge stored each capacitor C_1 , (Q_{C1}), C_2 (Q_{C2}) and C_3 (Q_{C3}) (6 marks)
 - c) The voltage across each capacitor C_1 (V_{C1}), C_2 (V_{C2}) and C_3 (V_{C3}) (6 marks)
 - d) The total charge, Q_T stored by the equivalent capacitor, C_{EQ} (4 marks)
- Q5** Refer to Figure Q5, calculate;
- a) The secondary voltage, V_S (4 marks)
 - b) The secondary current, I_S (4 marks)
 - c) The secondary power, P_S (4 marks)
 - d) The primary power, P_P (4 marks)
 - e) The primary current, I_P (4 marks)
- Q6** Refer to Figure Q6, determine;
- a) The total equivalent resistance, R_{EQ} (4 marks)
 - b) The branch currents, I_1 and I_2 (4 marks)
 - c) The total current, I_T (4 marks)
 - d) The power dissipated at each resistors, P_1 and P_2 (4 marks)
 - e) The total power supplied by the source, P_T (4 marks)

- Q7** (a) Figure Q7(a) shows a transistor biasing circuit;
- i) calculate collector saturation current ($I_{C(sat)}$) (1 mark)
 - ii) calculate collector-emitter off voltage ($V_{CE(off)}$) (1 mark)
 - iii) calculate current at the Q-point (I_{CQ}) (3 marks)
 - iv) calculate voltage at the Q-point (V_{CEQ}) (1 mark)
 - v) draw the DC load line for the transistor circuit (4 marks)
- (b) Figure Q7(b) shows a n-channel JFET circuit. What is the value of R_S that will provide drain current (I_D) of approximately one-half I_{DSS} ? (2 marks)
- (c) Referring to Figure Q7(b), for the values of R_S calculated in question Q7(b), determine:
- i) gate voltage (V_G) (2 marks)
 - ii) source voltage (V_S) (2 marks)
 - iii) gate-source voltage (V_{GS}) (2 marks)
 - iv) drain voltage (V_D) (2 marks)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT
COURSE CODE : DKE3273

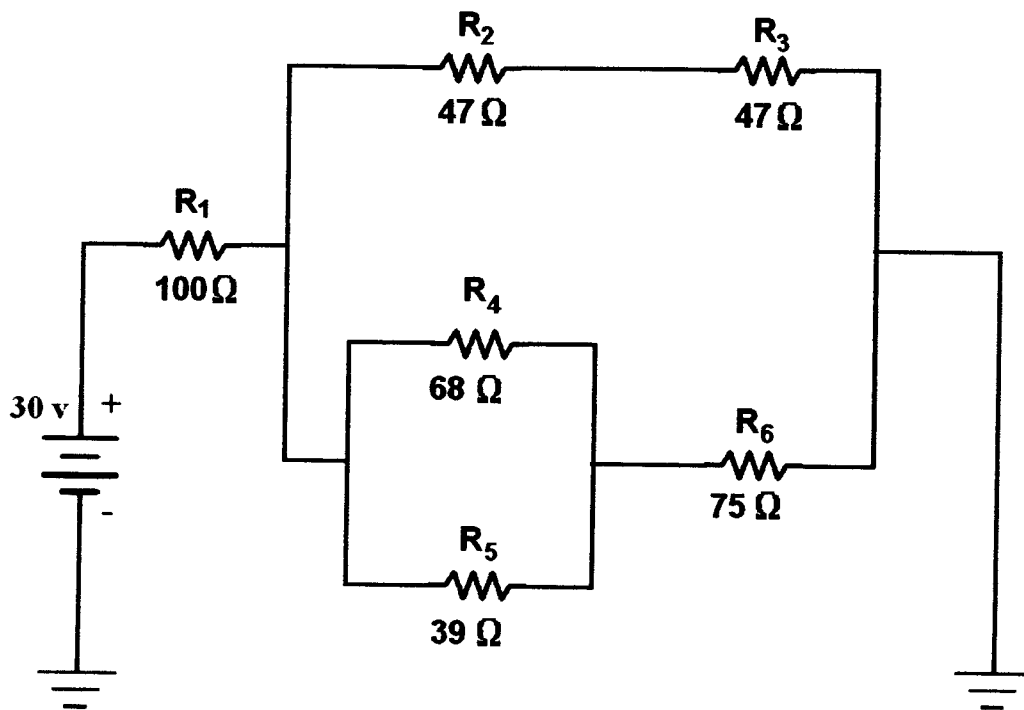


Figure Q1

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT
COURSE CODE : DKE3273

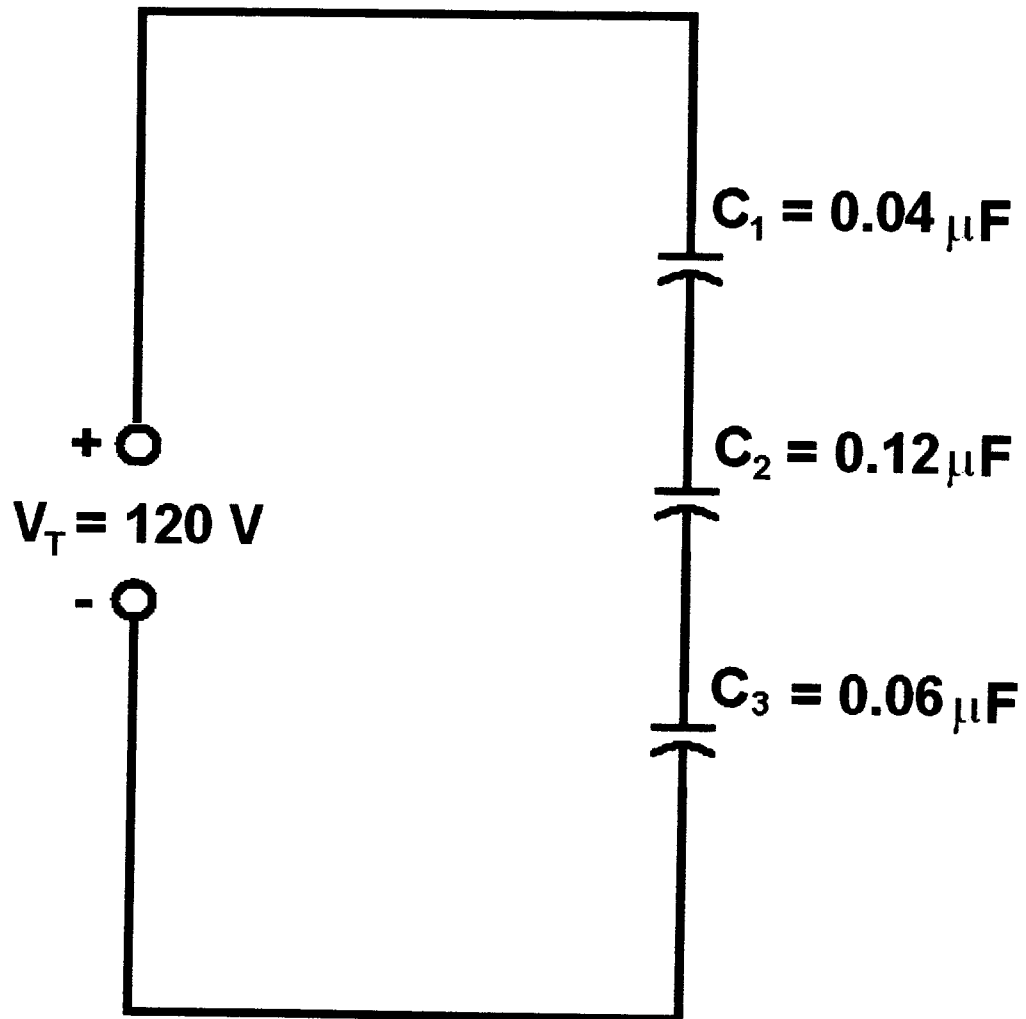


Figure Q4

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT
COURSE CODE : DKE3273

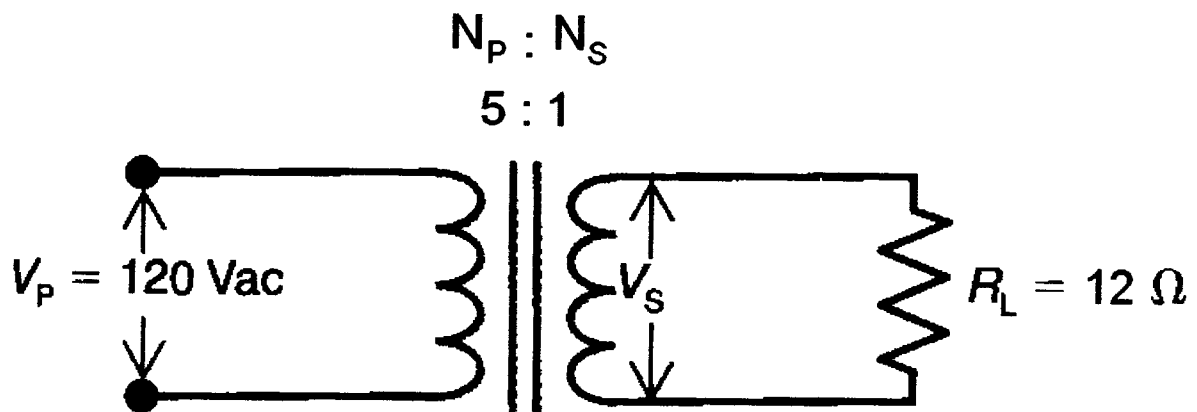


Figure Q5

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2010/2011
COURSE : BASIC ELECTRIC AND
ELECTRONICS

PROGRAMME : 3 DDT
COURSE CODE : DKE3273

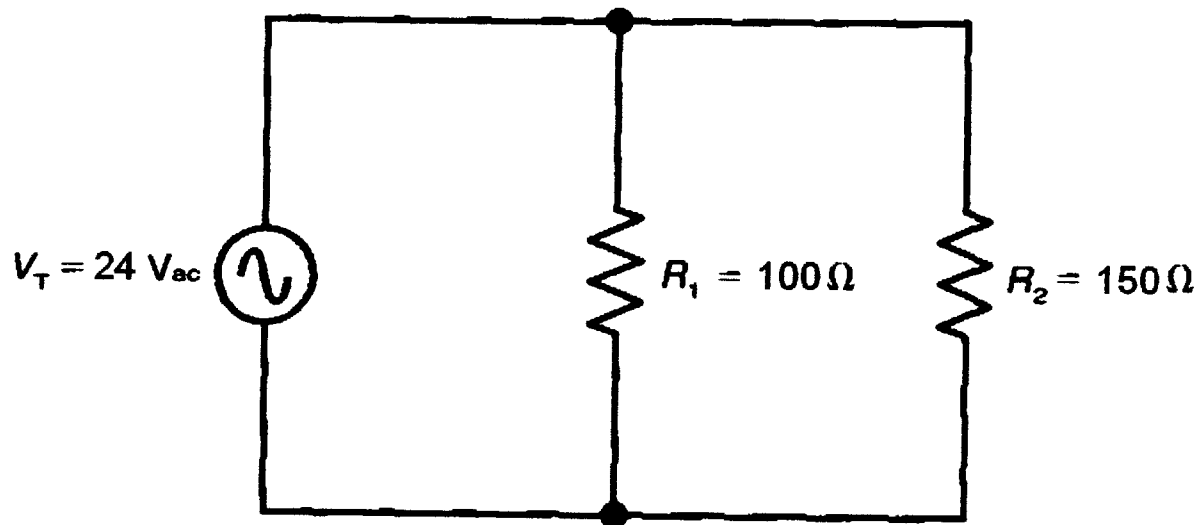


Figure Q6

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2010/2011
 COURSE : BASIC ELECTRIC AND
 ELECTRONICS

PROGRAMME : 3 DDT
 COURSE CODE : DKE3273

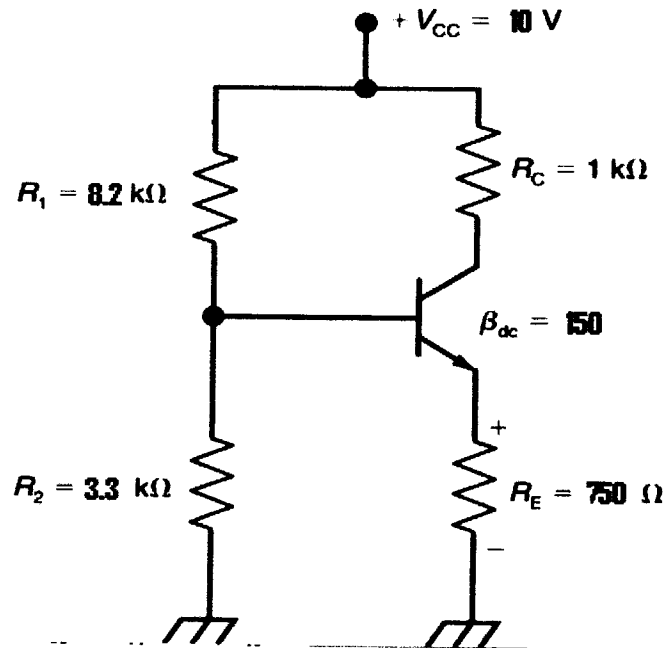


Figure Q7 (a)

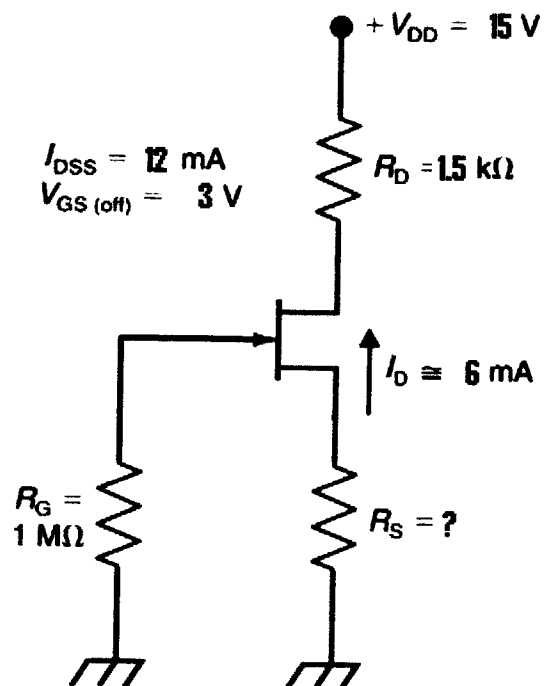













Figure Q7 (b)

References :

Band Color	Digit	Multiplier	Tolerance
Black	 0	1	---
Brown	 1	10	$\pm 1\%$
Red	 2	100	$\pm 2\%$
Orange	 3	1,000	$\pm 3\%$
Yellow	4	10,000	$\pm 4\%$
Green	 5	100,000	---
Blue	 6	1,000,000	---
Violet	 7	10,000,000	---
Gray	 8	100,000,000	---
White	 9	---	---
Gold	 ---	0.1	$\pm 5\%$
Silver	 ---	0.01	$\pm 10\%$
None	---	---	$\pm 20\%$