



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2015/2016**

COURSE NAME : POWER ELECTRONIC CONVERTERS

COURSE CODE : BNR 33603

PROGRAMME : 3 BNE

EXAMINATION DATE : DECEMBER 2015 / JANUARY 2015

DURATION : 3 HOURS

INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

- Q1** (a) State **THREE (3)** advantages of power diodes.
(3 marks)
- (b) The thyristors can be subdivided into different types. Justify minimum **FOUR (4)** types of thyristor.
(4 marks)
- (c) Explain the differences between power electronic switches and mechanical switches.
(4 marks)
- (d) There are **THREE (3)** methods of switching-off the silicon controlled rectifier, SCR. Justify all of the methods.
(3 marks)
- (e) The RC network across the transistor is known as a snubber circuit. As an electronics experts, design a static and dynamic equalisation circuit for series connection of a SCR with snubber circuit.
(11 marks)
- Q2** (a) The transistor is a current-driven device. Draw a structure and symbol of bipolar junction transistor (BJT) with detail labelling diagram.
(4 marks)
- (b) Based on the power transistor application, sketch and explain the purpose of Darlington pair transistor.
(5 marks)
- (c) Describe briefly about an Insulated Gate Bipolar Transistor (IGBT) and the operating principles.
(8 marks)

- (d) As an experienced technologist in power electronics, design a power efficient of electrical isolation driver circuit for the case of a power BJT half-bridge converter.

(8 marks)

- Q3** (a) The battery voltage in **FIGURE Q3(a)** is $E = 12$ V and its capacity is 100 Wh. The average charging current should be $I_{dc} = 5$ A. The primary input voltage is $V_p = 120$ V, 60 Hz, and the transformer has a turn ratio of $n = 2:1$.

Calculate:

- (i) Conduction angle, δ of the diode.
- (ii) Current-limiting resistance, R .
- (iii) Power rating, P_R of R .
- (iv) Charging time, h_0 in hours.
- (v) Rectifier efficiency, η .
- (vi) Peak inverse voltage, PIV of the diode.

(13 marks)

- (b) A three-phase bridge rectifier of **FIGURE Q3(b)**, has a purely resistive load of R .

Determine:

- (i) Efficiency, η .
- (ii) Form factor (FF).
- (iii) Ripple factor (RF).
- (iv) Transformer utilization factor (TUF).
- (v) Peak inverse (or reverse) voltage (PIV) of each diode.

(12 marks)

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2015/2016

PROGRAMME : 3 BNE

COURSE NAME : POWER ELECTRONIC CONVERTERS

COURSE CODE : BNR 33603

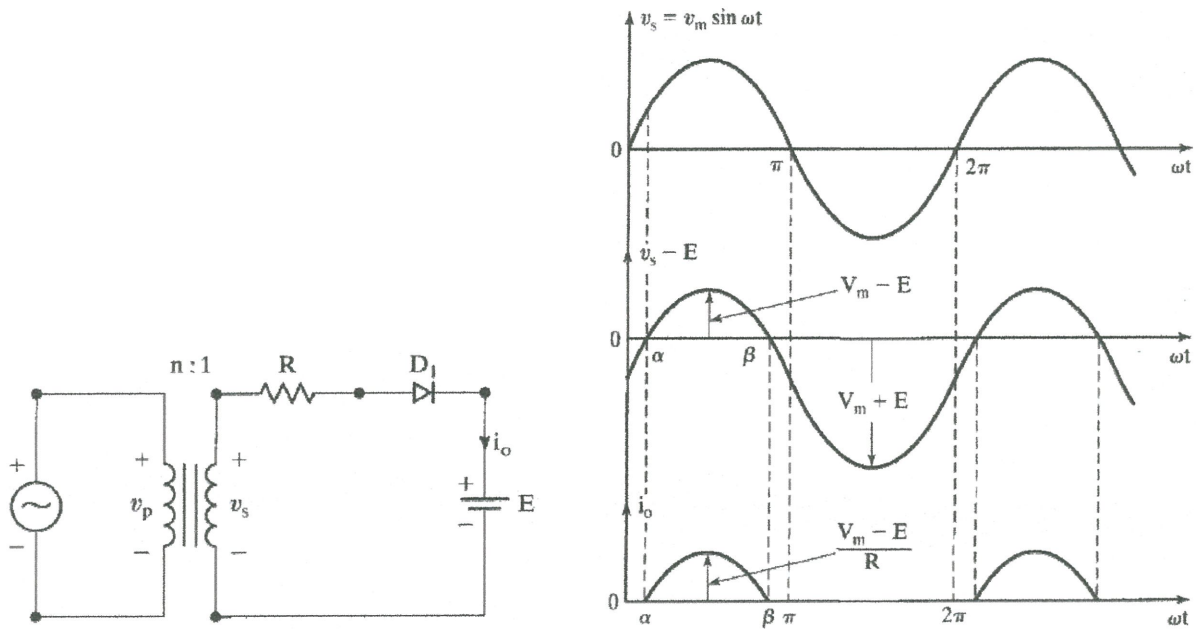


FIGURE Q3(a)

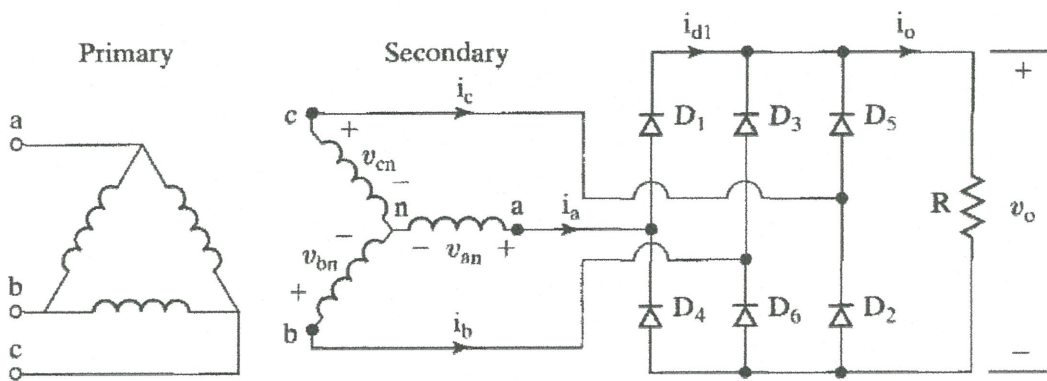


FIGURE Q3(b)

Q4 (a) Draw a block diagram of an inverter with proper notation.

(2 marks)

(b) Show the block diagram of voltage source inverter and current source inverter.

(5 marks)

(c) The single-phase half-bridge inverter has a resistive load of $R = 2.4 \Omega$ and the DC input voltage is 48V.

Find:

- (i) Efficiency, η .
- (ii) Form factor (FF).
- (iii) Ripple factor (RF).
- (iv) Transformer utilization factor (TUF).
- (v) Peak inverse (or reverse) voltage (PIV) of each diode.

(8 marks)

(d) The full-bridge inverter with DC input voltage of 100V, load resistor and inductor of 10Ω and 25mH respectively are operated at 60 Hz frequency.

Compute:

- (i) Amplitude of the Fourier series terms for the square-wave load voltage.
- (ii) Amplitude of the Fourier series terms for load current.
- (iii) Power absorbed by the load.
- (iv) Total harmonic distortion (THD) of the load voltage and load current for square-wave inverter.

(10 marks)

Q5 (a) Describe about DC-DC converter with suitable definition and application.

(3 marks)

(b) The buck DC-DC converter of **FIGURE Q5(b)**, has the following parameters:

$$\begin{aligned}
 V_s &= 50\text{V}; \\
 D &= 0.4; \\
 L &= 400\mu\text{H}; \\
 C &= 100\mu\text{F}; \\
 R &= 20\Omega; \\
 f &= 20\text{kHz}.
 \end{aligned}$$

Assuming ideal components, calculate:

- (i) Output voltage, V_o .
- (ii) Maximum and minimum inductor current.
- (iii) Output voltage ripple.

(10 marks)

(c) The Buck-Boost circuit of **FIGURE Q5(c)**, has the following parameters:

$$\begin{aligned}
 V_s &= 24\text{V}; \\
 D &= 0.4; \\
 L &= 100\mu\text{H}; \\
 C &= 400\mu\text{F}; \\
 R &= 5\Omega; \\
 f &= 20\text{kHz}.
 \end{aligned}$$

Determine:

- (i) Output voltage, V_o .
- (ii) Inductor current.
- (iii) Output voltage ripple.

(12 marks)

Q6 (a) State **THREE (3)** major applications of AC voltage controllers.

(3 marks)

(b) Discuss briefly about AC-AC controller based on **FIGURE Q6(b)**.

(4 marks)

- (c) A single phase 120V AC source control power to a 5Ω resistive load using integral cycle control.

Determine:

- (i) Average value of output current
- (ii) Maximum switch current
- (iii) Maximum power produced
- (iv) Duty cycle and the value of T_{on} to produce 1kW power
- (v) Power factor for part (iv)

(6 marks)

- (d) A 120V source control power to a 5Ω resistive load using a phase control switch. If the load power required is 1 kW.

Calculate:

- (i) Maximum load current.
- (ii) RMS value of load current.
- (iii) Delay angle α .
- (iv) RMS value of switch current if the switch is triac.
- (v) Average current in each of the two SCRs .
- (vi) Peak reverse voltage rating of the switch.
- (vii) Power factor.

(12 marks)

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2015/2016

PROGRAMME : 3 BNE

COURSE NAME : POWER ELECTRONIC CONVERTERS

COURSE CODE : BNR 33603

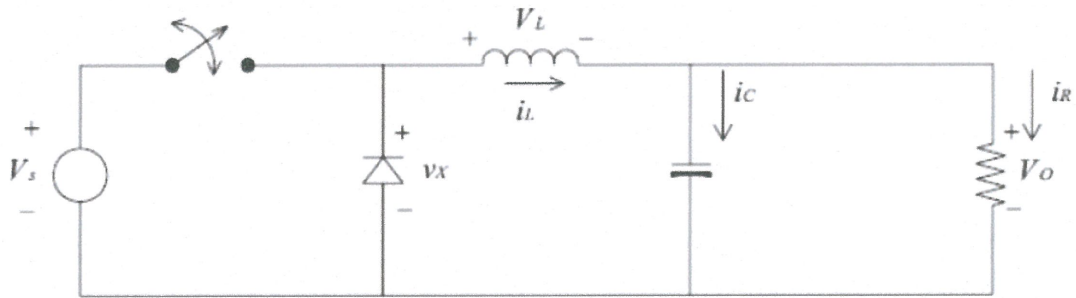


FIGURE Q5(b)

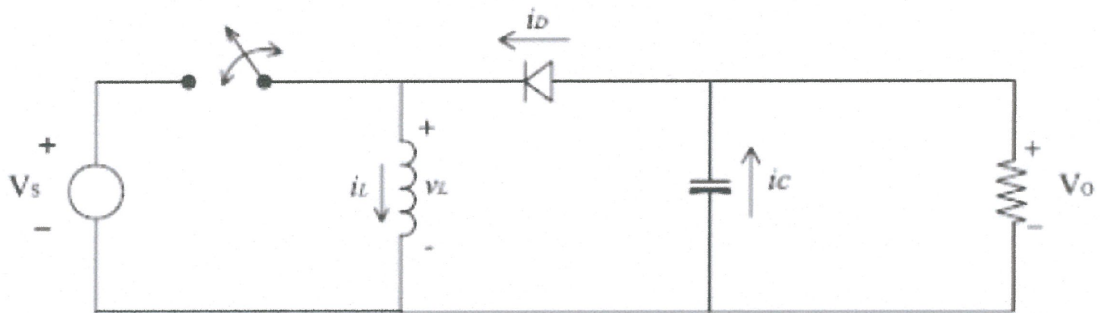


FIGURE Q5(c)


FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2015/2016


PROGRAMME : 3 BNE

COURSE NAME : POWER ELECTRONIC CONVERTERS

COURSE CODE : BNR 33603

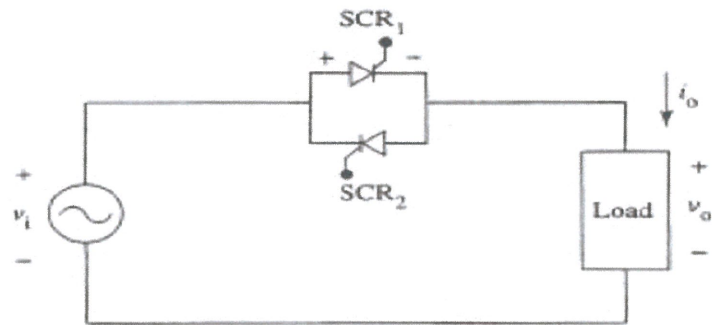

(a)

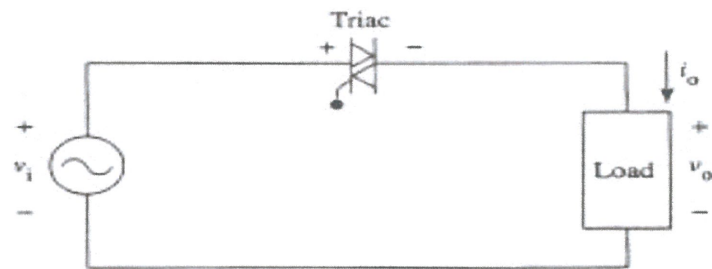

(b)

FIGURE Q6(b)