

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER II
SESSION 2015/2016**

COURSE NAME : ELECTRICAL TECHNOLOGY
COURSE CODE : BNB 30403
PROGRAMME CODE : BNB
EXAMINATION DATE : JUNE / JULY 2016
DURATION : 3 HOURS
INSTRUCTION : ANSWERS ALL QUESTIONS

THIS QUESTION PAPER CONSISTS OF **SIX (6)** PAGES

CONFIDENTIAL

- Q1**
- (a) Give an example of active and passive elements. (2 marks)
- (b) A 30 V source is applied to a resistor with 4-colour bands red, black, brown, and silver. Calculate the minimum and maximum currents based on the tolerance of the resistor. (3 marks)
- (c) Consider the circuit shown in **Figure Q1(c)**. Determine v_1 , v_2 and v_3 by using nodal analysis. (4 marks)
- (d) Let current $I = 2t$ A flow into a capacitor for 5 seconds. Determine:
- (i) The total charge, Q , in Coulomb. (3 marks)
- (ii) The capacitance if voltage across the capacitor is 5 V. (1 marks)
- (e) Draw a schematic diagram of the single phase distribution unit. (3 marks)
- (f) A ring circuit is the main power circuit found in some homes to feed sockets and lighting points. Draw a schematic diagram for 5 units 13 A switched socket outlets in ring connection. (4 marks)
- Q2**
- (a) Describe the differences between Kirchhoff Voltage Law and Kirchhoff Current Law with the aid of diagram/figures. (4 marks)
- (b) A circuit consists of three resistances 12 Ω , 18 Ω and 36 Ω respectively, joined in parallel, is connected in series with a fourth resistance of unknown value. The whole circuit is supplied at 60 V and it is found that the voltage of the 12 Ω resistance is 30 V.
- (i) Draw the circuit diagram of the configuration and label its parameter accordingly. (2 marks)
- (ii) Determine the value of the fourth resistance. (2 marks)
- (iii) Calculate the total power dissipated in the circuit.

(2 marks)

- (c) Five lamps having resistance 185Ω , 205Ω , 215Ω , 195Ω and 200Ω respectively are operated **in series** from the main supply. A voltmeter is connected to the 200Ω lamp and reads 85 V .
- (i) Calculate the supply voltage of the circuit. (2 marks)
- (ii) Obtain the total power consumed by the lamps. (2 marks)
- (d) Explain the difference between step-up and step-down transformer. (2 marks)
- (e) An ideal transformer with the primary terminal connected to a 240 V mains, supplies a 12 V , 150 W lamp. Calculate:
- (i) The transformer turns ratio. (1 marks)
- (ii) The current taken from the supply. (3 marks)

- Q3** (a) Name and briefly explain the most popular methods of electrical circuit protection. (4 marks)
- (b) In a modern home, each wiring circuit is protected by a circuit breaker rather than a wire fuse. Give **TWO (2)** advantages of a circuit breaker compared with a wire fuse. (3 marks)
- (c) The current in an AC circuit at any time, t seconds is given by the equation,

$$I = 120 \sin (100 \pi t + 0.36) \text{ A}$$

Find:

- (i) The peak value and the frequency. (2 marks)
- (ii) The value of the current when $t = 0 \text{ s}$. (2 marks)
- (iii) The value of the current when $t = 8 \text{ ms}$. (2 marks)
- (iv) The time when the current first reaches 60 A . (2 marks)

(d) Solve the following complex number and leaves the result in polar form.

(i) $\frac{15\angle 45^\circ}{3 - j4} + j2$ (2 marks)

(ii) $\frac{8\angle -20^\circ}{(2 + j)(3 - j4)} + \frac{10}{5 + j12}$ (3 marks)

- Q4** (a) State **FOUR (4)** possible connections for three phase system. (4 marks)
- (b) Explain briefly **TWO (2)** losses that occur in a transformer. (4 marks)
- (c) A certain type of transformer has a primary resistance of 940Ω and a primary current of 5 A . The secondary current is 90 A and the secondary voltage is 240 V . Determine the efficiency of the transformer. (4 marks)
- (d) Calculate the I_1 , I_2 and I_3 in the network shown in **Figure Q4(d)** using mesh analysis. (4 marks)
- (e) Describe the differences between Thevenin's Theorem and Norton's Theorem with the aid of diagram/figures. (4 marks)
- Q5** (a) Insulation layer is a critical part of a power cable. List **FOUR (4)** insulation types used to protect the cable core. (4 marks)
- (b) A 4 mm^2 p.v.c. sheathed circuit feeds a 6 kW water heater. The volt drop figure for 4 mm^2 two-core cable is 11 mV/A/m and has a length of 16 m . Permissible voltage drop is 4% and voltage supply is 240 V . Find the voltage drop and determines whether the cable meets the requirement. (6 marks)
- (c) Redraw the circuit in **Figure Q5(c)** into a circuit with an equivalent impedance Z_{total} . Then, evaluate and present I_{total} in polar form. (10 marks)

-END OF QUESTIONS -

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2015/2016
 COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BNB
 COURSE CODE : BNB 30403

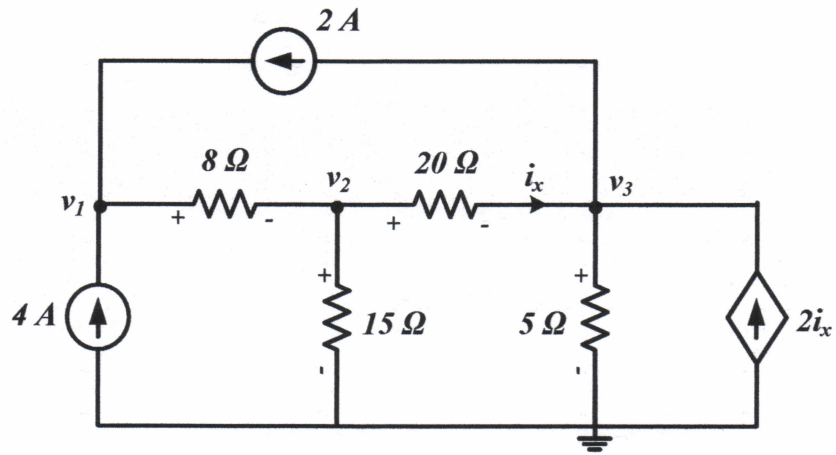


Figure Q1(c)

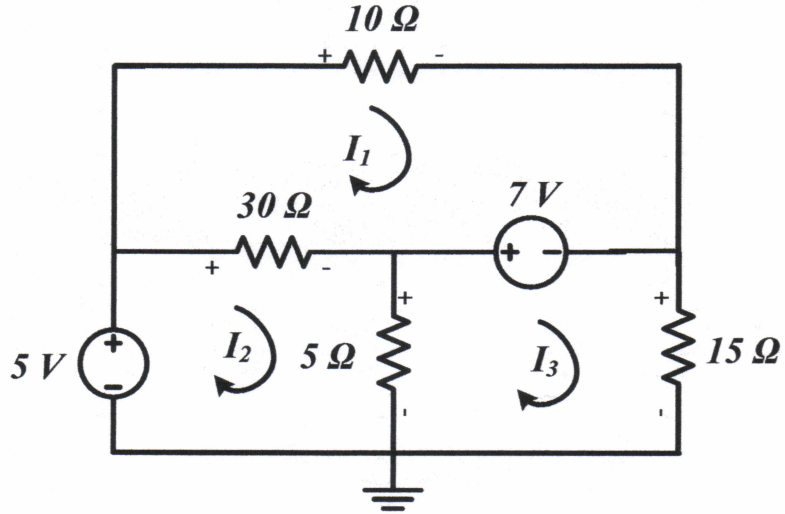


Figure Q4(d)

FINAL EXAMINATION

SEMESTER / SESSION : SEM II / 2015/2016
COURSE NAME : ELECTRICAL TECHNOLOGY

PROGRAMME CODE : BNB
COURSE CODE : BNB 30403

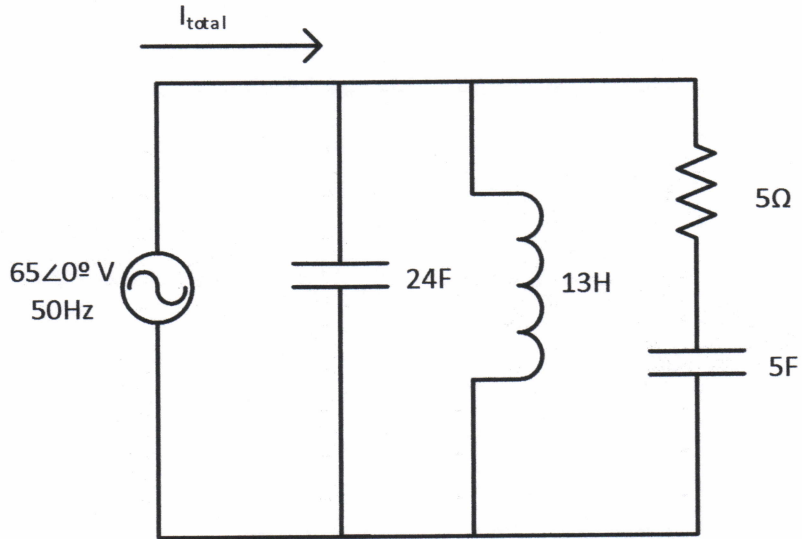


Figure Q5(c)

Faint, illegible text at the bottom right of the page, possibly a watermark or bleed-through.