

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION
SEMESTER I
SESSION 2016/2017**

COURSE NAME : DIGITAL ELECTRONICS
COURSE CODE : BNR 25402
PROGRAMME CODE : BND / BNF
EXAMINATION DATE : DECEMBER 2016 / JANUARY 2017
DURATION : 2 HOURS 30 MINUTES
INSTRUCTION : ANSWER **FOUR (4)** QUESTIONS ONLY

TERBUKA

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

- Q1** (a) Convert the binary number 101011011_2 to:
- (i) octal (1 mark)
 - (ii) hexadecimal (1 mark)
 - (iii) decimal (1 mark)
 - (iv) BCD (1 mark)

- (b) Perform the following arithmetic operations. Show all steps.
- (i) $58 - 63$ using 2's complement. (2 marks)
 - (ii) $A1_{\text{hex}} - 72_{\text{hex}}$ using 2's complement. (2 marks)

- (c) Write the next four numbers in this hexadecimal counting sequence:
 $8FD, 8FE, \underline{\hspace{1cm}}, \underline{\hspace{1cm}}, \underline{\hspace{1cm}}, \underline{\hspace{1cm}}$. (2 marks)

- (d) Use Karnaugh map to simplify the following function.

$$f(A, B, C, D) = \sum(0,1,3,5,14,15) + d(4,7,11,13)$$

(5 marks)

- (e) (i) Simplify the following Boolean expression using Boolean algebra and verify the result using a Karnaugh map:

$$F = XY\bar{Z} + XY + X\bar{Y}Z$$

- (ii) Implement the simplified expression using NAND gates only. (6 marks)

TERBUKA

(4 marks)

- Q2** (a) For the circuit in **Figure Q2(a)**,

- (i) Write the Boolean Expression for outputs X, Y and Z. (3 marks)
- (ii) Obtain the truth table showing all inputs and outputs. (4 marks)

- (b) Waveforms A, B and C of **Figure Q2(b)** are applied to a logic circuit. The output waveform, F is as shown in **Figure Q2(b)**.
- (i) Obtain the truth table. (2 marks)
 - (ii) Write the logic expression for F. (2 marks)
 - (iii) Draw the logic circuit for function F. (2 marks)
- (c) From the truth table in **Table Q2(c)**.
- (i) Write the standard sum of product (SOP) expression for output F. (2 marks)
 - (ii) Write the standard product of sum (POS) expression for F (2 marks)
 - (iii) Use the K map to get the minimum sum of product (SOP) expression for F. (4 marks)
 - (iv) Implement the simplified expression of F with NAND gates only. (4 marks)

- Q3** (a) Build the truth table of a half-adder circuit showing all inputs and outputs (SUM and carry (C_0)). Write the expression for both outputs. (7 marks)
- (b) The following is the output expression for a Full Adder circuit. Illustrate how a full-adder can be implemented using 2 half-adders.

$$\text{SUM} = A \oplus B \oplus C_{in}$$

$$C_0 = C_{in} (A \oplus B) + AB$$

(6 marks)

- (c) Build the truth table for a full adder circuit showing all inputs and outputs (SUM and carry (C_0)).
- (i) Write the expression for both outputs in sum of minterms form. (7 marks)
 - (ii) Implement the full adder circuit using the 74138 IC shown in **Figure Q3(c)**. Label all inputs and outputs. (5 marks)



- Q4** (a) With the aid of truth tables, describe the differences between the following flip flops:
- (i) RS flip flop (3 marks)
 - (ii) JK flip flop (2 marks)
 - (iii) D flip flop (2 marks)
- (b) **Figure Q4(b)** shows a 7476 JK flip-flop and timing diagram showing 3 inputs: clock input (CLK), J and K. Assume that the two asynchronous inputs CLEAR and PRESET is high. Q is initially LOW. Draw the Q output waveform. (6 marks)
- (c) **Figure Q4(c)(i)** shows two flip flops connected together.
- (i) Sketch the output waveform for Q₀ and Q₁ in **Figure Q3(c)(ii)**. (5 marks)
 - (ii) Determine the output frequency at Q₁ if the input frequency (CLK) is 2 kHz. (3 marks)
 - (iii) Explain its operation (4 marks)
- Q5** (a) With the aid of diagrams, describe the following devices:
- (i) A decoder
 - (ii) A multiplexer (6 marks)
- (b) Given the following function: $F = \overline{X}\overline{Y} + \overline{Y}Z + XY\overline{Z}$
- (i) Represent F in sum of minterms. (Hint: use K-maps or truth table). (4 marks)
 - (ii) Implement F using the 3 x 8 decoder. (3 marks)
 - (iii) Implement F using a 8 x 1 multiplexer. (3 marks)

TERBUKA

- (c) State **TWO (2)** differences between synchronous and asynchronous counters. (4 marks)
- (d) Design a MOD 8 asynchronous counter using JK flip-flops.
- (i) Draw the circuit. (2½ marks)
- (ii) Determine the counting sequence. (2½ marks)
- Q6** (a) The 4-bit serial input register in **Figure Q6(a)** has 1011 (Q,R,S,T) stored in it and data inputs are low. Show the register operations for four clock transitions by doing the following:
- (i) Draw a table showing the state sequence (5 marks)
- (ii) Draw the timing diagram. (5 marks)
- (b) Briefly explain **TWO (2)** advantages of digital techniques over analog. Give **ONE (1)** major drawback of digital techniques. (4 marks)
- (c) Two conversion are necessary to interface real world, analog signals with a digital circuit. Name and describe briefly the function of the two circuits used. (3 marks)
- (d) The circuit in **Figure Q6(d)(i)** is used in digital and analog interface.
- (i) State the function of this circuit.
- (ii) Determine the output V_{out} and record its value in **Table Q6(d)** if the 4-bit numbers D_3, D_2, D_1 and D_0 are applied to the inputs. (8 marks)

- END OF QUESTIONS -

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : BND/BNF
 COURSE CODE: BNR 25402

 


Figure Q2(a)

 


Figure Q2(b)

TABLE Q2(c)

INPUT			OUTPUT
X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : BND/BNF
COURSE CODE: BNR 25402

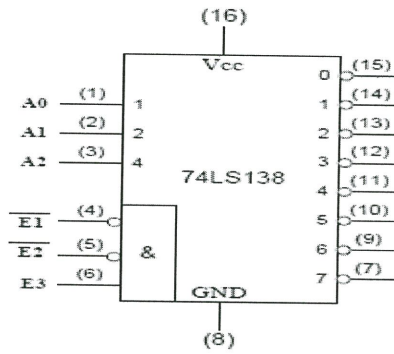


Figure Q3(c)

 


Figure Q4(b)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : BND/BNF
 COURSE CODE: BNR 25402

 


Figure Q4(c)(i)

 


Figure Q4(c)(ii)

 


Figure Q6(a)

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017
 COURSE NAME : DIGITAL ELECTRONICS

PROGRAMME : BND/BNF
 COURSE CODE: BNR 25402

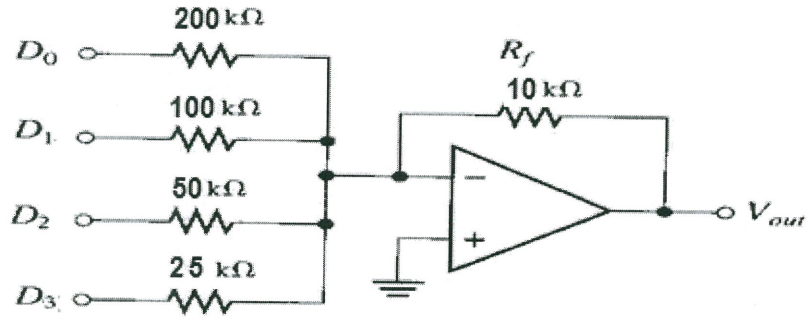


Figure Q6(d)(i)

Table Q6(d)

D_3	D_2	D_1	D_0	V_{out} (V)
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

TERBUKA