



**UTHM**  
Universiti Tun Hussein Onn Malaysia

**UNIVERSITI TUN HUSSEIN ONN MALAYSIA**

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2016/2017**

COURSE NAME : ELECTRICAL PRINCIPLES I  
COURSE CODE : BNR 10203  
PROGRAMME : 1BND/1BNE/1BNF  
EXAMINATION DATE : DECEMBER 2016 / JANUARY 2017  
DURATION : 2 HOURS 30 MINUTES  
INSTRUCTION : ANSWER **FOUR(4)** QUESTIONS ONLY

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF **TEN (10)** PAGES

- Q1**
- (a) Define “Kirchhoff’s Current Law” (KCL) and “Kirchhoff’s Voltage Law” (KVL).  
(2 marks)
  - (b) Describe Ohm’s law.  
(2 marks)
  - (c) Compute the branch currents  $I_1$  to  $I_5$  for the circuit shown in **Figure Q1(c)** using KCL.  
(5 marks)
  - (d) Determine  $I_1$  to  $I_5$  for the circuit shown in **Figure Q1(d)**.  
(12 marks)
  - (e) The Rotating Machine in **Figure Q1(e)** is rated at 120 V, 3 A. Calculate  $V_s$  in order to make the Rotating Machine operates at the rated conditions.  
(4 marks)
- Q2**
- (a) Calculate the currents mesh  $I_1$  to  $I_3$  in **Figure Q2(a)** using mesh analysis.  
(10 marks)
  - (b) Using nodal analysis, determine  $I_o$  and  $V_o$  in the circuit of **Figure Q2(b)**.  
(11 marks)
  - (c) Analyze the transistor circuit of **Figure Q2(c)**, find  $I_C$ , if  $\beta = 200$ ,  $V_o = 5.4$  V and  $V_{BE} = 0.7$  V.  
(4 marks)
- Q3**
- (a) In the circuit of **Figure Q3(a)**, calculate  $I_o$  when  $V_s = 12$  V, 13 V and 34 V.  
(7 marks)
  - (b) Given the circuit in **Figure Q3(b)**, use superposition to obtain  $I_o$ .  
(13 marks)
  - (c) Use Thevenin theorem to find  $V_{TH}$  and  $R_{TH}$  at the terminal  $a - b$  in **Figure Q3(c)**.  
(5 marks)

**TERBUKA**

- Q4** (a) Describe “Inverting Amplifier” and “Noninverting Amplifier”. (3 marks)
- (b) Obtain  $V_o$  and  $I_o$  for the ideal op amp circuits in **Figure Q4(a)**. (7 marks)
- (c) Determine  $I_o$  by analyzing the inverting amplifier circuit shown in **Figure Q4(b)**. (7 marks)
- (d) Determine  $I_o$  in the cascaded op amp circuit shown in **Figure Q4(c)**. (8 marks)
- Q5** (a) Obtain the equivalent capacitance between terminal  $a$  and  $b$  of the circuit shown in **Figure Q5(a)**. (6 marks)
- (b) Calculate the current through 15 mH inductor if the voltage across it is:
- $$v(t) = \begin{cases} 450t^4, & t > 0 \\ 0, & t < 0 \end{cases}$$
- Also, determine the energy stored at  $t = 3$  s, assume  $i(v) > 0$ . (6 marks)
- (b) In the circuit of **Figure Q5(b)**, let  $I_s = 60e^{-3t}$  A and  $V_1(0) = 70$  V,  $V_2(0) = 120$  V. Analyze:
- (i)  $V_1(t)$  and  $V_2(t)$
- (ii) The energy in each capacitor at  $t = 0.75$  s. (9 marks)
- (c) Determine the equivalent inductance at terminals  $a$  and  $b$  of the circuit shown in **Figure Q5(c)**. (4 marks)

TERBUKA

- END OF QUESTION -

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
COURSE CODE : BNR10203

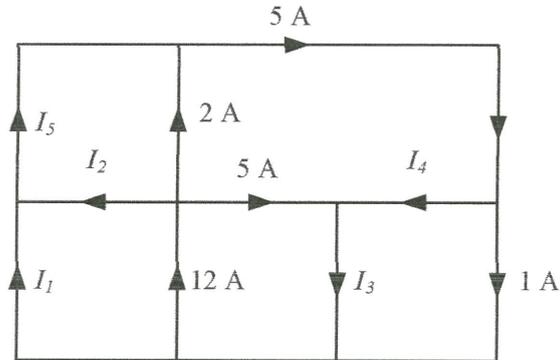


FIGURE Q1(c)

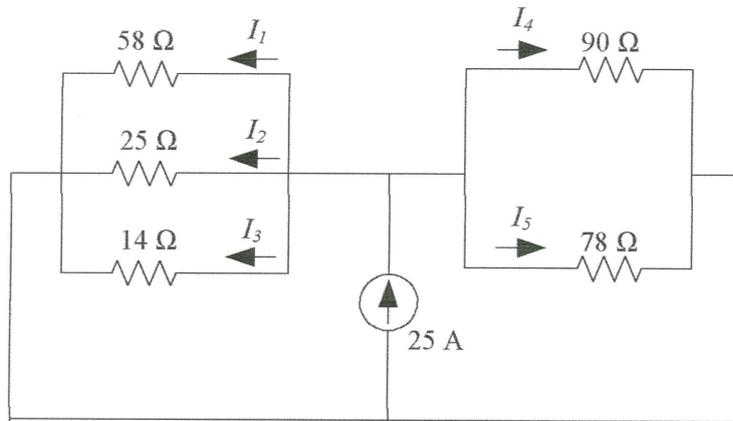


FIGURE Q1(d)

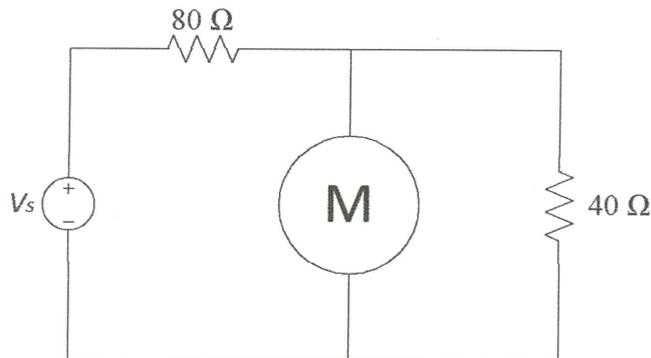


FIGURE Q1(e)

TERBUKA

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
 COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
 COURSE CODE : BNR10203

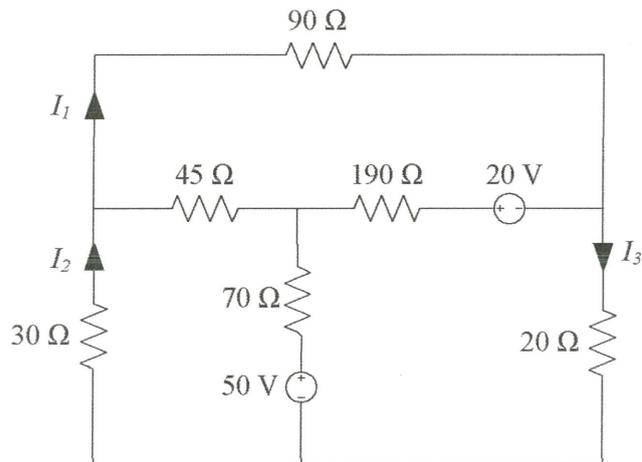


FIGURE Q2(a)

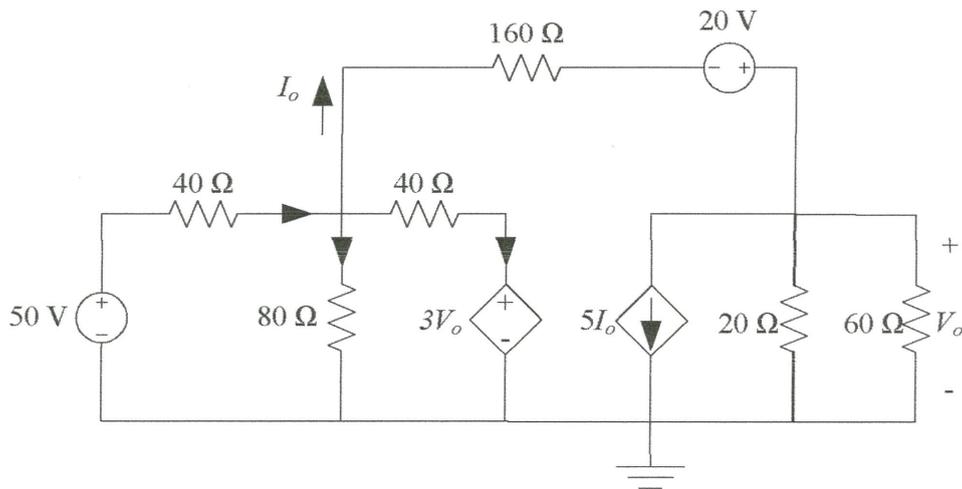


FIGURE Q2(b)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
COURSE CODE : BNR10203

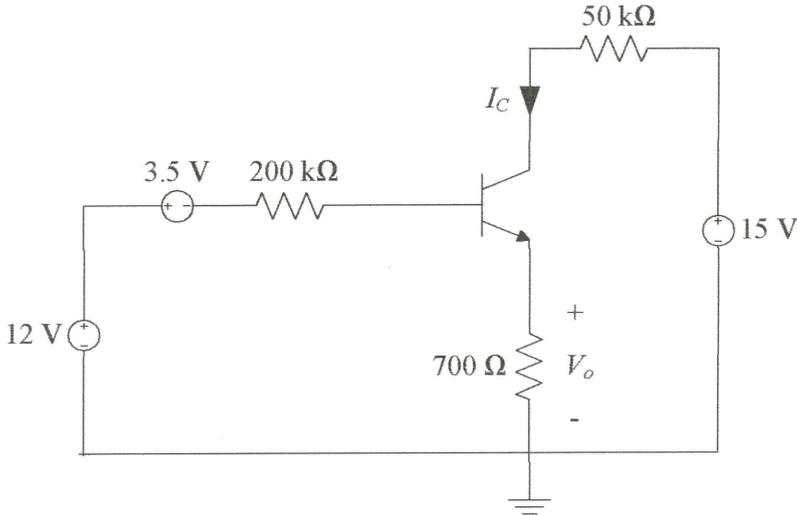


FIGURE Q2(c)


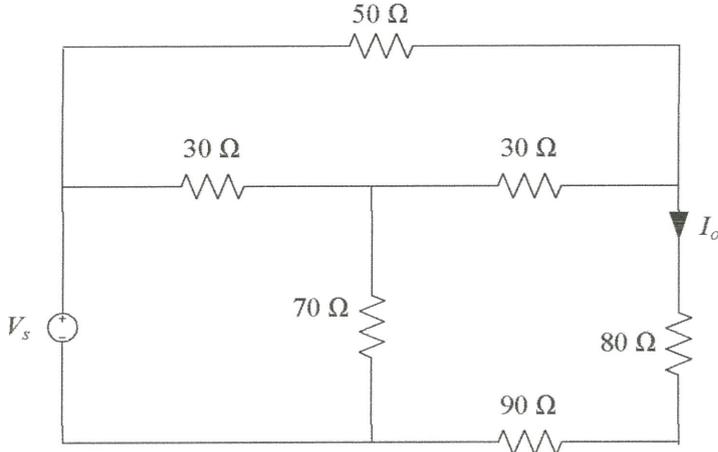


FIGURE Q3(a)

**TERBUKA**

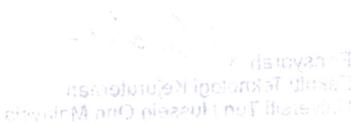

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
COURSE CODE : BNR10203

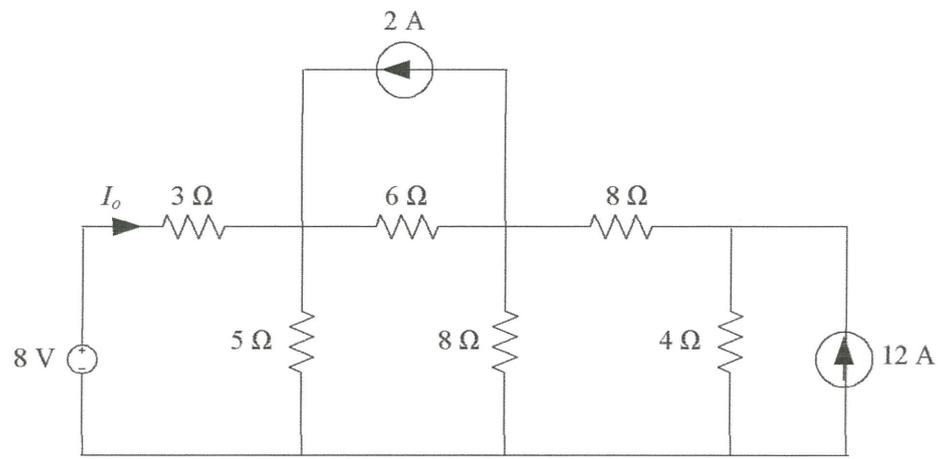


FIGURE Q3(b)

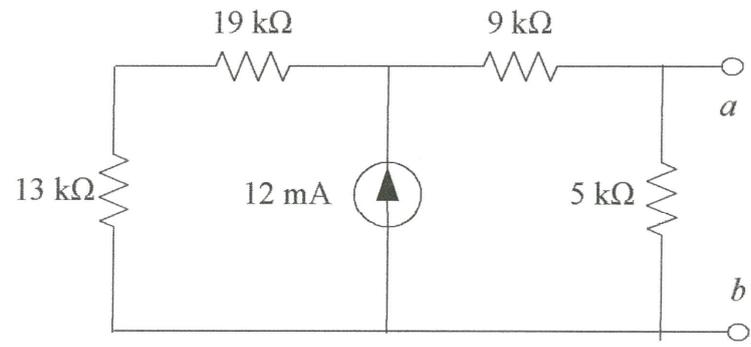


FIGURE Q3(c)

**TERBUKA**

*[Faint signature and stamp]*  
Fakulti Teknologi Kejuruteraan  
Universiti Teknikal Malaysia Melaka

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
COURSE CODE : BNR10203

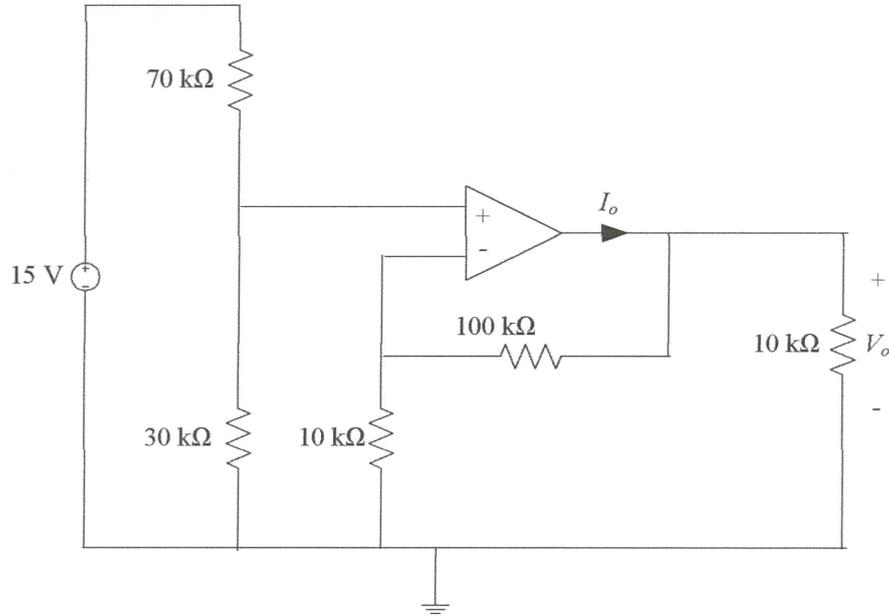


FIGURE Q4(a)

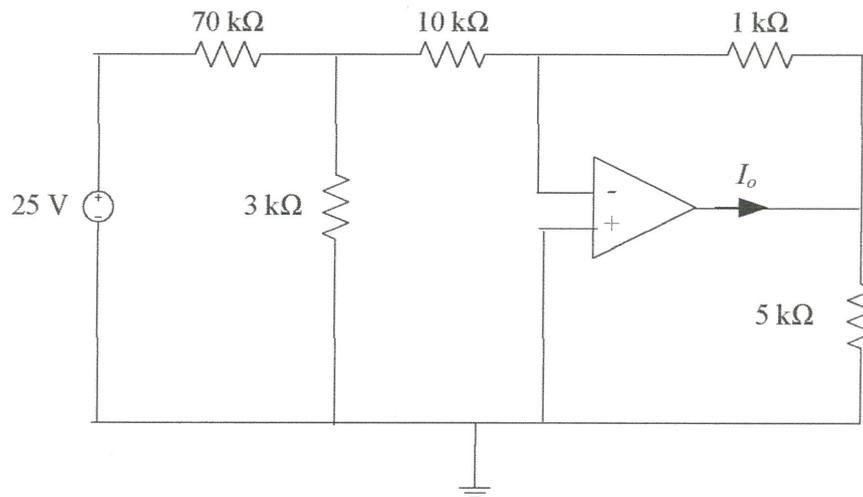


FIGURE Q4(b)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
COURSE CODE : BNR10203

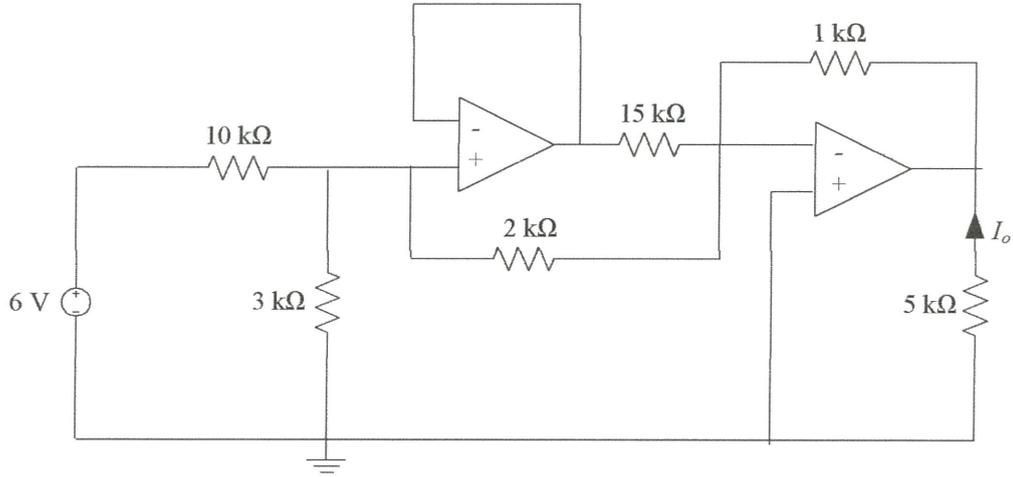


FIGURE Q4(c)

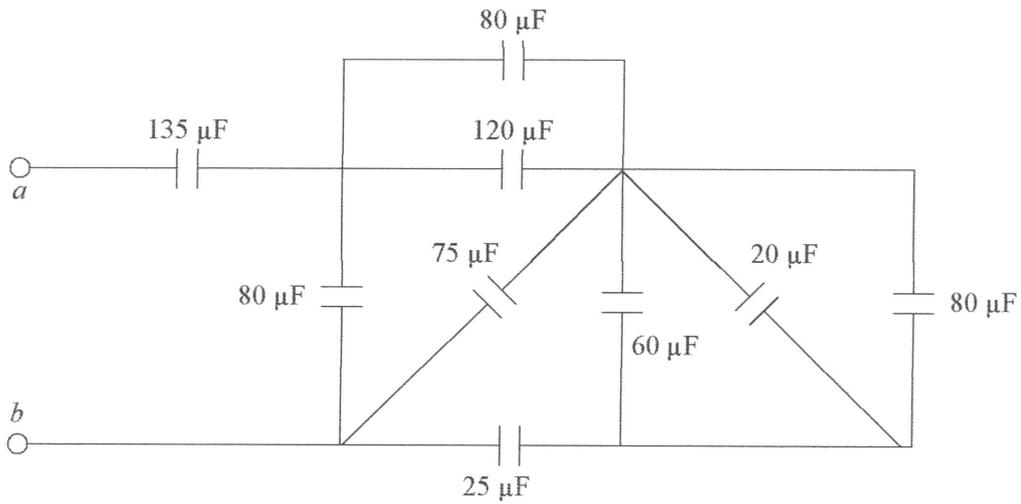


FIGURE Q5(a)

**TERBUKA**

FINAL EXAMINATION

SEMESTER / SESSION : SEM I / 2016/2017  
COURSE : ELECTRICAL PRINCIPLE 1

PROGRAMME : BND/BNE/BNF  
COURSE CODE : BNR10203

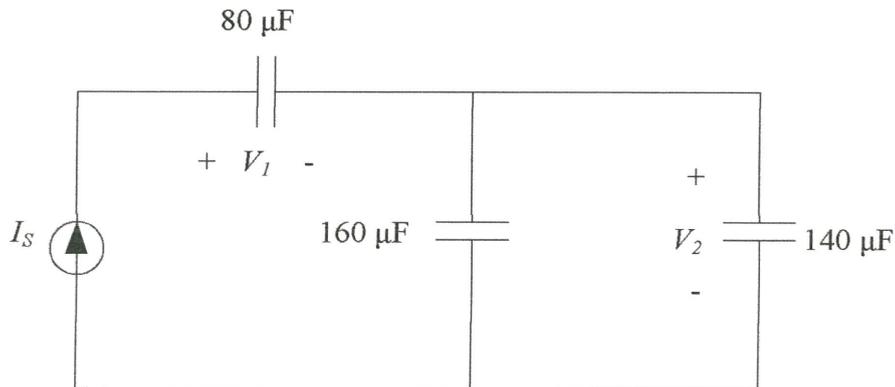


FIGURE Q5(b)

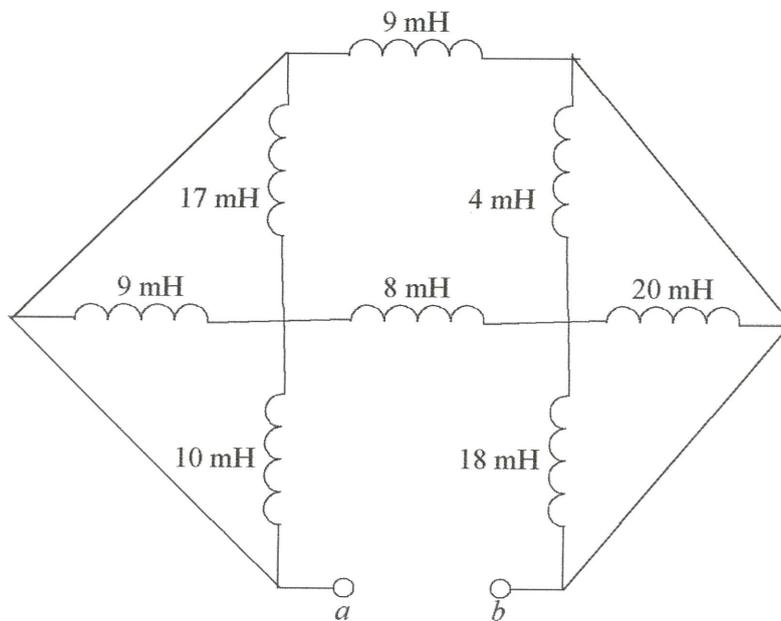


FIGURE Q5(c)

**TERBUKA**

Handwritten signature and stamp at the bottom of the page.