

CONFIDENTIAL



UNIVERSITI TUN HUSSEIN ONN MALAYSIA

**FINAL EXAMINATION  
SEMESTER I  
SESSION 2016/2017**

COURSE NAME : ELECTRONIC DEVICES AND  
CIRCUITS I

COURSE CODE : BNR25803

PROGRAMME CODE : BNE

EXAMINATION DATE : DECEMBER 2016 / JANUARY 2017

DURATION : 2 HOURS 30 MINUTES

INSTRUCTION : ANSWERS **FOUR (4)** QUESTIONS  
ONLY

**TERBUKA**

THIS QUESTION PAPER CONSISTS OF NINE (9) PAGES

CONFIDENTIAL

- Q1**
- (a) Describe briefly on the following diode circuits:
- (i) Clipper (2 marks)
  - (ii) Clamper (2 marks)
- (b) Determine the currents  $I_1$ ,  $I_2$  and  $I_{D2}$  for the network of **Figure Q1 (b)**. (5 marks)
- (c) Plot the output voltage,  $V_o(t)$ , for each of the circuits in **Figure Q1 (c)** if the input voltage is  $V_i$ . (5 marks)
- (d) In the voltage regulator circuit in **Figure Q1 (d)**, let  $V_i = 6.3\text{V}$ ,  $R = 12\Omega$ , and  $V_z = 4.8\text{V}$ . The zener diode current is to be limited to the range  $5 \leq I_z \leq 100 \text{ mA}$ .
- (i) Determine the range of possible load currents and load resistances. (6 marks)
  - (ii) Determine the power rating required for the Zener diode and the load resistor,  $R_L$ . (5 marks)
- Q2**
- (a) A power supply circuit is energized by a  $240 \text{ V}_{\text{rms}}$ ,  $50\text{Hz}$  AC source. The transformer step-down ratio is 16:1 and it uses a full-wave bridge rectifier with a single  $1000\mu\text{F}$  electrolytic capacitor filter,  $C_f$ . Do the following:
- (i) Draw the schematic diagram for this DC power supply circuit. (3 marks)
  - (ii) Calculate the peak value of the ripple voltage  $V_{r(p)}$  and the DC output voltage,  $V_{r(dc)}$  for this power supply if the load current is  $0.1 \text{ A}$ . Assume that the forward voltage drops of each diode is  $0.7 \text{ V}$ . (7 marks)
  - (iii) Sketch the output voltage,  $V_{out}$  and label the peak value and dc level. (3 marks)
  - (iv) Determine the percentage of ripple factor ( $r \%$ ) for this the circuit. (3 marks)

**TERBUKA**

- (b) In order to improve the previous ripple factor of the power supply circuit in **Q2(a)**, the output of this circuit is now connected to the LC filter circuit as shown in **Figure Q2(b)**. Calculate the new ripple factor ( $r\%$ ) of the output waveform. Given  $C_2 = C_1$  and the inductor has winding resistance of  $2\Omega$ .  
(9 marks)

- Q3** (a) With the aid of appropriate diagrams, explain the following devices:
- (i) Gate turn-off switch (*GTO*) (5 marks)
  - (ii) Silicon controlled rectifier (*SCR*) (5 marks)
- (b) Describe two techniques for turning an *SCR* (silicon-controlled rectifier) ON and OFF. (5 marks)
- (c) For a unijunction transistor (*UJT*) with  $V_{BB} = 20\text{ V}$ ,  $\eta = 0.65$ ,  $R_{B1} = 2\text{ k}\Omega$  ( $I_E = 0$ ), and  $V_D = 0.7\text{ V}$ , determine:
- (i)  $R_{B1}$   $R_{B2}$  (2 marks)
  - (ii)  $R_{BB}$  (2 marks)
  - (iii)  $V_{RB1}$  (2 marks)
  - (iv)  $V_P$  (2 marks)
- (d) Draw the *UJT* equivalent circuit completed with all the values to represent the *UJT* at part **Q3(c)**. (2 marks)
- Q4** (a) Differentiate between Bipolar Junction Transistor (*BJT*) and Field Effect Transistor (*FET*). (4 marks)
- (b) Explain with a suitable diagram, **THREE (3)** operating region of a *BJT*. (6 marks)

**TERBUKA**

- (c) Prove that the relationship between current gain of a BJT,  $\alpha$  and  $\beta$  are as shown below if  $\alpha = I_C/I_E$  and  $\beta = I_C/I_B$ .

$$\alpha = \frac{\beta}{\beta + 1} \quad \text{or} \quad \beta = \frac{\alpha}{1 - \alpha}$$

(5 marks)

- (d) An n-channel enhancement-type MOSFET (*E-MOSFET*) has following parameters;  $V_{GS(on)} = 4 \text{ V}$ ,  $I_{D(on)} = 3 \text{ mA}$ ,  $k = 0.4 \times 10^{-3} \text{ A/V}^2$ .

- (i) Determine the threshold voltage,  $V_{GS(TH)}$  and write the general expression for  $I_D$ .

(3 marks)

- (ii) Sketch and completely label the transfer characteristics for this E-MOSFET.

(3 marks)

- (iii) Determine  $I_D$  for  $V_{GS} = 3\text{V}$ ,  $6\text{V}$  and  $10\text{V}$ .

(4 marks)

- Q5** (a) Draw the BJT logic gates that represents *OR* and *AND* gate. Give the truth table for both gates.

(6 marks)

- (b) For a bipolar transistor constant current source as shown in **Figure Q5(b)**, calculate the constant current,  $I$ .

(5 marks)

- (c) For the transistor voltage regulator circuit shown in **Figure Q5(c)**, calculate the output voltage,  $V_o$  and zener current,  $I_Z$  for  $R_L = 1 \text{ k}\Omega$ . The transistor has  $\beta = 50$ .

(7 marks)

- (d) Give the differences between Class A, Class B, Class AB and Class C power amplifier. Identify the major problem occurs in Class B power amplifier compared to other classes. Discuss your answer.

(7 marks)

TERBUKA

- Q6** (a) Differentiate between negative feedback and positive feedback. (4 marks)
- (b) **Figure Q6 (b)** is a block diagram of a system with feedback network. Derive the closed-loop gain,  $A_f$  of the system. (6 marks)
- (c) **Figure Q6 (c)** shows an amplifier with a negative feedback network. Given  $Z_{of} = 100 \text{ k}\Omega$ ,  $Z_o = 5 \text{ k}\Omega$  and  $A_f = 50$ .
- (i) State the feedback topology and the amplifier type. (2 marks)
- (ii) Calculate the gain without feedback,  $A$  and the feedback factor,  $\beta$ . (6 marks)
- (iii) If the low cutoff frequency of the amplifier with feedback network ( $f_{Lp}$ ) is 100 Hz, calculate the low cutoff frequency ( $f_L$ ) if the amplifier does not have the feedback network. (3 marks)
- (iv) Sketch and label the values of the frequency response for both conditions, with and without feedback. (4 marks)

- END OF QUESTION -

TERBUKA

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017

PROGRAMME: 2BNE

COURSE NAME: ELECTRONIC DEVICES AND CIRCUITS 1

COURSE CODE: BNR25803

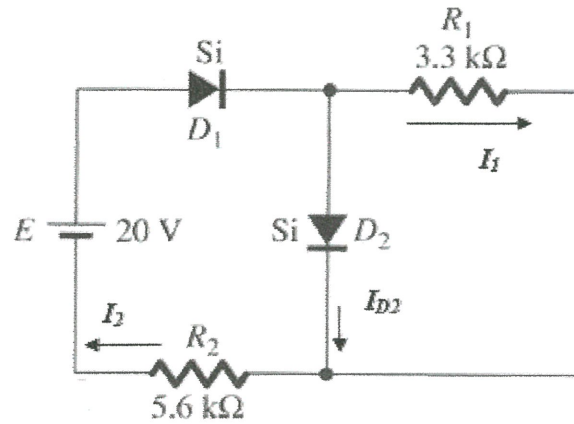


FIGURE Q1 (b)

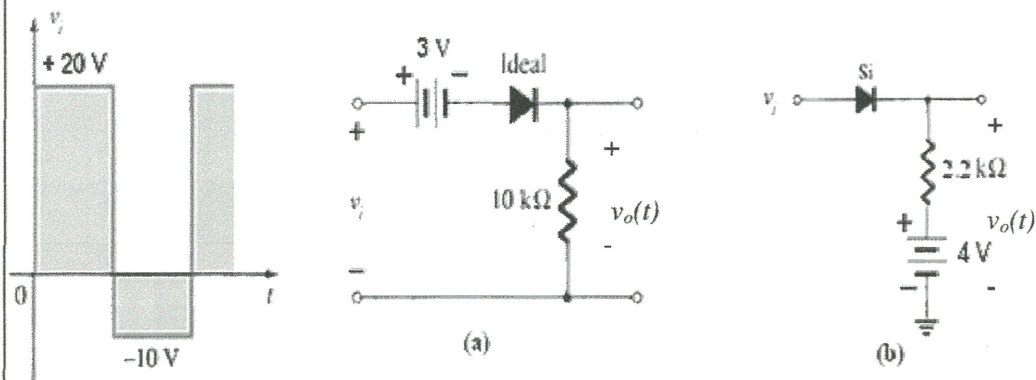


FIGURE Q1 (c)

**TERBUKA**

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017

PROGRAMME: 2BNE

COURSE NAME: ELECTRONIC DEVICES AND CIRCUITS 1 COURSE CODE: BNR25803

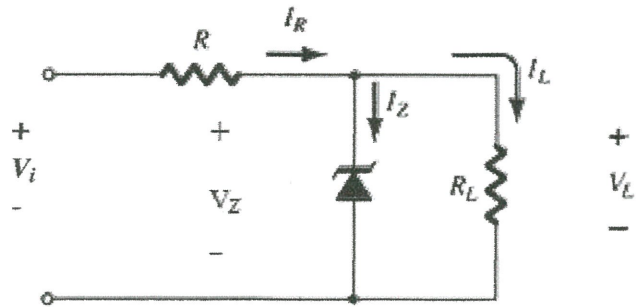


FIGURE Q1(d)

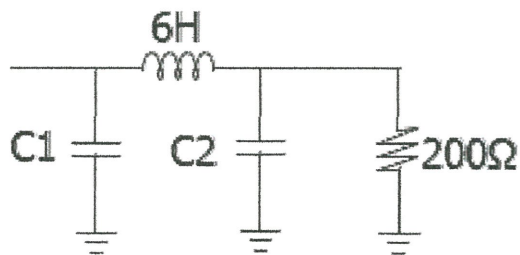


FIGURE Q2 (b)

**TERBUKA**

FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017

PROGRAMME: 2BNE

COURSE NAME: ELECTRONIC DEVICES AND CIRCUITS 1

COURSE CODE: BNR25803

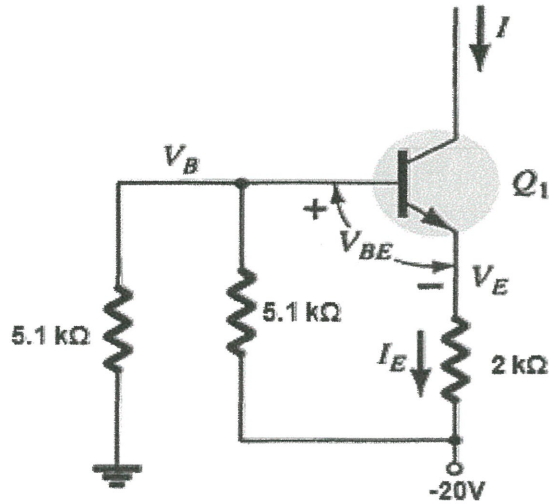


FIGURE Q5(b)

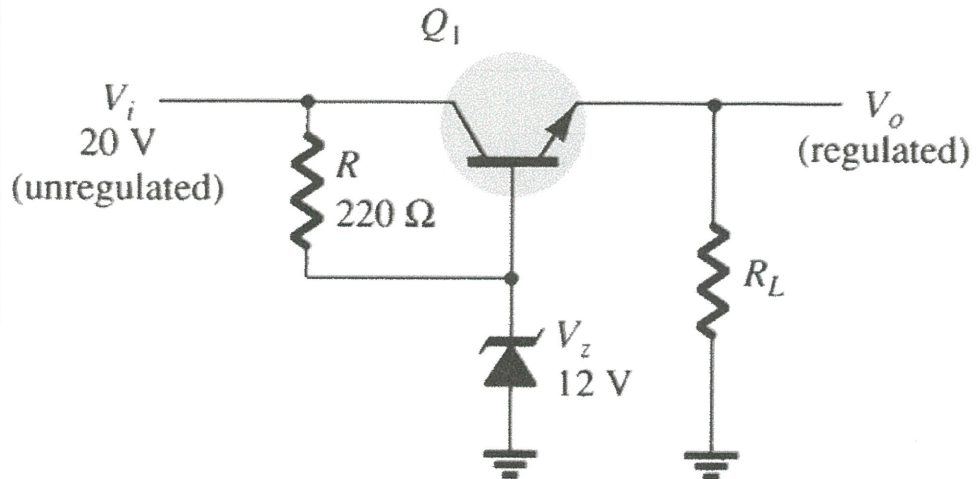


FIGURE Q5(c)

TERE JKA



FINAL EXAMINATION

SEMESTER/SESSION: SEM I/2016/2017

PROGRAMME: 2BNE

COURSE NAME: ELECTRONIC DEVICES AND CIRCUITS 1 COURSE CODE: BNR25803

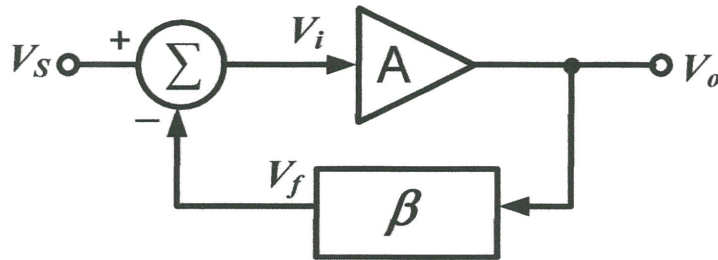


FIGURE Q6 (b)

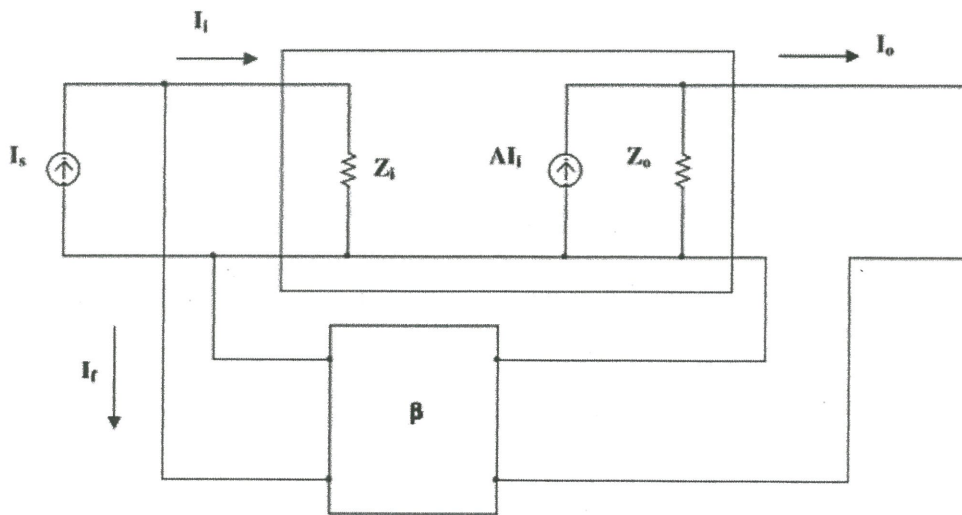


FIGURE Q6 (c)

**TERBUKA**